

Week 9

Logic Gates

Logic Circuits Course AIU-IE

Ch. 3

Logic Gates




Logic Gates

- The term gate is used to describe a circuit that performs a basic logic operation

Logic Gates

1. Inverter
2. AND Gate
3. OR Gate
4. NAND Gate
5. NOR Gate
6. Exclusive-OR Gate
7. Exclusive-NOR Gate
8. Fixed-Function Logic

The Inverter

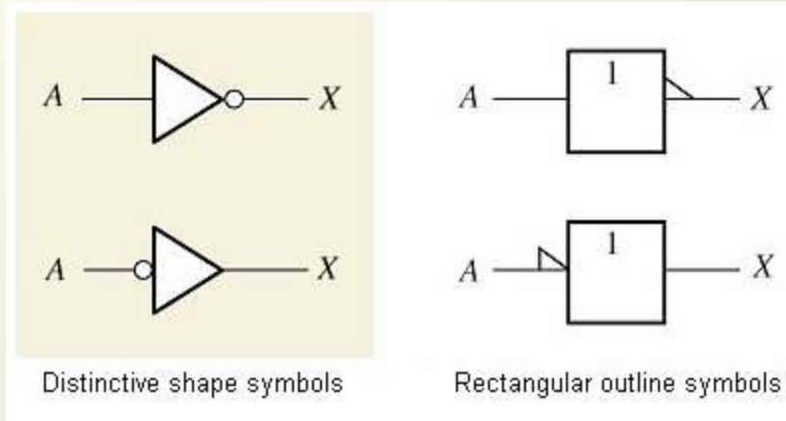


A	X
0	1
1	0

$$X = \bar{A}$$

Truth table

Boolean expression


0 = LOW
1 = HIGH

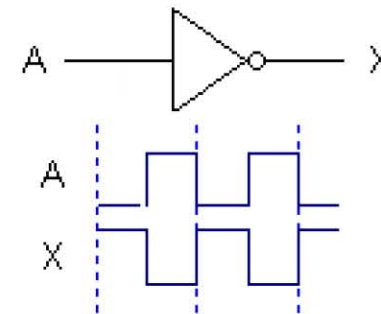

Pulsed waveforms


The output of an inverter is always the complement (opposite) of the input.

Binary number

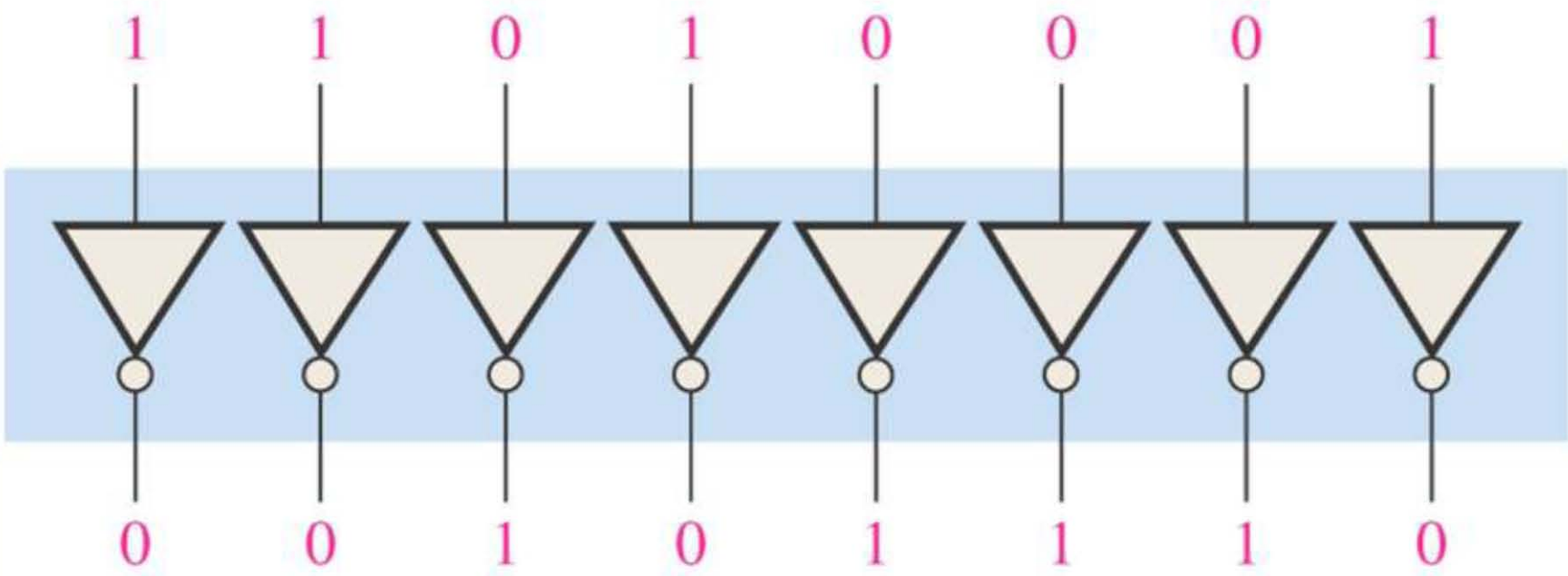


1's complement

The AND Gate

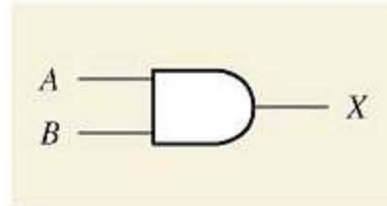

Distinctive shape symbol

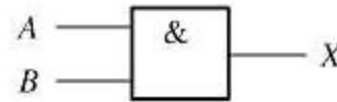



Rectangular outline symbol

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

Truth table

0 = LOW
1 = HIGH

$X = AB$
Boolean expression

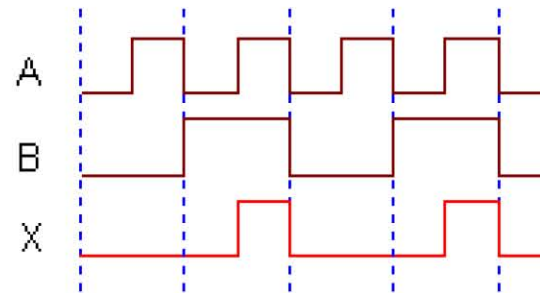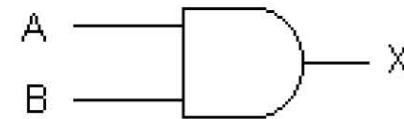


Pulsed waveforms


The output of an AND gate is HIGH only when all inputs are HIGH.

Timing diagram shows input output relationship

The AND Gate

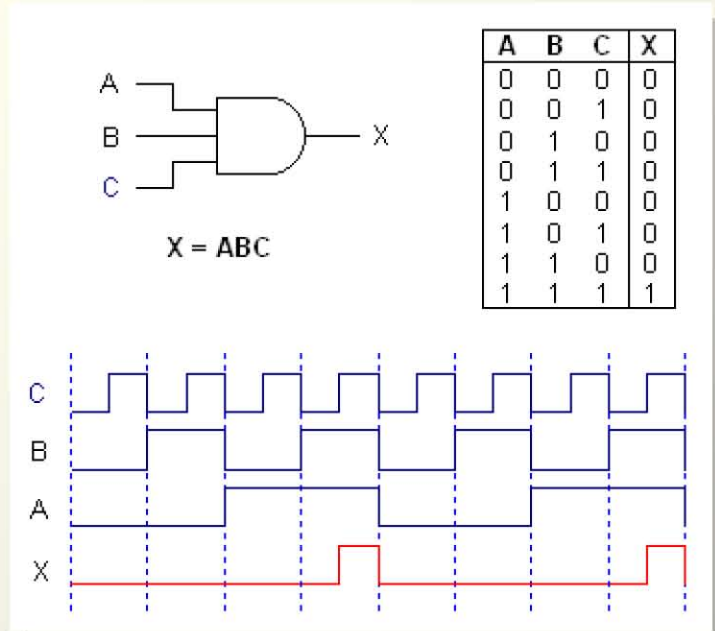


3-Input AND Gate

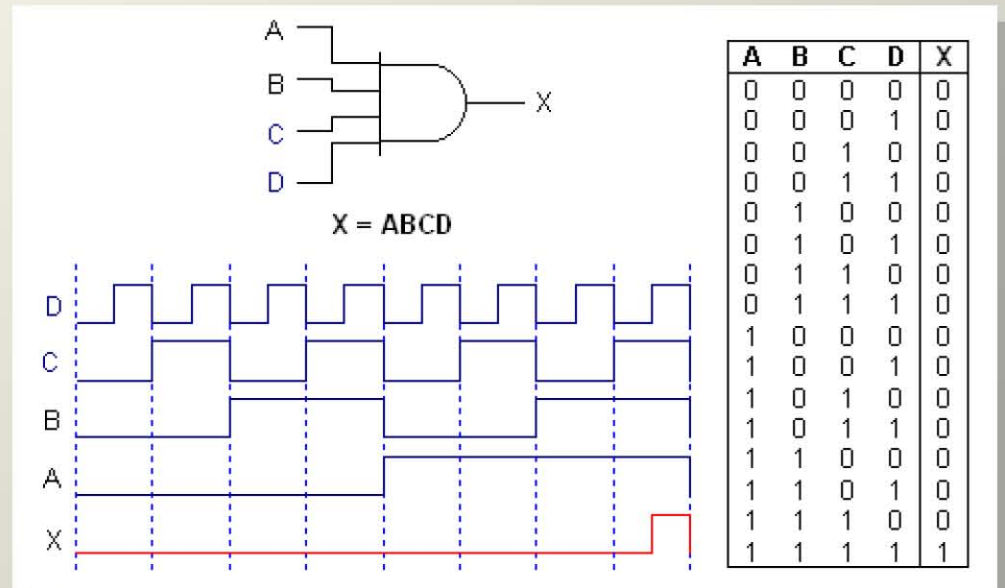


4-Input AND Gate

The OR Gate

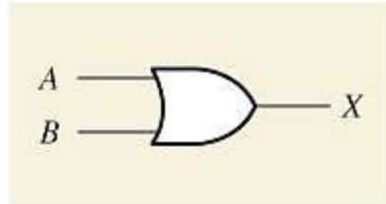

Distinctive shape symbol

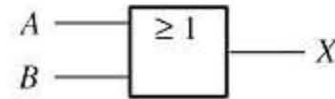

Rectangular outline symbol


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

$$X = A + B$$

Boolean expression

Truth table


0 = LOW
1 = HIGH

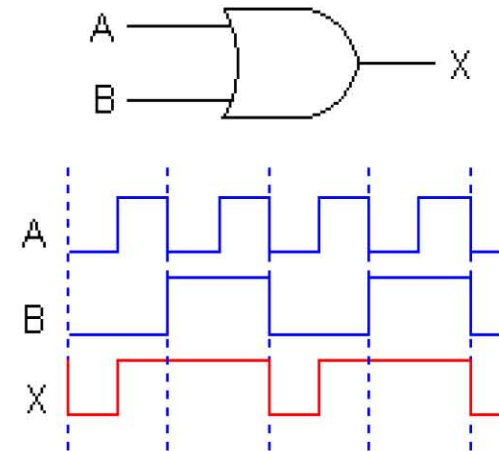


Pulsed waveforms

The output of an OR gate is HIGH whenever one or more inputs are HIGH

The OR Gate

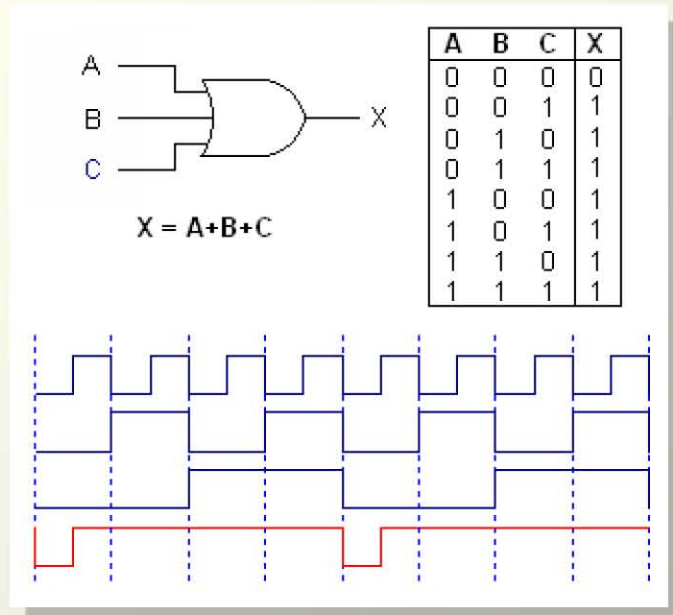

3-Input OR Gate

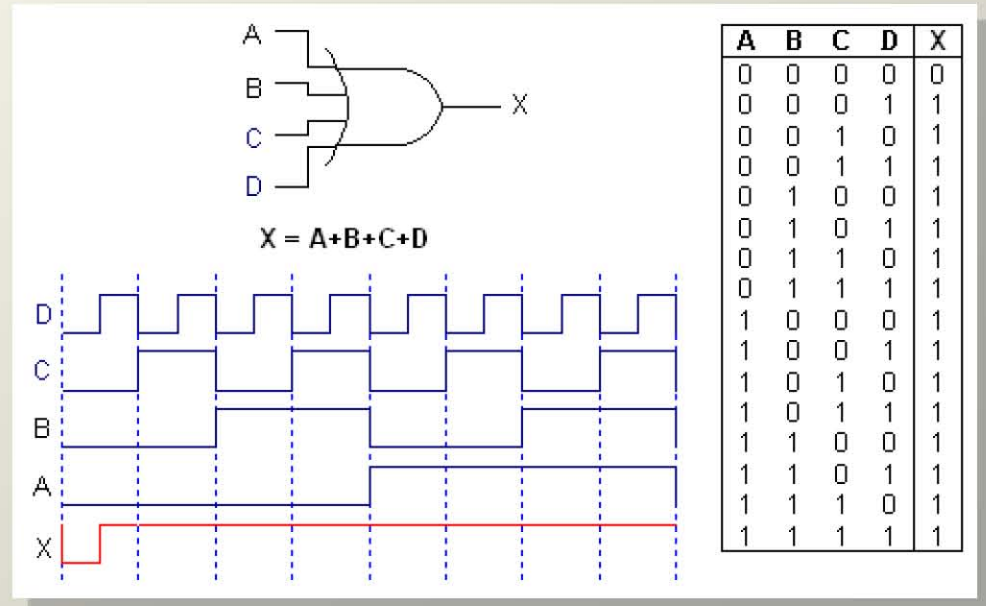


4-Input OR Gate


A simplified intrusion detection system using an OR gate. Open door or window alarm

Open door/window
sensors


HIGH = Open
LOW = Closed

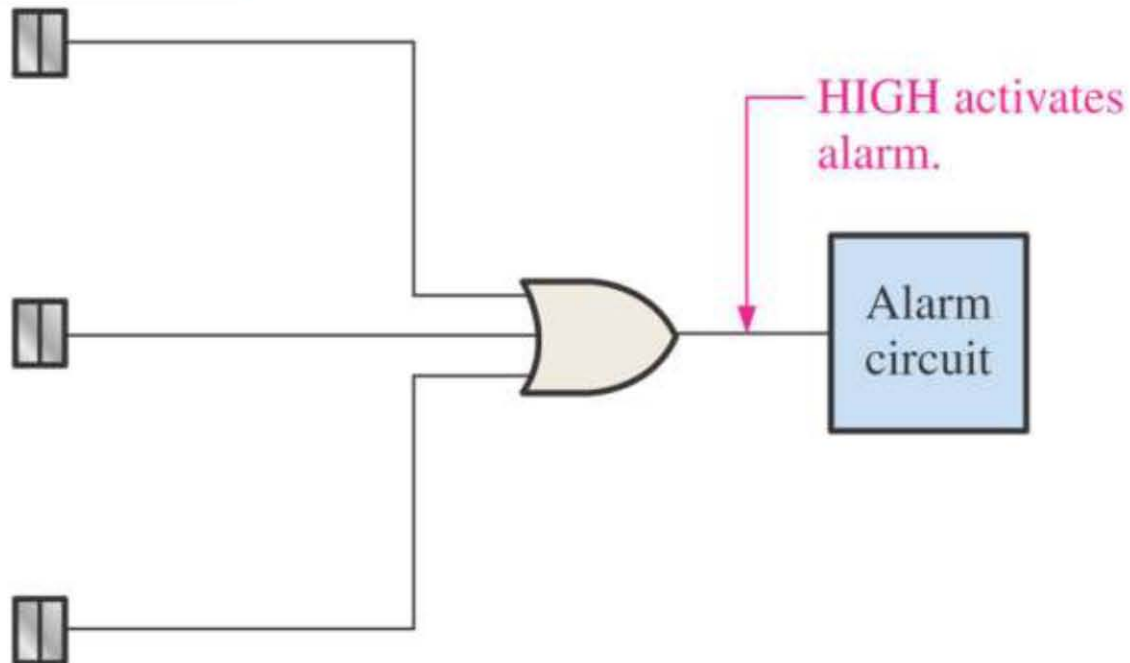


The NAND Gate

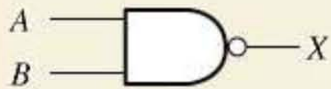

Distinctive shape symbol

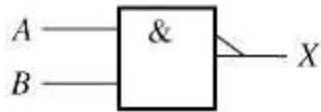

Rectangular outline symbol

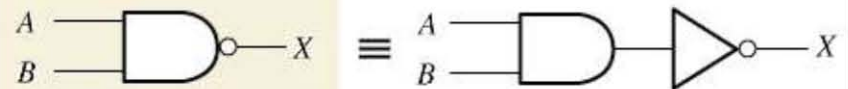



A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Truth table

0 = LOW
1 = HIGH

$$X = \overline{AB}$$


Boolean expression

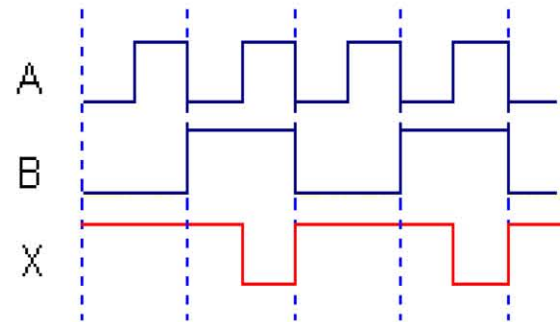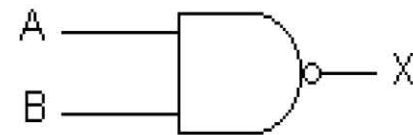


Pulsed waveforms

The output of a NAND gate is HIGH whenever one or more inputs are LOW.

The NAND Gate

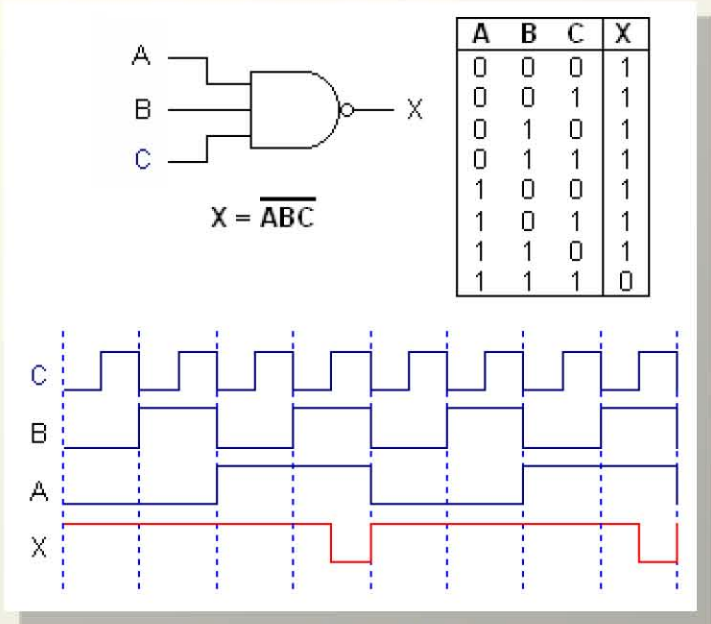


3-Input NAND Gate

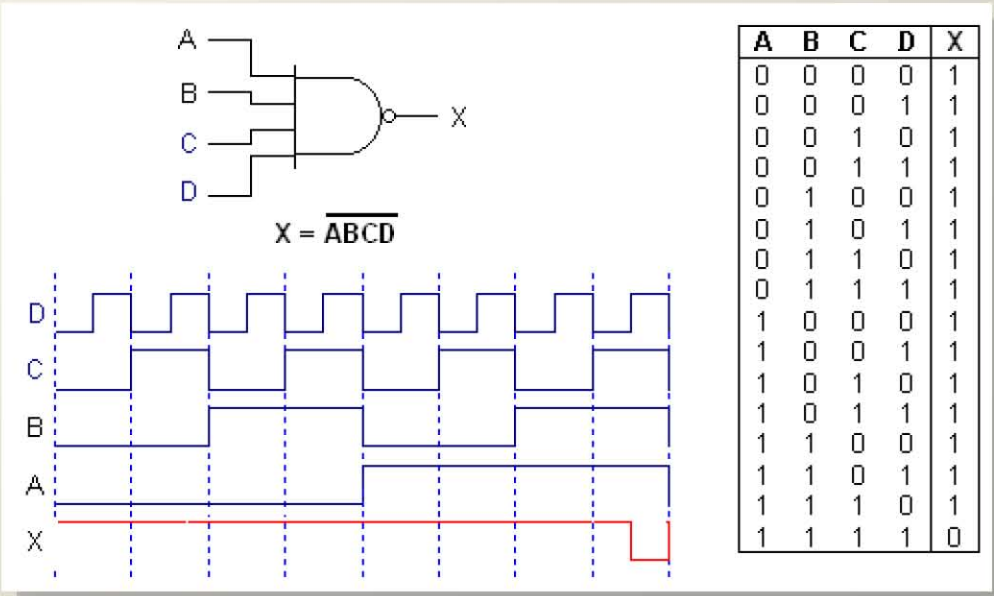


4-Input NAND Gate

The NAND Gate

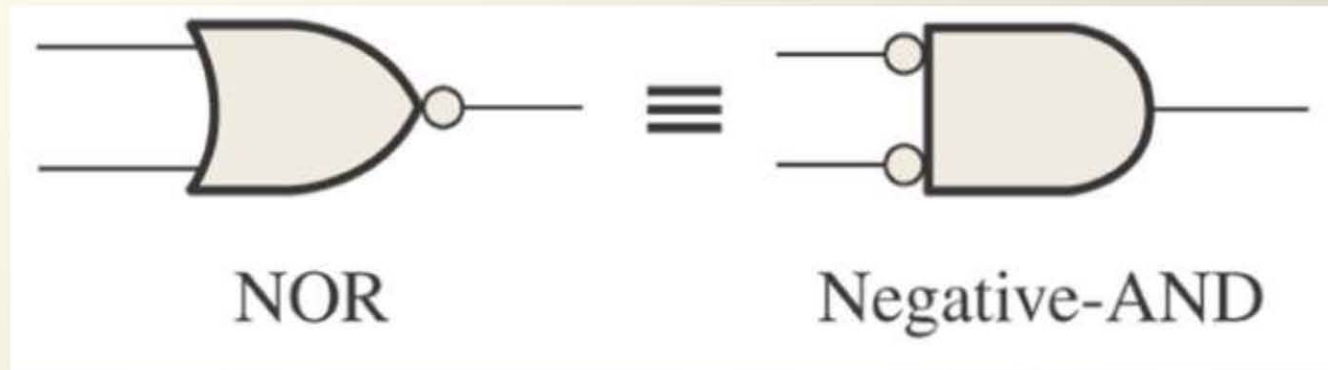


Standard symbols representing the two equivalent operations of a NOR gate.

Liquid Level detector, green light off

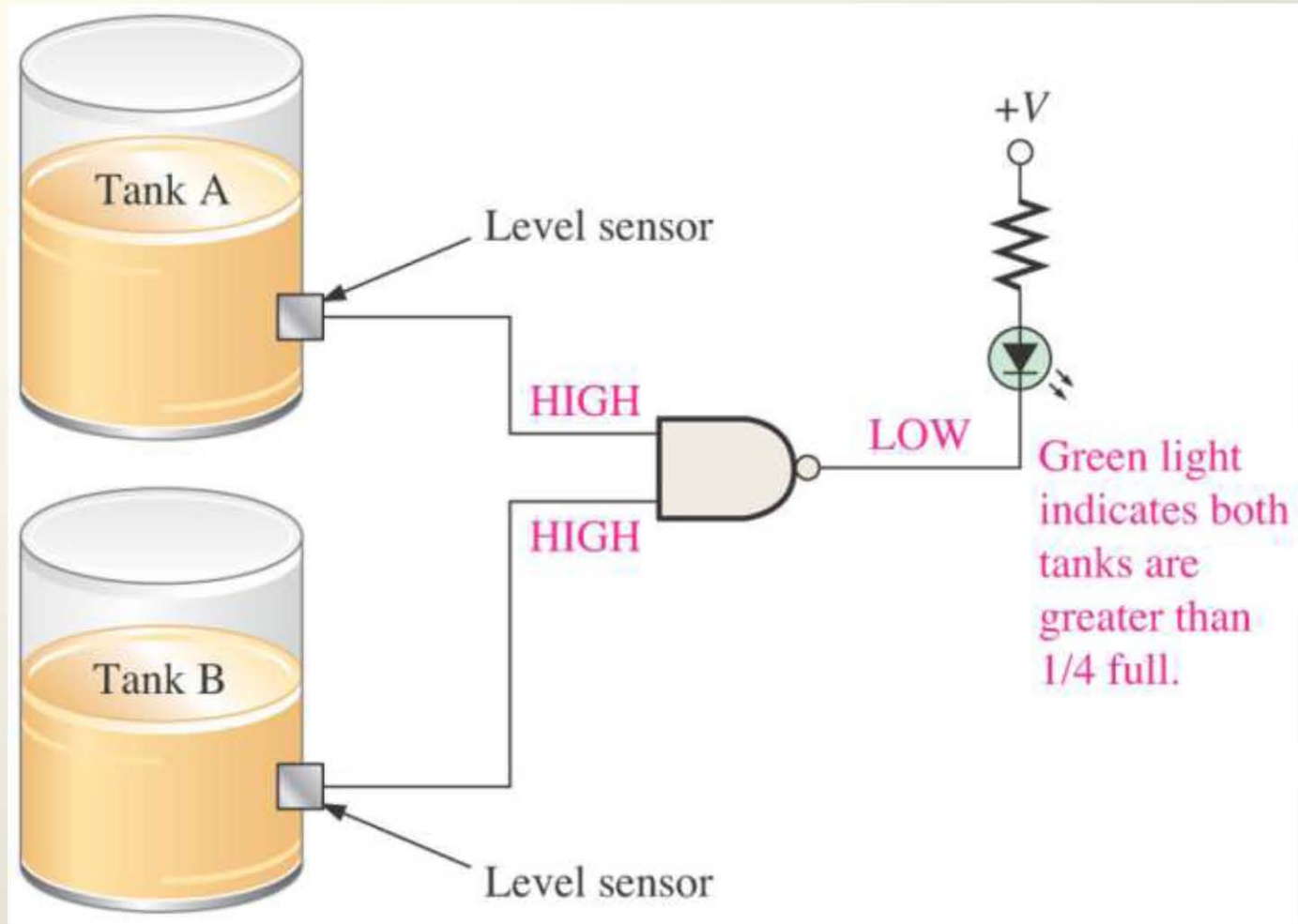


The Level sensors produce High level of 5 volt when the tanks are more than one-quarter full. When the volume of chemical drop to one-quarter full, the sensor puts out a Low level of 0 volt

Liquid Level detector, Red light on

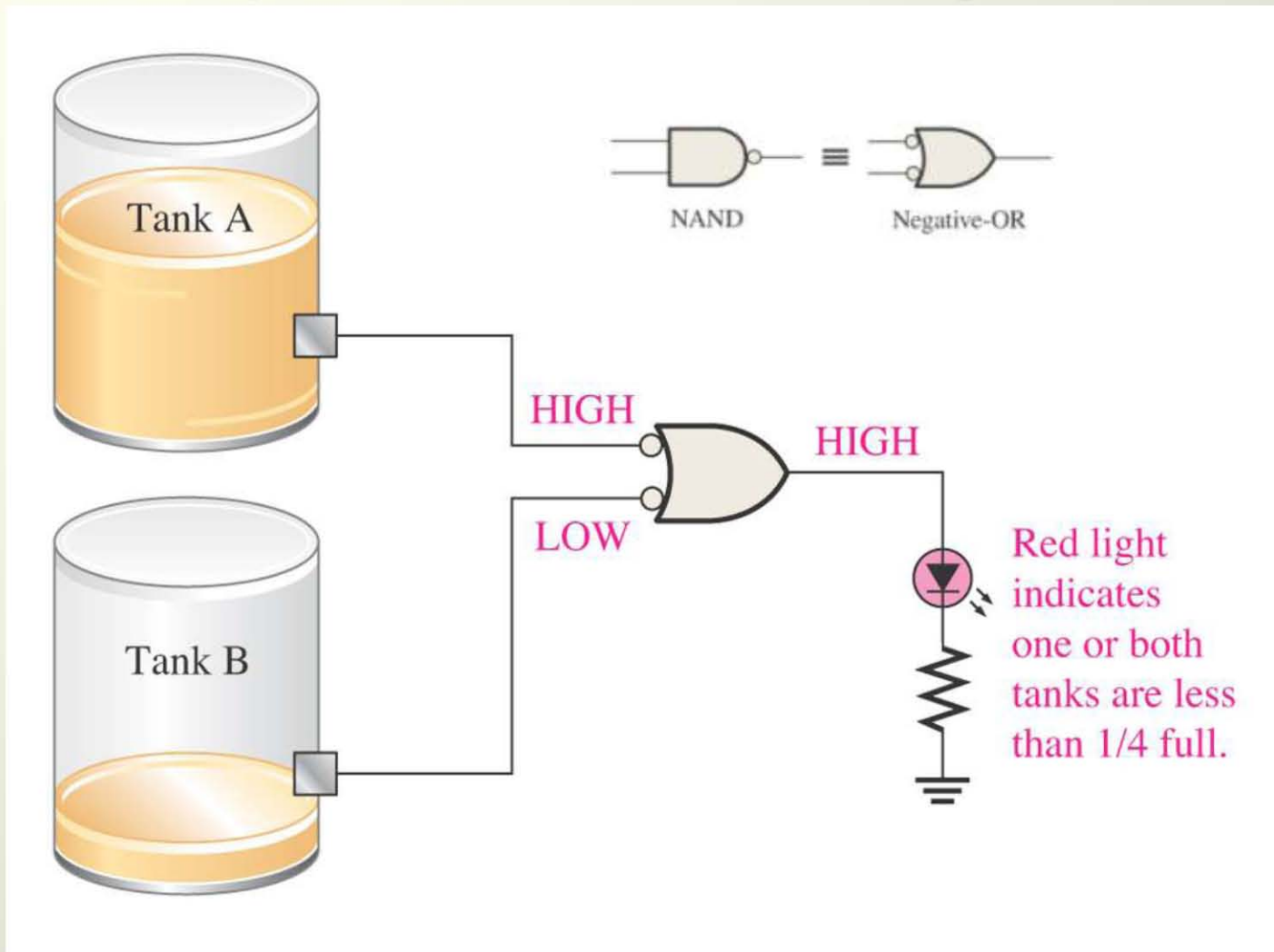


the volume of chemical drop to one-quarter full, the sensor puts out a Low level of 0 volt


The NOR Gate

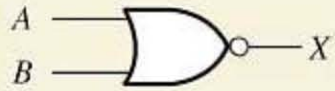

Distinctive shape symbol

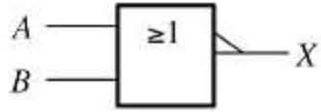

Rectangular outline symbol

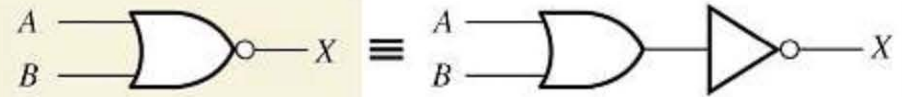


A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

Truth table

0 = LOW
1 = HIGH

$$X = \overline{A + B}$$

Boolean expression

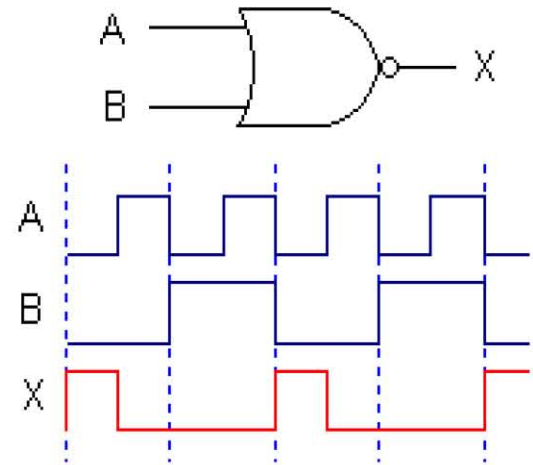

Pulsed waveforms

The output of a NOR gate is LOW whenever one or more inputs are HIGH.