

**University of Anbar
College of Engineering
Dept. of Electrical Engineering**



**Electric physics II
Assist. Lac. Yasameen Kamil
2020 - 2021**

**Electric physics II
Electric circuits
By
Assist. Lac. Yasameen Kamil
2020 - 2021**


Basic concepts

Electricity: *Physical phenomenon arising from the existence and interactions of **electric charge***

- ☒ Charge
- ☒ Current
- ☒ Voltage
- ☒ Power and Energy



Electric current

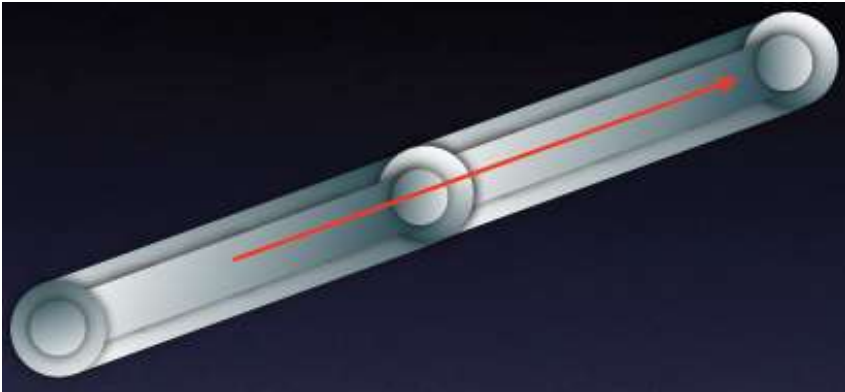

$$I = \frac{\text{charge}}{\text{time}} = \frac{\text{coulombs}}{\text{seconds}}$$

$$I = \frac{Q}{t} \text{ amperes}$$

An **ampere (A)** is the number of electrons having a total charge of 1 C moving through a given cross section in 1 sec.

As defined, current flows in direction of **positive charge** flow

Current density

- It is the amount of current flowing in a unit area and its symbol (J).


- $J = \frac{I}{A}$


- The unite of current density is $\left(\frac{A}{m^2}\right)$

Electric circuit

*An electric circuit is an interconnection of electrical elements linked together in a **closed path** so that electric current may flow continuously*

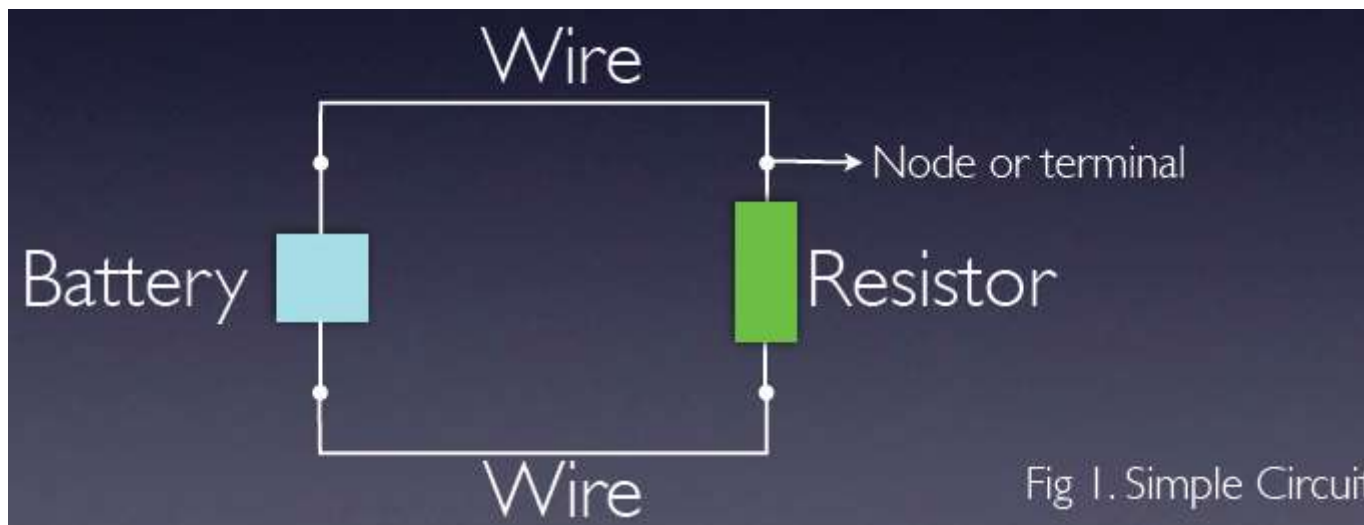Circuit diagrams are the standard for electrical engineers




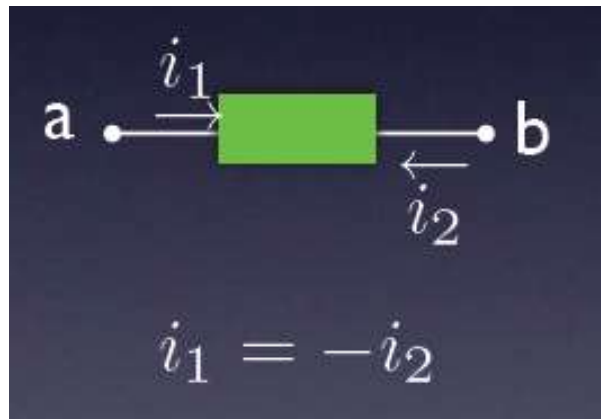


i_1 → Rate of flow of charge form **node a to node b**

← i_2 Rate of flow of charge form **node b to node a**

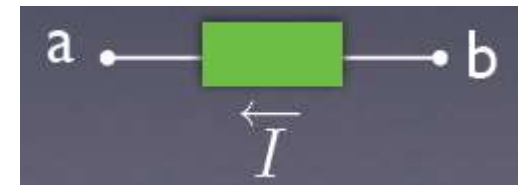A **direct current (dc)** is a current of constant magnitude




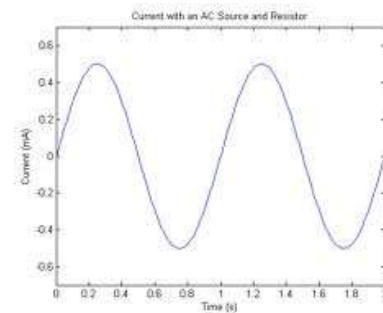An **alternating current (ac)** is a current of varying magnitude and direction



Voltage

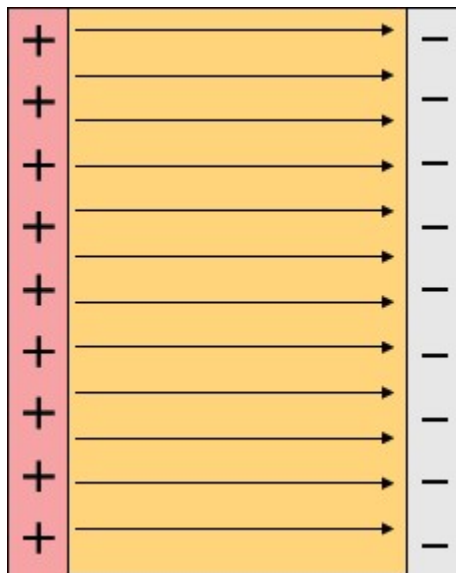The voltage across an element is the work (energy) required to move a unit of positive charge from the “-” terminal to the “+” terminal



$$V = \frac{W}{Q} = \frac{\text{joules}}{\text{coulombs}} = \text{volts}$$

A **volt** is the potential difference (voltage) between two points when **1 joule of energy** is used to move **1 coulomb of charge** from one point to the other


Power

The rate at which energy is converted or work is performed

$$P = \frac{W}{t} = \frac{\text{joules}}{\text{second}} = \text{watt}$$
$$P = IV$$

A **watt** results when **1 joule of energy** is converted or used in **1 second**


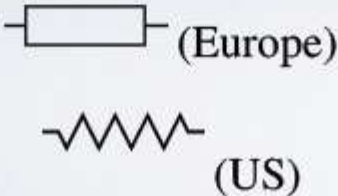
Power Dissipated in Resistor



$P = VI = \frac{V^2}{R} = I^2 R$

The diagram shows a resistor symbol with a zigzag line. To its left, a vertical bracket indicates a voltage V across it, with a red arrow pointing up and another red arrow pointing down. To its right, a vertical arrow labeled I indicates current flowing downwards through the resistor.

Resistors

Resistor	
	
Three resistors	
Type	Passive
Electronic symbol	
	


Resistance (R) is the physical property of an element that impedes the flow of current . The units of resistance are **Ohms (Ω)**

Resistivity (ρ) is the ability of a material to resist current flow. The units of resistivity are **Ohm-meters ($\Omega\cdot\text{m}$)**

Example:


Resistivity of copper	$1.68 \times 10^{-8} \Omega\cdot\text{m}$
Resistivity of glass	10^{10} to $10^{14} \Omega\cdot\text{m}$

Resistors

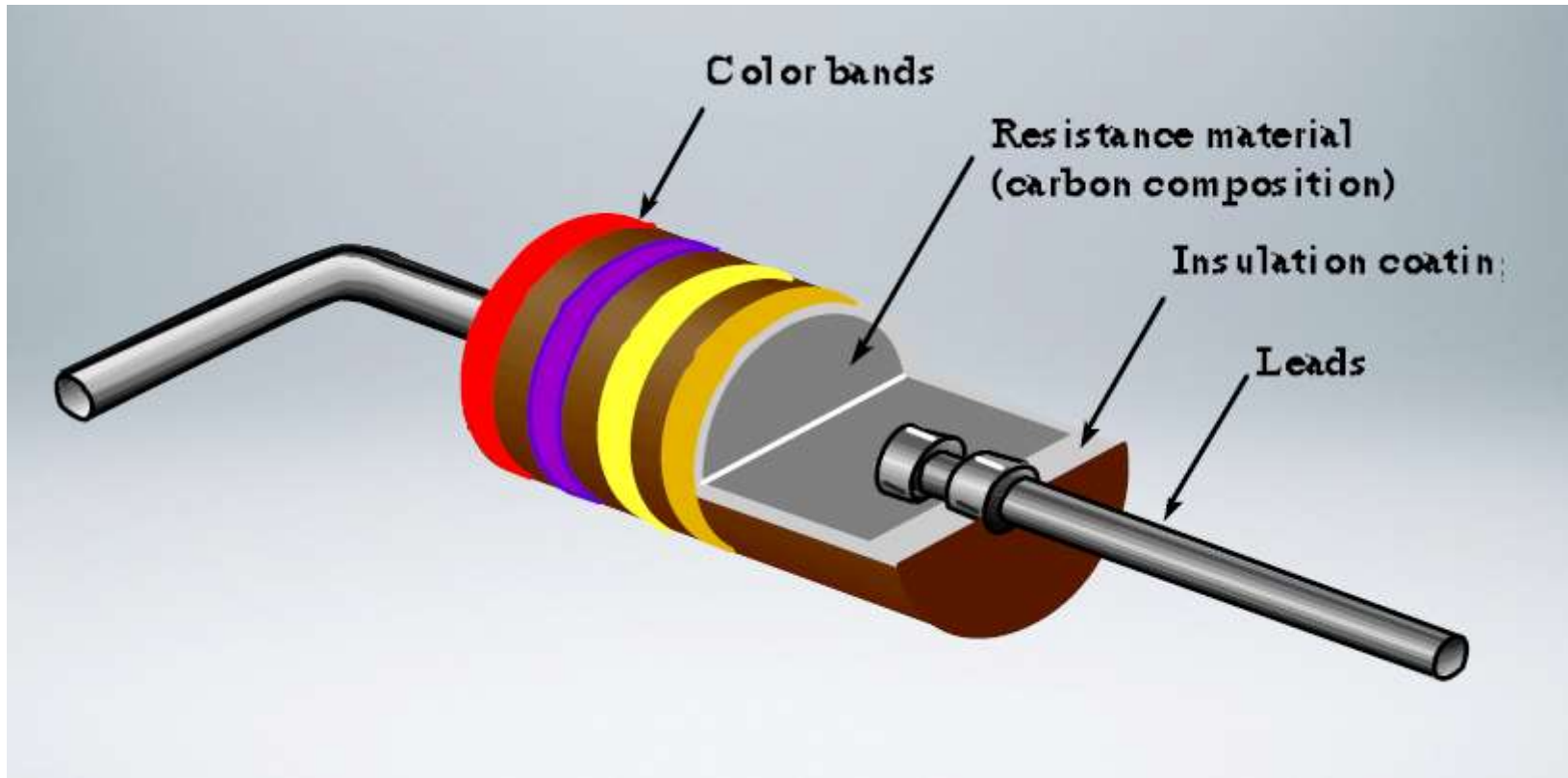


Resistors

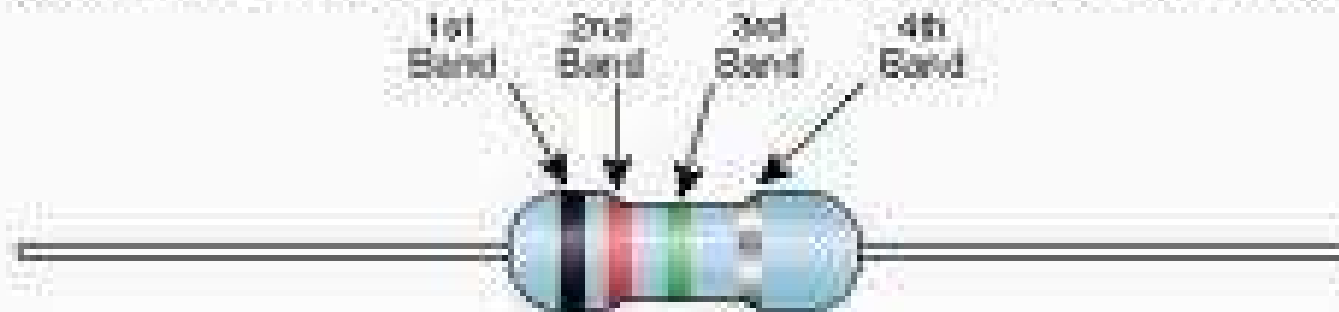Standard EIA Color Code Table 4 Band: $\pm 2\%$, $\pm 5\%$, and $\pm 10\%$



Color	1st Band (1st figure)	2nd Band (2nd figure)	3rd Band (multiplier)	4th Band (tolerance)
Black	0	0	10^0	
Brown	1	1	10^1	
Red	2	2	10^2	$\pm 2\%$
Orange	3	3	10^3	
Yellow	4	4	10^4	
Green	5	5	10^5	
Blue	6	6	10^6	
Violet	7	7	10^7	
Gray	8	8	10^8	
White	9	9	10^9	
Gold			10^{-1}	$\pm 5\%$
Silver			10^{-2}	$\pm 10\%$

Ohm's Law



A circuit diagram on a dark blue background. On the left, a green circle contains a white plus sign above a white minus sign. To its right is a white rectangular loop representing a wire.

$$I = \frac{AV}{\rho L}$$

A = Cross-sectional area of wire
 L = length of wire

$$R = \frac{\rho L}{A}$$

Ohm's Law

$$V = RI$$

(remember, R is in Ω
and ρ is in $\Omega.m$)

- The resistor consume energy this energy is consumed as a heat

If the temperature increase the resistivity (ρ) also increase du to the following formula

$$\rho = \rho_0(1 + \alpha(T - T_0))$$







Where α is the **temperature coefficient of resistivity and its unite ($\frac{1}{^\circ\text{C}}$)**

And (T) measured **in kelvin or centigrade**

Can find the resistance from the above formula above

$$R = R_0(1 + \alpha(T - T_0))$$

Electrical sources

	
Voltage source	Current Source
	
Controlled Voltage Source	Controlled Current Source
	
Battery of cells	Single cell


An **electrical source** is a **voltage** or **current generator** capable of supplying energy to a circuit

Examples:

- AA batteries
- 12-Volt car battery
- Wall plug


Ideal voltage source

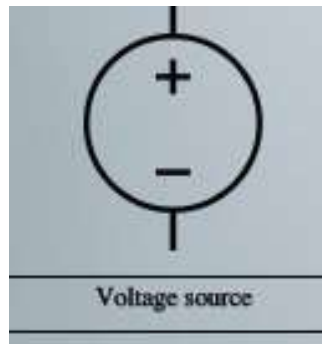An **ideal voltage source** is a circuit element where the **voltage across the source is independent of the current through it.**



Recall Ohm's Law: $V=IR$

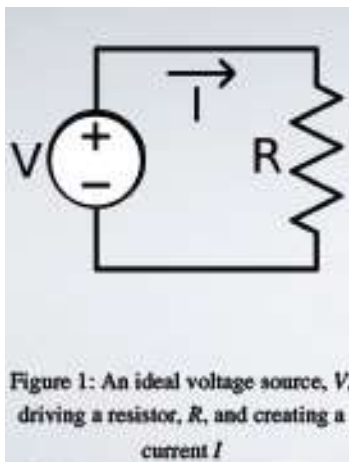
The internal resistance of an ideal voltage source is zero.



If the current through an ideal voltage source is completely determined by the external circuit, it is considered an **independent voltage source**

Ideal current source

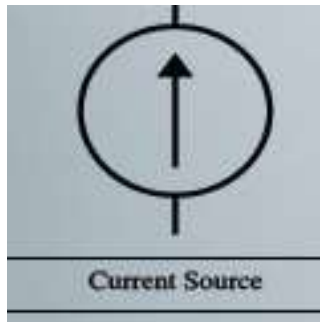An **ideal current source** is a circuit element where the **current through the source is independent of the voltage across it.**





Recall Ohm's Law: $I = V/R$

The internal resistance of an ideal current source is infinite.

If the voltage across an **ideal current source** is completely determined by the external circuit, it is considered an **independent current source**

Dependent Sources

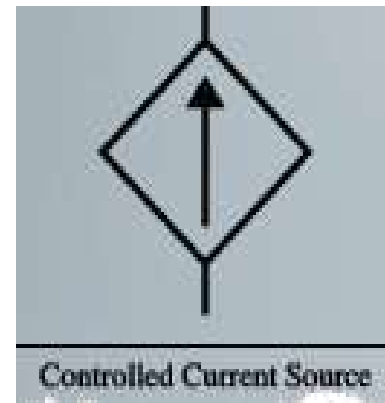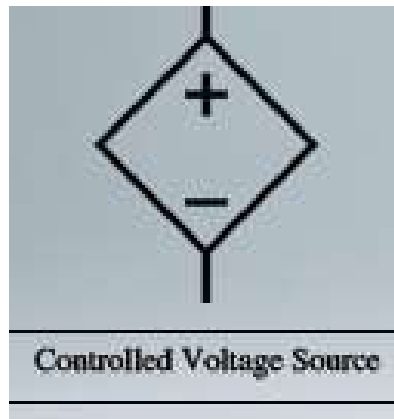
A **dependent** or **controlled** source depends upon a different voltage or current in the circuit




Electric Circuit Design Principles

Resistors in series

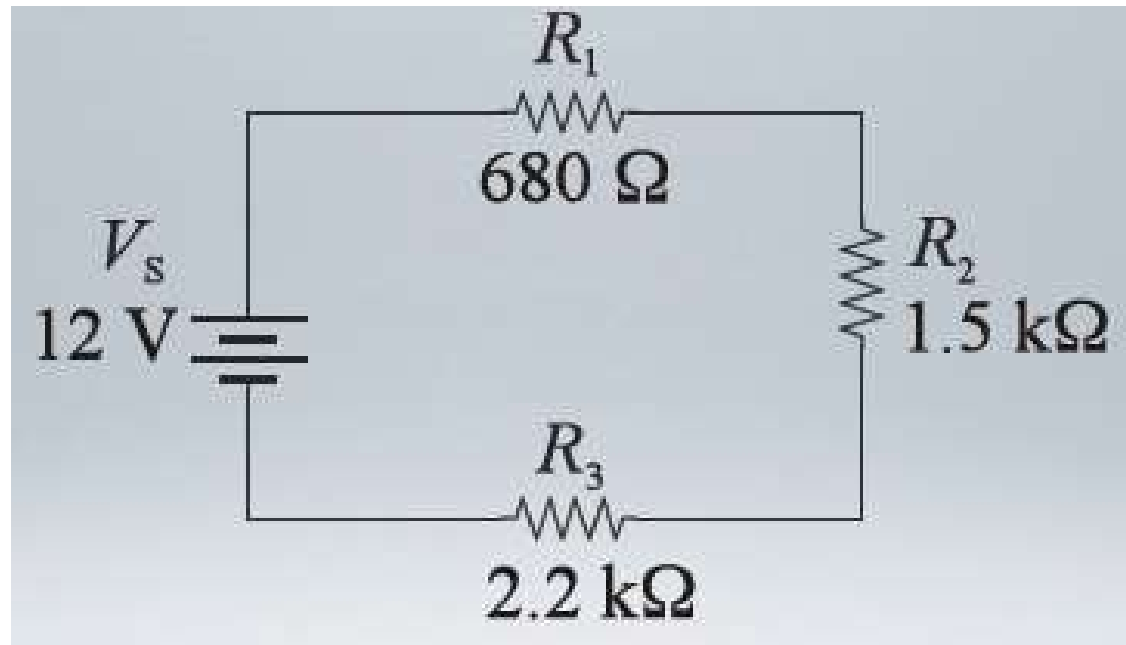The resistors in a series circuit are $680\ \Omega$, $1.5\ \text{k}\Omega$, and $2.2\ \text{k}\Omega$. What is the total resistance?




Series circuits

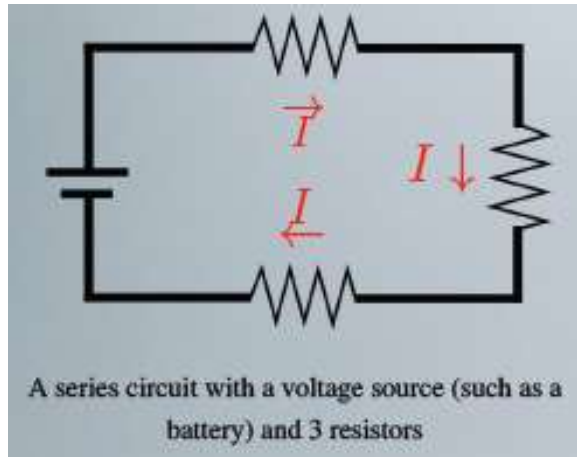


A **series circuit** has only **one current path**

Current through each component is the same

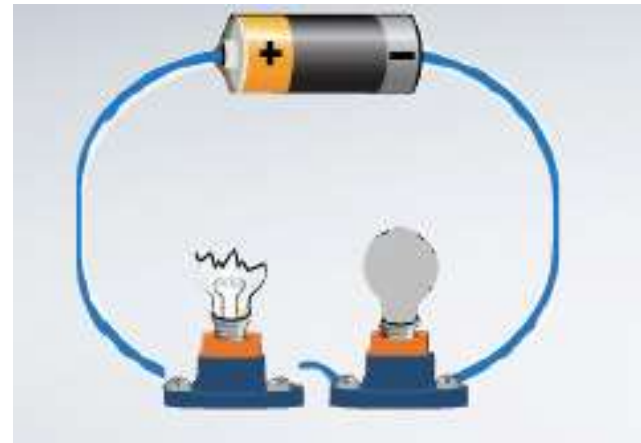
In a series circuit, all elements must function for the circuit to be complete




Multiple elements in a series circuit

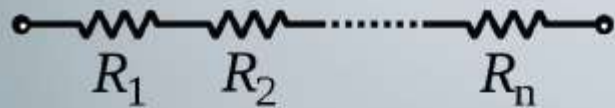


$$R_{total} = R_1 + R_2 + \dots + R_n$$

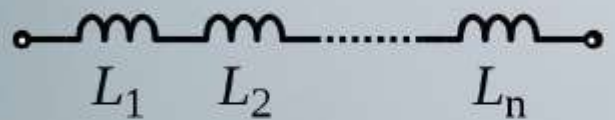

$$L_{total} = L_1 + L_2 + \dots + L_n$$

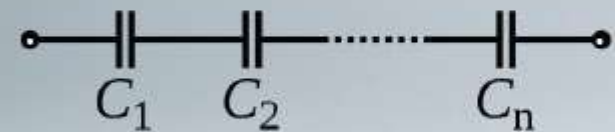

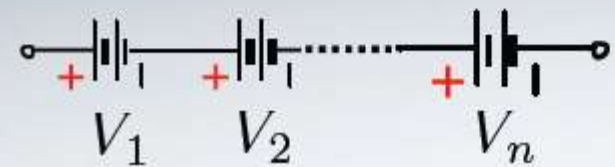
$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$



$$V_{total} = V_1 + V_2 + \dots + V_n$$

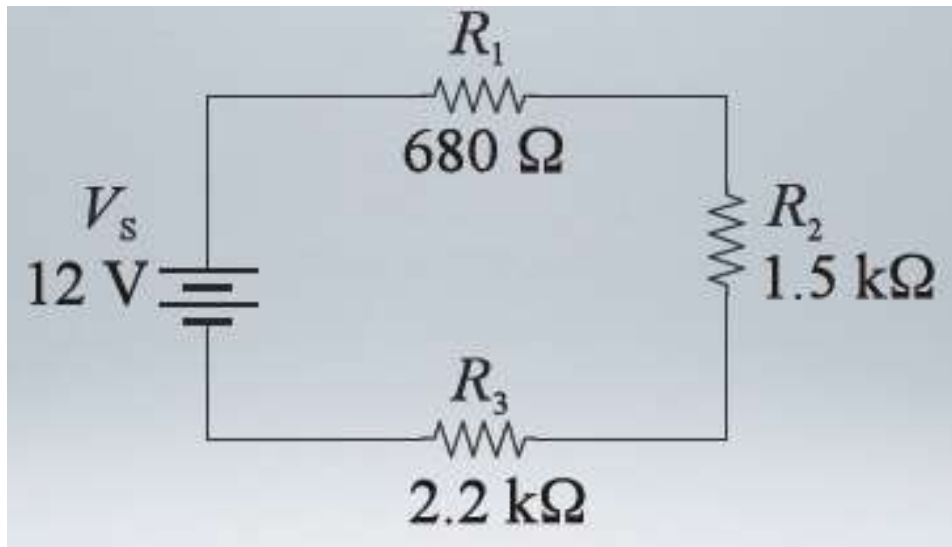Example: Resistors in series

The resistors in a series circuit are $680\ \Omega$, $1.5\ \text{k}\Omega$, and $2.2\ \text{k}\Omega$. What is the total resistance?



$$\begin{aligned}R_{total} &= R_1 + R_2 + R_3 \\ &= 680\Omega + 1500\Omega + 2200\Omega \\ &= 4380\Omega \\ &= 4.38\text{k}\Omega\end{aligned}$$


The current through each resistor?

$$I = \frac{V}{R_{total}} = \frac{12V}{4380\Omega} = 2.74\text{mA}$$

Example: Voltage sources in series


Find the total voltage of the sources shown

$$V_{total} = V_1 + V_2 + V_3 = 27V$$

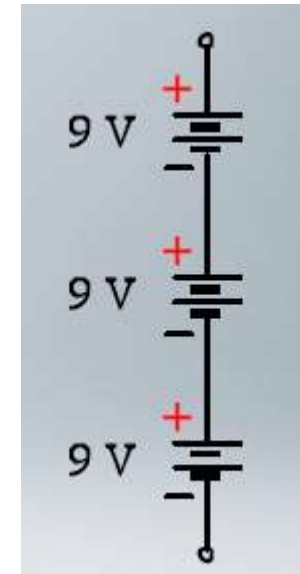


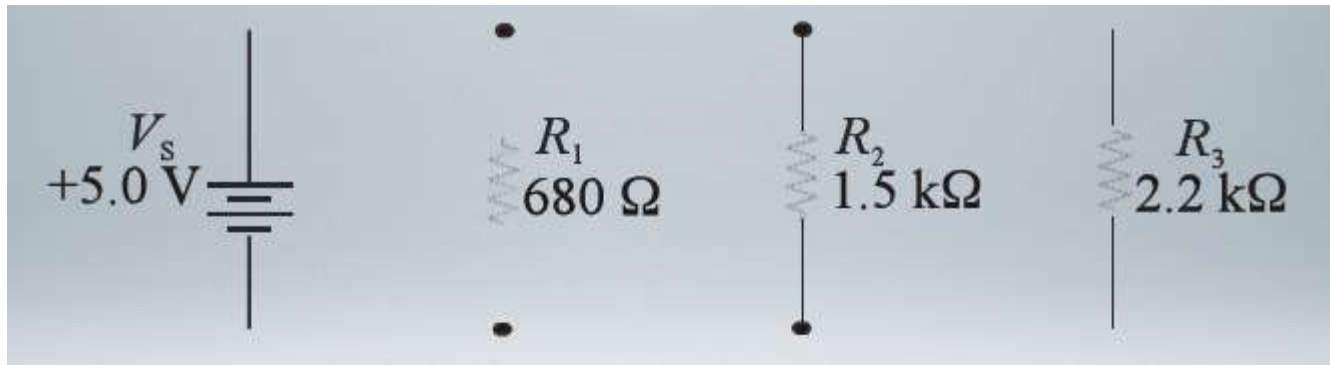Example: Resistors in parallel

The resistors in a parallel circuit are $680\ \Omega$, $1.5\ \text{k}\Omega$, and $2.2\ \text{k}\Omega$.
What is the total resistance?





Parallel circuits

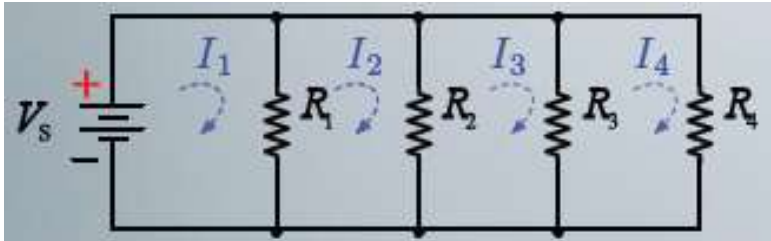



A **parallel circuit** has **more than one current path** branching from the energy source

Voltage across each pathway is the same

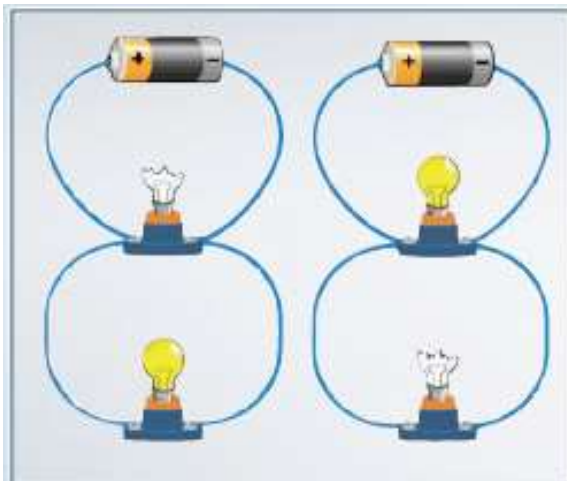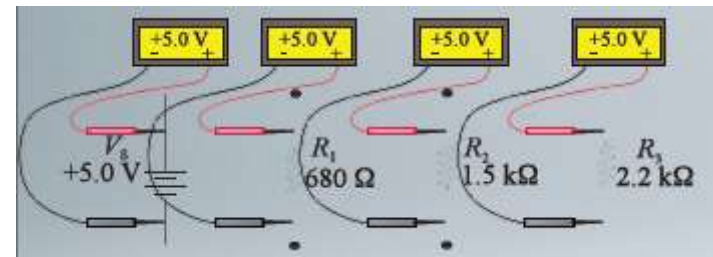

In a parallel circuit, separate current paths function independently of one another


Multiple elements in a parallel circuit

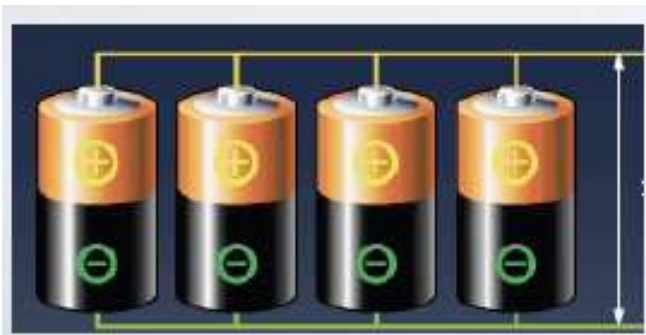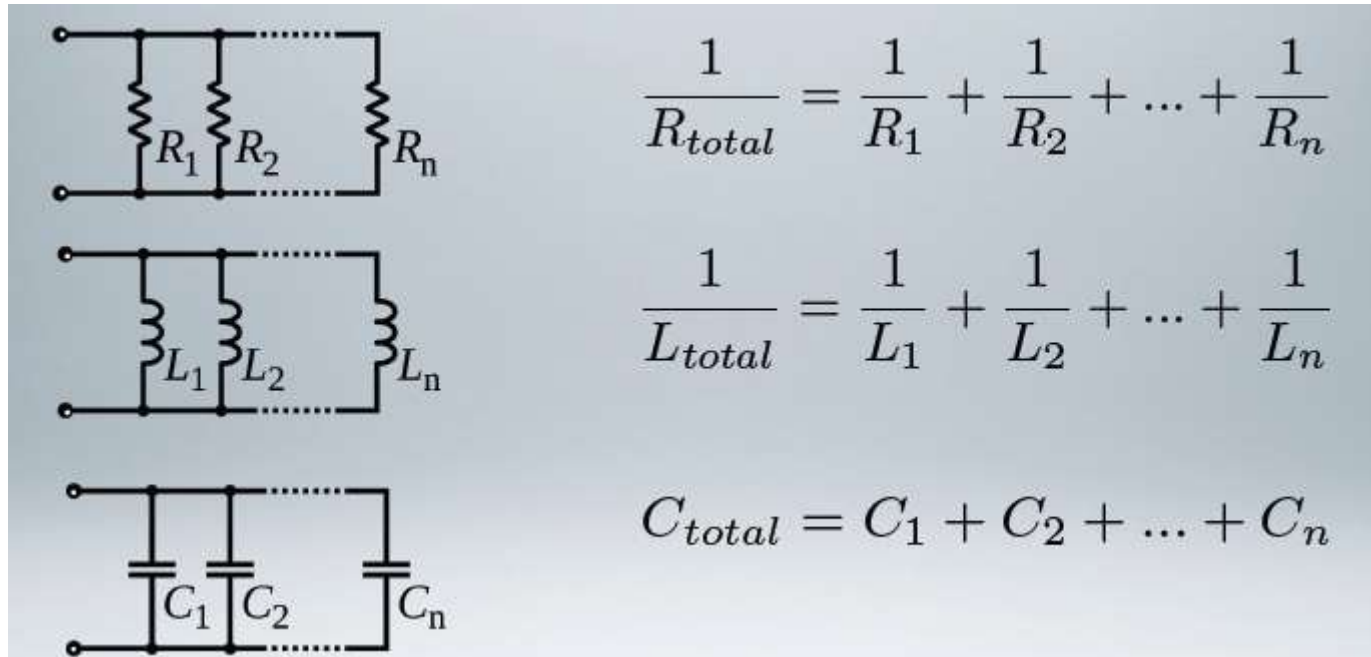

For parallel voltage sources, the voltage is the same across all batteries, but the current supplied by each element is a fraction of the total current

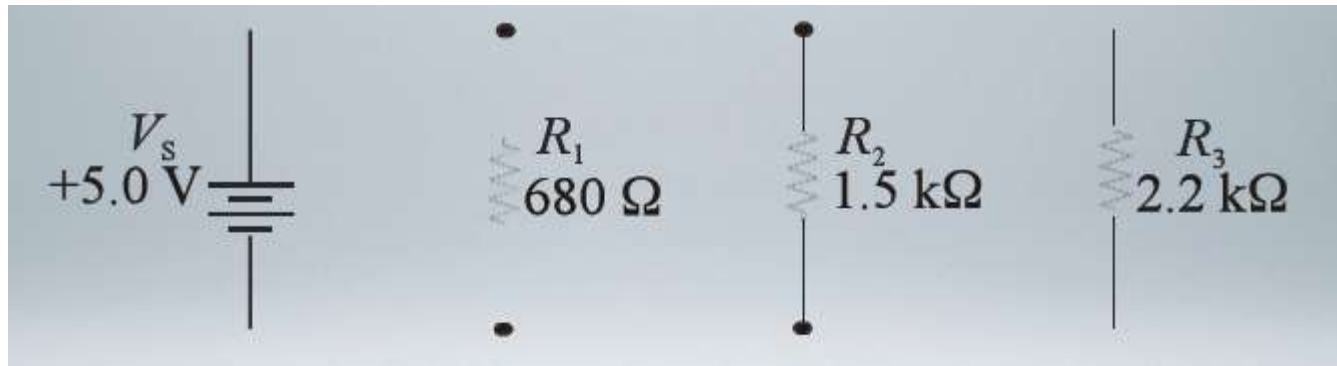Example: Resistors in parallel

The resistors in a parallel circuit are $680\ \Omega$, $1.5\ \text{k}\Omega$, and $2.2\ \text{k}\Omega$. What is the total resistance?



$$\begin{aligned} R_{total} &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \\ &= 386\ \Omega \end{aligned}$$

Voltage across each resistor?

Dissipated power?


Current through each resistor?

Circuit Definitions

- **Node** – any point where 2 or more circuit elements are connected together
 - Wires usually have negligible resistance
 - Each node has one voltage (w.r.t. ground)
- **Branch** – a circuit element between two nodes
- **Loop** – a collection of branches that form a closed path returning to the same node without going through any other nodes or branches twice


Example

- How many nodes, branches & loops?

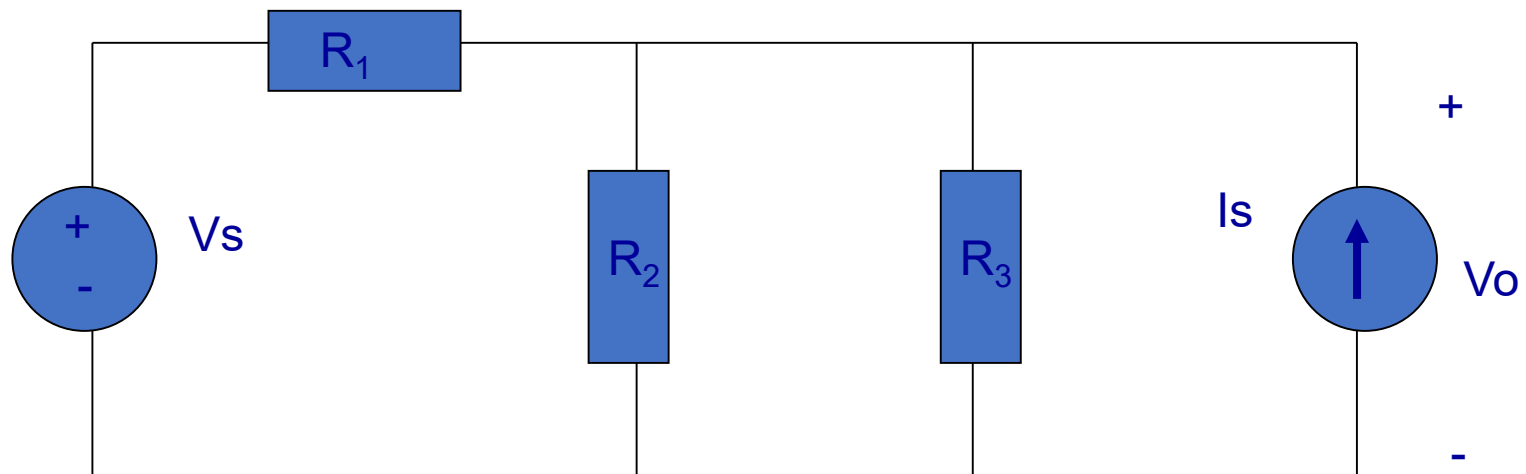


Example

- Three nodes

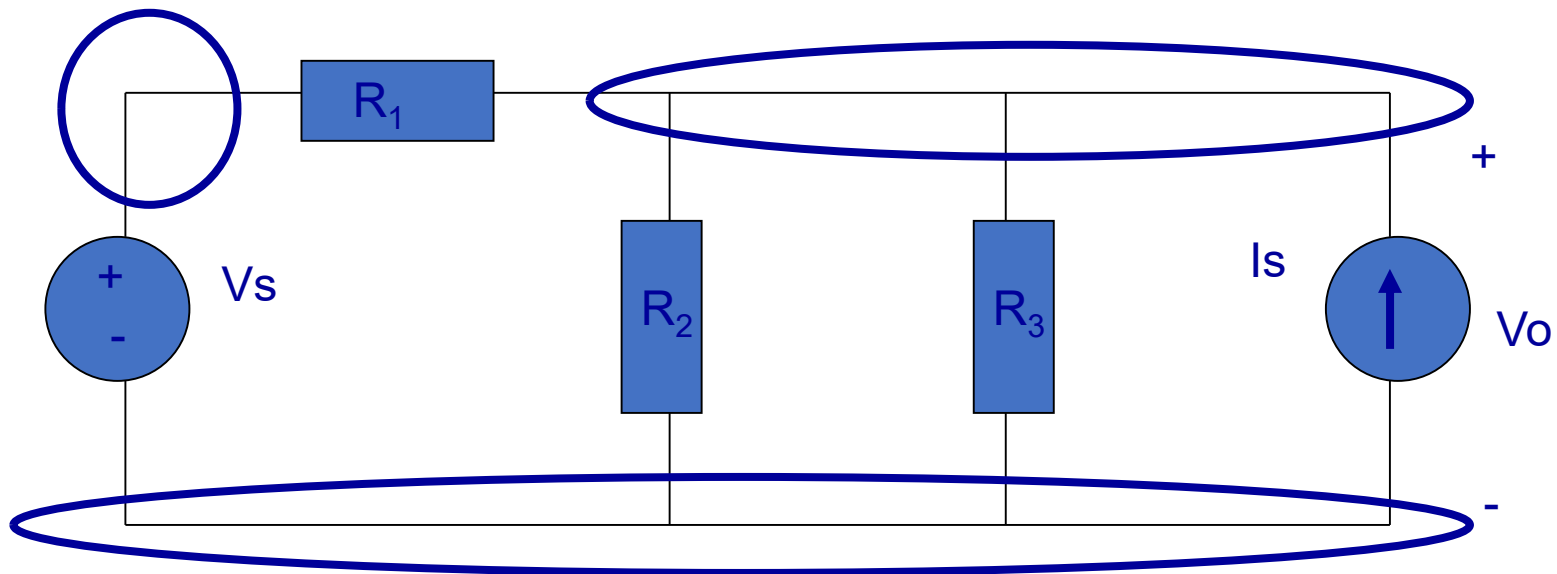


Example

- 5 Branches

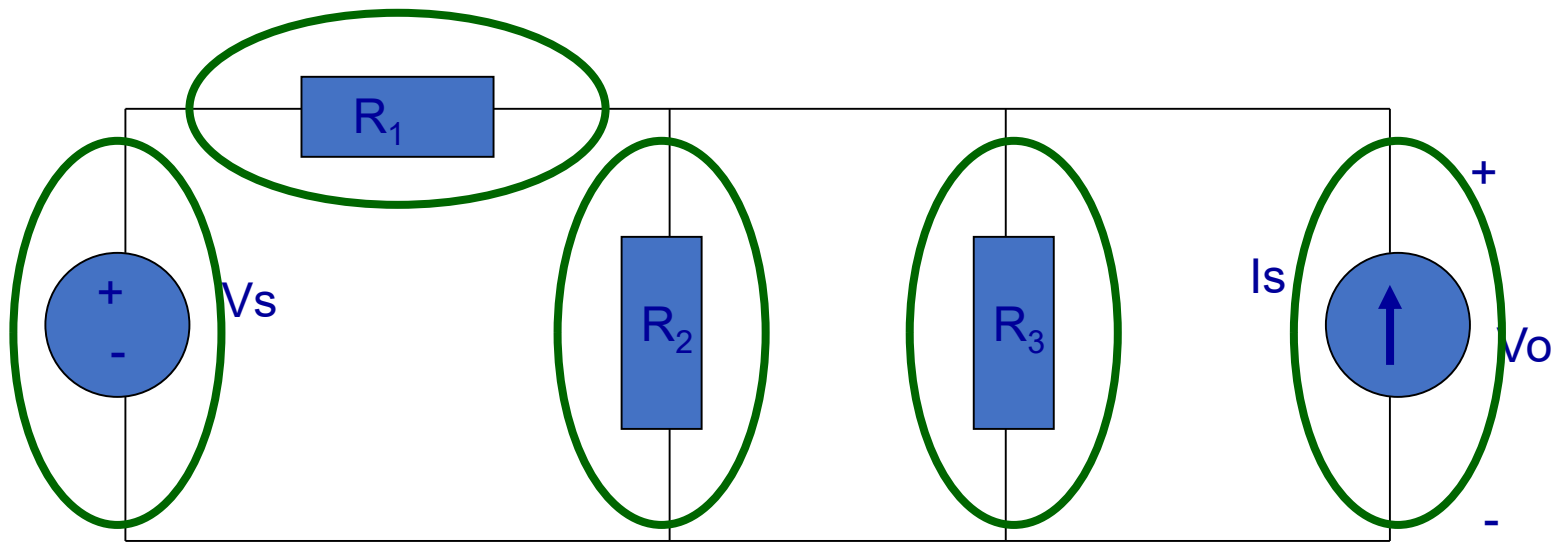

Example

- Three Loops, if starting at node A

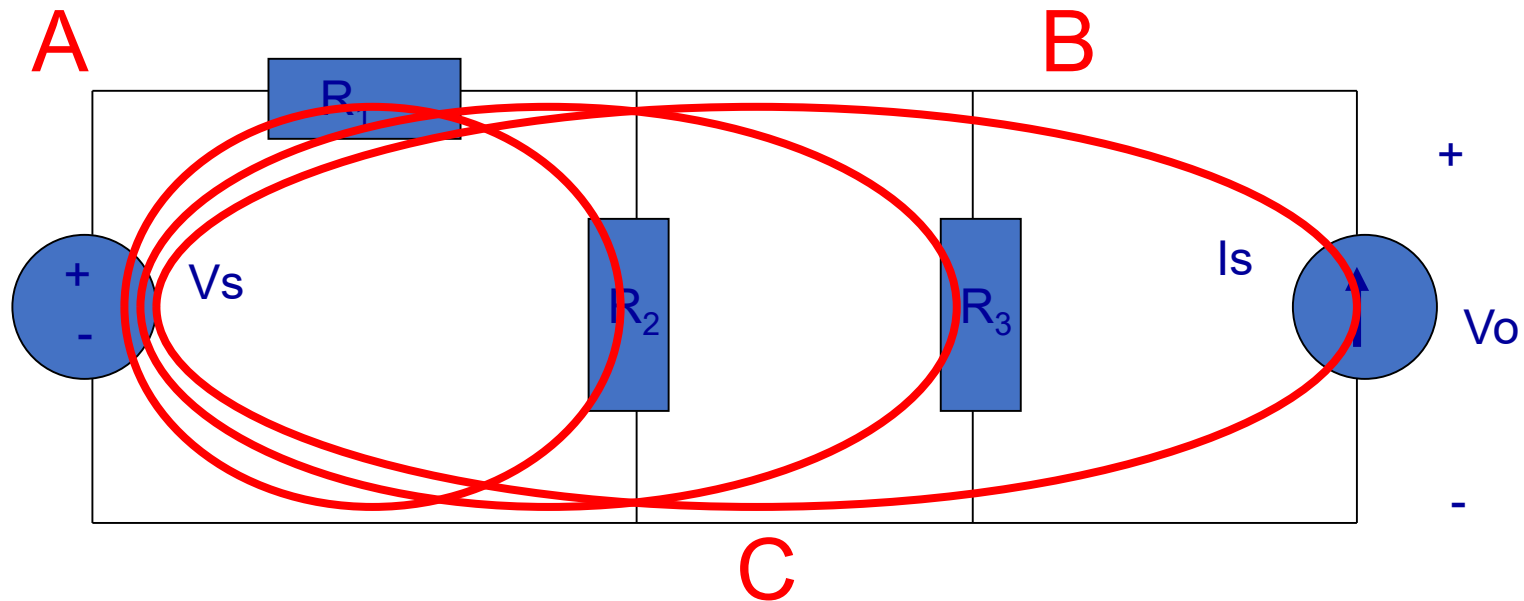


Kirchoff's Voltage Law (KVL)

- The algebraic sum of voltages around each loop is zero
 - Beginning with one node, add voltages across each branch in the loop (if you encounter a + sign first) and subtract voltages (if you encounter a – sign first)
- Σ voltage drops - Σ voltage rises = 0
- Or Σ voltage drops = Σ voltage rises

Example

- Kirchoff's Voltage Law around 1st Loop

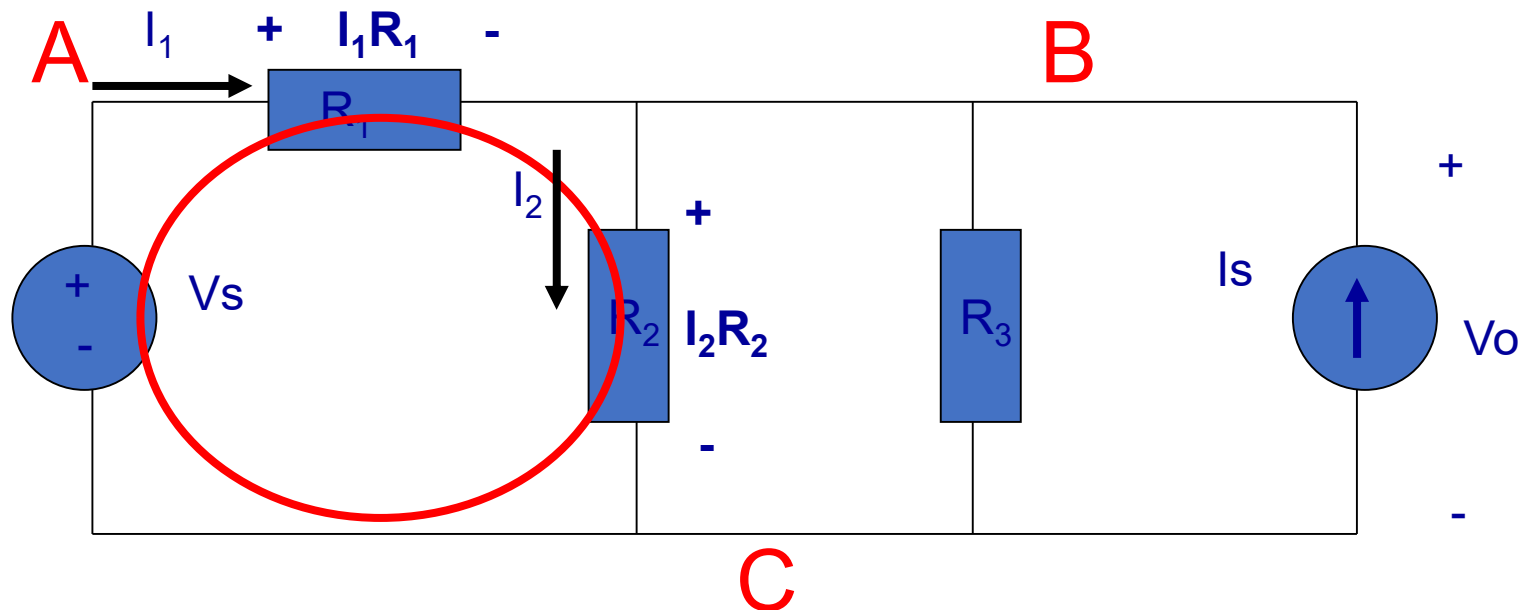


Assign current variables and directions

Use Ohm's law to assign voltages and polarities consistent with passive devices (current enters at the + side)

Example


- Kirchoff's Voltage Law around 1st Loop

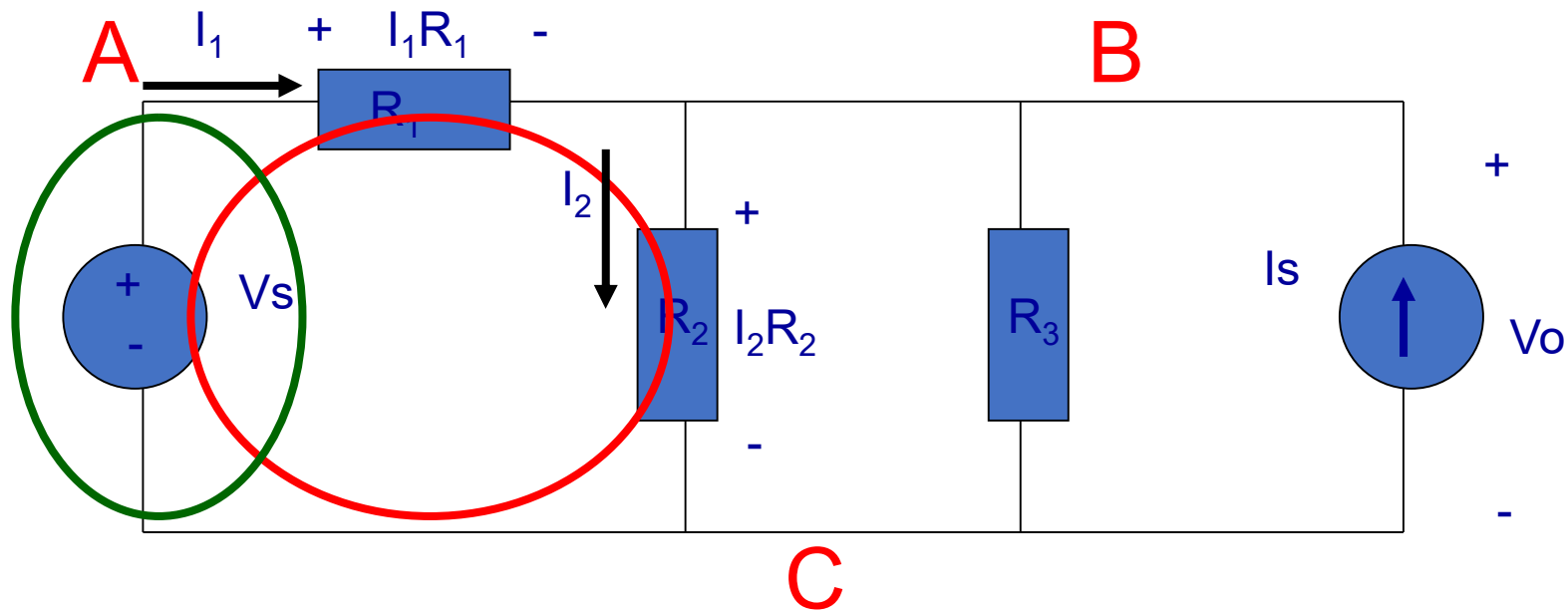

$$-I_1 R_1 - I_2 R_2 + V_s = 0$$


Circuit Analysis

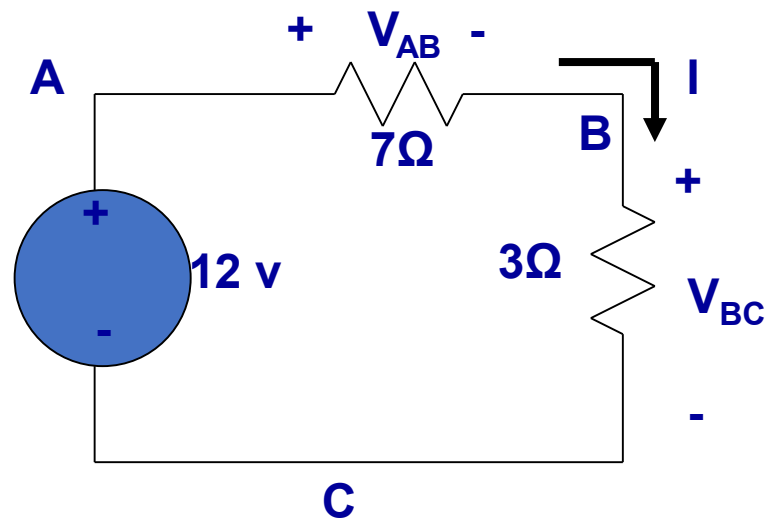- When given a circuit with sources and resistors having fixed values, you can use Kirchhoff's two laws and Ohm's law to determine all branch voltages and currents



Series Resistors

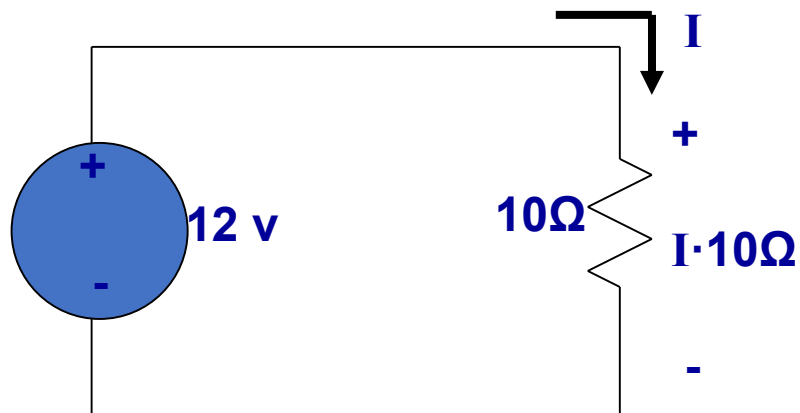- KVL: $+I \cdot 10\Omega - 12\text{ v} = 0$, So $I = 1.2\text{ A}$
- From the viewpoint of the source, the 7 and 3 ohm resistors in series are equivalent to the 10 ohms




Circuit Analysis

- By Ohm's law: $V_{AB} = I \cdot 7\Omega$ and $V_{BC} = I \cdot 3\Omega$
- By KVL: $V_{AB} + V_{BC} - 12\text{ v} = 0$
- Substituting: $I \cdot 7\Omega + I \cdot 3\Omega - 12\text{ v} = 0$
- Solving: $I = 1.2\text{ A}$

Since $V_{AB} = I \cdot 7\Omega$ and $V_{BC} = I \cdot 3\Omega$

And $I = 1.2\text{ A}$

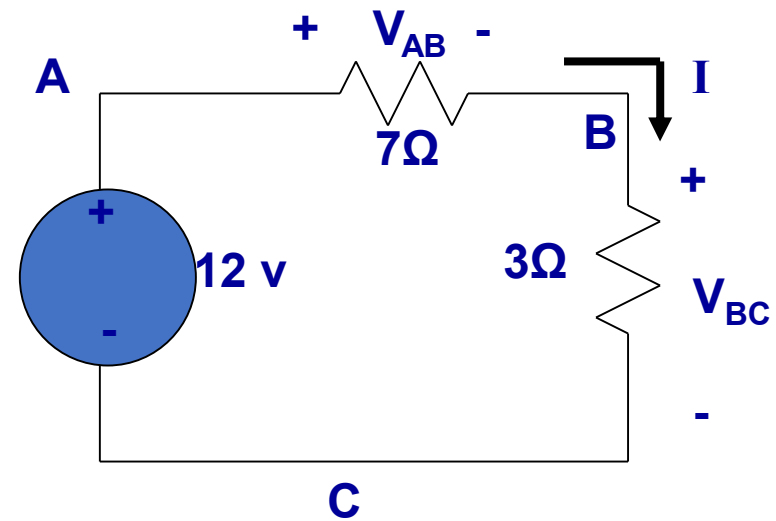So $V_{AB} = 8.4\text{ v}$ and $V_{BC} = 3.6\text{ v}$




Kirchoff's Current Law (KCL)

- The algebraic sum of currents entering a node is zero
 - Add each branch current entering the node and subtract each branch current leaving the node
- $\Sigma \text{ currents in} - \Sigma \text{ currents out} = 0$
- Or $\Sigma \text{ currents in} = \Sigma \text{ currents out}$

Example


- Kirchoff's Current Law at B

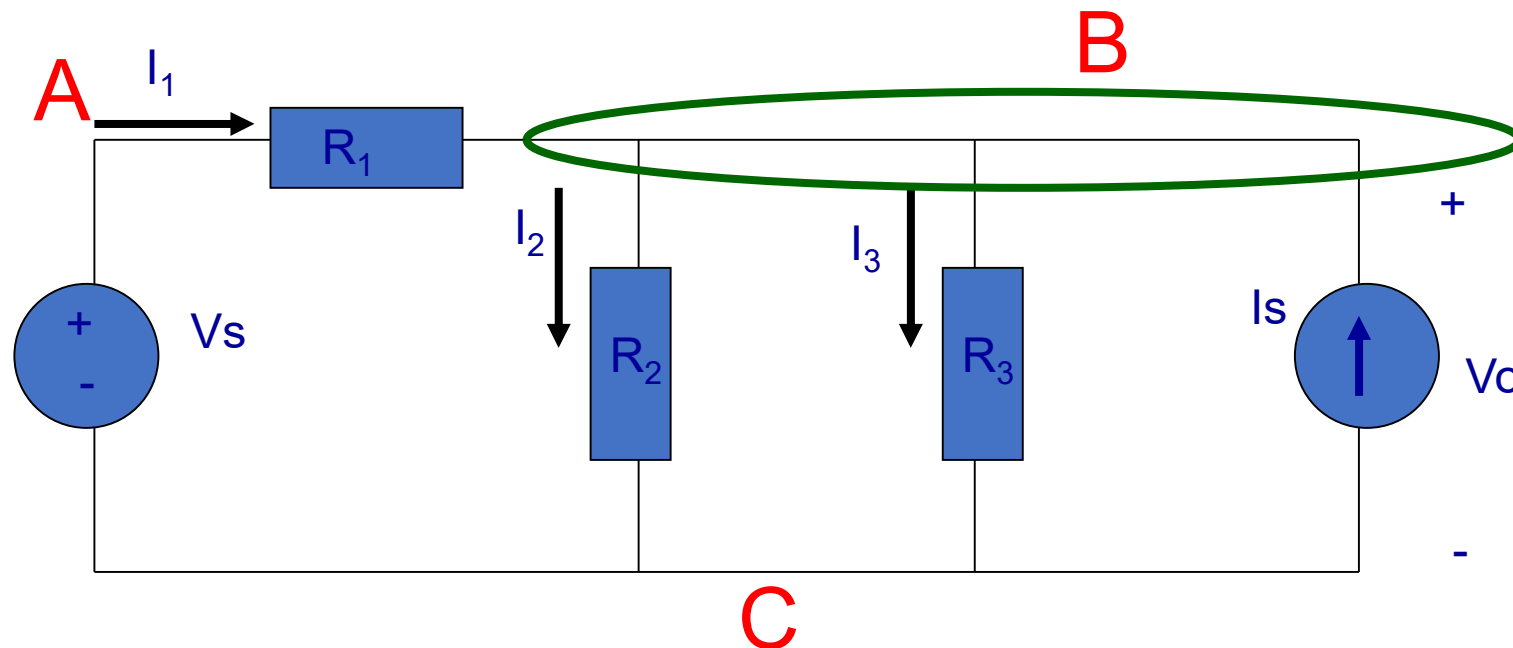

Assign current variables and directions

Add currents in, subtract currents out: $I_1 - I_2 - I_3 + I_s = 0$

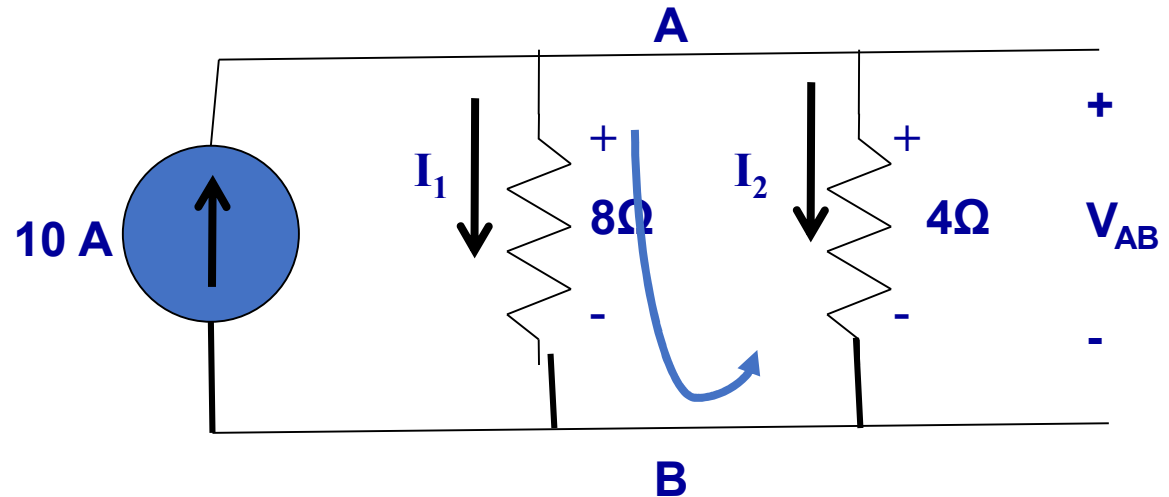Example: Find V_{AB} for the Figure below



By KVL:

$$-I_1 \cdot 8\Omega + I_2 \cdot 4\Omega = 0 \quad \longrightarrow \quad I_2 = 2 \cdot I_1$$

By KCL:

$$10A = I_1 + I_2$$

Substituting:


$$10A = I_1 + 2 \cdot I_1 = 3 \cdot I_1$$

So

$$I_1 = 3.33 A \quad \longrightarrow \quad I_2 = 6.67 A$$

And $V_{AB} = I_2 \cdot 4 = 26.33$ volts

Another Way

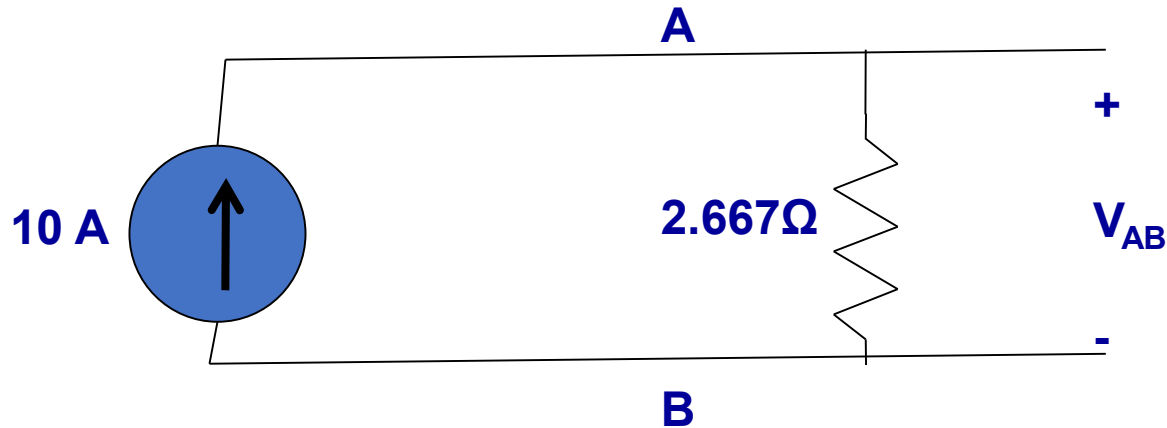

By Ohm's Law: $V_{AB} = 10 \text{ A} \cdot 2.667 \text{ } \Omega$

So $V_{AB} = 26.67 \text{ volts}$

Replacing two parallel resistors (8 and 4 Ω) by one equivalent one produces the same result from the viewpoint of the rest of the circuit.