



LECTURE 03
KIRCHHOFF'S CURRENT LAWS
KIRCHHOFF'S VOLTAGE LAWS-
DEPENDENT VOLTAGE SOURCES
DEPENDENT CURRENT SOURCES



Topics

- ▶ Kirchhoff's Voltage Law
- ▶ Fundamental Laws of Electric Circuits
- ▶ Dependent Voltage Source
- ▶ Dependent Current Source



Objectives


- ▶ Apply Kirchhoff's voltage law
- ▶ Recognize invalid circuits
- ▶ Use the fundamental laws to analyze electric circuits
- ▶ Recognize the symbol of a dependent source
- ▶ Distinguish between the four possible types of dependent sources
- ▶ Analyze circuits that contain dependent sources



What is the terms node ?

A nodes is a point where two or more elements ioin


3- nodes shown in the figure

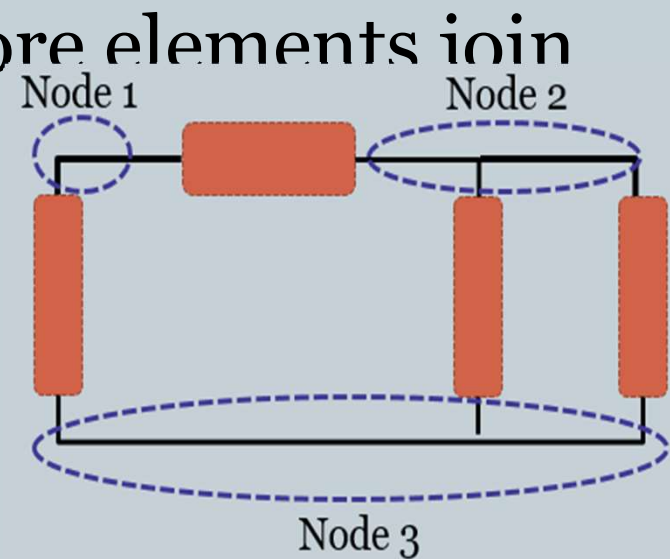

What is the terms loop?

Any closed path in the circuit.


3- loops shown in figure

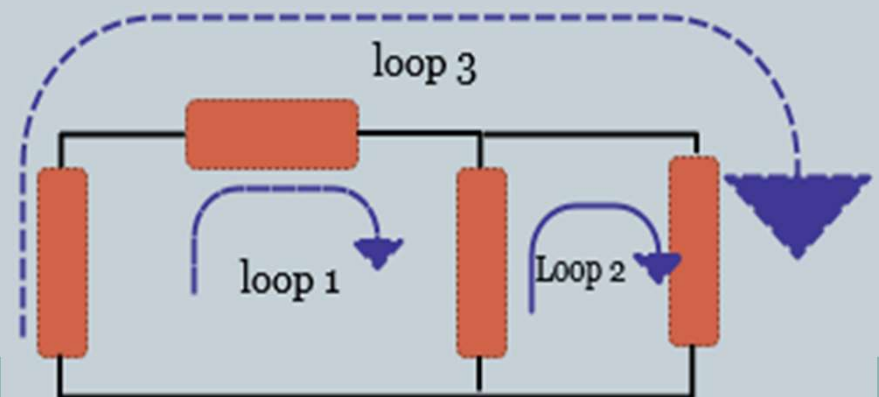



Kirchhoff's Current Law (KCL)

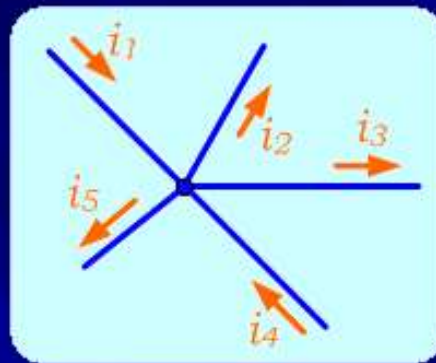The sum of currents *entering* a node (interconnection of two or more branches) is equal to the sum of currents *leaving* that node



$$i_1 + i_4 = i_2 + i_3 + i_5$$

Equivalent Statement of KCL:


The algebraic sum of currents entering a node (currents entering the node is taken as positive) is equal to zero

$$i_1 - i_2 - i_3 + i_4 - i_5 = 0$$



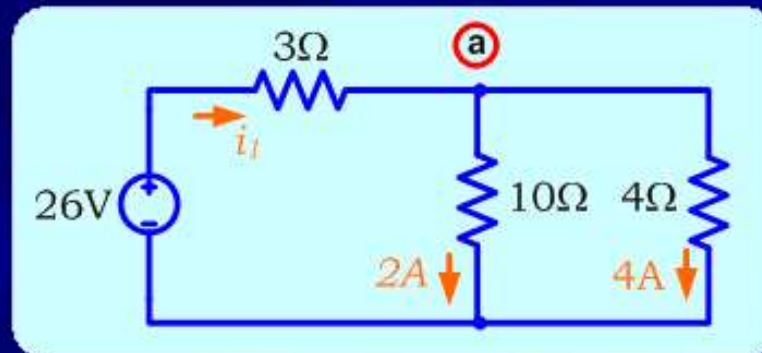Example 1

Calculate the unknown current in the following circuit




Solution:

$$\text{KCL at node a} \Rightarrow i_1 = 2 + 4 = 6 \text{ A}$$

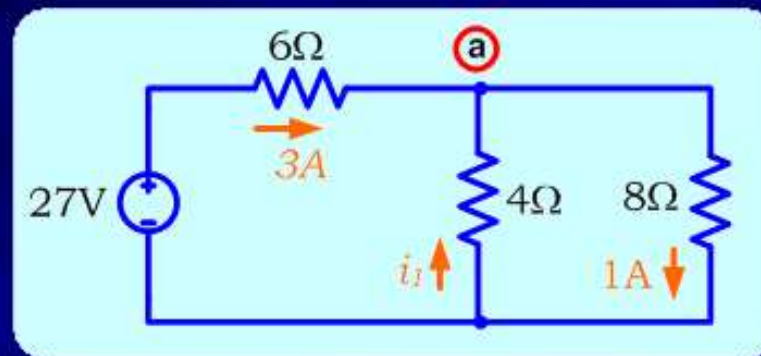Example 2

Calculate the unknown current in the following circuit



Solution:

$$\text{KCL at node a} \Rightarrow 3 + i_1 = 1 \Rightarrow i_1 = -2A$$


Alternatively,

$$\text{KCL at node a} \Rightarrow 3 + i_1 - 1 = 0 \Rightarrow i_1 = -2A$$



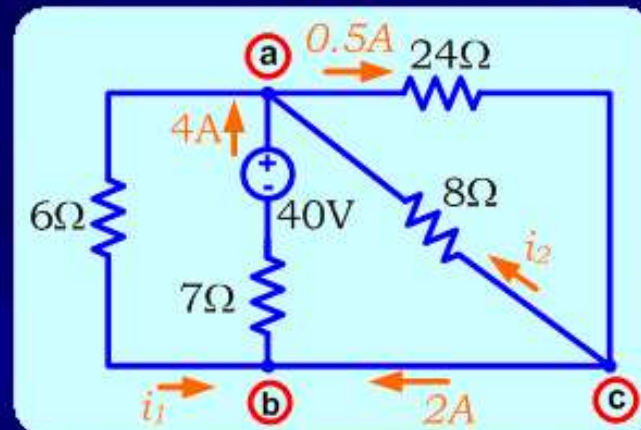Example 3

Calculate the unknown currents in the following circuit



Solution:

$$\text{KCL at node b} \quad \Rightarrow \quad i_1 - 4 + 2 = 0 \quad \Rightarrow \quad i_1 = 2A$$


$$\text{KCL at node c} \quad \Rightarrow \quad 0.5 - i_2 - 2 = 0 \quad \Rightarrow \quad i_2 = -1.5A$$

$$\text{Check KCL at node a} \quad \Rightarrow \quad -i_1 + 4 + i_2 - 0.5 = -(2) + 4 + (-1.5) - 0.5 = -4 + 4 = 0$$



Supernode

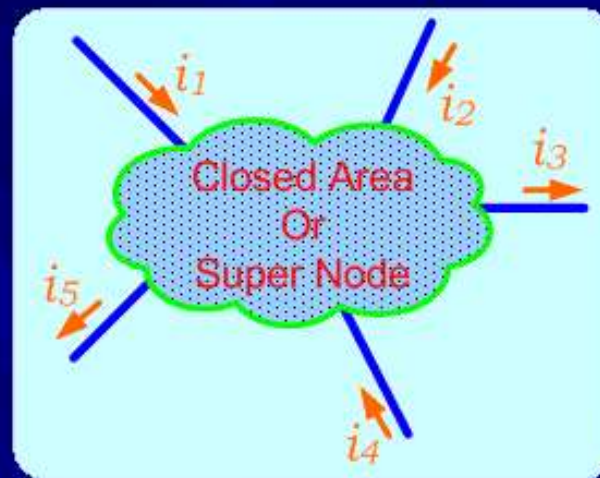KCL is also applicable to a *closed area* (super node)




The algebraic sum of currents entering a super node is equal to zero

$$i_1 + i_2 - i_3 + i_4 - i_5 = 0$$



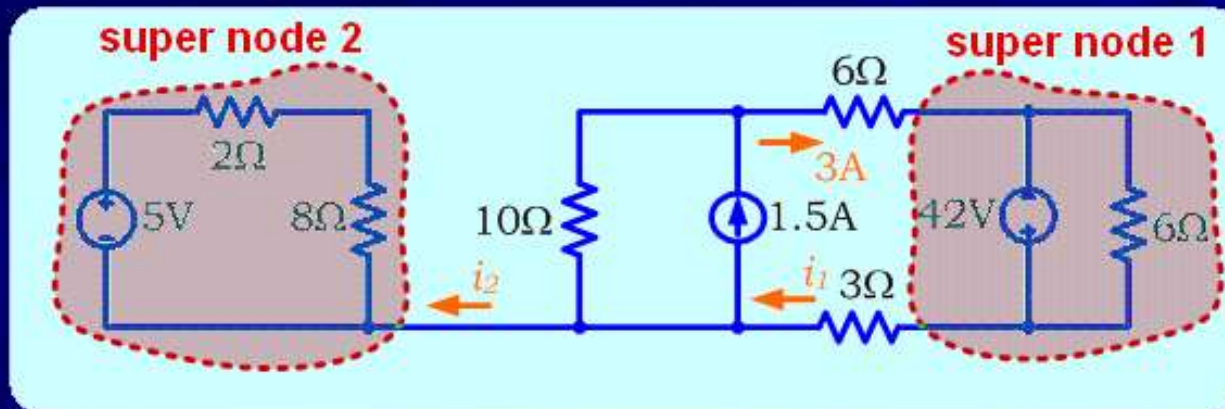Example 4

Calculate the unknown currents in the circuit shown below



Solution:


$$\text{KCL at super node 1} \Rightarrow 3 - i_1 = 0 \Rightarrow i_1 = 3A$$

$$\text{KCL at super node 2} \Rightarrow i_2 = 0 \Rightarrow i_2 = 0A$$



Self Test

In the circuit shown below, calculate:

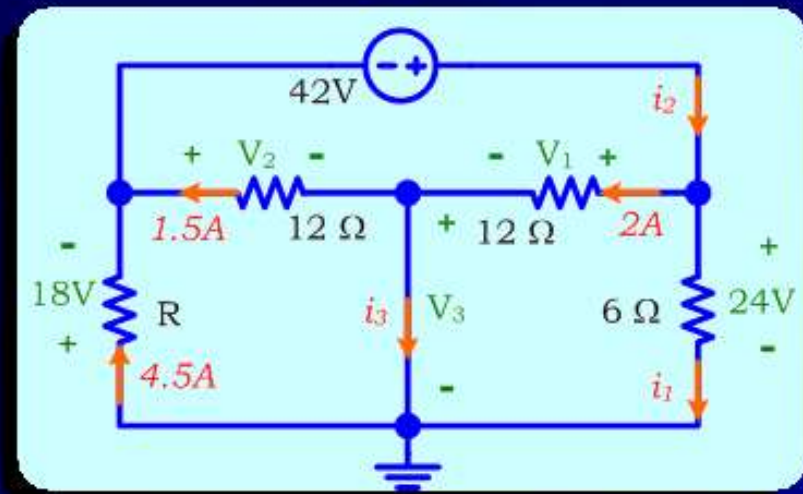


(a) i_1

- A $i_1 = 144A$
- B $i_1 = -4A$
- C $i_1 = 4A$
- D $i_1 = 1/4 A$
- E $i_1 = -1/4 A$



Kirchhoff's Voltage Law (KVL)

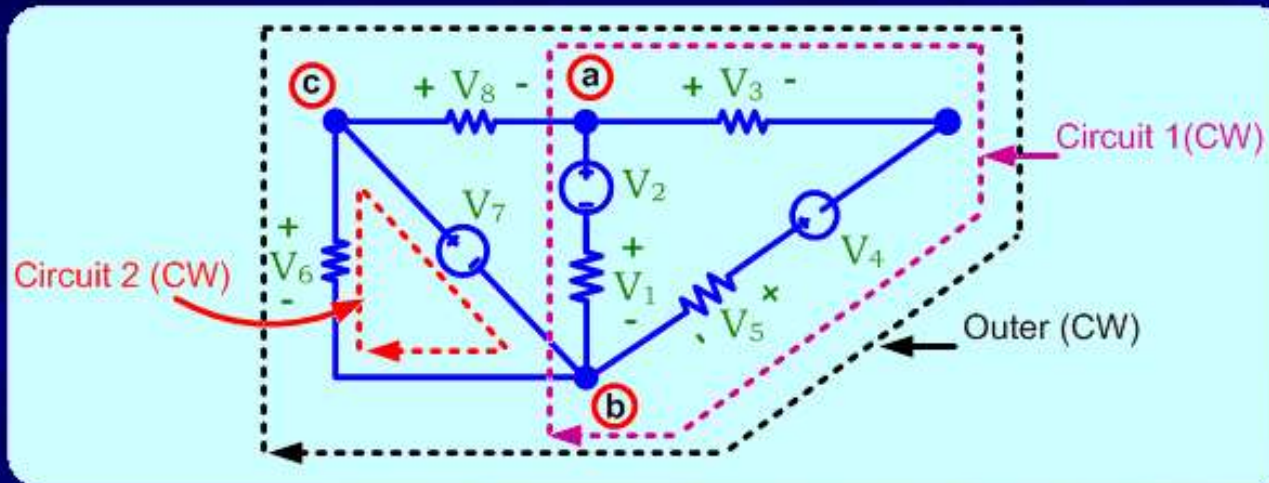The *algebraic* sum of voltages around *any closed* circuit is equal to zero



$$\text{KVL around circuit 1 (CW)} \Rightarrow -v_1 - v_2 + v_3 - v_4 + v_5 = 0 \dots\dots\dots (1)$$

$$\text{KVL around circuit 1 (CCW)} \Rightarrow -v_5 + v_4 - v_3 + v_2 + v_1 = 0 \dots\dots\dots (2) \text{ [Same as (1)]}$$

CW = Clockwise direction & CCW = Counter clockwise direction


$$\text{KVL around outer circuit (CW)} \Rightarrow -v_6 + v_8 + v_3 - v_4 + v_5 = 0 \dots\dots\dots (3)$$

$$\text{KVL around circuit 2 (CW)} \Rightarrow -v_6 + v_7 = 0 \Rightarrow v_6 = v_7 \text{ [Parallel elements]}$$



Alternate statement for KVL

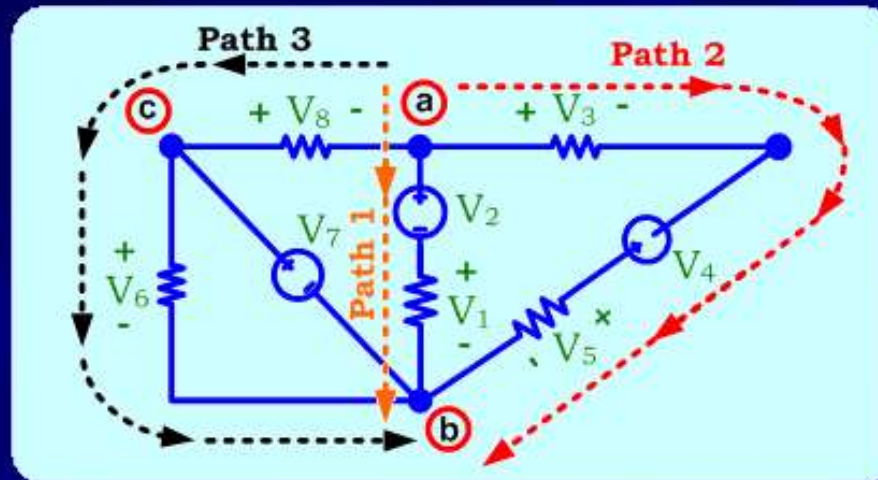The *algebraic* sum of voltages between two nodes is *independent* of the path taken from the first node to the second node




KVL $Node\ a \xrightarrow{path\ 1\ \&\ 2} Node\ b \Rightarrow +v_2 + v_1 = +v_3 - v_4 + v_5 \dots \dots \dots (4)$ Same as (1) in the previous slide

KVL $Node\ a \xrightarrow{path\ 2\ \&\ 3} Node\ b \Rightarrow +v_3 - v_4 + v_5 = -v_8 + v_6 \dots \dots \dots (5)$ Same as (3) in the previous slide

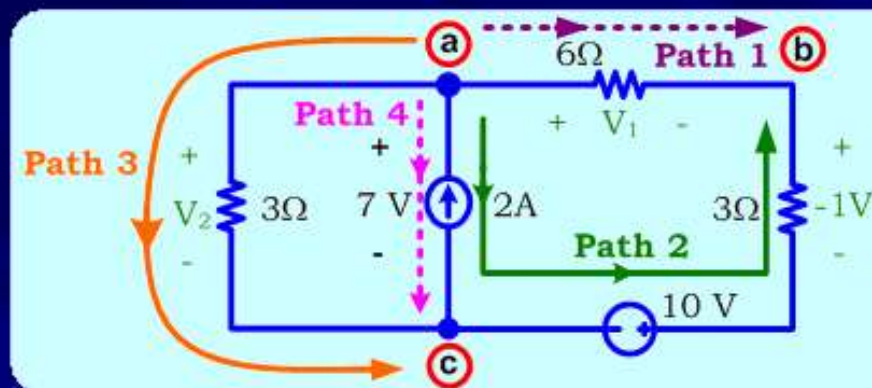Example 1

Calculate the unknown voltages in the given circuit



Solution:

Applying KVL

$$\text{Right-hand circuit (CW)} \Rightarrow -(7) + v_1 + (-1) + 10 = 0 \Rightarrow v_1 = -2V$$

$$\text{Right-hand circuit (CCW)} \Rightarrow +(7) - (10) - (-1) - v_1 = 0 \Rightarrow v_1 = -2V$$

$$\text{Node } a \xrightarrow{\text{path 1 \& 2}} \text{Node } b \Rightarrow +v_1 = +(7) - (10) - (-1) \Rightarrow v_1 = -2V$$

Same answer
in all cases

$$\text{Left-hand circuit (CW)} \Rightarrow +(7) - (v_2) = 0 \Rightarrow v_2 = 7V$$

$$\text{Node } a \xrightarrow{\text{path 3 \& 4}} \text{Node } c \Rightarrow +v_2 = +7 \Rightarrow v_2 = 7V$$

Same answer
in both cases




Fundamental Laws of Electric Circuits

1. Ohm's Law, KCL and KVL are the fundamental laws of electric circuits
2. *All* the fundamental laws of electric circuits *must be satisfied*
3. If a given circuit violates *at least one* of the fundamental laws, the circuit is *not valid*



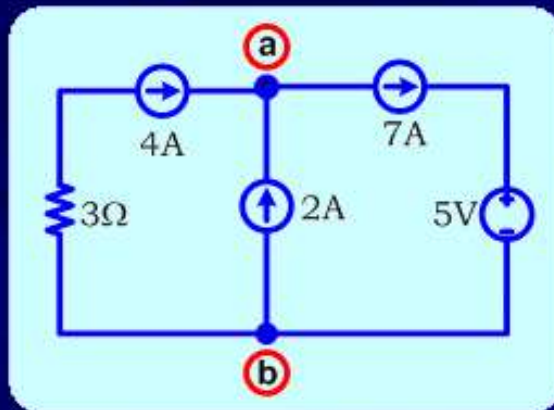Example 2

All the given circuits below are invalid, why?




(a)

(a) KCL at node a

$$\Rightarrow 4 + 2 = 7$$

\Rightarrow KCL not satisfied

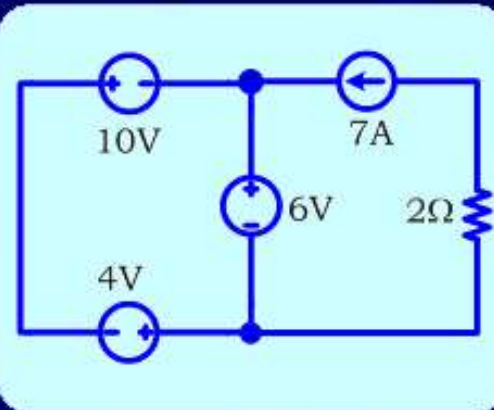


(b)

(b) KVL around left hand

$$\Rightarrow +10 + 6 + 4 = 0$$

$$\Rightarrow 20 = 0$$

\Rightarrow KVL not satisfied

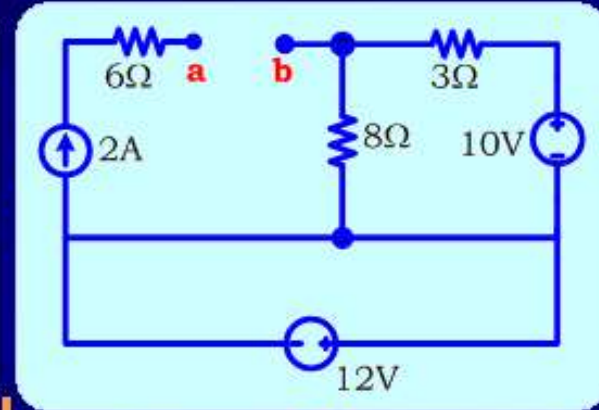

(c)

(c) KCL at node a

$$\Rightarrow 2 = 0$$

\Rightarrow KCL not satisfied

KVL around lower part of the circuit $\Rightarrow 12 = 0$

\Rightarrow KVL not satisfied

Example 3

In the given circuit calculate the unknown quantities

Solution:


$$\text{KCL at node a} \Rightarrow 3 = 2 + I_1 \Rightarrow I_1 = 1\text{A}$$

$$\text{Ohm's Law} \Rightarrow v_2 = +7I_1 = 7 \times 1 = 7\text{V}$$

$$\begin{aligned} \text{KVL around left hand circuit} &\Rightarrow v_1 + 10 - v_2 = 0 \\ &\Rightarrow v_1 + 10 - 7 = 0 \\ &\Rightarrow v_1 = -3\text{V} \end{aligned}$$

$$\text{Ohm's Law} \Rightarrow v_3 = -3 \times 4 = -12\text{V}$$

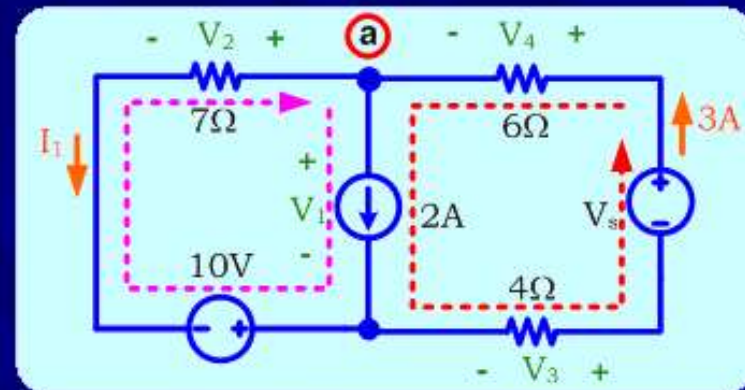
$$\begin{aligned} \text{KVL around right hand circuit} &\Rightarrow +v_4 + v_1 - v_3 - v_s = 0 \\ &\Rightarrow +(3 \times 6) + v_1 - v_3 - v_s = 0 \quad (\text{Ohm's Law } v_4 = 18\text{V}) \\ &\Rightarrow +18 + (-3) - (-12) - v_s = 0 \\ &\Rightarrow v_s = 27\text{V} \end{aligned}$$






Ideal Dependent Sources

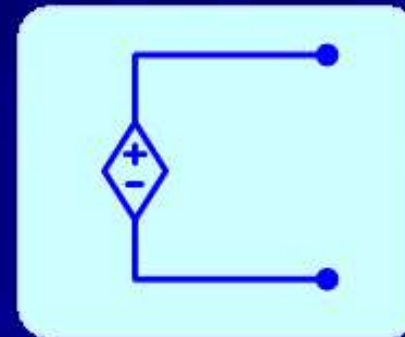A voltage source whose voltage depends on another voltage or current is called a *dependent voltage source*




A current source whose current depends on another voltage or current is called a *dependent current source*

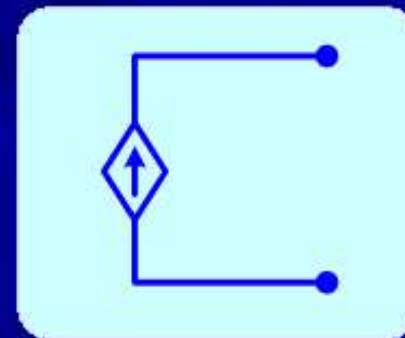




Example 4

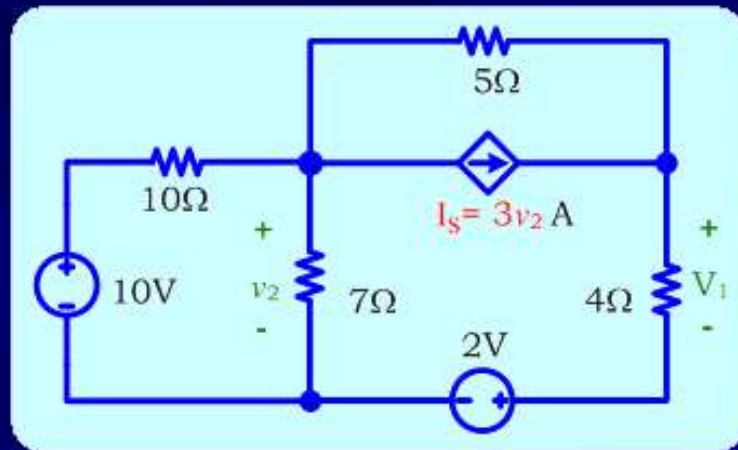

(a)

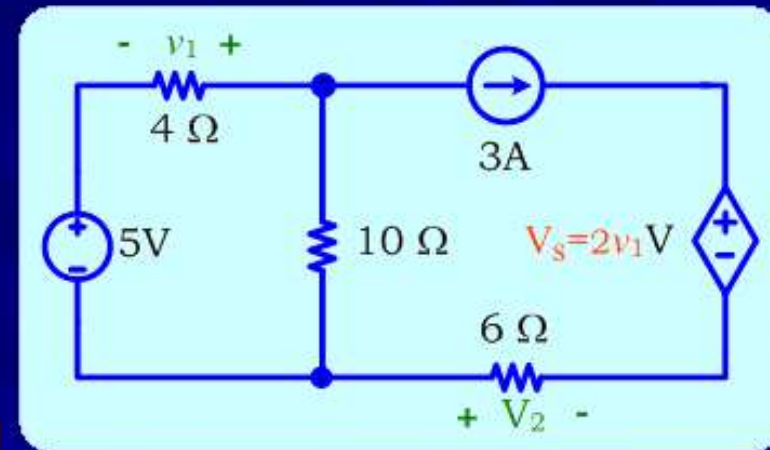Circuit (a) I_S depends on v_2
 $\Rightarrow I_S$ is *voltage dependent* current source



(b)

Circuit (b) V_S depends on v_1
 $\Rightarrow V_S$ is *voltage dependent* voltage source



Types of Dependent Sources

Four possible types of dependent sources

1. Voltage dependent voltage source (it is a *voltage source* that depends on another voltage)
2. Current dependent voltage source (it is a *voltage source* that depends on another current)
3. Voltage dependent current source (it is a *current source* that depends on another voltage)
4. Current dependent current source (it is a *current source* that depends on another current)

Example 5

(a) Calculate the value of the dependent current source

(b) Show that the power generated is equal to the power dissipated

Solution: (a)

KCL at node a

$$\Rightarrow -i - i_2 + 4i = 0$$

$$\Rightarrow i_2 = 3i \quad (1)$$

KVL around left hand circuit

$$\Rightarrow -v_2 + v_1 + 20 = 0$$

$$\Rightarrow -(40i_2) + (20i) + 20 = 0 \quad (\text{Ohm's Law})$$


$$\Rightarrow -(40 \times 3i) + 20i + 20 = 0 \quad [\text{using (1)}]$$

$$\Rightarrow -120i + 20i + 20 = 0$$

$$\Rightarrow i = \frac{20}{100} = \frac{1}{5} \text{ A}$$

Value of dependent current source \Rightarrow
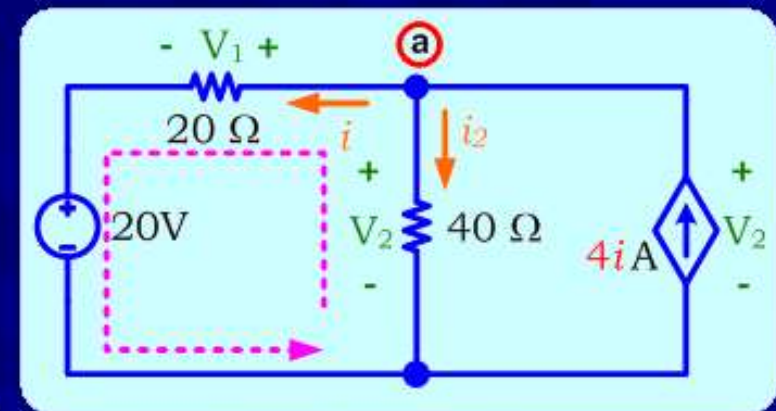
$$4i = 4 \times \frac{1}{5} = \frac{4}{5} \text{ A}$$



Example 5 (Contd...)

- (a) Calculate the value of the dependent current source
- (b) Show that the power generated is equal to the power dissipated

Solution: (b)

From previous slide part (a) $\Rightarrow i = \frac{1}{5} \text{ A}$


$$P_{20V} = +20i = +20 \times \frac{1}{5} = \frac{20}{5} = 4 \text{ W}$$

$$P_{20\Omega} = +iv_1 = +\left(\frac{1}{5}\right)(20 \times \frac{1}{5}) = +\left(\frac{1}{5}\right)(4) = \frac{4}{5} \text{ W}$$

$$i_2 = 3i = \frac{3}{5} \text{ A} \quad \& \quad v_2 = +40i_2 = +40 \times \frac{3}{5} = 24 \text{ V}$$

$$P_{40\Omega} = +i_2v_2 = +\frac{3}{5} \times 24 = \frac{72}{5} \text{ W}$$
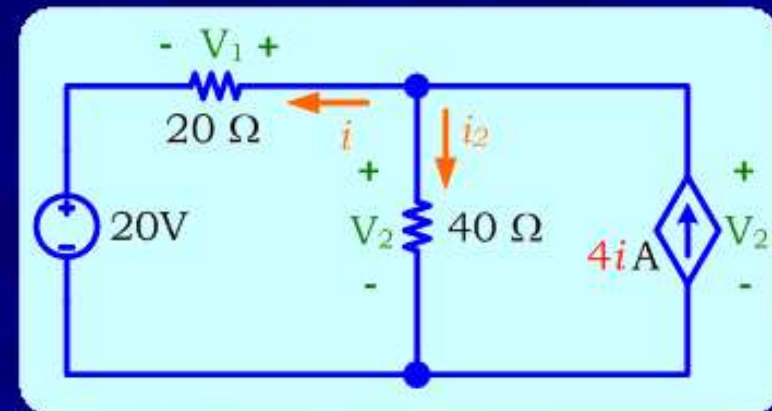
$$P_{4iA} = -(4i)v_2 = -\left(\frac{4}{5}\right) \times 24 = -\frac{96}{5} = -19.2 \text{ W}$$



$$\sum P_{dis} = 4 + \frac{4}{5} + \frac{72}{5} = \frac{96}{5} = 19.2 \text{ W}$$

$$\sum P_{gen} = 19.2 \text{ W}$$

$$\therefore \sum P_{dis} = \sum P_{gen} = 19.2 \text{ W}$$