

## The Voltage Divider Rule


The total voltage across the *series* resistors  $R_1, R_2, \dots, R_N$  is  $V$

$$i = \frac{V}{R_{eq}} = \frac{V}{\sum_{i=1}^N R_i}$$

$$v_x = iR_x = \frac{V}{\sum_{i=1}^N R_i} R_x = \left( \frac{R_x}{\sum_{i=1}^N R_i} \right) V$$

$$\text{VDR} \Rightarrow v_x = \left( \frac{R_x}{\sum_{i=1}^N R_i} \right) V$$
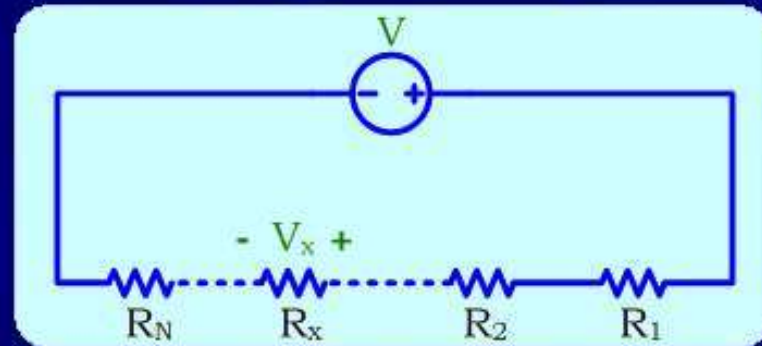
$$\therefore v_{resistor} = \frac{\text{resistor}}{\text{sum}} \times (\text{total voltage})$$




The VDR is valid for *any* number of resistors in *series*



### Example 3

Calculate the unknown voltages

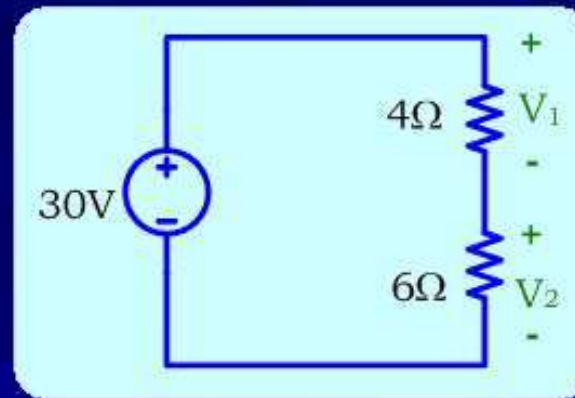

Solution

$$\text{VDR} \Rightarrow v_1 = \frac{4}{4+6} \times 30 = 12\text{V}$$



$$\text{VDR} \Rightarrow v_2 = \frac{6}{4+6} \times 30 = 18\text{V}$$

VDR  $\Rightarrow$  Higher voltage drop across the higher resistance



## Example 4

Calculate the unknown voltages

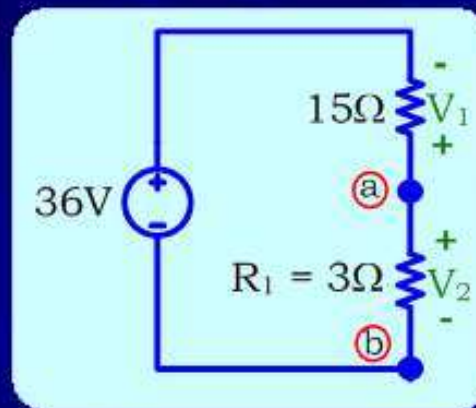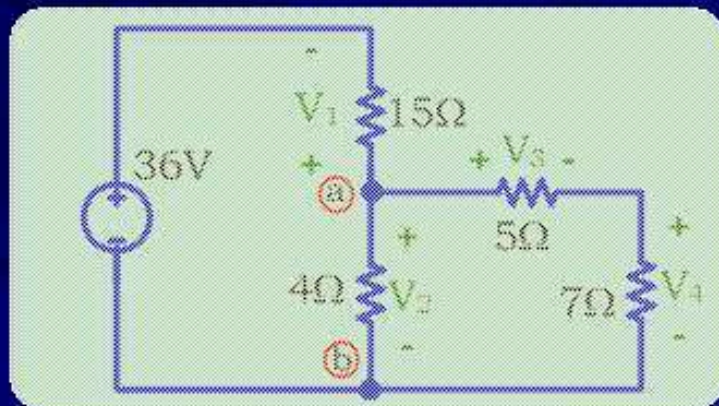

Solution



$$5 + 7 = 12\Omega \Rightarrow R_1 = \frac{4 \times 12}{4 + 12} = 3\Omega$$

$$\text{VDR} \Rightarrow v_1 = -\frac{15}{15+3} \times 36 \quad (\text{a minus sign is required here. Why?}) \Rightarrow v_1 = -30\text{V}$$

$$\text{VDR} \Rightarrow v_2 = \frac{3}{15+3} \times 36 \Rightarrow v_2 = 6\text{V}$$

$$\text{Check: KVL} \Rightarrow -36 - v_1 + v_2 = -36 - (-30) + (6) = -36 + 30 + 6 = 0$$

## Example 4 (Contd...)

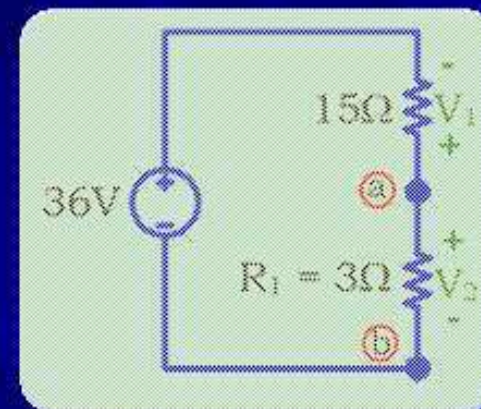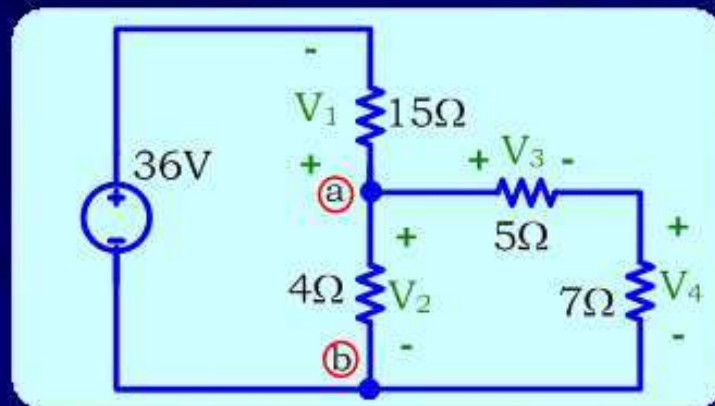

From previous slide

$$v_1 = -30\text{V}$$

$$v_2 = 6\text{V}$$

$$\text{VDR} \Rightarrow v_3 = \frac{5}{5+7} \times v_2 = \frac{5}{12} \times 6 \Rightarrow v_3 = 2.5\text{V}$$

$$\text{VDR} \Rightarrow v_4 = \frac{7}{5+7} \times v_2 = \frac{7}{12} \times 6 \Rightarrow v_4 = 3.5\text{V}$$





## The Current Divider Rule

The total current entering into the *parallel* combination of resistors  $R_1$  &  $R_2$  is  $I$

$$V = IR_{eq} = I \frac{R_1 R_2}{R_1 + R_2}$$


$$I_1 = \frac{V}{R_1} \quad \& \quad I_2 = \frac{V}{R_2}$$

$$I_1 = \frac{1}{R_1} \times \frac{R_1 R_2}{R_1 + R_2} I \Rightarrow I_1 = \frac{R_2}{R_1 + R_2} I \dots \dots (1)$$

Similarly  $I_2 = \frac{R_1}{R_1 + R_2} I \dots \dots (2)$

CDR  $\Rightarrow$   $I = \frac{\text{other resistor sum}}{\text{sum}} \times \text{total current}$

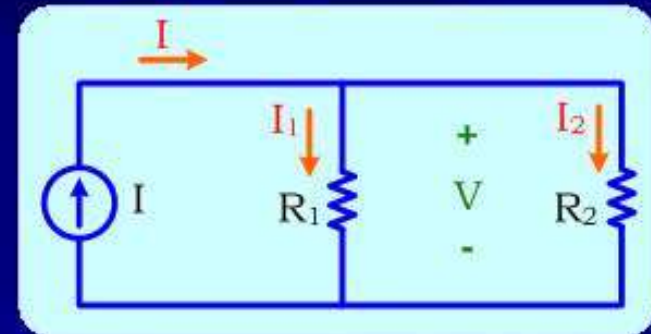CDR applies to *only two* resistors in *parallel*



nt

## Example 5

- (a) Use CDR to calculate  $I_1$  and  $I_2$   
(b) Verify your results by checking KCL


Solution

(a) CDR  $\Rightarrow I_1 = \frac{2}{2+5} \times 3 \Rightarrow I_1 = \frac{6}{7} \text{ A}$

CDR  $\Rightarrow I_2 = \frac{5}{2+5} \times 3 \Rightarrow I_2 = \frac{15}{7} \text{ A}$

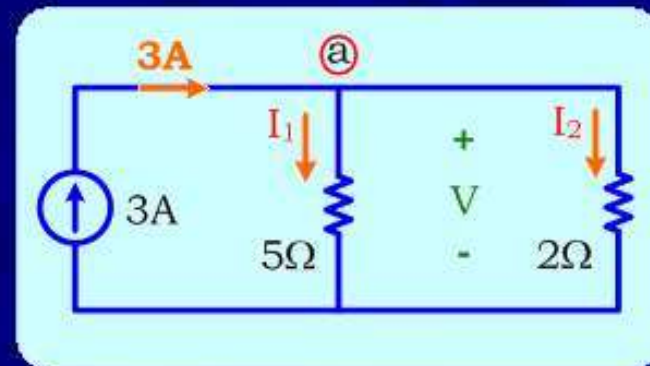
(b) KCL at node a  $\Rightarrow I_s - I_1 - I_2 = 3 - \frac{6}{7} - \frac{15}{7} = 3 - \frac{21}{7} = 0$  (KCL verified)

CDR  $\Rightarrow$  Higher current passes through the lower resistance


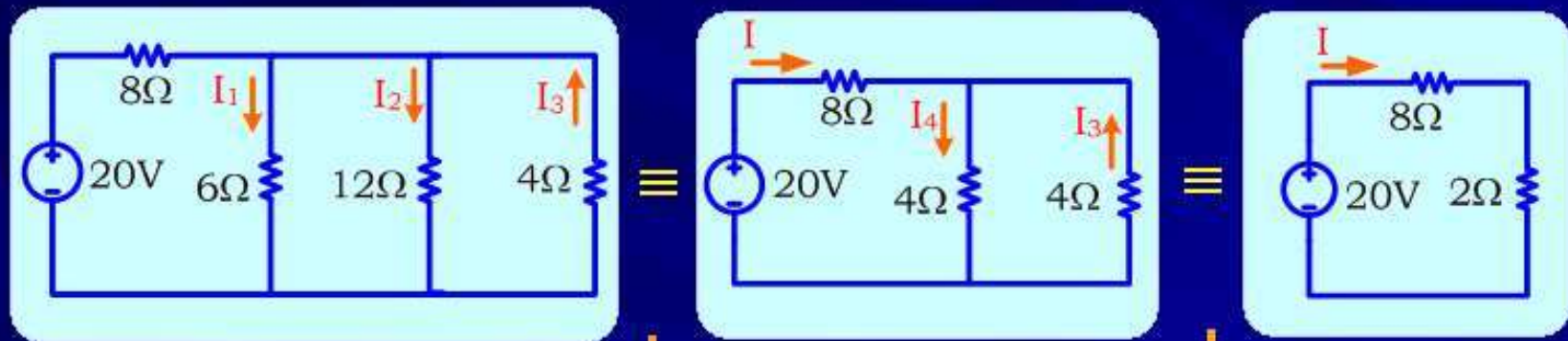
## Example 6

Use CDR to calculate  $I_1$ ,  $I_2$  and  $I_3$



$6\Omega$  &  $12\Omega$  are in parallel  $\Rightarrow \frac{6 \times 12}{6 + 12} = \frac{72}{18} = 4\Omega$


$4\Omega$  &  $4\Omega$  are in parallel  $\Rightarrow \frac{4 \times 4}{4 + 4} = \frac{16}{8} = 2\Omega$

$\therefore R_{eq} = 8 + 2 = 10\Omega$

$\Rightarrow I = \frac{20}{R_{eq}} = \frac{20}{10} = 2A$
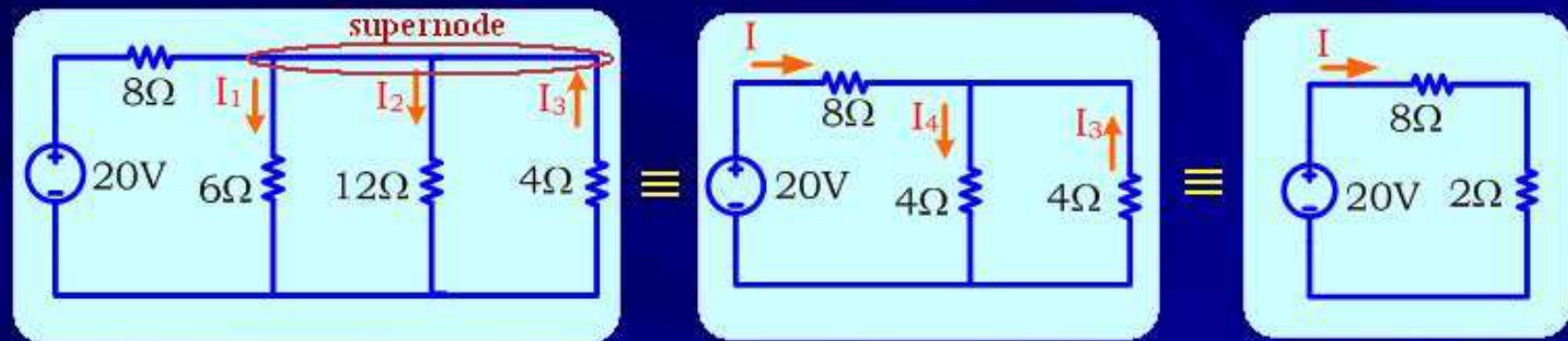
## Example 6

Use CDR to calculate  $I_1$ ,  $I_2$  and  $I_3$



$$I = \frac{20}{R_{eq}} = \frac{20}{10} = 2A$$

CDR  $\Rightarrow I_4 = \frac{4}{4+4} \times 2 = 1A$  ,  $I_3 = -\frac{4}{4+4} \times 2 = -1A$  (the minus sign is necessary for  $I_3$ , why?)

CDR  $\Rightarrow I_1 = \frac{12}{6+12} \times I_4 = \frac{2}{3}A$  ,  $I_2 = \frac{6}{6+12} \times I_4 = \frac{1}{3}A$  ( $I_4$  is the total current through 6Ω and 12Ω)

Check KCL at supernode  $\Rightarrow I - I_1 - I_2 + I_3 = 2 - \frac{2}{3} - \frac{1}{3} + (-1) = 1 - 1 = 0$  (KCL is verified)