

Al-Anbar University  
College of engineering  
Electrical Engineering Department

fundamental of Electric Circuit 1  
Assist. Lect. Yasameen Kamil  
Stage 1  
2021-2022



**LECTURE 9**  
**MESH ANALYSIS**



## Topics

- ▶ Mesh Analysis without Current Sources
- ▶ Mesh Analysis with Current Sources



## Objectives


- ▶ Understand mesh currents
- ▶ Relate currents through elements to mesh currents
- ▶ Apply Mesh Analysis in the absence of current sources
- ▶ Understand the concept of a super mesh
- ▶ Apply Mesh Analysis in the presence of current sources


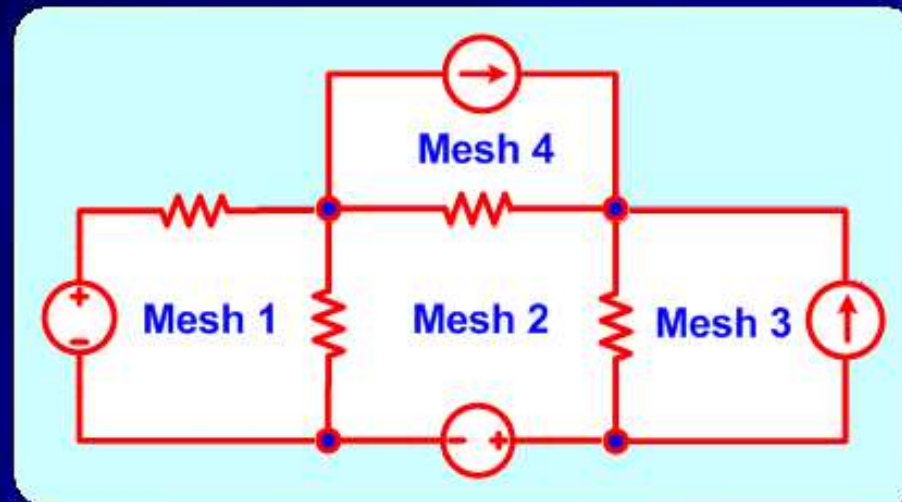
## Definition of a Mesh

A mesh is simply a window in an electric circuit.

This circuit contains four windows (meshes).





## Currents through Elements and Mesh Currents

The currents  $i_a$ ,  $i_b$ , and  $i_c$  are currents through elements.

KCL at node 1:

$$\Rightarrow i_a = i_b + i_c \Rightarrow i_b = i_a - i_c$$



The imaginary currents  $i_1$ , and  $i_2$  are mesh currents.

We imagine  $i_1$  to circulate around mesh 1 (Clockwise).

We imagine  $i_2$  to circulate around mesh 2 (also Clockwise).

$$i_a = i_1 \quad i_c = i_2$$

$$i_b = i_a - i_c = i_1 - i_2$$

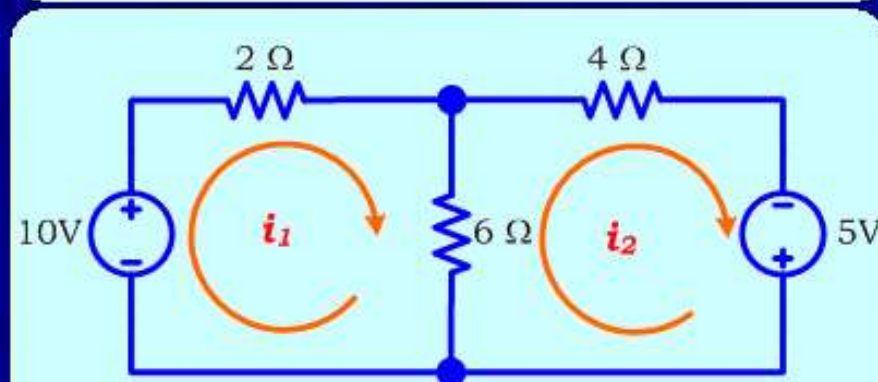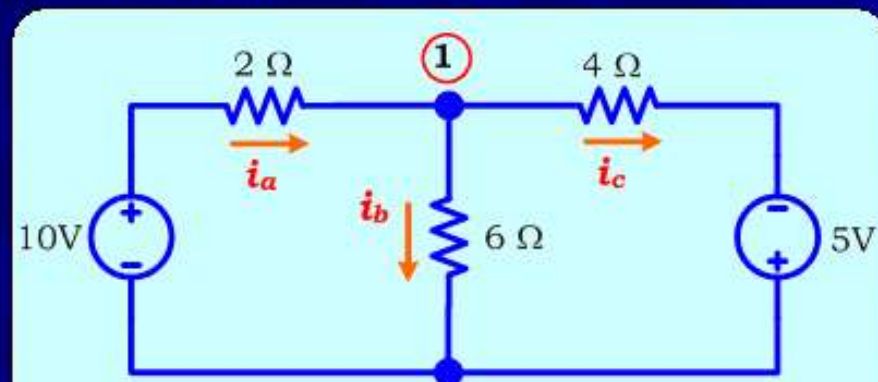




### Example:

Express the currents through elements (CTE)  $i_w$ ,  $i_x$ ,  $i_y$ , and  $i_z$  in terms of mesh currents (MC) currents  $i_1$ ,  $i_2$ , and  $i_3$

Solution:
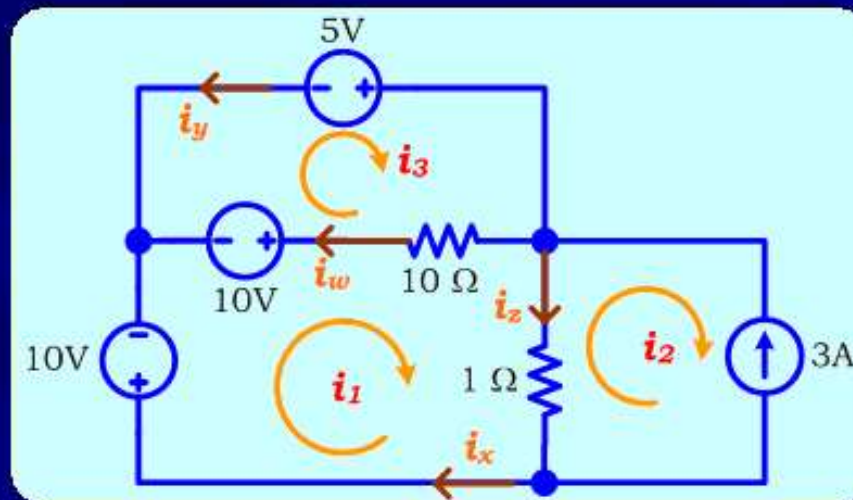
$$\begin{aligned}i_x &= i_1 \\i_y &= -i_3 \\i_z &= i_1 - i_2 \\i_w &= i_3 - i_1\end{aligned}$$



Number of MC  $\leq$  Number of CTE

We know all MC  $\Rightarrow$  We know all CTE





## Mesh Analysis without Current Sources

The Mesh Analysis procedure for circuits without current sources will be considered first. This procedure is illustrated below:

### Mesh Analysis

Step 1: KVL



Step 2: Ohm's Law



Step 3: KCL

Mesh Analysis



VOC

**Example 1:** Calculate the mesh currents  $i_1$  and  $i_2$

**Solution:**

**Procedure:**

First we will deal with Mesh 1

1. KVL:  $\Rightarrow -10 + V_a + V_b = 0$


2. Ohm's Law:

$$\Rightarrow -10 + 2i_a + 6i_b = 0$$

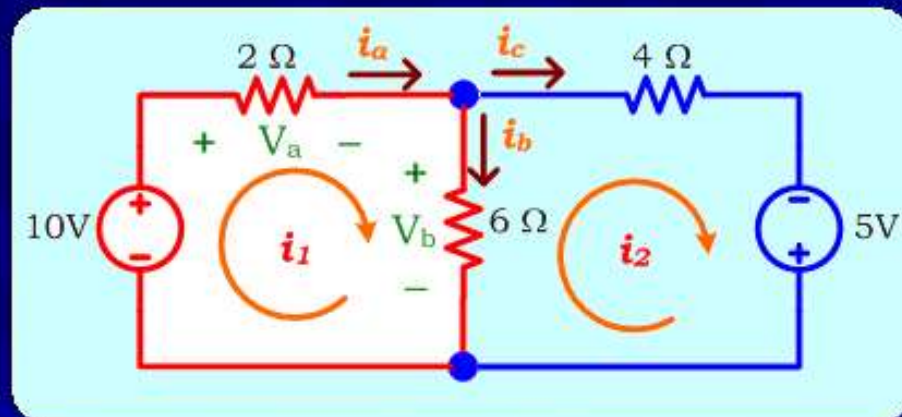3. KCL:

$$\Rightarrow -10 + 2i_1 + 6(i_1 - i_2) = 0 \quad (\text{CTE are expressed in terms of MC})$$

Simplify:  $\Rightarrow 8i_1 - 6i_2 = 10 \quad (1)$





## Solution (contd):

We will repeat the procedure for Mesh 2

1. KVL:  $\Rightarrow -V_b + V_c - 5 = 0$

2. Ohm's Law:

$$\Rightarrow -6i_b + 4i_c - 5 = 0$$

3. KCL:  $\Rightarrow -6(i_1 - i_2) + 4i_2 - 5 = 0$  (CTE are expressed in terms of MC)


Simplify:  $\Rightarrow -6i_1 + 10i_2 = 5$  (2)

From the previous slide

$$8i_1 - 6i_2 = 10 \quad (1)$$

Equations (1) and (2) contain only mesh unknowns  $i_1$  and  $i_2$

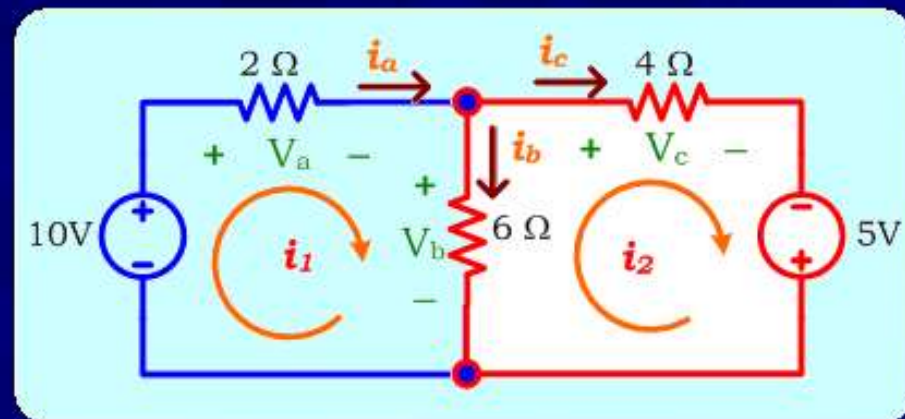Solving (1) and (2), we get:  $\Rightarrow i_1 = 2.955A \quad i_2 = 2.273A$



## Example 2:

Calculate the mesh currents  $i_1$  and  $i_2$ . Repeat the previous example by combining steps 1, 2, and 3.

Solution:

Mesh 1: KVL, & Ohm's Law, & KCL


$$\Rightarrow -10 + 2i_1 + 6(i_1 - i_2) = 0$$

$$8i_1 - 6i_2 = 10 \quad (1)$$

Mesh 2: KVL, & Ohm's Law, & KCL

$$\Rightarrow 6(i_2 - i_1) + 4i_2 - 5 = 0$$


$$-6i_1 + 10i_2 = 5 \quad (2)$$

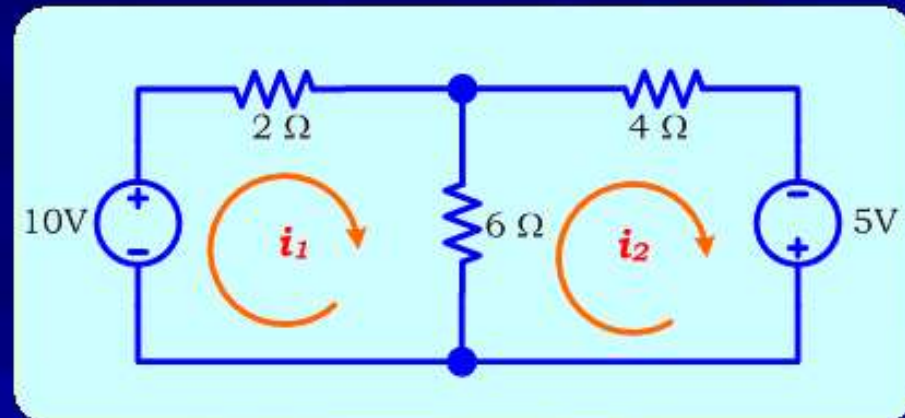

Current through resistors = CTR  
Always imagine CTR to be in the same direction as KVL.

Express the imagined CTR in terms of MC (Mesh Currents).

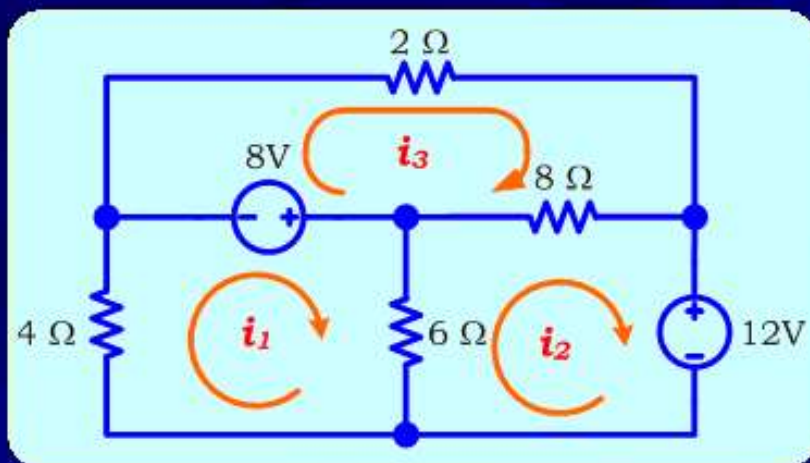**Example 3:** Calculate the mesh currents  $i_1$ ,  $i_2$  and  $i_3$ .



**Solution:**

$$\text{Mesh 1: } \Rightarrow 4i_1 - 8 + 6(i_1 - i_2) = 0 \quad \Rightarrow 10i_1 - 6i_2 = 8 \quad (1)$$

$$\text{Mesh 2: } \Rightarrow 6(i_2 - i_1) + 8(i_2 - i_3) + 12 = 0 \quad \Rightarrow -6i_1 + 14i_2 - 8i_3 = -12 \quad (2)$$

$$\text{Mesh 3: } \Rightarrow 2i_3 + 8(i_3 - i_2) + 8 = 0 \quad \Rightarrow -8i_2 + 10i_3 = -8 \quad (3)$$

$$\text{Solving (1), (2), and (3), we get: } \Rightarrow i_1 = -1.24\text{A} \quad i_2 = -3.40\text{A} \quad i_3 = -3.52\text{A}$$





## Mesh Analysis with Current Sources

When the circuit contains current sources, the previous procedure is modified.

Example 1: Calculate the mesh currents  $i_1$ ,  $i_2$  and  $i_3$

Solution:


KVL around Mesh 1:

$$1i_1 + 2(i_1 - i_3) + V_x = 0 \text{ (problem!)}$$

We cannot directly replace  $V_x$  by mesh currents, because Ohm's law does not apply to current sources.

KVL around Mesh 2:
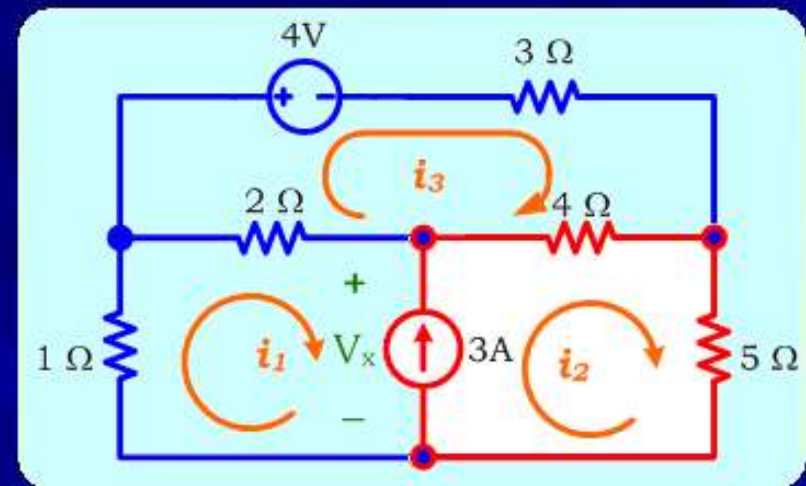
$$-V_x + 4(i_2 - i_3) + 5i_2 = 0 \text{ (similar problem!)}$$



### Solution (contd):

Mesh 1 & 2 contain a current source  
(they share the 3A source)

What to do in this case?

Combine Mesh 1 & Mesh 2 into a  
Super Mesh (SM).

To avoid  $V_x$ , apply KVL around SM


$$\Rightarrow 1i_1 + 2(i_1 - i_3) + 4(i_2 - i_3) + 5i_2 = 0$$

$$3i_1 + 9i_2 - 6i_3 = 0 \quad (1)$$

Mesh 3 does not contain a current source  $\Rightarrow$  No special treatment

$$\text{KVL around Mesh 3} \Rightarrow 4 + 3i_3 + 4(i_3 - i_2) + 2(i_3 - i_1) = 0 \Rightarrow -2i_1 - 4i_2 + 9i_3 = -4 \quad (3)$$
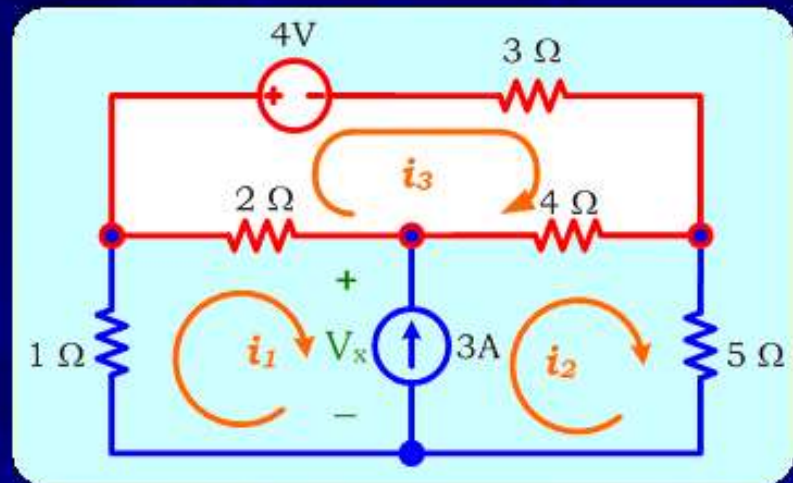
$$\text{Solving (1), (2) and (3), we get:} \Rightarrow i_1 = -2.708A \quad i_2 = 0.292A \quad i_3 = -0.917A$$




We need one more equation.

$$\text{Apply KCL} \Rightarrow i_2 - i_1 = 3 \quad (2)$$



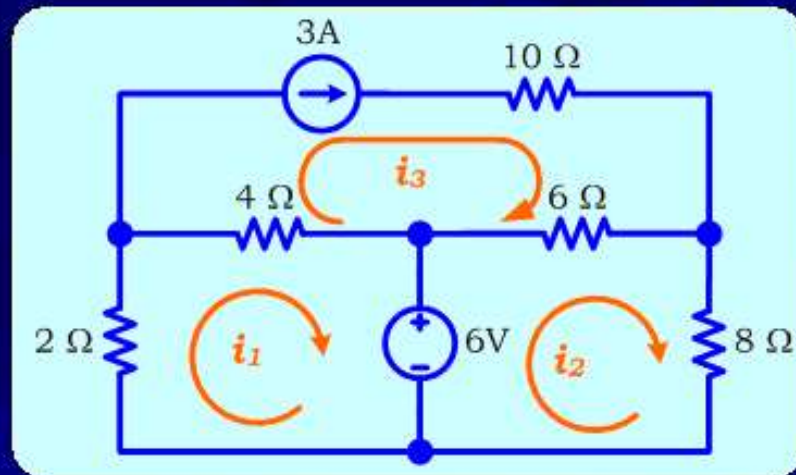**Example 2:** Calculate the mesh currents  $i_1$ ,  $i_2$  and  $i_3$ .



**Solution:** Mesh 1 & 2 does not contain current sources.

⇒ Just apply KVL around Mesh 1 & 2

KVL around Mesh 1:

$$\Rightarrow 2i_1 + 4(i_1 - i_3) + 6 = 0$$

$$\Rightarrow 6i_1 - 4i_3 = -6 \quad (1)$$

KVL around Mesh 2:

$$\Rightarrow -6 + 6(i_2 - i_3) + 8i_2 = 0$$


$$\Rightarrow 14i_2 - 6i_3 = 6 \quad (2)$$

## Solution (contd):

From the previous slide,

$$6i_1 - 4i_3 = -6 \quad (1)$$

$$14i_2 - 6i_3 = 6 \quad (2)$$

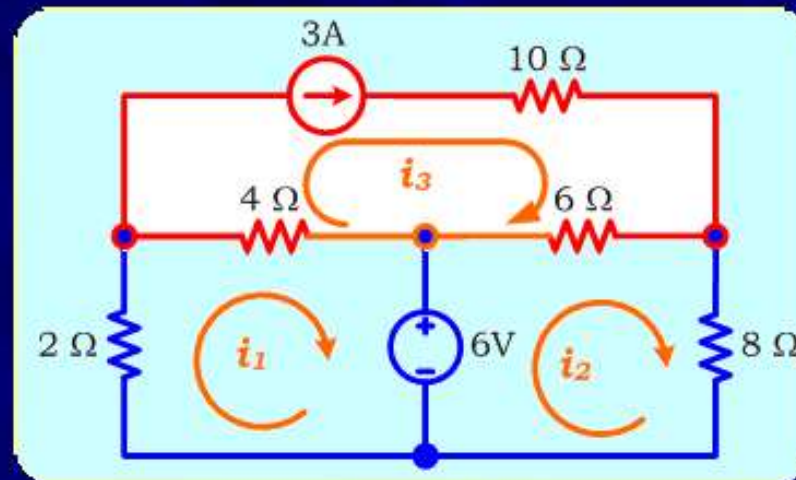

Mesh 3 contains a 3A current source (not shared by another mesh)

Do not apply KVL (because KVL involves voltage across the current source).

Apply only KCL  $\Rightarrow i_3 = 3 \quad (3)$

[Note: Since we need only one equation from mesh 3, KCL provides it]

Solving (1), (2), and (3), we get:  $\Rightarrow i_1 = 1.000A \quad i_2 = 1.714A \quad i_3 = 3.000A$



## Mesh Analysis with Current Sources : Summary

If a current source is shared by two meshes, then follow the procedure described below:

1. Combine the two meshes into a Super Mesh
2. Apply KVL around the Super Mesh
3. Apply KCL

If a current source is in one mesh only (not shared), then:

⇒ Apply KCL only (do NOT apply KVL)