



LECTURE 9
CIRCUIT ANALYSIS TECHNIQUE
SOURCE TRANSFORMATION



Topics

- ▶ Source Transformation
- ▶ Use of Source Transformation in Circuit Analysis





Objectives

- ▶ Understand the meaning of Source Transformation
- ▶ Apply Source Transformation
- ▶ Recognize when Source Transformation is not applicable
- ▶ Use Source Transformation to analyze and simplify circuits



Source Transformation

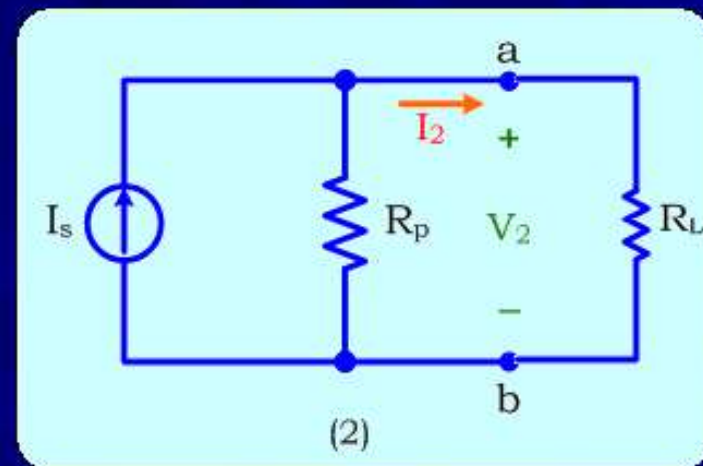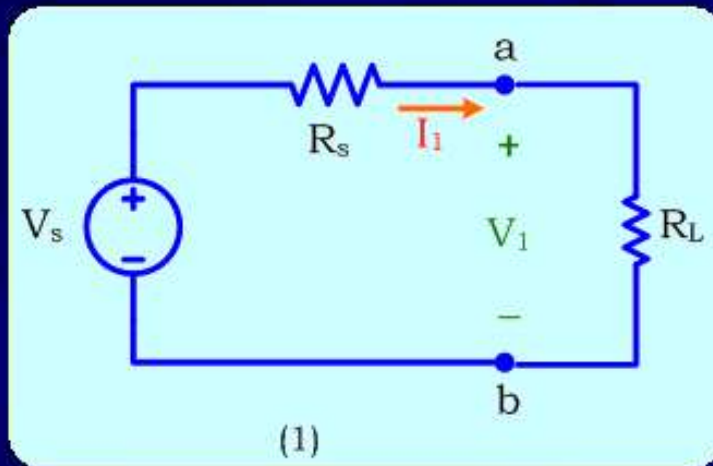

Given an ideal voltage V_s
in series with a resistor R_s





Given an ideal current I_s
in parallel with a resistor R_p

Connect the same load R_L across the terminal "a-b" in both circuits

If circuits (1) and (2) are equivalent: $\Rightarrow I_1 = I_2$ & $V_1 = V_2$



Source Transformation

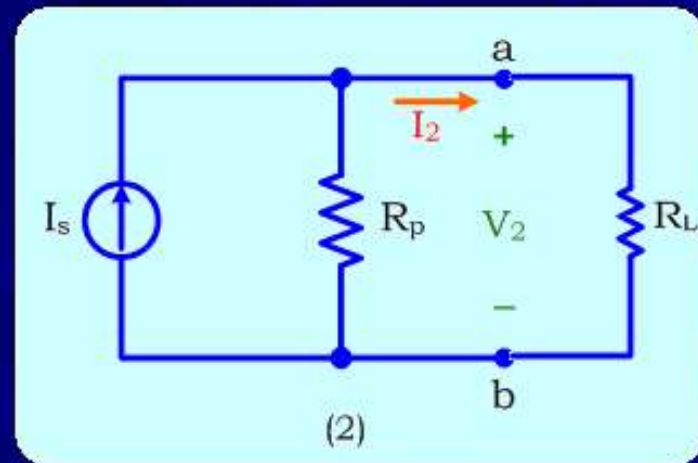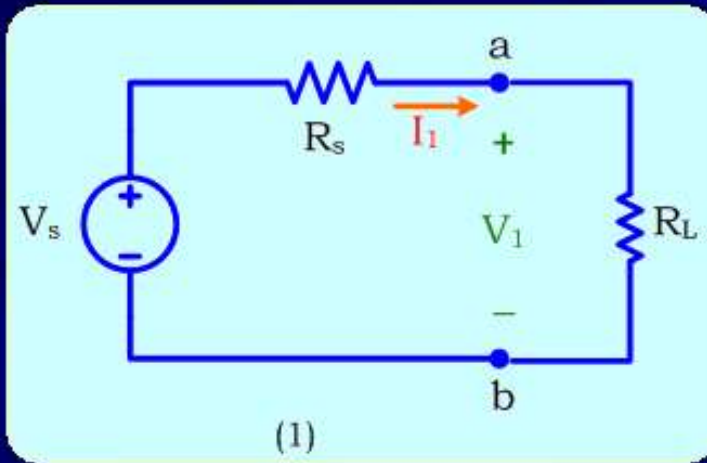

If circuits (1) and (2) are equivalent: $\Rightarrow I_1 = I_2$ & $V_1 = V_2$

$$I_1 = \frac{V_s}{R_{eq}} = \frac{V_s}{R_s + R_L}$$

$$I_2 = \frac{R_p}{R_p + R_L} I_s$$


$$I_1 = I_2 \Rightarrow \frac{V_s}{R_s + R_L} = \frac{R_p I_s}{R_p + R_L}$$

If we choose: $R_p = R_s \Rightarrow V_s = I_s R_p = I_s R_s$

$$\therefore R_s = R_p \text{ \& } V_s = I_s R_s$$

$\Rightarrow V_s$ in series with $R_s \Leftrightarrow I_s$ in parallel with R_p

Source Transformation: Comments

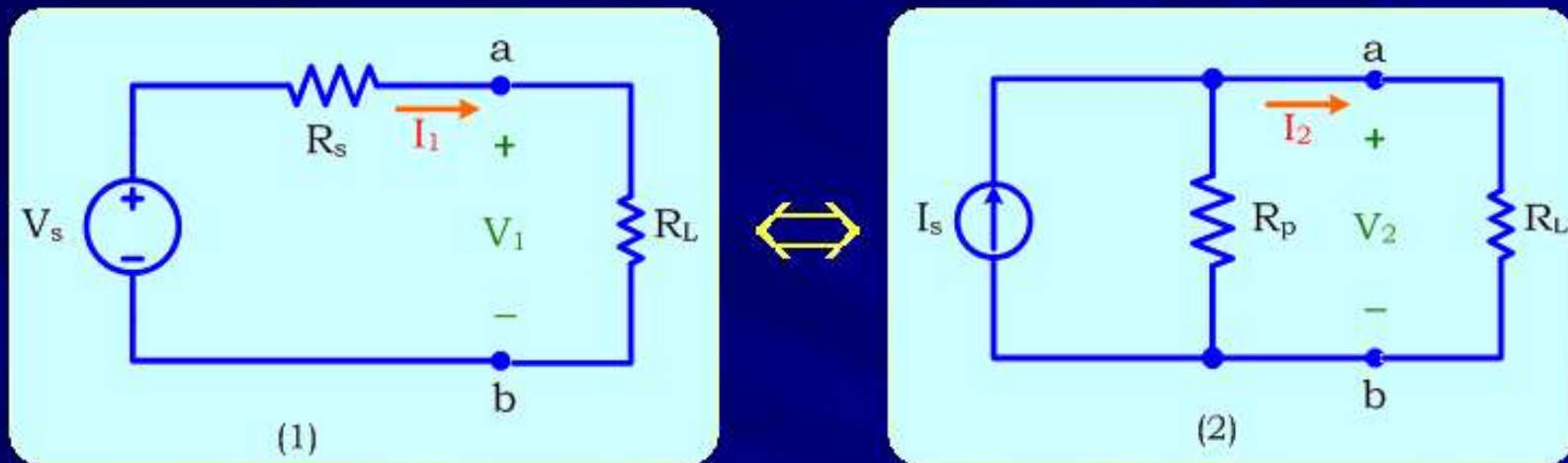

The above conversion is called *Source Transformation (ST)*.



Circuits (1) and (2) are equivalent. However, they are not the same.

When any load is connected to terminals "a" & "b" of circuits (1) and (2), the load cannot distinguish between the two circuits.

Circuits (1) and (2) are *equivalent from the outside* when accessed from terminals "a" & "b". But, they are *different from the inside*.





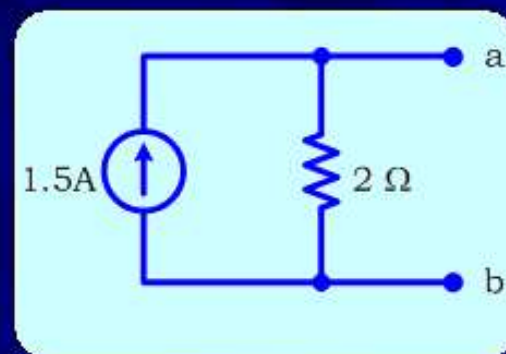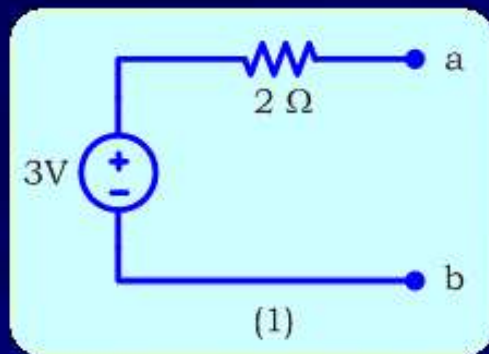Example 1: Convert the following circuits using Source Transformation.



$$R_p = R_s = 2\Omega$$
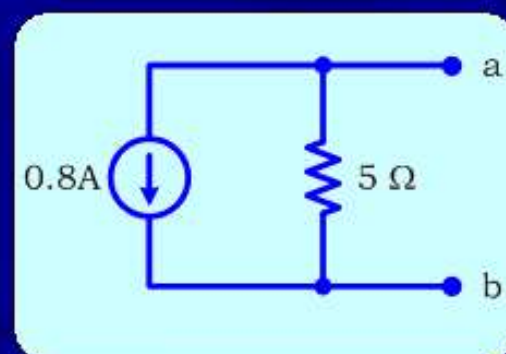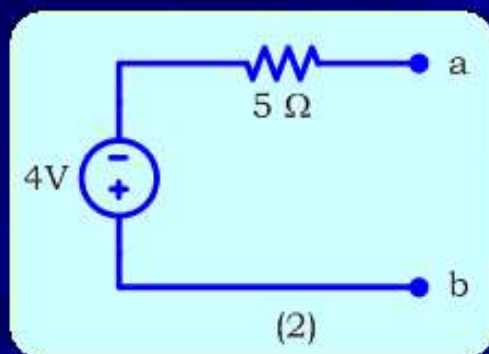
$$I_s = \frac{V_s}{R_s} = \frac{3}{2} = 1.5A$$





$$R_p = R_s = 5\Omega$$

$$I_s = \frac{V_s}{R_s} = \frac{4}{5} = 0.8A$$



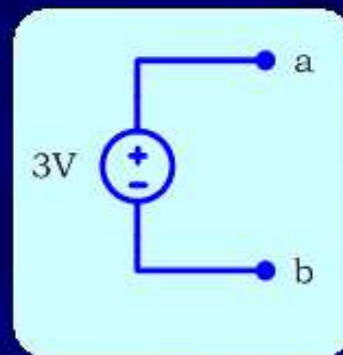
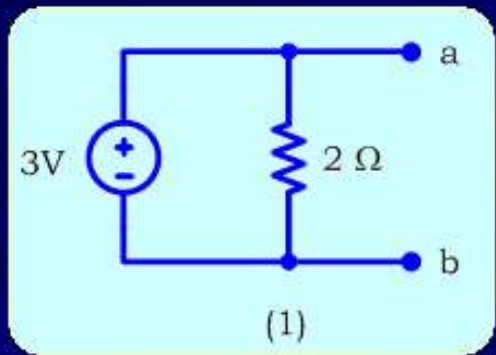
Example 2 Convert the following circuits using Source Transformation.



A resistor in parallel with a voltage source (not in series)

⇒ equivalent to a voltage source

⇒ ST does not apply

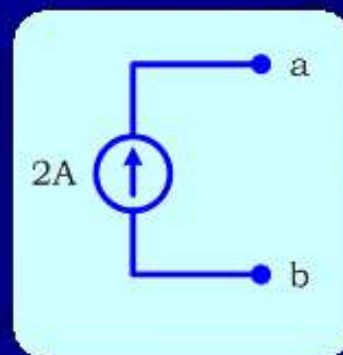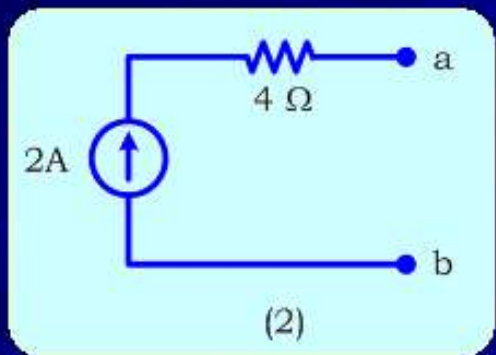


A resistor in series with a current source (not in parallel)

⇒ equivalent to a current source

⇒ ST does not apply



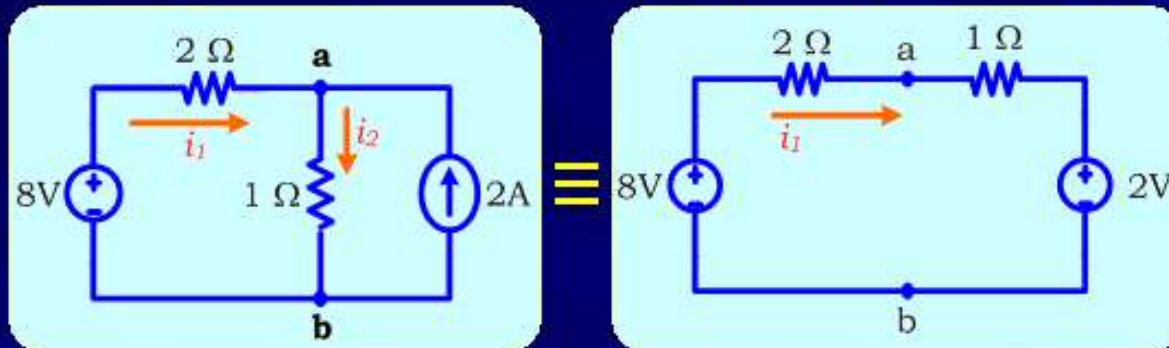Example 3 Use ST to calculate i_1 and i_2 .



Solution: Apply ST to the $2A$ and 1Ω combination $\Rightarrow V = IR = 2(1) = 2V$

Notice that i_2 cannot be drawn. It disappears. **Why?**


The current through the 1Ω of the transformed circuit is not i_2 . **Why?**

Reason: $R_p = R_s$ means the two resistors have the same value. It does not mean we have the same resistor!!

Since, 1Ω & 2Ω are in series \Rightarrow current through the 1Ω of the transformed circuit is i_1 .



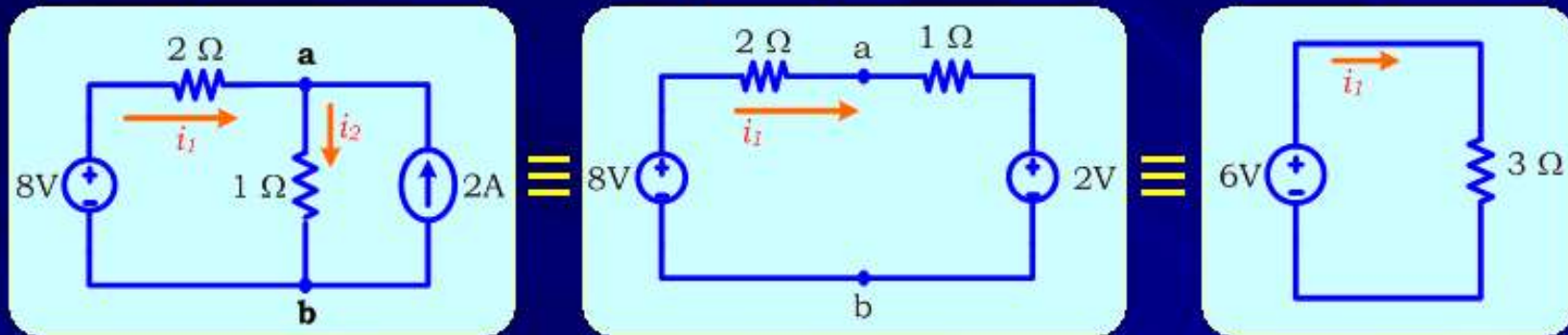Example 3 Use ST to calculate i_1 and i_2 .



Solution: We have 2Ω & 1Ω are in series $\Rightarrow 3\Omega$




We also have $8V$ and $2V$ are in series $\Rightarrow 8 - 2 = 6V$

Therefore, $i_1 = \frac{6}{3} = 2A$

KCL at node a (of the original circuit)

$$i_2 = i_1 + 2 = 2 + 2 = 4A$$

Example 4 Use ST to calculate V .

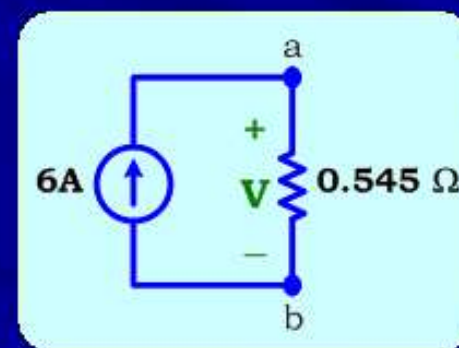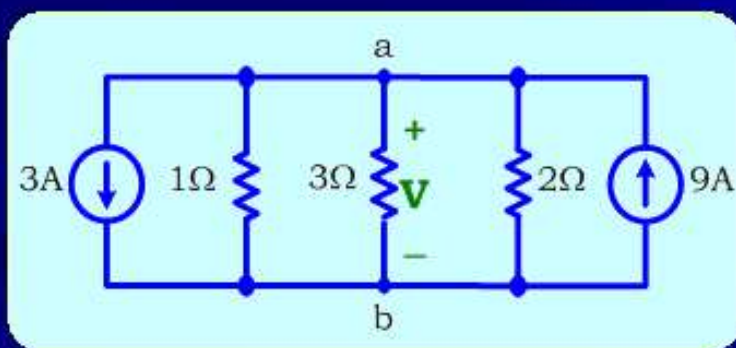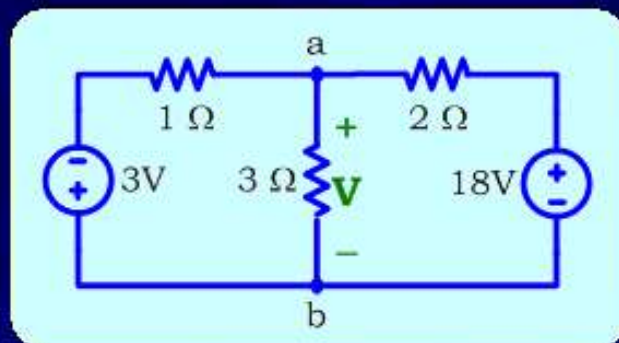

Solution:

Apply ST to $(3V/1\Omega)$ and to $(18V/2\Omega)$

$$\Rightarrow I_{s1} = \frac{3}{1} = 3A \quad \& \quad I_{s2} = \frac{18}{2} = 9A$$

$$\Rightarrow R_{eq} = \frac{1}{1 + \frac{1}{3} + \frac{1}{2}} = 0.545\Omega \quad [1\Omega \parallel 3\Omega \parallel 2\Omega]$$

$$I_{eq} = 9 - 3 = 6A \quad [3A \parallel 9A]$$

$$\therefore V = I_{eq} R_{eq} = 6(.545) = 3.273V$$

Practice Problem

Find the currents i_1 & i_2 for the circuit shown:

Answer:

$$i_1 = -1A \text{ \& } i_2 = 0.8A$$

