



## Experiment No.5

### JFET Characteristics

#### Object

The purpose of this experiment is to determine and sketch the characteristics of the JFET and to find its parameters.

#### Required Parts and Equipment's

1. Electronic Test Board. (M100)
2. Dual Polarity Variable DC Power Supply
3. Digital Multimeters.
4. N-Channel JFET 2N3823/3824
5. Resistors 207K $\Omega$ , 220  $\Omega$ .

#### Theory

The Junction Field Effect Transistor (JFET) is a three-terminal device with one terminal (called the gate) capable of controlling the current between the other two terminals (drain and source). The primary difference between FET and BJT transistors is the fact that the BJT transistor is a current-controlled device, while the JFET transistor is a voltage-controlled device. The FET transistor is a unipolar device depending on either electron conduction (N-channel JFET) or hole conduction (P-channel JFET). In contrast, the BJT transistor is a bipolar device, meaning that the conduction depends on two charge carriers (electrons and holes) in the same time.

Another difference between two devices is the high input impedance of the JFET when compared with the BJT. The input impedance is usually larger than 1 M $\Omega$ . However, typical AC voltage gains for BJT amplifiers are greater than those for FET amplifiers. Furthermore, FETs are more temperature stable than BJTs and are usually smaller in size, making them particularly useful in integrated circuit chips.

The basic construction of an N-channel JFET is shown in Fig.1 together with its symbol.

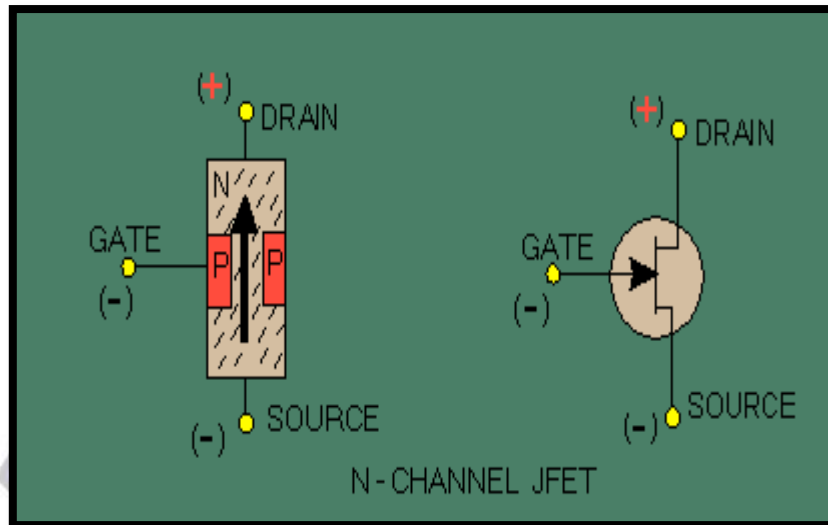


Figure 1: N-Channel JFET Structure and Symbol

The drain current ( $I_D$ ) of the JFET is controlled by the application of reverse-biased voltage between gate and source terminals ( $V_{GS}$ ). The relationship between  $I_D$  and  $V_{GS}$  is defined by the well-known Shockley's equation:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \dots\dots\dots(1)$$

Where  $V_P$  is called the pinch-off voltage and  $I_{DSS}$  is known as the drain saturation current. When  $V_{GS} = V_P$  then  $I_D = 0$ , and the FET is in the cut-off region. Equation (1) indicates that the FET is a square-law device.

The relation between  $I_D$  and  $V_{GS}$  is also referred as the transfer characteristic of the JFET and is presented in Fig.2. This curve is obtained by varying the negative voltage  $V_{GS}$  between  $V_P$  and 0 and measuring  $I_D$  for a given value of the drain to source voltage ( $V_{DS}$ ). Equation (1) can approximate this curve to an acceptable level.

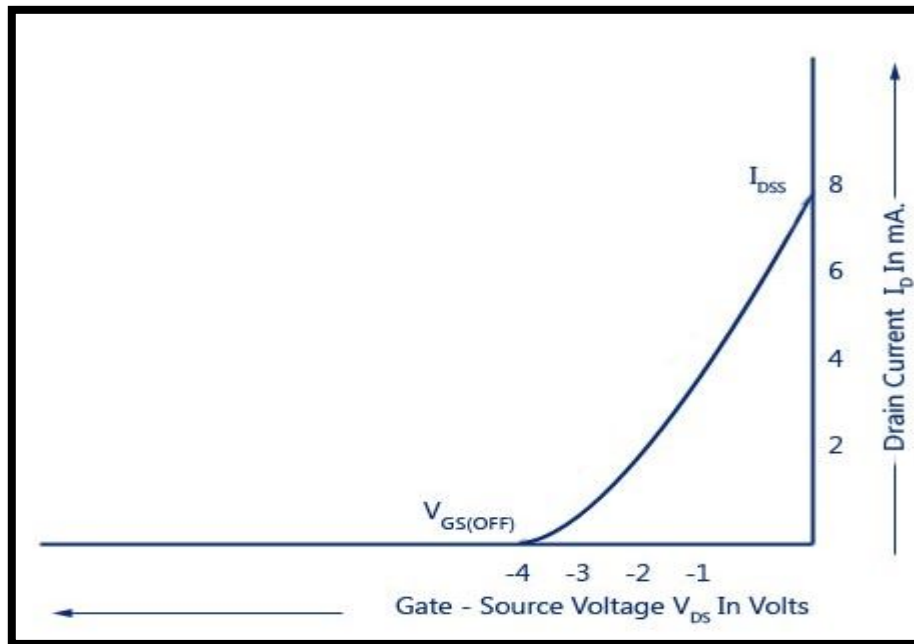


Figure 2: The Transfer Characteristics of the JFET

The circuit used to obtain the JFET characteristics is shown in Fig.3. To obtain the transfer characteristic, the drain supply voltage  $V_{DD}$  should be maintained at a certain value, and the gate supply voltage is adjusted to several negative values while recording  $I_D$  in each step.


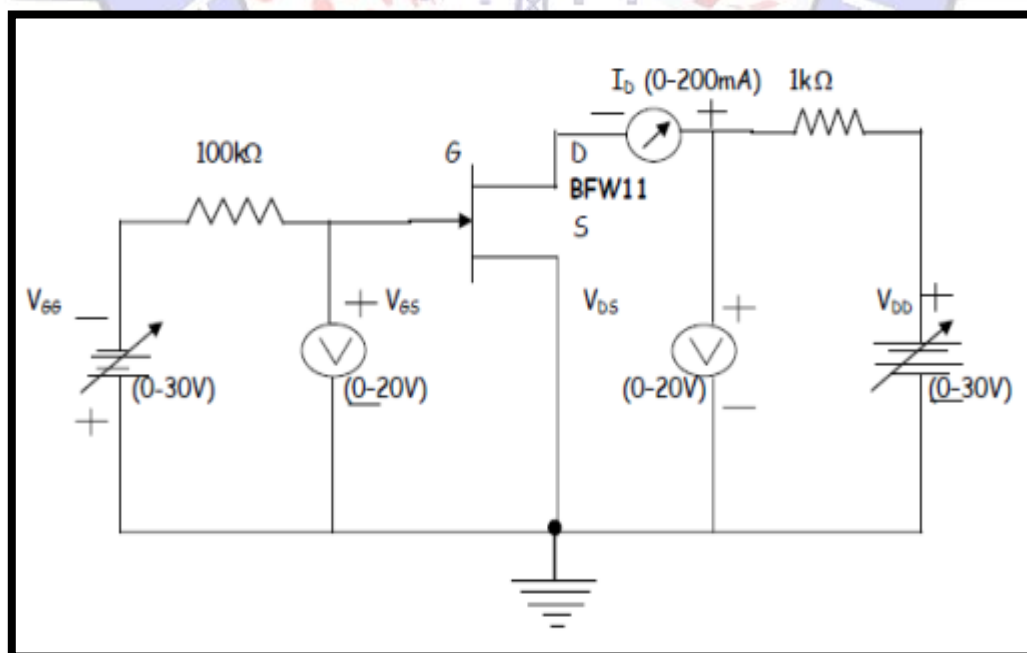


Figure 3: A Test Circuit for Getting JFET Characteristics

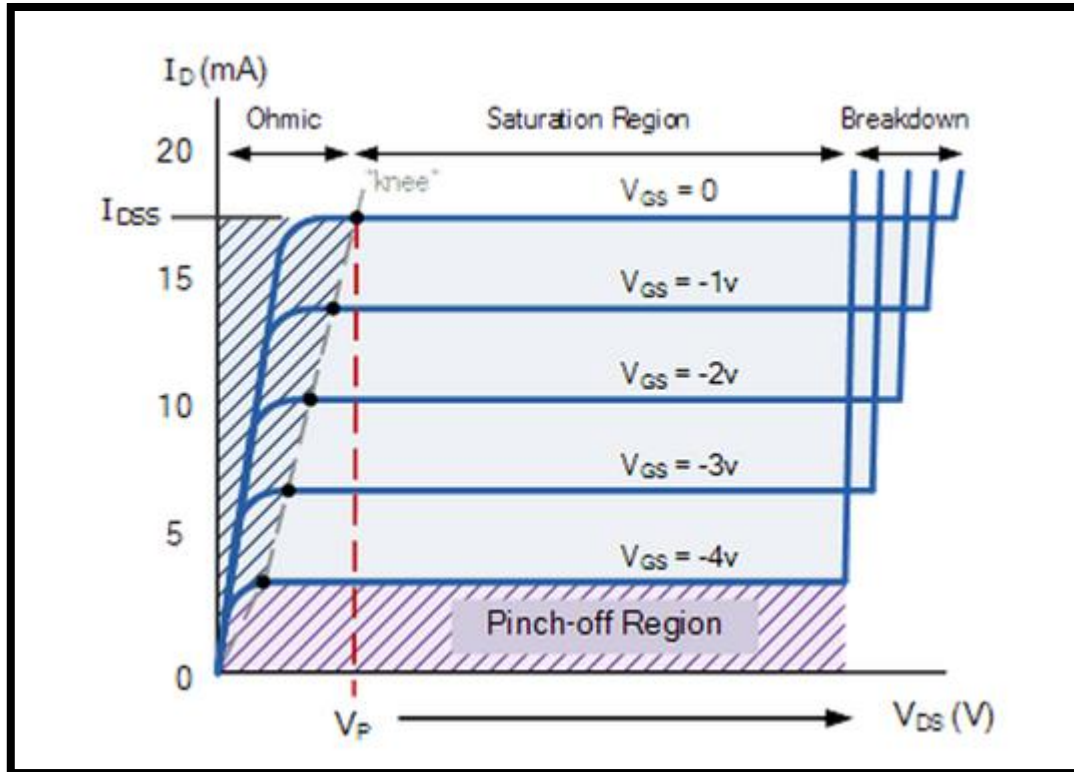

On the other hand, to sketch the drain characteristic, the gate-source voltage  $V_{GS}$  must be kept at a certain level while varying  $V_{DS}$  in several steps and recording  $I_D$  in each step. Figure 4 shows the drain (or output) characteristics of the JFET.



As shown from Fig.4, for small values of  $V_{DS}$  ( $V_{DS} < |V_P|$ ) the drain current increases linearly with  $V_{DS}$ . This region is called the linear or Ohmic region in which the JFET behaves as a voltage-controlled resistor. For larger values of  $V_{DS}$  ( $V_{DS} > |V_P|$ ), the drain current ( $I_D$ ) is approximately constant and enters the saturation region.

The transconductance of the JFET ( $g_m$ ) is defined as the change in drain current ( $\Delta I_D$ ) for a given change in gate-to-source voltage ( $\Delta V_{GS}$ ) with the drain-to-source voltage ( $V_{DS}$ ) kept constant. It has the unit of siemens (S).

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_P} \right)$$

.....(2)



Because the transfer characteristic curve for a JFET is nonlinear,  $g_m$  varies in value depending on the location on the curve as depicted in Fig.5. A datasheet normally gives the value of  $g_m$  measured at  $V_{GS} = 0$ , which is referred as  $g_{mo}$ .

Theoretically,  $g_m$  can be calculated at any point on the transfer characteristic curve from the following equation:

$$g_m = g_{mo} \left( 1 - \frac{V_{GS}}{V_P} \right) \dots\dots\dots(3)$$

Where  $g_{mo}$  is found from:

$$g_{mo} = \frac{2I_{DSS}}{|V_P|} \dots\dots\dots(4)$$

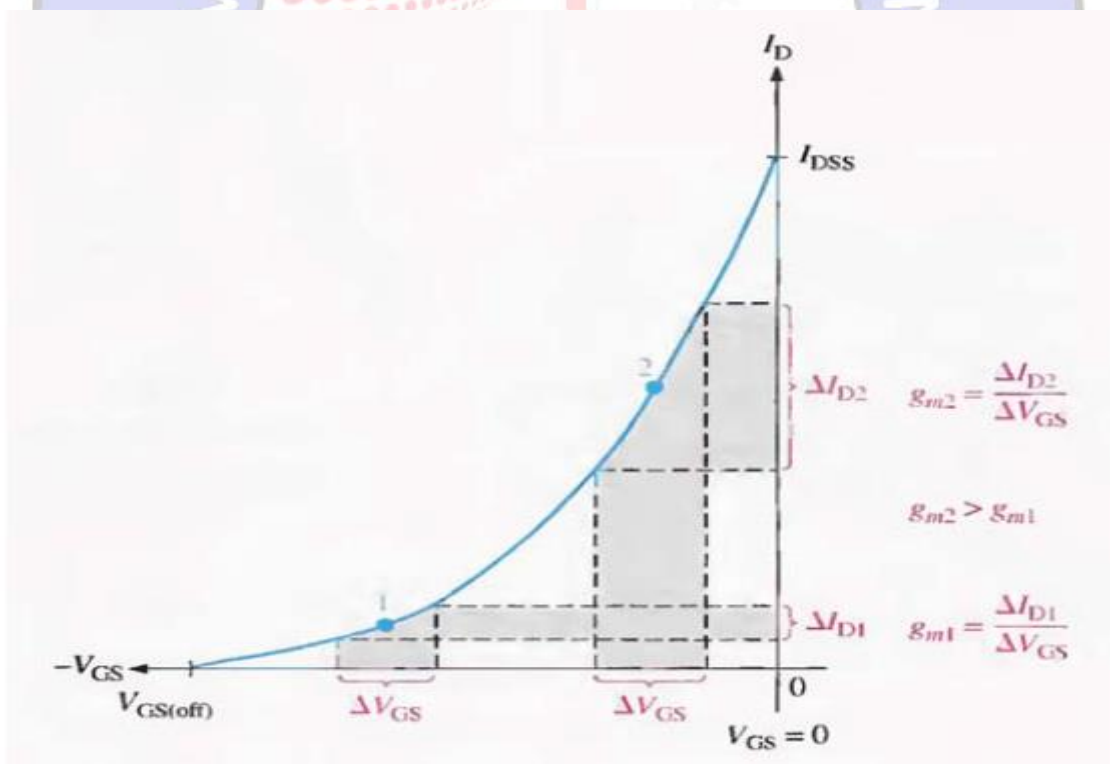


Figure 5: Graphical Determination of the JFET Transconductance

## Procedure

1. Connect the circuit shown in Fig.6.

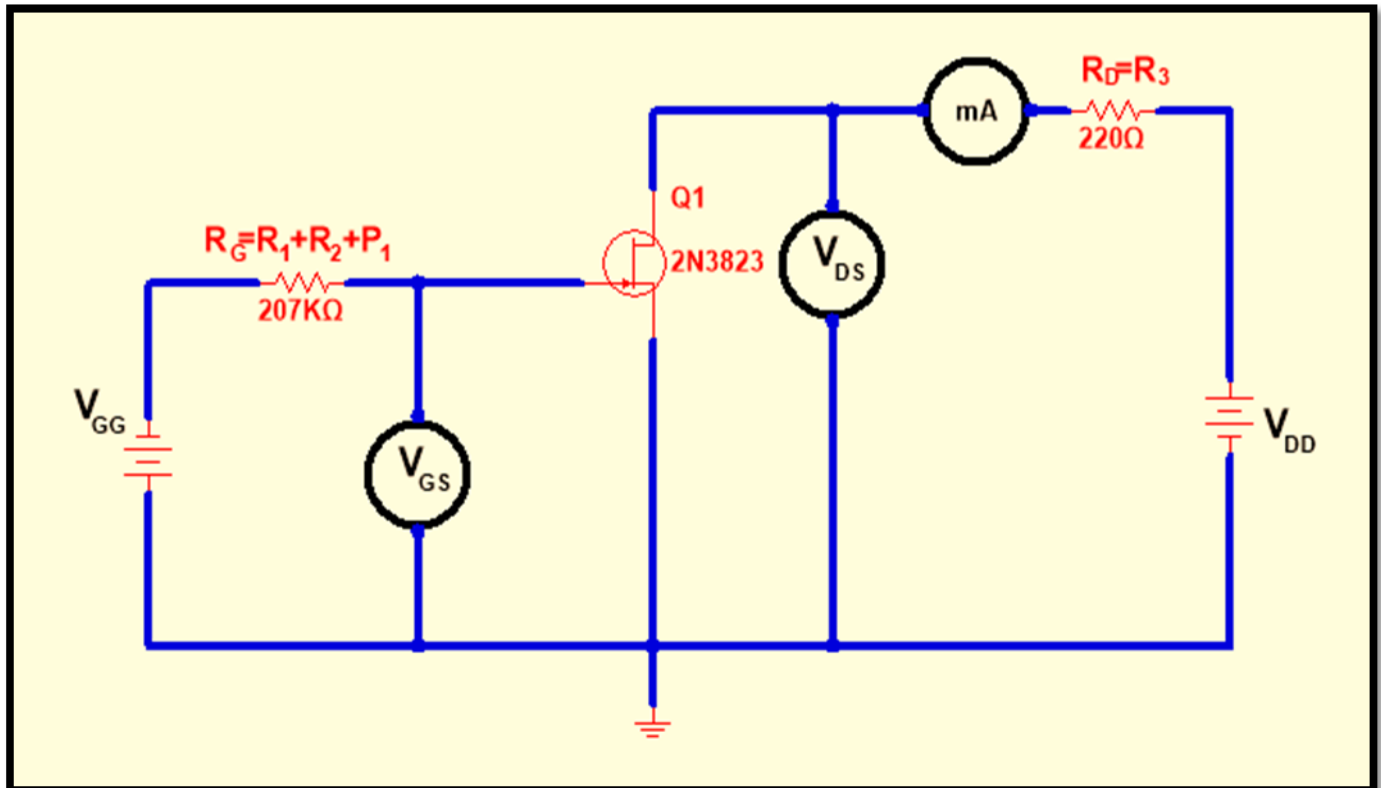


Figure 6: The Test Circuit for Getting JFET Characteristics

2. Adjust  $V_{DD}$  so that  $V_{DS} = 5V$ , and vary  $V_{GG}$  to change  $V_{GS}$  from  $0V$  to  $-3V$  in different steps recording  $I_D$  for each step. Repeat with  $V_{DS} = 10V$ . Tabulate your results as shown in Table-1.
3. Set  $V_{GG}$  to  $0V$  so that  $V_{GS} = 0V$  and vary  $V_{DD}$  so that  $V_{DS}$  changes in several steps recording  $I_D$  in each step. Repeat with  $V_{GS} = -1V$ . Tabulate your results as illustrated in Table 2.



**Table 1: Recorded Data for the JFET Transfer Characteristics**

VDS = 5V		VDS = 10V	
VGS(V)	ID (mA)	VGS(V)	ID (mA)
0		0	
-0.25		-0.25	
-0.5		-0.5	
-0.75		-0.75	
-1		-1	
-1.25		-1.25	
-1.5		-1.5	
-1.75		-1.75	
-2		-2	
-2.25		-2.25	
-2.5		-2.5	
-2.75		-2.75	
-3		-3	

**Table 2: Recorded Data for the JFET Drain Characteristics**

VDS = 0V		VDS = -1V	
VGS(V)	ID (mA)	VGS(V)	ID (mA)
0		0	
0.5		0.5	
1		1	
1.5		1.5	
2		2	
2.5		2.5	
3		3	
4		4	
5		5	
6		6	
7		7	
8		8	
9		9	
10		10	



## Discussion

1. From the obtained data, sketch the transfer characteristics of the JFET.
2. Determine the values of  $V_P$  and  $I_{DSS}$  from the plot.
3. Calculate theoretically the value of  $g_m$  at  $V_{GS} = -1V$  and  $V_{GS} = -2V$  when  $V_{DS} = 10V$  and compare them with the measured quantities.
4. Sketch the drain characteristics of the JFET from the obtained data.
5. From the linear region of the drain characteristic, determine the value of the drain to source resistance  $r_{ds}$  when  $V_{GS} = 0V$ .
6. Compare between the JFET and the BJT.

