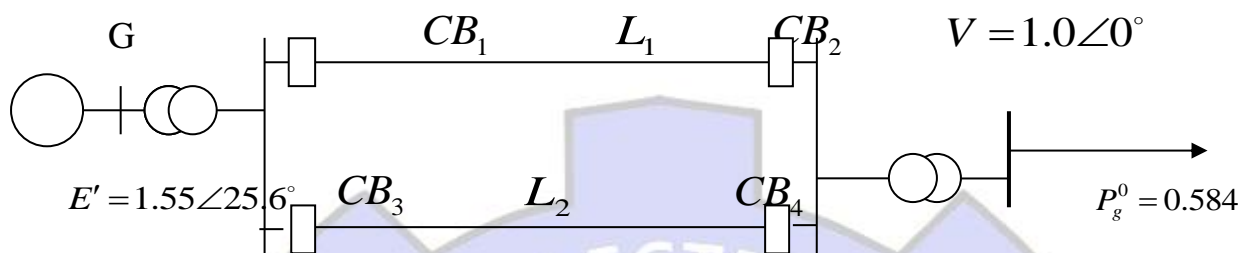




**Example (1)** : For the circuit shown in fig. below , it is assumed that both lines are first open and then re-closed , determine the maximum time ( $t_{ON}$ ) ( time of re-closed) during which the system is capable of preserving its transient stability when energy is not supplied to it .



$$P_T^0 = P_g^0 = 0.584$$


$$X_{EV} = 1.15 ; M = 7 \text{ Sec.}$$

Solution:

$$P_{\max}^I = P_{\max}^{III} = \frac{|E'| |V|}{X_{EV}} = \frac{1.55 \times 1}{1.15} = 1.35 \text{ pu}$$

When both lines are switched off  $P_{\max}^{II} = 0$

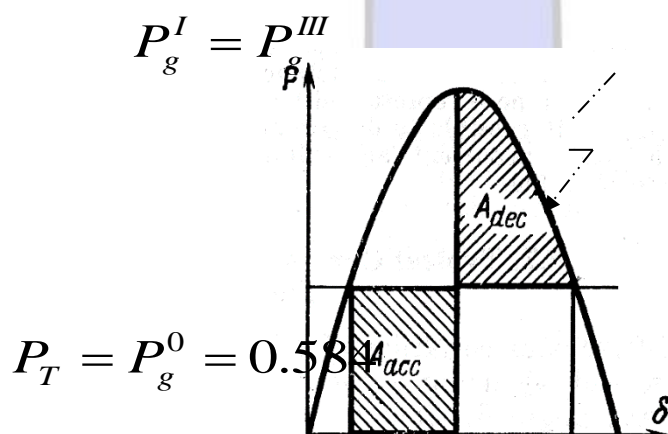$\delta_c (\delta_{ON})$  - is the max. angle at which the lines should be switched ON ( re-closed ) .





$$P_g^{II} = 0$$

$\delta_0$     $\delta_c$     $\delta_m$  180

$$\cos \delta_c = \frac{P_g^0 (\delta_m - \delta_0) - P_{\max}^{II} \cos \delta_0 + P_{\max}^{III} \cos \delta_m}{P_{\max}^{III} - P_{\max}^{II}}$$

$$\delta_m = 180^\circ - \delta_0 = 180^\circ - \sin^{-1} \frac{P_g^0}{P_{\max}^I}$$

$$= 180^\circ - \sin^{-1} \frac{0.584}{1.35} = 154.4^\circ$$

$$\cos \delta_c = \frac{0.584(154.6^\circ - 25.6^\circ) \frac{\pi}{180} - 0 + 1.35 \cos 154.6^\circ}{1.35 - 0} = 0.0665$$

$$\delta_c = \cos^{-1} 0.0665 = 86.2^\circ$$


$$t_{ON} = \sqrt{\frac{2M(\delta_{ON} - \delta_0)}{P^0}} = \sqrt{\frac{2 \frac{7}{2\pi f_0} (86.2 - 25.6) \frac{\pi}{180}}{0.584}}$$

$$= \sqrt{\frac{7(86.2 - 25.6)}{0.584 \times 180 \times 50}} = 0.284 \text{ Sec.}$$

Example (2) :

For the circuit shown in fig. , if the fault occurs on one line .

Determine the critical clearing angle .

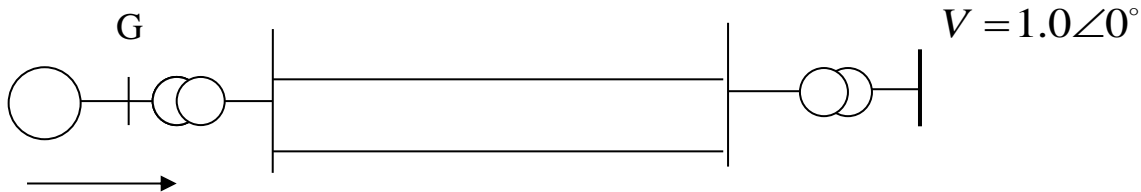


$$P_g^0 = P_T^0 = 1.0$$

$$P_{\max}^I = 2.0 \quad ; \quad P_{\max}^{II} = 0.5 \quad ; \quad P_{\max}^{III} = 1.5$$

Solution :

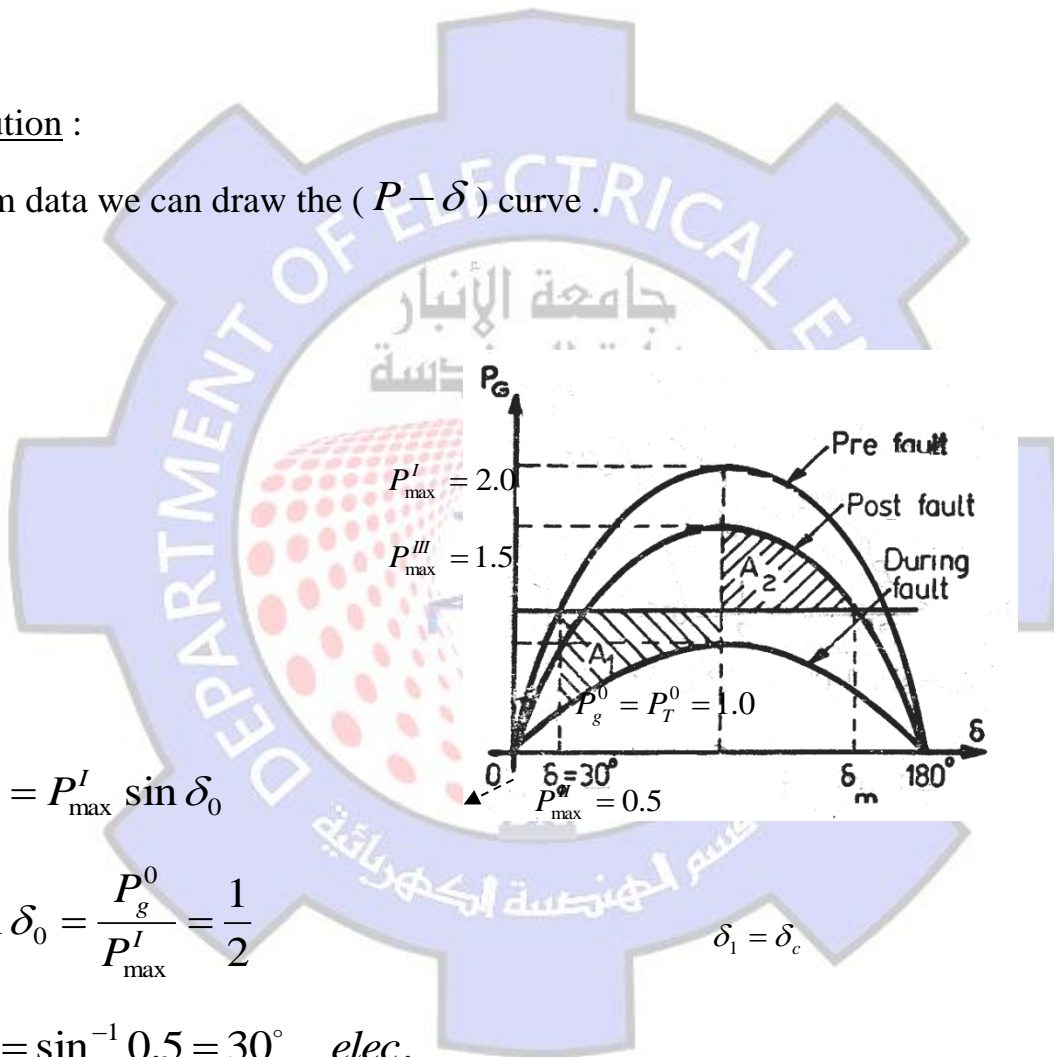From data we can draw the ( $P-\delta$ ) curve .



$$P_g^0 = P_{\max}^I \sin \delta_0$$

$$\sin \delta_0 = \frac{P_g^0}{P_{\max}^I} = \frac{1}{2}$$

$$\delta_0 = \sin^{-1} 0.5 = 30^\circ \text{ elec.}$$

$$\delta_m = 180^\circ - \sin^{-1} \frac{P_g^0}{P_{\max}^{III}}$$

$$= 180^\circ - \sin^{-1} \frac{1}{1.5} = 138.2^\circ$$




$$\cos \delta_c = \frac{1 \times (138.2^\circ - 30^\circ) \frac{\pi}{180} - 0.5 \cos 30^\circ + 1.5 \cos 138.2^\circ}{1.5 - 0.5} = 0.337$$

$$\delta_c = \cos^{-1} 0.337 = 70.3^\circ \text{ elect.}$$

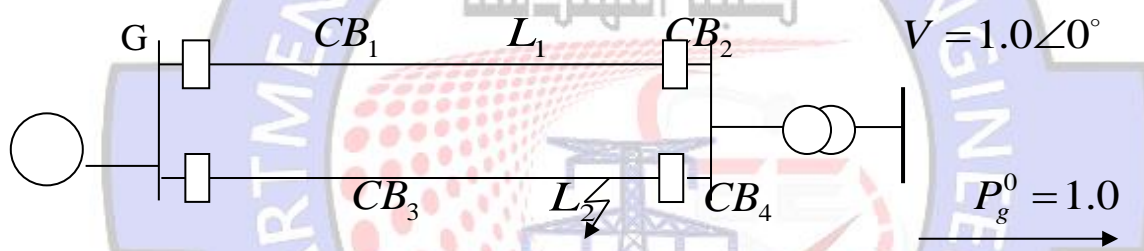Example (3) :

For the circuit shown in fig. , find the critical fault clearing angle , when 3-phase short circuit occurs at point shown in fig. The breakers  $CB_3$  and  $CB_4$  are opened after the fault .



$$|E| = 1.25$$

$$P_T^0 = P_g^0 = 1.0$$

$$X_d = j0.25 ; X_T = j0.06 ; X_{L1} = X_{L2} = 0.5 ;$$


i) pre fault operation :

$$X^I = 0.25 + \frac{0.5 \times 0.5}{0.5 + 0.5} + 0.06 = 0.56$$

$$P_{\max}^I = \frac{1.25 \times 1}{0.56} = 2.232$$

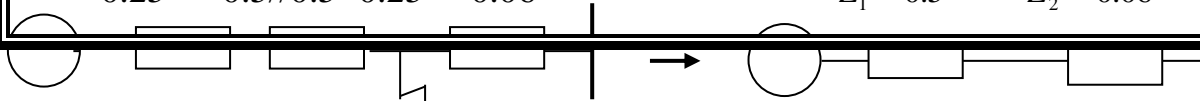
ii) during fault :

$$0.25 \quad 0.5//0.5=0.25 \quad 0.06 \quad Z_1 = 0.5 \quad Z_2 = 0.06$$





F

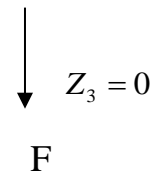

$$X'' = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$$

$$X'' = j0.5 + j0.06 + \frac{j0.5 \times j0.06}{j0.0} = \infty$$

That is mean , no transfer power at the receiving end .

$$P''_{\max} = 0$$

iii) post fault operation ( $CB_3$  and  $CB_4$  are opened)

$$X''' = 0.25 + 0.5 + 0.06 = 0.81$$

$$P'''_{\max} = \frac{1.25 \times 1}{0.81} = 1.543$$

$$P_g^0 = P'''_{\max} \sin \delta_0$$

$$\sin \delta_0 = \frac{1}{2.232} = 0.448 \quad ; \quad \delta_0 = \sin^{-1} 0.448 = 26.6^\circ$$

$$\delta_m = 180 - \sin^{-1} \frac{P_g^0}{P'''_{\max}} = 180 - \sin^{-1} \frac{1}{1.54} = 139.6^\circ$$

$$\cos \delta_c = \frac{1 \times (139.6 - 26.6) \frac{\pi}{180} - 0 + 1.543 \cos 139.6}{1.543 - 0} = 0.516$$

$$\delta_c = \cos^{-1} 0.516 = 58.9^\circ$$