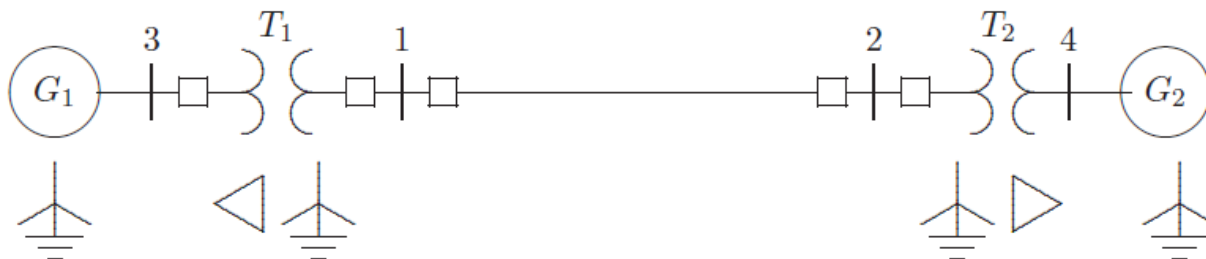




### HW

Q1/ The reactance data for the power system shown in Figure in per unit on a common base is as follows:




Item	$X^1$	$X^2$	$X^0$
$G_1$	0.10	0.10	0.05
$G_2$	0.10	0.10	0.05
$T_1$	0.25	0.25	0.25
$T_2$	0.25	0.25	0.25
Line 1-2	0.30	0.30	0.50

Obtain the Thevenin sequence impedances for the fault at bus 1 and compute the fault current in per unit for the following faults:

- A bolted three-phase fault at bus 1.
- A bolted single line-to-ground fault at bus 1.
- A bolted line-to-line fault at bus 1.
- A bolted double line-to-ground fault at bus 1.

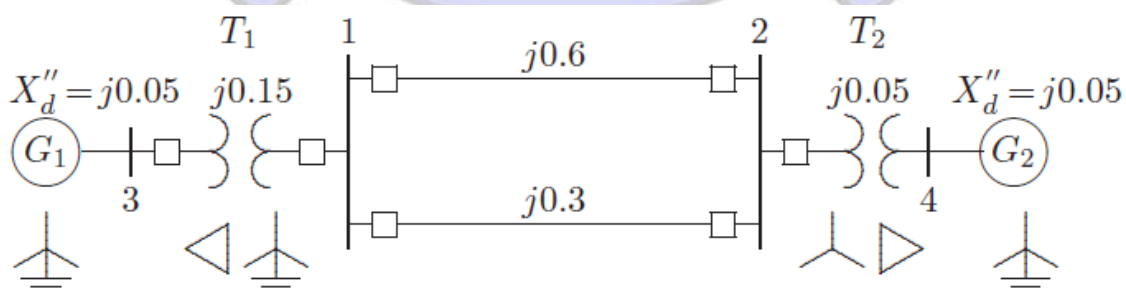Q2/ The positive-sequence reactances for the power system shown in Figure are in per unit on a common MVA base. Resistances are neglected and the negative-sequence impedances are assumed to be the same as the positive-sequence impedances. A bolted line-to-line fault occurs between phases  $b$  and  $c$  at bus 2. Before the fault occurrence, all bus voltages are 1.0 per unit. Obtain the positive sequence bus impedance matrix. Find the fault current, the three-phase bus voltages during fault, and the line currents in each phase.



Q3/ The single-line diagram of a three-phase power system is shown in Figure. Equipment ratings are given as follows:




**Synchronous generators:**

G1	1000 MVA	15 kV	$X_d'' = X_2 = 0.18, X_0 = 0.07$ per unit
G2	1000 MVA	15 kV	$X_d'' = X_2 = 0.20, X_0 = 0.10$ per unit
G3	500 MVA	13.8 kV	$X_d'' = X_2 = 0.15, X_0 = 0.05$ per unit
G4	750 MVA	13.8 kV	$X_d'' = 0.30, X_2 = 0.40, X_0 = 0.10$ per unit

**Transformers:**

T1	1000 MVA	15 kV $\Delta$ /765 kV Y	$X = 0.10$ per unit
T2	1000 MVA	15 kV $\Delta$ /765 kV Y	$X = 0.10$ per unit
T3	500 MVA	15 kV Y/765 kV Y	$X = 0.12$ per unit
T4	750 MVA	15 kV Y/765 kV Y	$X = 0.11$ per unit

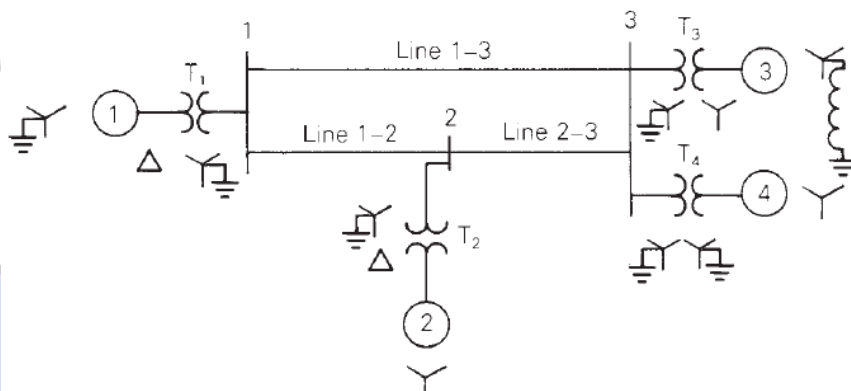


**Transmission lines:**

1-2	765 kV	$X_1 = 50 \Omega, X_0 = 150 \Omega$
1-3	765 kV	$X_1 = 40 \Omega, X_0 = 100 \Omega$
2-3	765 kV	$X_1 = 40 \Omega, X_0 = 100 \Omega$

The inductor connected to Generator 3 neutral has a reactance of 0.05 per unit using generator 3 ratings as a base. Draw the zero-, positive-, and negative-sequence reactance diagrams using a 1000-MVA, 765-kV base in the zone of line 1-2.

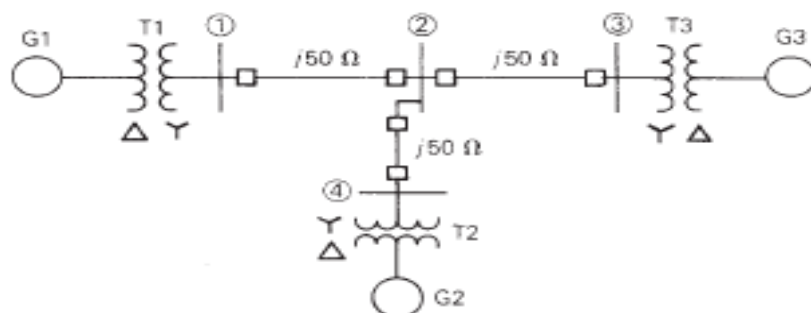Q4/ Equipment ratings for the four-bus power system shown in Figure are given as follows:





- Generator G1: 500 MVA, 13.8 kV,  $X_d'' = X_2 = 0.20$ ,  $X_0 = 0.10$  per unit
- Generator G2: 750 MVA, 18 kV,  $X_d'' = X_2 = 0.18$ ,  $X_0 = 0.09$  per unit
- Generator G3: 1000 MVA, 20 kV,  $X_d'' = 0.17$ ,  $X_2 = 0.20$ ,  $X_0 = 0.09$  per unit
- Transformer T1: 500 MVA, 13.8 kV  $\Delta$ /500 kV Y,  $X = 0.12$  per unit
- Transformer T2: 750 MVA, 18 kV  $\Delta$ /500 kV Y,  $X = 0.10$  per unit
- Transformer T3: 1000 MVA, 20 kV  $\Delta$ /500 kV Y,  $X = 0.10$  per unit
- Each line:  $X_1 = 50$  ohms,  $X_0 = 150$  ohms

The inductor connected to generator G3 neutral has a reactance of 0.028 pu. Draw the zero-, positive-, and negative-sequence reactance diagrams using a 1000-MVA, 20-kV base in the zone of generator G3

Q5/ A single-line diagram of a four-bus system is shown in Figure for which ZBUS is given below:

$$Z_{BUS} = j \begin{bmatrix} 0.25 & 0.2 & 0.16 & 0.14 \\ 0.2 & 0.23 & 0.15 & 0.151 \\ 0.16 & 0.15 & 0.196 & 0.1 \\ 0.14 & 0.151 & 0.1 & 0.195 \end{bmatrix} \text{ per unit}$$

Let a three-phase fault occur at bus 2 of the network.

- (a) Calculate the initial symmetrical rms current in the fault.
- (b) Determine the voltages during the fault at buses 1, 3, and 4.
- (c) Compute the fault currents contributed to bus 2 by the adjacent un faulted buses 1, 3, and 4.
- (d) Find the current flow in the line from bus 3 to bus 1. Assume the pre fault voltage  $V_f$  at bus 2 to be  $1 \angle 0$  pu, and neglect all pre fault currents.

