



## 2-6 Energy Diagram:

$$\begin{aligned} \sum P_{losses} &= P_1 - P_2 \\ &= P_{fe} + P_{cua} + P_{cue} + P_{fw} + P_{add} \end{aligned}$$

$P_{fe}$ : Iron Losses

$P_{cua}$ : Copper Losses in Armature


$P_{cue}$ : Copper Losses in Excitation Winding

$P_{fw}$ : Friction and Winding Losses

$P_{add}$ : Addition Losses

$$P_{cua} = 3I_a^2 R_a$$

$$P_{cue} = I_e^2 R_e$$

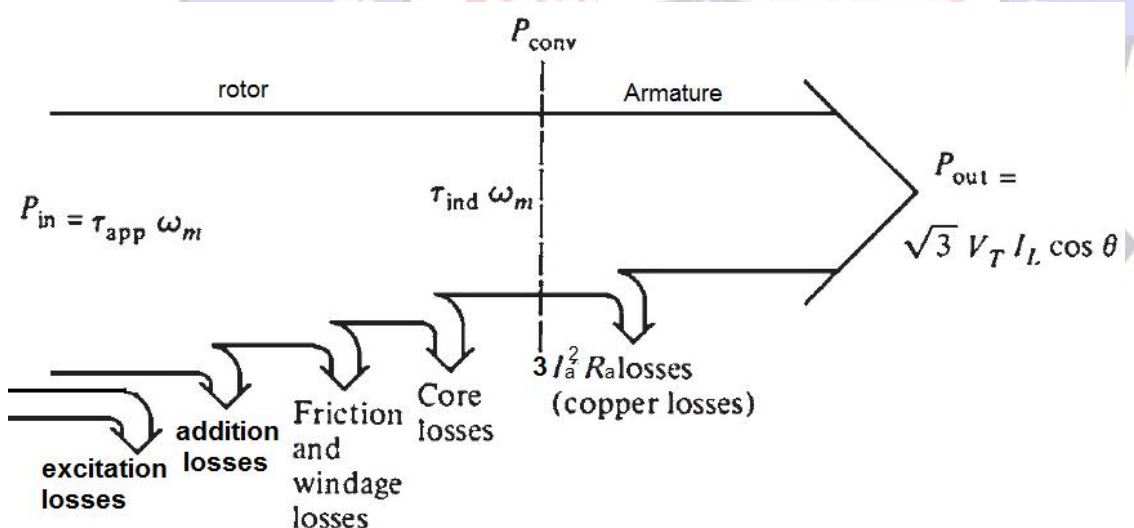

The power flow diagram of a synchronous generator.

$$P_{add} = 0.5\% P_1 \quad , \quad P_{fw} = 50\% P_{losses}$$

$$P_{em} = P_2 + P_{cua} \quad \text{or} \quad P_2 = P_{em} - P_{cua}$$

:For separate excitation then



$$P_i = P_1 + P_{ex}$$

For self-excitation, then:

$$P_o = P_2 - P_{ex}$$

$$\eta\% = \frac{P_o}{P_i} \times 100\% = \frac{P_o}{P_o + P_{fw} + P_{fe} + P_{cua} + P_{ad}} \times 100\%$$

## 2-7 Measuring parameters of synchronous generator model

The three quantities must be determined in order to describe the generator model:

1. The relationship between field current and flux (and therefore between the field current  $I_f$  and the internal generated voltage  $E_A$ );
2. The synchronous reactance;
3. The armature resistance.

### Open circuit Test:


The generator is rotated at the rated speed,

- all the terminals are disconnected from loads,
- the field current is set to zero first.
- Next, the field current is increased in steps and the phase voltage (which is equal to the internal generated voltage  $E_A$  since the armature current is zero) is measured.

Since the unsaturated core of the machine has a reluctance thousands times lower than the reluctance of the air-gap, the

resulting flux increases linearly

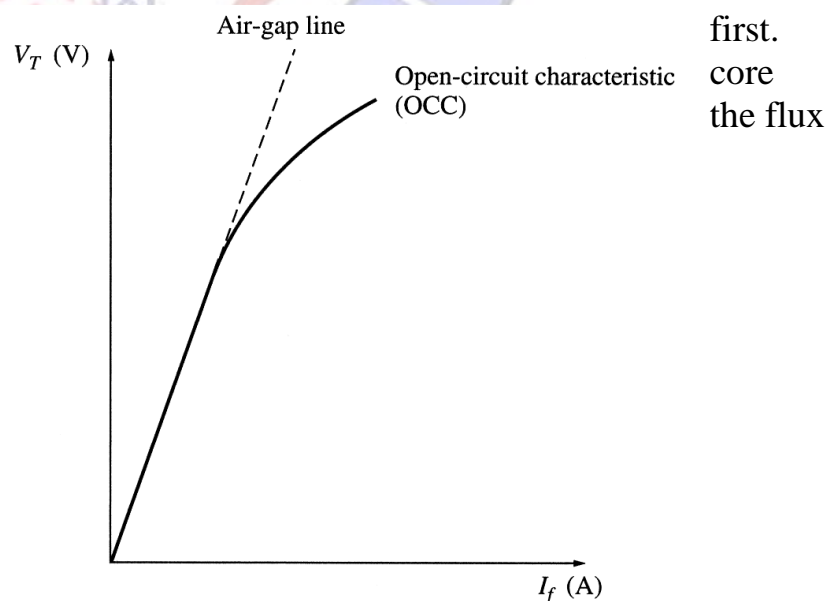When the saturation is reached, the reluctance greatly increases causing to increase much slower with the increase of the mmf.






## Short Circuit Test


In here,

- The generator is rotated at the rated speed, with the field current is set to zero first, and all the terminals are short-circuited through ammeters.
- Next, the field current is increased in steps and the armature current  $I_A$  is measured as the field current is increased. The plot of armature current (or line current) vs. the field current is the short-circuit characteristic (SCC) of the generator.

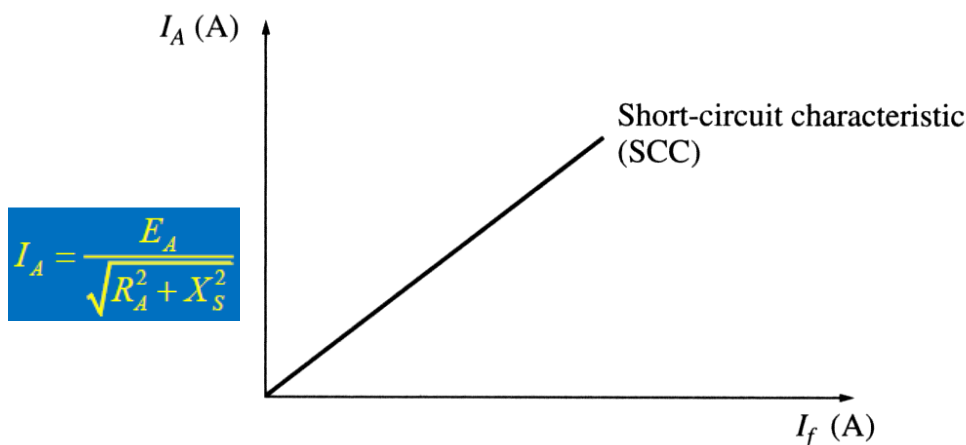The SCC is a straight line since, for the short-circuited terminals, the magnitude of the armature current is



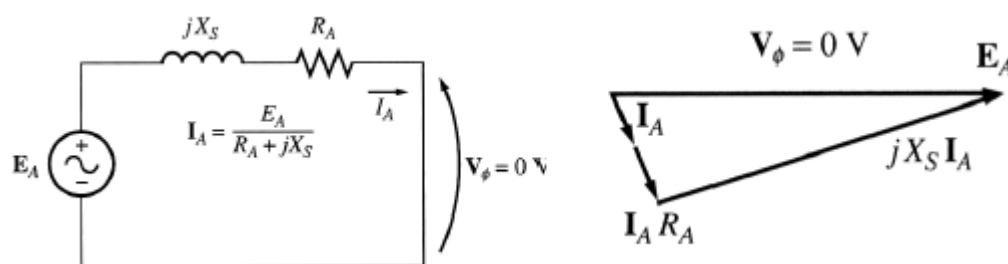The equivalent generator's circuit during SC



An approximate method to determine the synchronous reactance  $X_S$  at a given field current:

1. Get the internal generated voltage  $E_A$  from the OCC at that field current.
2. Get the short-circuit current  $I_{A,SC}$  at that field current
3. Find  $X_S$  from

$$X_S \approx \frac{E_A}{I_{A,SC}}$$

from the SCC.

Since the internal machine impedance is



$$Z_S = \sqrt{R_A^2 + X_S^2} = \frac{E_A}{I_{A,SC}} \approx X_S \quad \{ \text{since } X_S \approx R_A \}$$

