



(3) SAMPLE-AND-HOLD (USING MULTISIM)

1. OBJECTIVES

Experiment the sample-and-hold in Multisim.

2. SAMPLING USING TRANSISTOR

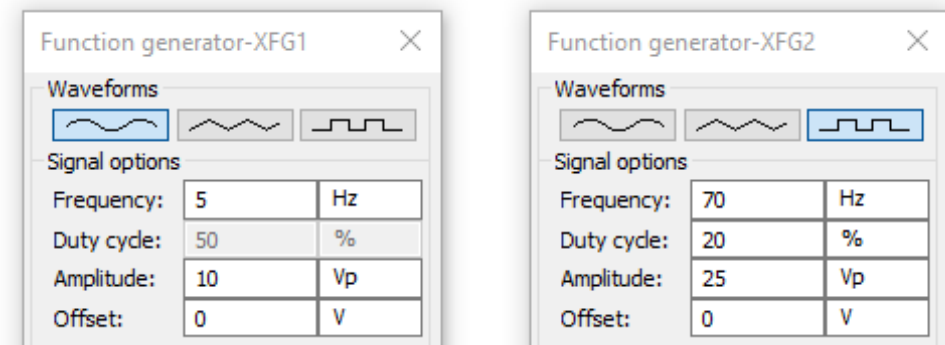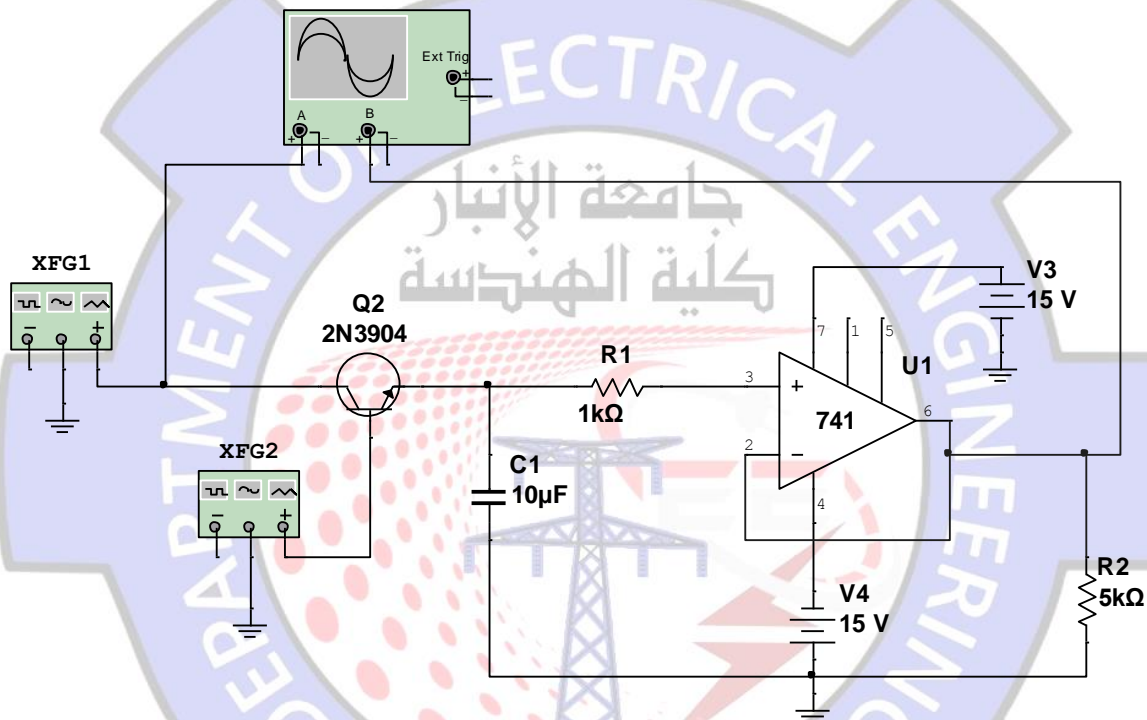- (1) Design and implement the following simple sampling circuit in Multisim.
- (2) Examine the output for different values for the given parameters.



3. HOMEWORK

Change some values of the given circuit to show: “good” and “bad” sampling. Print these results and comment on these cases.