


(6) ANALOG TO DIGITAL CONVERTER USING MULTISIM

1. OBJECTIVES

Design and implement a simple ADC circuit in Multisim.

2. QUANTIZATION AND COMPARISON

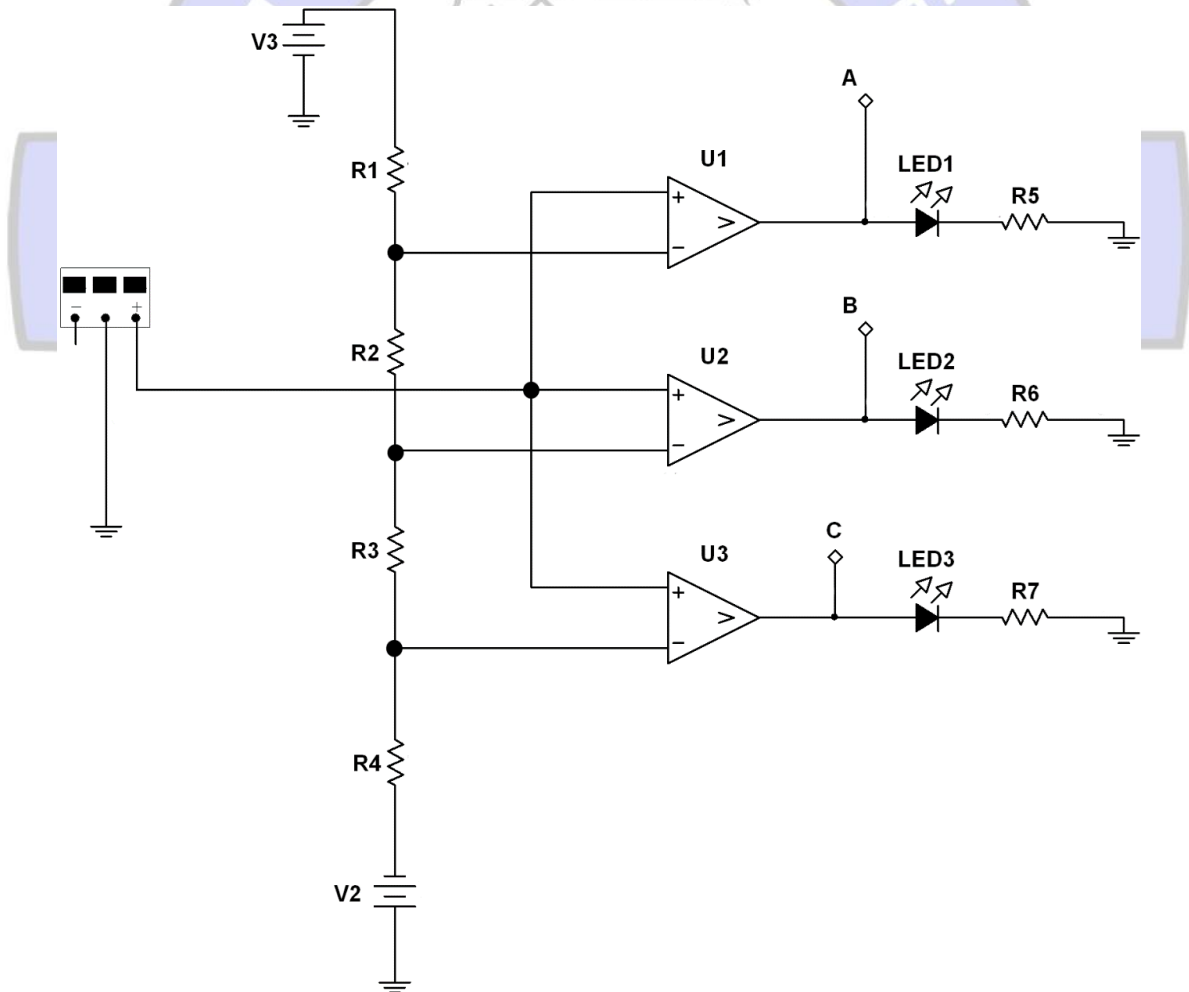- (1) Use a function generator to supply a triangular waveform with $V_p = 6V$ and a frequency of 10Hz.
- (2) Use identical values for the resistors R1 through R4.
- (3) Set the values of the voltage sources V2 and V3 to be the same as V_p above.
- (4) Use a combination of (an ideal comparator, a LED, and a resistor) in three groups.
- (5) Study, run, and explain.





3. BINARY ENCODING

- (1) From the above circuit, the indicated outputs A, B, and C can be mapped to the binary codeword as:

A	B	C	MSB	LSB
0	0	0	0	0
0	0	1	0	1
0	1	1	1	0
1	1	1	1	1

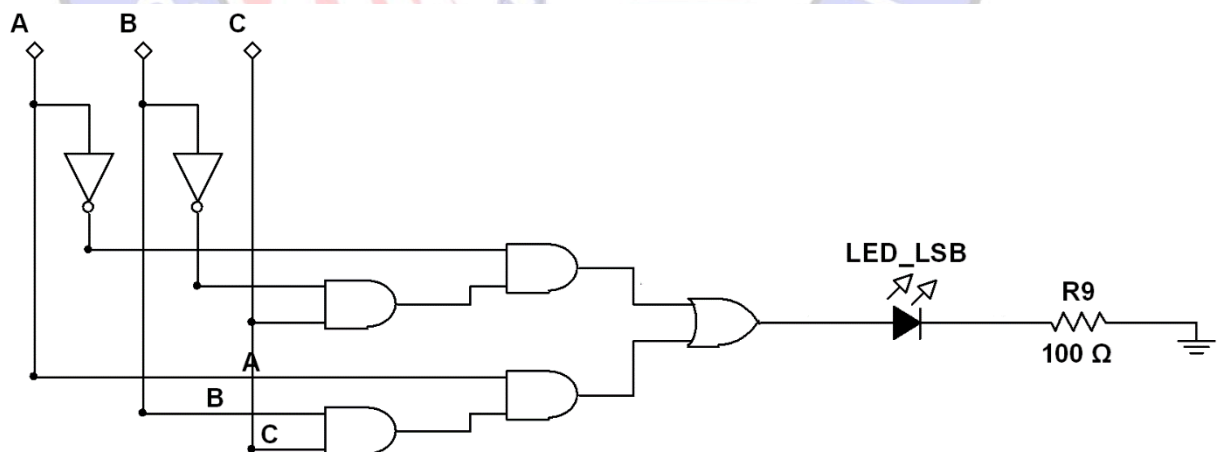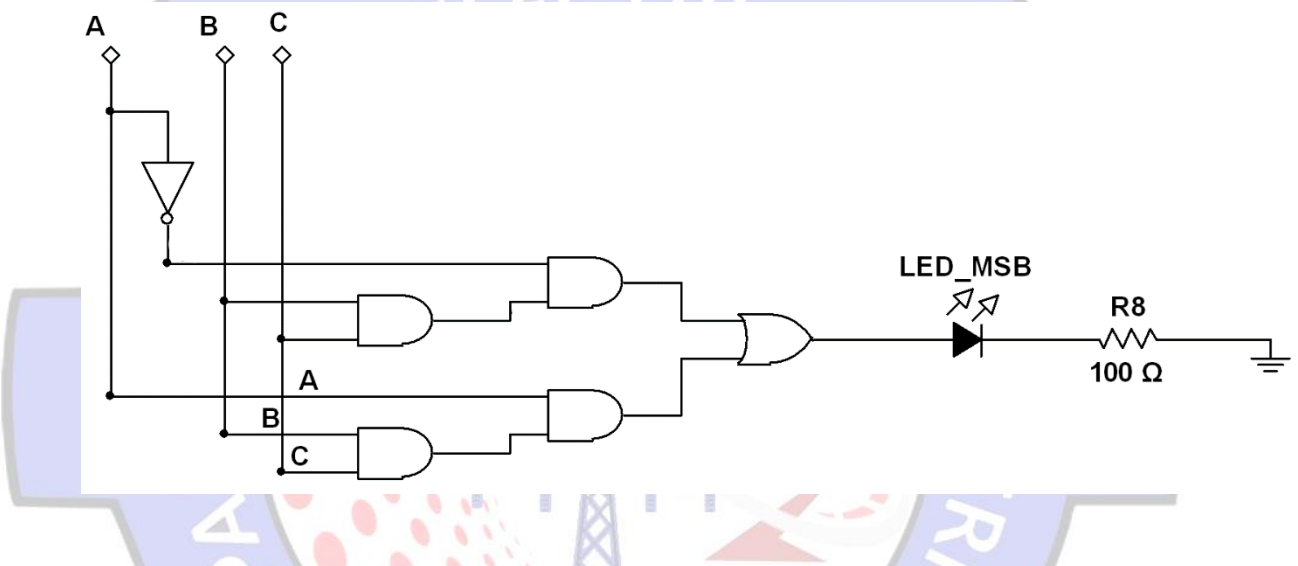- (2) Simple logic circuits can be used to achieve this mapping. So, add the following logic circuits to the main electronic circuit above.



4. HOMEWORK

- Examine different frequencies and voltages at the input and the sampling.
- Simplify the logic circuits.