

Experiment No.8

Norton's Theorems

Object

To prove Norton's theorem practically.

Theory

Norton's theorem states the following: "Any two terminal linear D.C network can be replaced by any equivalent circuit consisting of a constant current source (I_N) and a parallel resistance (R_N), as shown in Fig.1(a).

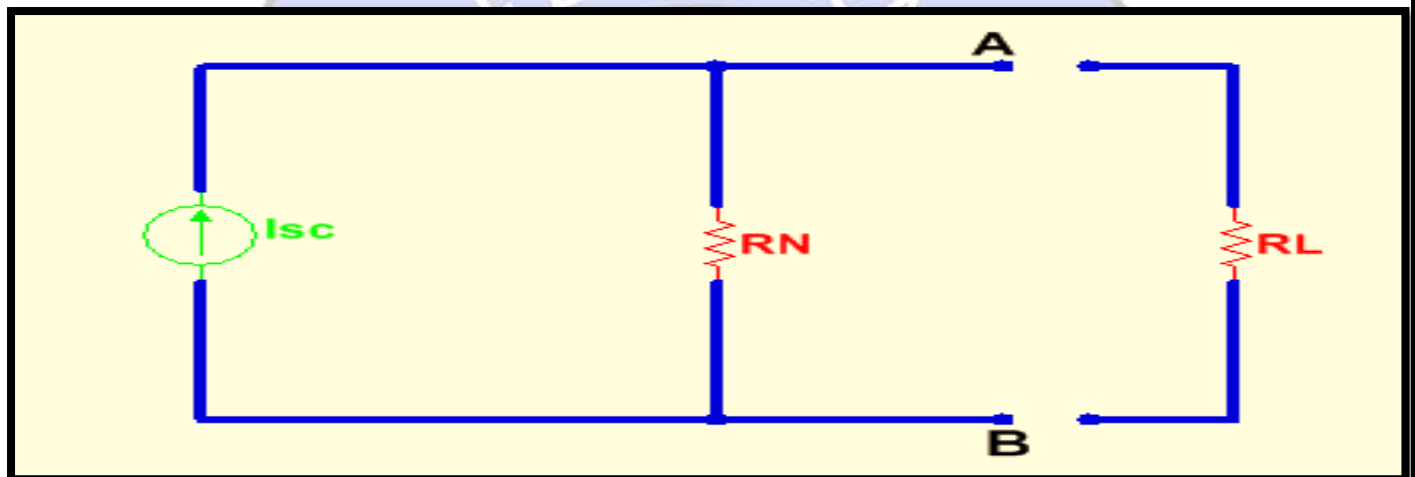


Fig.1(a) Equivalent circuit according to Norton theorem

The constant current is equal to the current which would flow in a short circuit placed across the terminals A and B as shown in Fig.1(b), and is called ($I_{SC} = I_N$).

Where:

I_{SC} : is the short circuit current.

I_N : is the Norton current.

The parallel resistance is the resistance of the network when viewed from A-B open terminals after all voltage and current has been removed and replaced by short or open circuits respectively, as shown in Fig.2

Then according to Fig.2, the current through R_L (when R_L is connected to Norton equivalent circuit) will be:

$$I_L = I_N * R_N / (R_N + R_L)$$

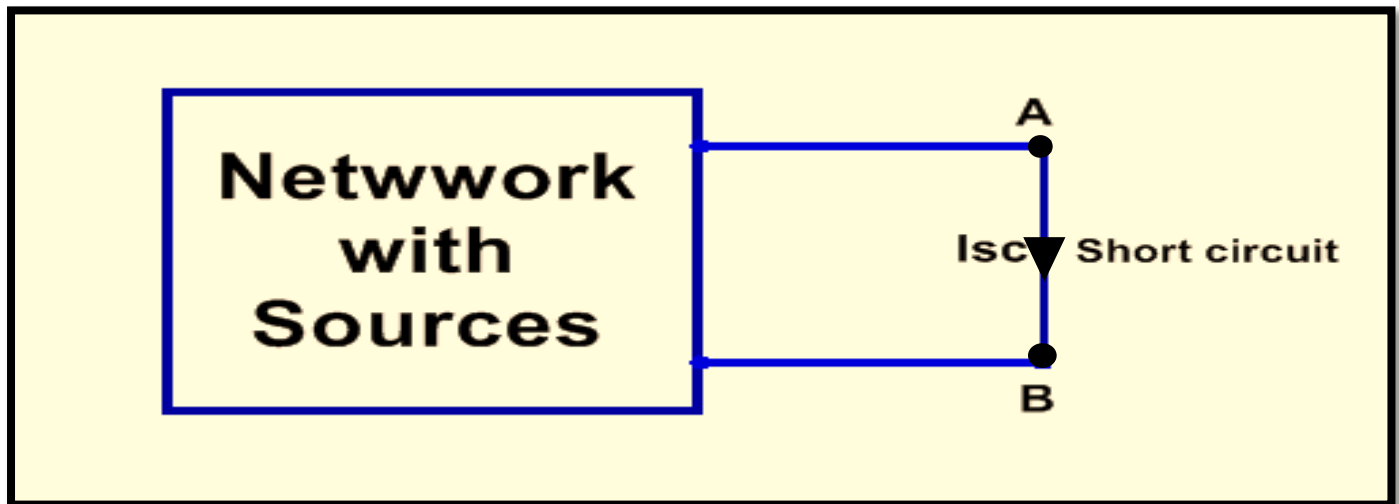


Fig.1(b) Calculating the constant current source $I_{SC} = I_N$

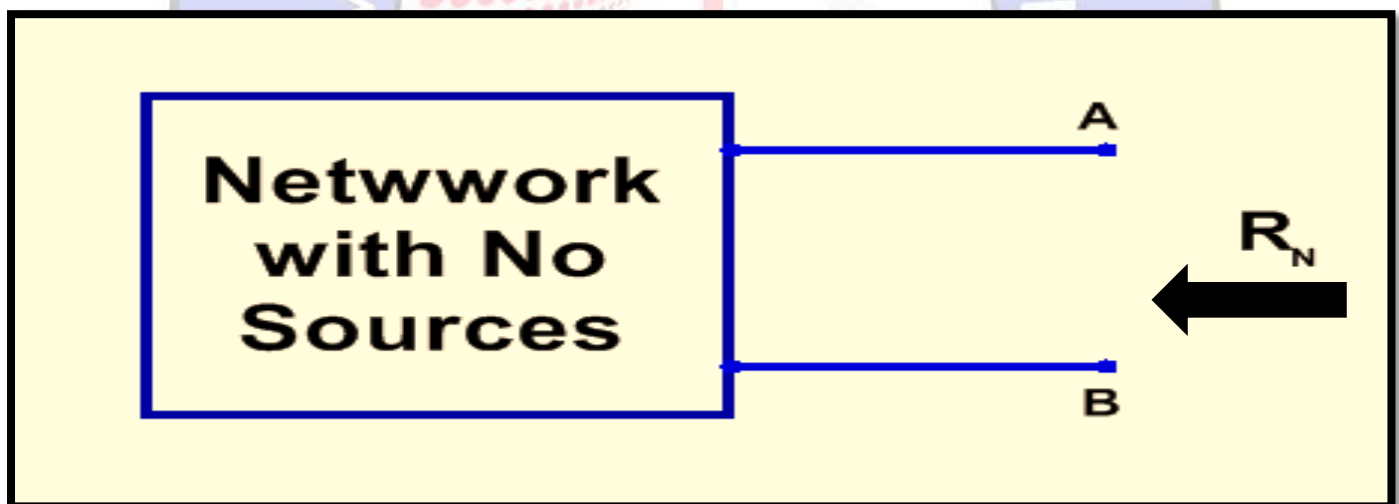


Fig.1(c) Calculating the equivalent parallel resistance R_N

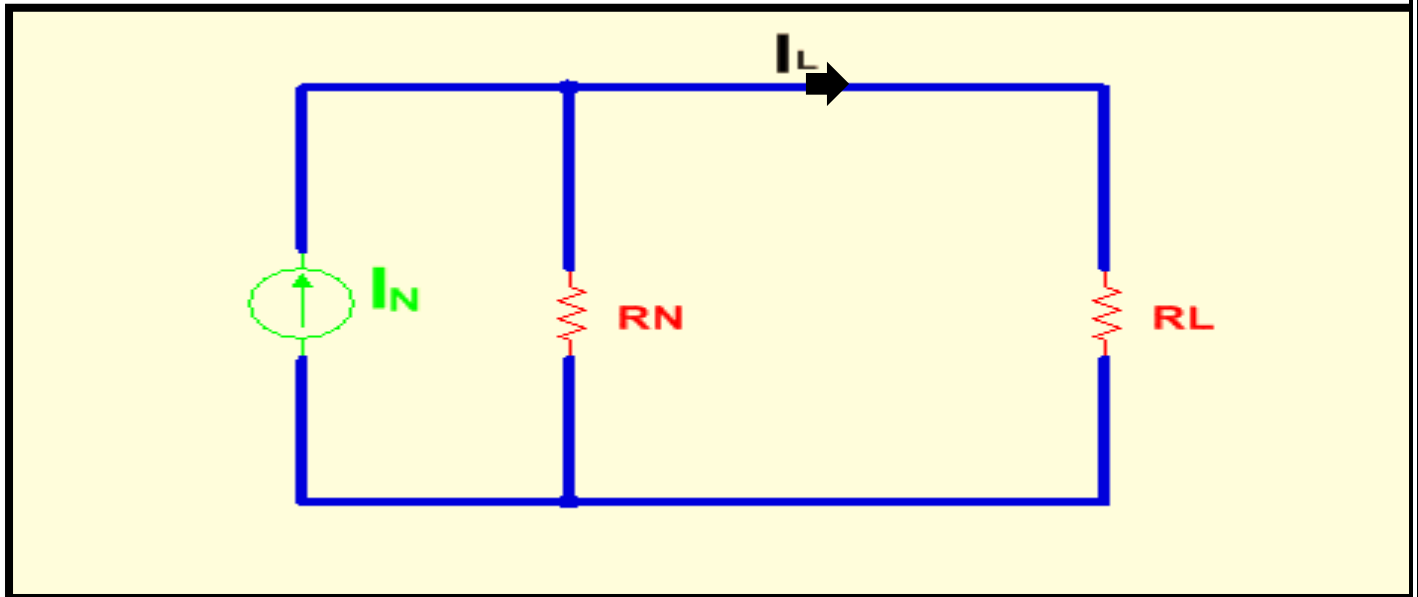


Fig.2 The equivalent Norton circuit with R_L

Apparatus

1. Power supply
2. AVO meter
3. Four resistors

Procedure

1. Connect the circuit as shown in Fig.3

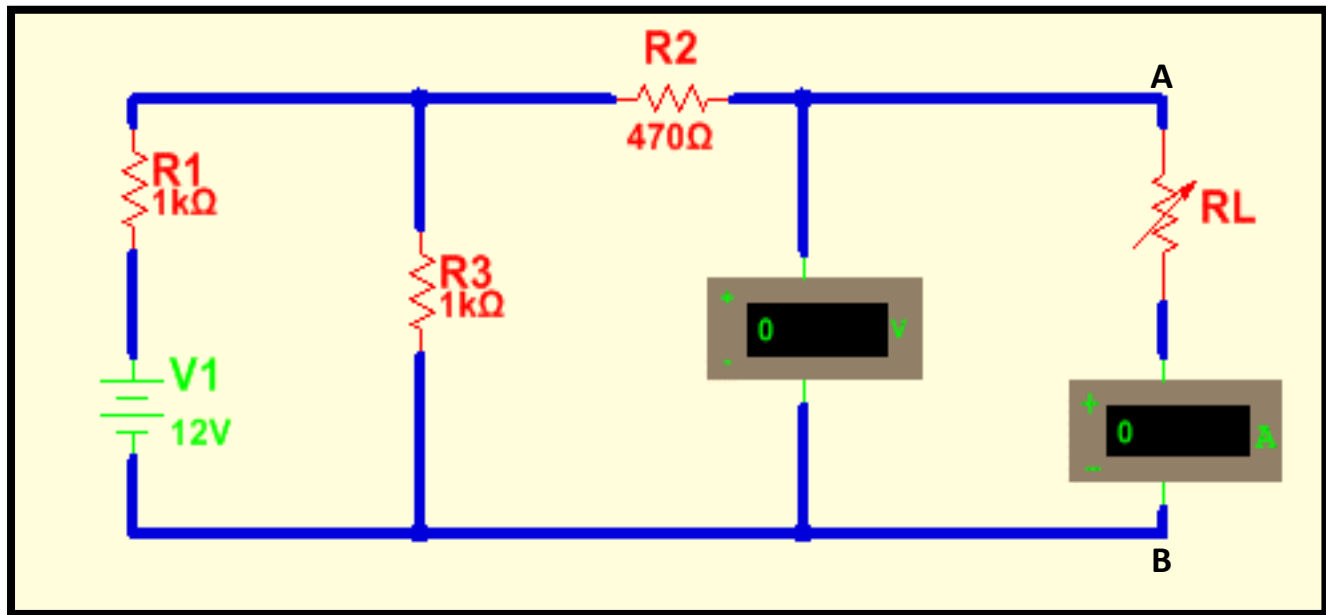



Fig.3

2. Vary R_L resistance as shown in Table (1), measured I_L and V_L in each step, Record your results in the second and third column of Table (1).

R_L Ω	Fig.3		Fig.4	
	I_L (mA)	V_L (Volt)	I_L (mA)	V_L (Volt)
400				
500				
600				
700				
800				

Table.1 Practical Result

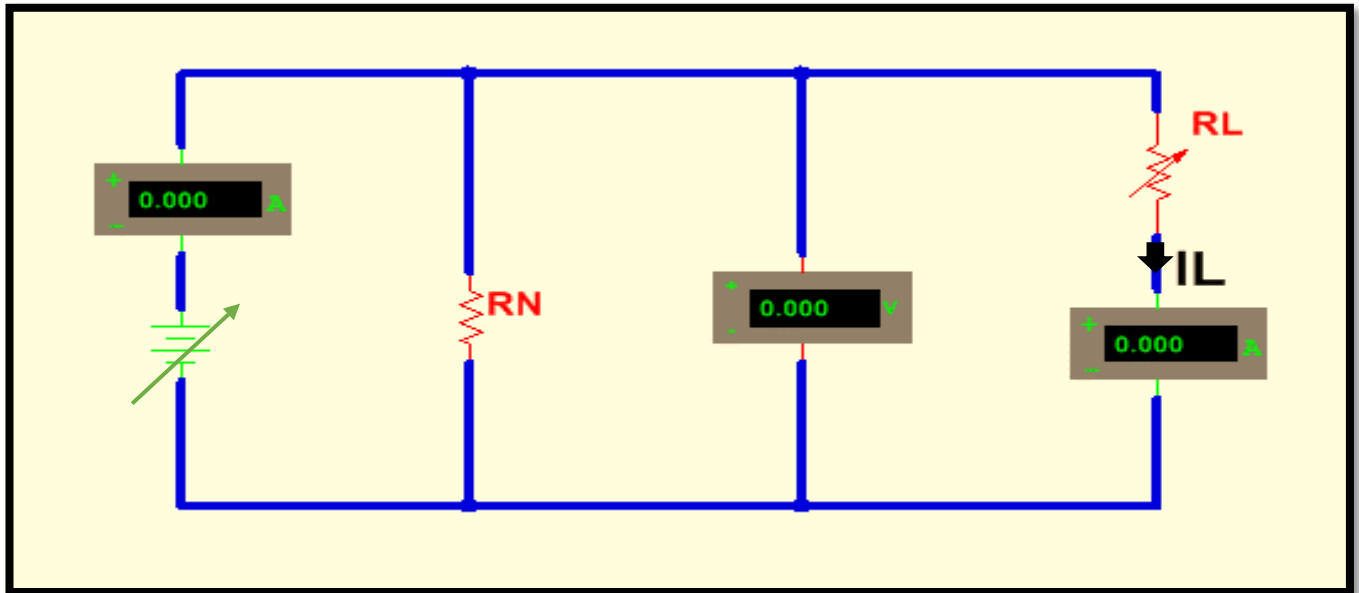3. Disconnect R_L , then measure the short circuit current (I_{SC}) between A and B terminals.
4. Calculate R_N theoretically and connect Norton equivalent circuit as shown in Fig.4. Make sure that the constant current source is remains constant in each step of varying R_L , by means of varying the D.C power supply.



5. Repeat step (2) and record your results in the fourth and fifth column of Table (1).

R_L Ω	Fig.3		Fig.4	
	I_L (mA)	V_L (Volt)	I_L (mA)	V_L (Volt)
400				
500				
600				
700				
800				

Table.2 Theoretical Result

Discussion

1. Calculate I_t and V_i theoretically from Fig.3 and Fig.4, then record your results in Table (2)
2. Compare briefly between the practical and theoretical results.



3. Find the voltage between the open terminals A and B for the network shown in Fig.5 using Norton theorem. And the value of R_L is one half the value of R_N , find the current through R_L

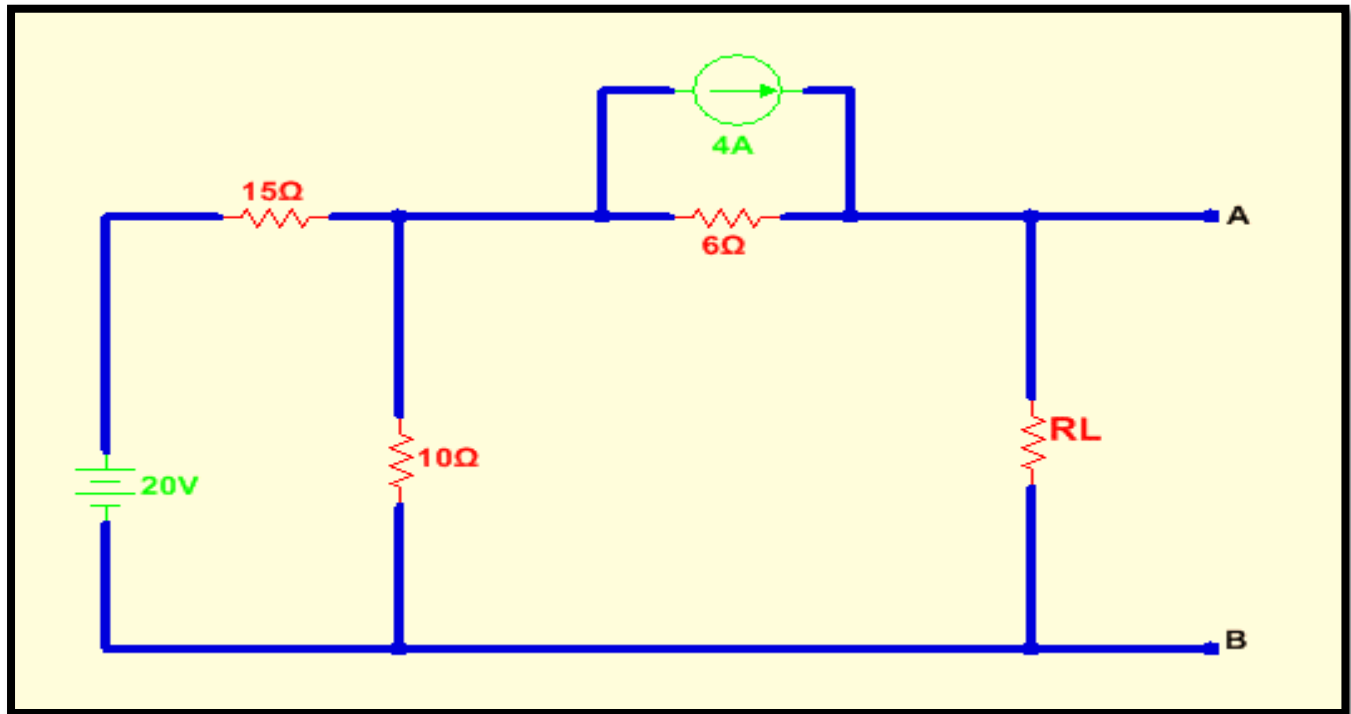


Fig.5