

CHAPTER THREE:

Transformers

NO. of EXP.	NAME of EXP.	PAGE NO.
3.1	Open circuit & Short circuit test on Single – phase Transformer.	53
3.2	Polarity Marking & Conversion of Two-Winding Transformer into Auto Transformer.	57
3.3	Back To Back Test On Single-Phase Transformers.	59
3.4	Regulation & Efficiency of Three- Phase Transformer By Direct Loading.	61
3.5	SCOTT. Connections of Transformer.	63



OPEN CIRCUIT & SHORT CIRCUIT

TEST ON SINGLE – PHASE TRANSFORMER

Apparatus: 1) 230/115V, 1KVA Single Phase transformer (1No.)
2) 0-250V, Single Phase dimmerstat (1No.)

FOR O.C. TEST


3) Voltmeter (0-300 V) (0-150 V) AC. each 1 No.
4) Ammeter (0-1 A) AC, 1 No.
5) Wattmeter (300V, 1A) 1No.

FOR S.C. TEST


6) Voltmeter (0-75 V.) AC. 1No.
7) Ammeter (0-5 A), (0-10 A) Ac. 1 each.
8) Wattmeter (75 V, 5 A) 1No.

Circuit Diagram:

FOR O.C. TEST.

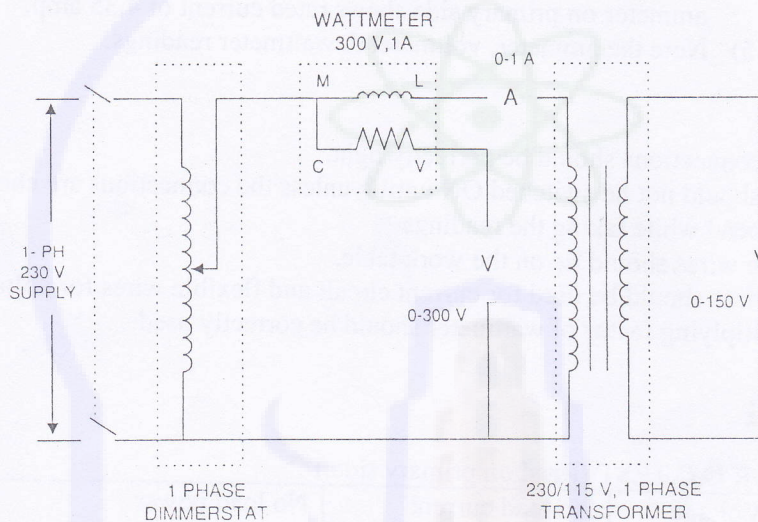

FOR S.C. TEST.

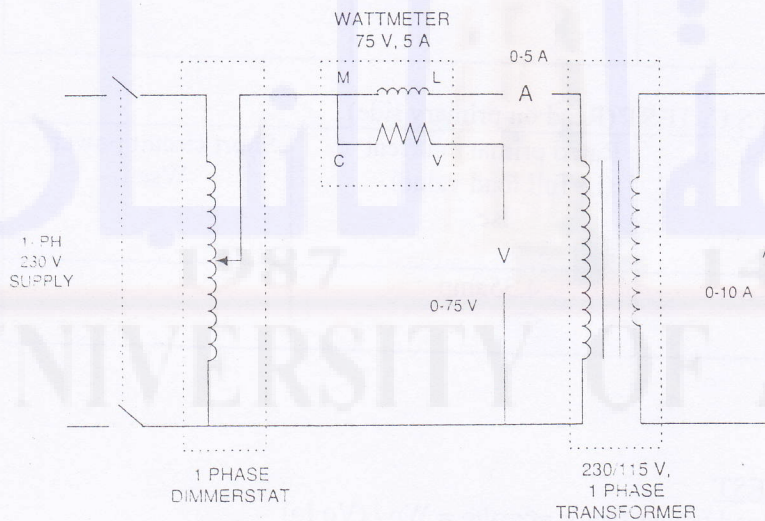

Theory: It should cover the following

- 1) Purpose of O.C. & S.C. test.
- 1) Brief explanation about connection diagram.
- 2) Simplified equivalent circuit of a transformer and its parameters.

- 3) Formulae for efficiency and regulation.
- 4) Formulae for voltage drop for different power factor loads.

Procedure:

FOR O.C. TEST

- 1) Connect the circuit as shown.
- 2) Ensure that the dimmerstat Position is at zero.
- 3) Switch on the single phase AC. Supply.
- 4) Apply rated voltage of 230V, to the primary side of transformer.
- 5) Note the ammeter, voltmeter and wattmeter readings.

FOR S.C. TEST

- 1) Connect the circuit as shown.
- 2) Ensure that the dimmerstat position is at '0' (zero).
- 3) Switch on the single phase AC. Supply.
- 4) Slowly increase the output voltage of the dimmerstat till the ammeter on primary side shows rated current of 4.35 amp.
- 5) Note the ammeter, voltmeter & wattmeter readings.

Precautions:

- 1) All the connections should be perfectly tight.
- 2) Supply should not be switched ON until & unless the connections are checked by the teacher.
- 3) Do not bend while taking the readings
- 4) No loose wires should lie on the work table.
- 5) Thick wires should be used for current circuit and flexible wires for voltage circuits.
- 6) The multiplying factor of wattmeter should be correctly used.

Observations:

FOR O.C. TEST (Read on primary side.)

Rated input Voltage V_0	No load current I_0	No load power W_0
230V		

FOR S.C. TEST (Read on primary side)

Short circuit voltage V_{sc}	Rated primary current (i.e full load value) I_{sc}	Short circuit power W_{sc}
	4.35amp	

Calculations:

FOR O.C. TEST

No load power factor $= \cos\Phi_0 = W_0 / (V_0 I_0)$

Magnetising component of $I_0 = I_\mu = I_0 \sin\Phi_0$ amps.

Core loss component of $I_0 = I_c = I_0 \cos\Phi_0$ amps.

Core loss resistance $R_0 = V_0 / I_c$ ohm.

Magnetising reactance $X_0 = V_0 / I_\mu$ ohms.

Core loss in transformer at any load = W_0

FOR S.C. TEST

Short circuit power factor $\cos\Phi_{sc} = W_{sc} / (V_{sc} I_{sc})$

Short circuit impedance $Z_{sc} = V_{sc} / I_{sc} \Omega$

Short circuit resistance $R_{sc} = W_{sc} / I_{sc}^2 \Omega$

Short circuit reactance $X_{sc} = \sqrt{Z_{sc}^2 - R_{sc}^2} \Omega$

Copper loss in transformer at full load = W_{sc} watts.

Copper loss in transformer at half full load = $W_{sc}/4$ watts.

EFFICIENCIES:

- 1) At full load and at 0.8 power factor

$$\eta = \frac{\text{Full load kVA} \times 10^3 \times \cos\Phi \times 100}{\text{Full load KVA} \times 10^3 \times \cos\Phi + \text{core loss} + \text{copper loss at full load}}$$

- 2) All half full load and U.P.F.

$$\eta = \frac{\text{Half load KVA} \times 10^3 \times \cos\Phi \times 100}{\text{Half load KVA} \times 10^3 \times \cos\Phi + \text{core loss} + \text{copper loss at half load}}$$

REGULATIONS:

- 1) At full load and 0.8 power factor lagging.

Voltage drop = $I_{sc} (R_{sc} \cos\Phi + X_{sc} \sin\Phi)$

$$\% \text{ Regulation} = \frac{\text{Voltage drop} \times 100}{\text{Rated primary voltage (V}_0\text{)}}$$

- 2) At full load and 0.8 power factor leading.

Voltage drop = $I_{sc} (R_{sc} \cos\Phi - X_{sc} \sin\Phi)$

$$\% \text{ Regulation} = \frac{\text{Voltage drop} \times 100}{\text{Rated primary voltage (V}_0\text{)}}$$

- 3) At full load and U.P.F.

Voltage drop = $I_{sc} R_{sc} \cos\Phi$

$$\% \text{ Regulation} = \frac{\text{Voltage drop} \times 100}{\text{Rated primary voltage (V}_0\text{)}}$$

Equivalent Circuit:

Draw simplified equivalent circuit showing calculated values of all parameters on it.

- Result: -** Full load efficiency at 0.8 p.f. =
Full load efficiency at U.P.F. =
Full load regulation at 0.8 lagging p.f. =
Full load regulation at 0.8 leading p.f. =
Full load regulation at U.P.F. =
 $R_o =$; $X_o =$
 $R_{sc} =$; $X_{sc} =$

Viva Questions: -

- Q.1. What is the significance of O.C. & S.C. test?
- Q.2. Why h.v. winding is kept open during O.C. test and l.v. winding is shorted during S.C. test in case of large transformers?
- Q.3. In O.C. test, a voltmeter is connected across secondary winding and still it is called as O.C. test. Why?
- Q.4. What will happen if dc supply instead of ac supply is applied to a transformer?
- Q.5. Which is the alternate method for finding efficiency and regulation of a transformer other than O.C. & S.C. tests ? What are their advantages over each other?
- Q.6. What is the importance of equivalent circuit?
- Q.7. Why regulation of transformer is negative for leading p.f. load?
- Q.8. " The wattmeter reading during O.C. test is considered as core loss while wattmeter reading during S.C. test is considered as copper loss" Justify.

