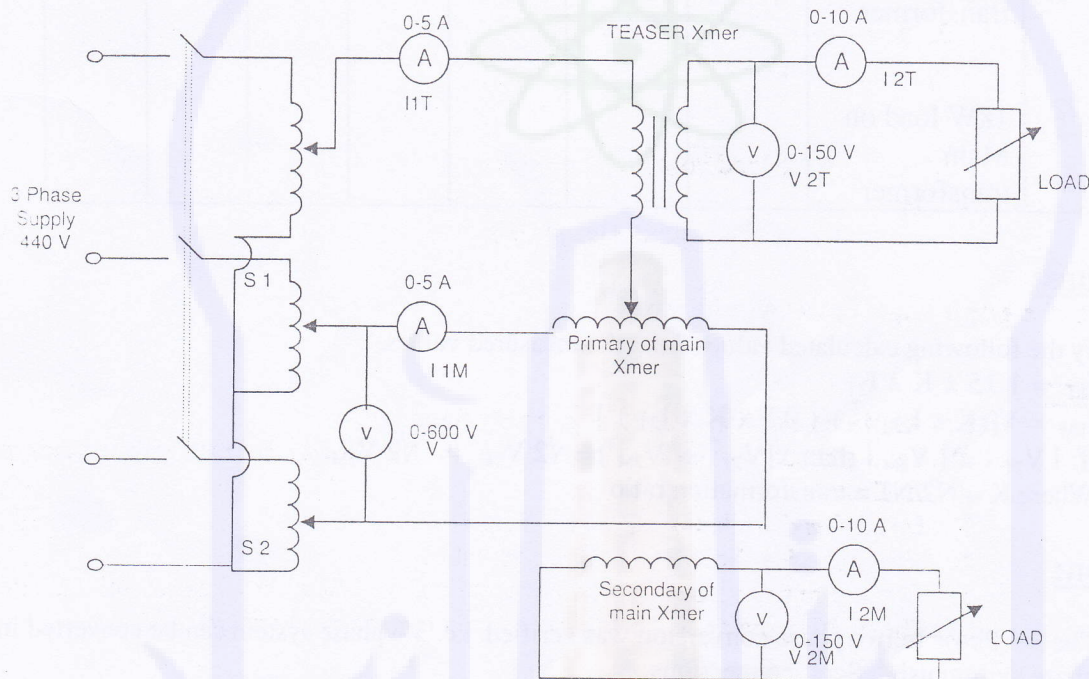


SCOTT. CONNECTIONS OF TRANSFORMER

Apparatus: Ammeters (0-5 A, AC) 3 Nos ; (0-10 A, AC) 2 Nos.
 Voltmeters (0-600 V; AC) 1 Nos, (0-150 V; AC) 2 Nos.
 Transformer 1-phase, 1 kVA, with 86.6% tap on 415V side
 Transformer 1-phase, 1 kVA, with 50% tap on 415V side
 Dimmer stat (0-440 V, 3 phase) 1 Nos.
 Connecting wires, etc.

Circuit Diagram:



Theory: It should cover the following.

1. Explanation and mathematical proof of how a balanced two-phase supply can be obtained by using Scott connection.
2. Phasor diagram illustrating the phase quadrature between the secondary voltages of the two transformers.

Procedure:

1. Connect the circuit as shown.
2. Use 86.6% tapping for teaser transformer and 50% tapping for main transformer.
3. Keep both loads zero
4. Switch on the 3-ph. supply and take the readings.
5. Vary the loads as per given in observation table and take the readings.

Observation Table:

[A]FOR BALANCED LOAD

S. No.	Load condition	Teaser transformer			Main transformer			
		I _{1T}	I _{2T}	V _{1T}	I _{1M}	I _{2M}	V _{1M}	V _{2M}
1.	No load							
2.	1kW load on both transformers							

[B]FOR UNBALANCED LOAD

S. No.	Load condition	Teaser transformer			Main transformer			
		I _{1T}	I _{2T}	V _{1T}	I _{1M}	I _{2M}	V _{1M}	V _{2M}
1.	1kW load on Teaser transformer							
2.	1kW load on Main transformer							

Calculations:

Verify the following calculated values from the measured values.

- $I_{1T} = 1.15 \times K \times I_{2T}$
- $I_{1M} = \sqrt{[(K \times I_{2M})^2 + (0.5 \times K \times I_{2T})^2]}$
- If $|V_{2T}| = |V_{2M}|$ then $\sqrt{[V_{2T}^2 + V_{2M}^2]} = \sqrt{2} V_{2T} = \sqrt{2} V_{2M}$
Where $K = N_2/N_1 =$ transformation ratio

Conclusion:

The 3 – Phase to two phase conversion was verified. i.e. 3 – phase system can be converted in to two phase system using Scott-connections.

Viva Questions:

- 1) Is it possible to obtain a 3- phase a.c. supply from 2 – phase a.c. supply by using Scott-connection ?
- 2) Where dose the Scott-connection find its use?
- 3) If the two transformers used in Scott. Connection are identical, then how many primary turns of the teaser transformer are actually used?
- 4) What is the ratio of number of turns on the primaries of teaser transformer in case of Scott-connection?
- 5) Are the two transformers connected for Scott-connection coupled magnetically?
- 6) Do you know any other method of conversion of 3-phase a.c. supply from 2-phase a.c. supply?