



# Fundumantal of Electronic I

## Second Class

Chapter02: Diode Applications

Lec02\_p4


**Munther N. Thiyab**

**2019-2020**



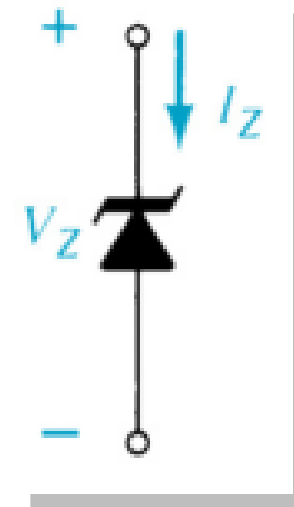
## Zener Diodes

- A **Zener diode** is a type of diode that permits current not only in the forward direction like a normal diode, but also in the reverse direction if the voltage is larger than the breakdown voltage known as "Zener voltage" ( $V_Z$ ).
- Common Zener voltages are between 1.8 V and 200 V.
- Zener diode is used as regulator.





## Zener Diodes

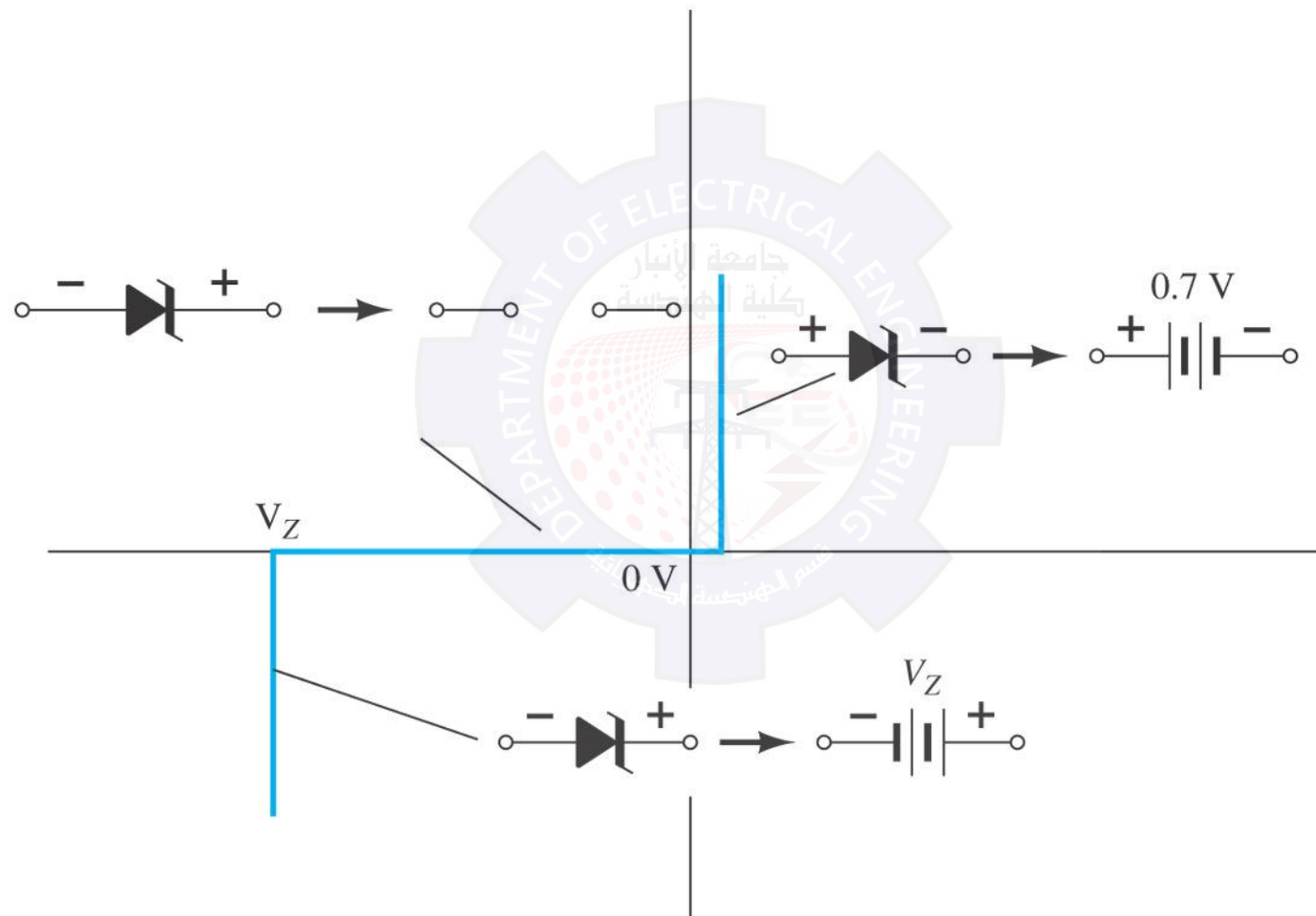

**Approximate equivalent circuits for the Zener diode in the three possible regions of application.**



**Example 2.24** Determine the reference voltages provided by the network which uses a white LED (4V) to indicate power is on. What is the power delivered to the LED and to the 6 V Zener diode.

$$V_{o1} = V_{Z2} + V_K = 3.3 + 0.7 = 4V$$

$$V_{o2} = V_{o1} + V_{Z1} = 4 + 6 = 10V$$

The 4-V across the white LED

$$I_R = I_{LED} = \frac{40 - V_{o2} - V_{LED}}{1.3k} = \frac{40 - 10 - 4}{1.3k} = \frac{26}{1.3k} = 20mA$$

the power delivered by the supply


$$P_S = E \times I_S = E \times I_R = (40V) \times (20mA) = 800mW$$

the power absorbed by the LED

$$P_{LED} = V_{LED} \times I_{LED} = (4V) \times (20mA) = 80mW$$

the power absorbed by 6-V Zener diode


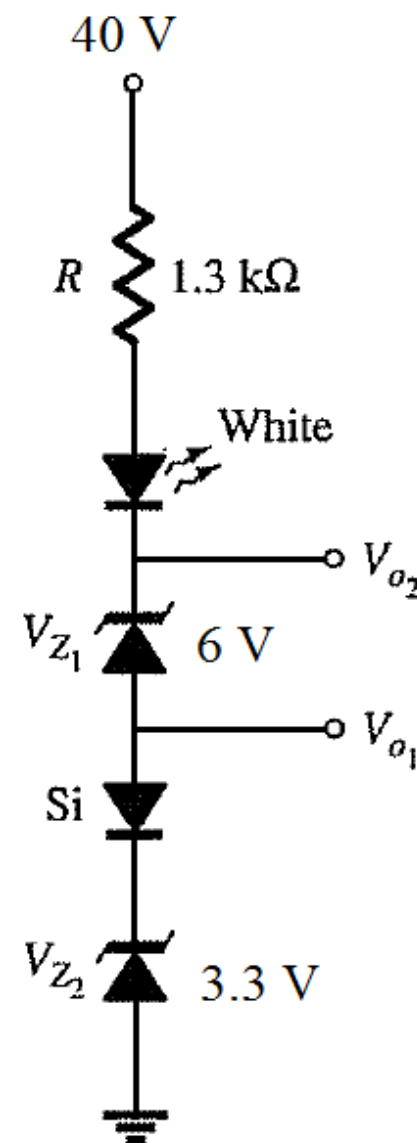
$$P_Z = V_Z \times I_Z = (6V) \times (20mA) = 120mW$$





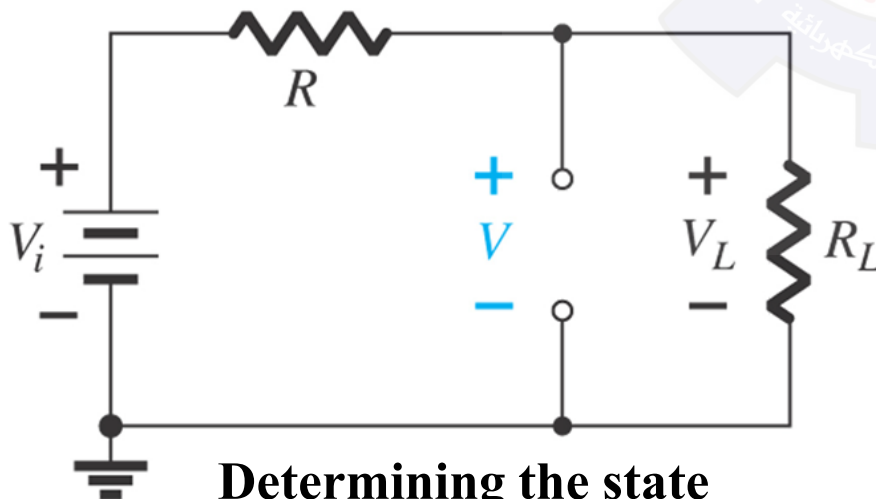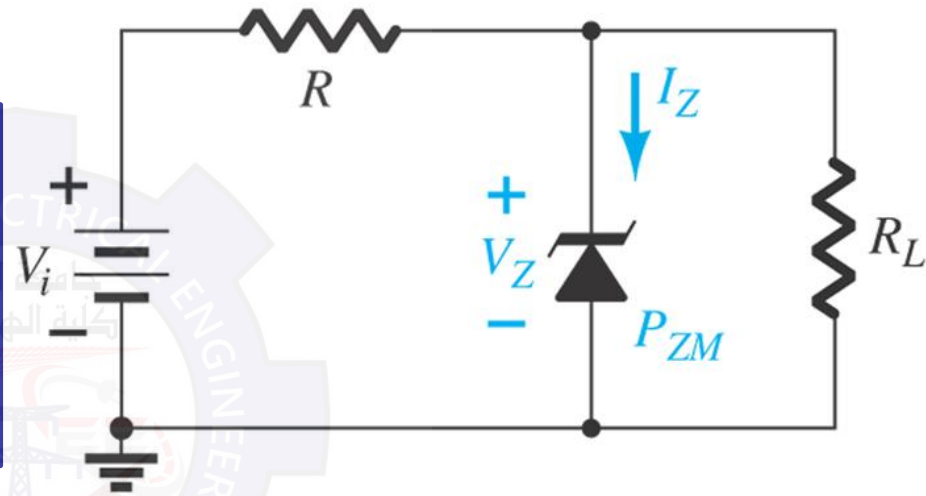
## Basic Zener Regulator

Remove Zener diode from network.  
Calculate  $V$  across open circuit.  
If  $V \geq V_Z$ , Zener diode is on.  
If  $V < V_Z$ , Zener diode is off.



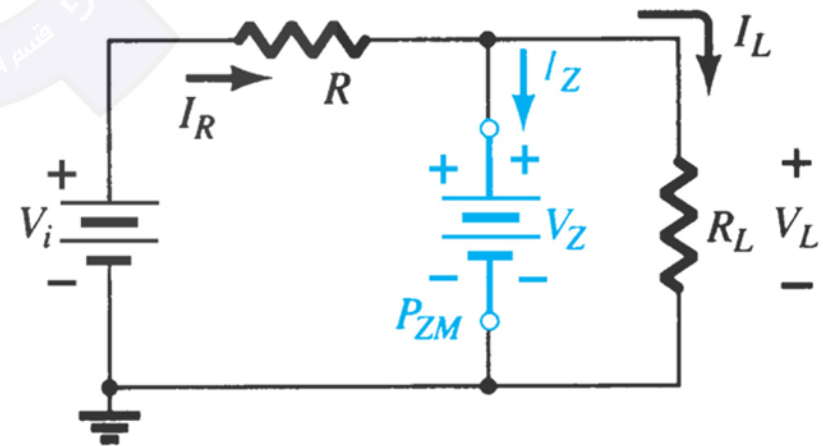Determining the state  
of the Zener diode.




Substituting the Zener equivalent  
for the "on" situation



## Example 2.26

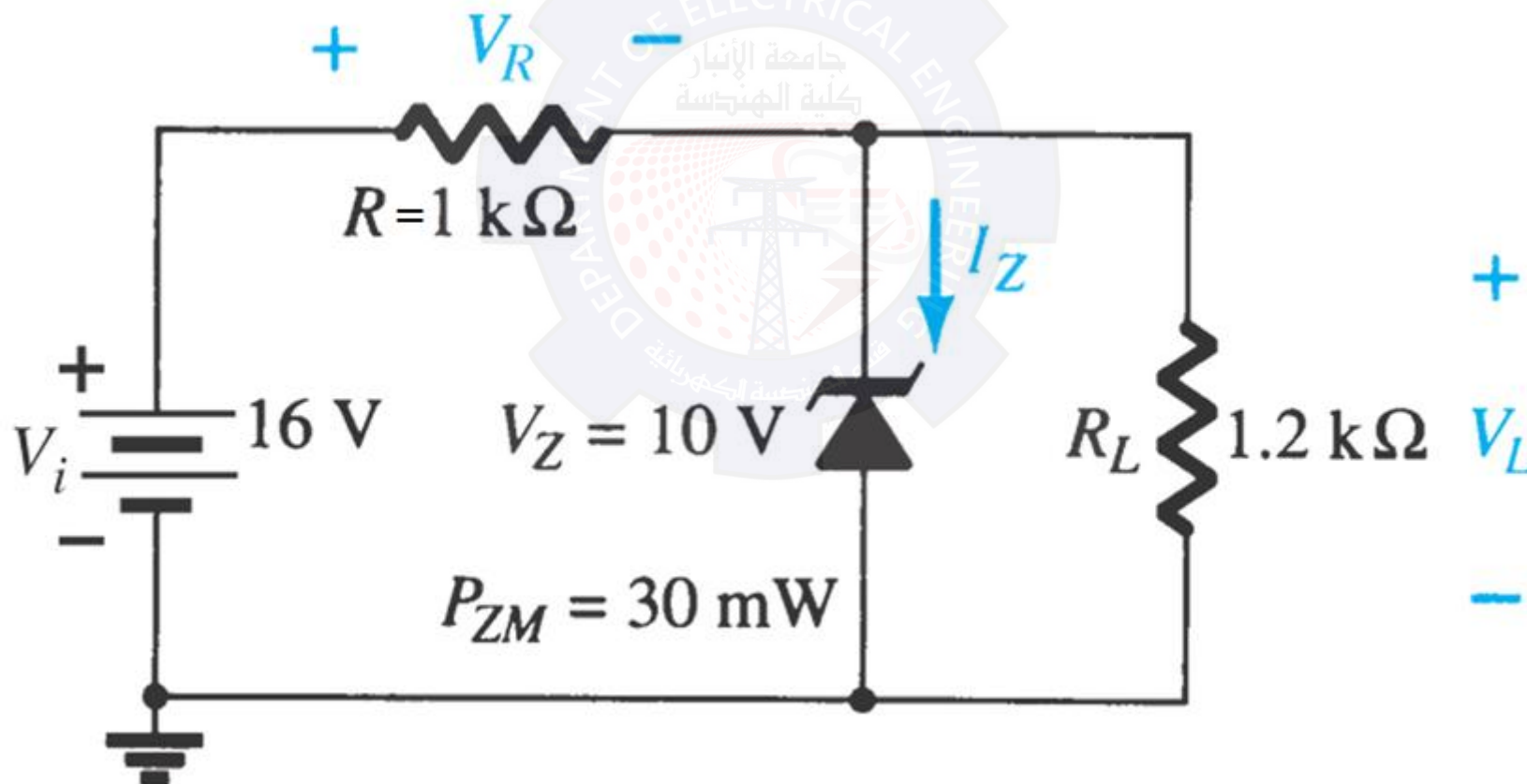
- (a) For the Zener diode network, determine  $V_L$ ,  $V_R$ ,  $I_Z$  and  $P_Z$ .  
(b) Repeat part (a) with  $R_L = 3 \text{ k}\Omega$ .






## Example 2.26 - Solution

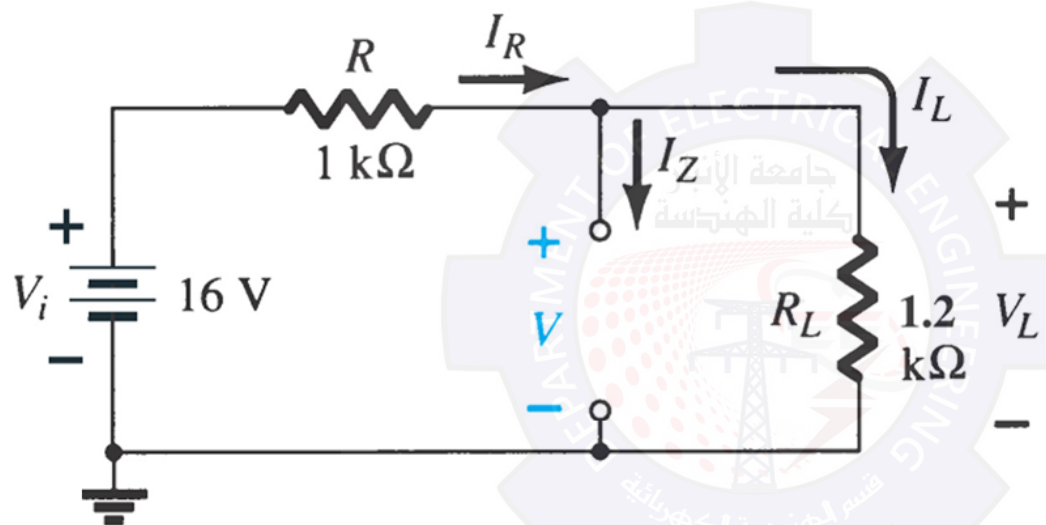(a) determine  $V_L$ ,  $V_R$ ,  $I_Z$  and  $P_Z$ . ( $R_L=1.2 \text{ k}\Omega$ )




$V=8.73 \text{ V } (<10)$   
 $I_Z=0$

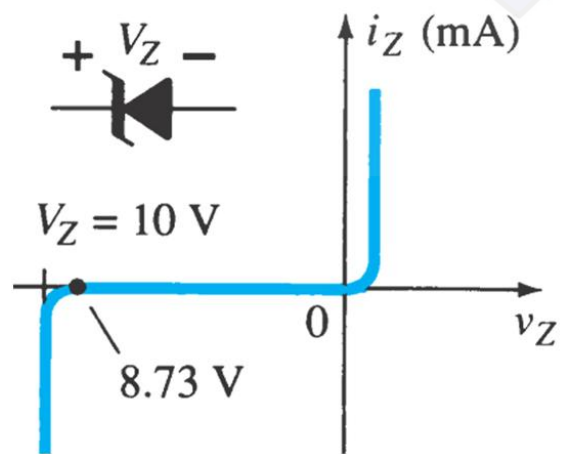




## Example 2.26 - Solution

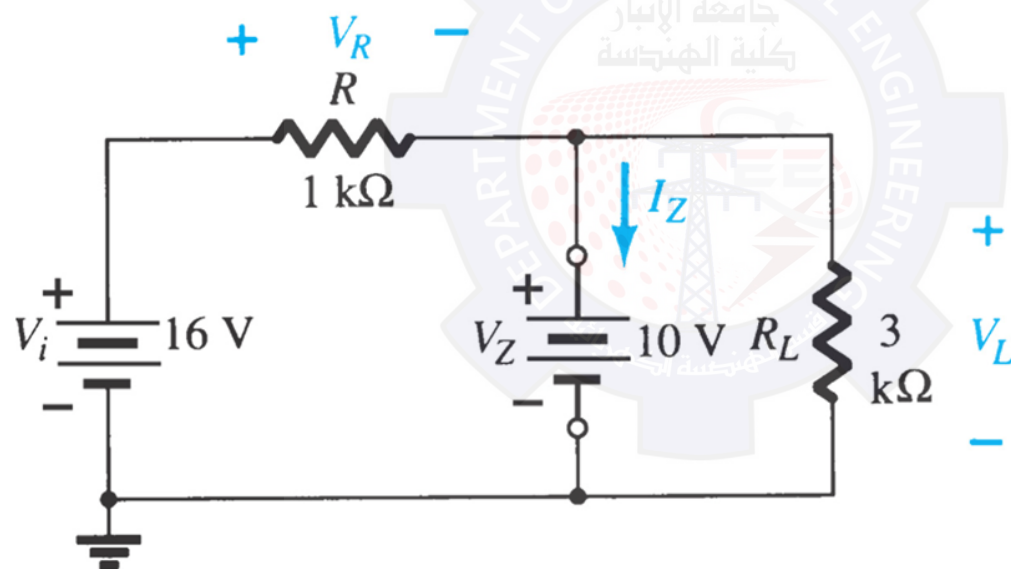(b) determine  $V_L$ ,  $V_R$ ,  $I_Z$  and  $P_Z$ . ( $R_L=3 \text{ k}\Omega$ )





## Voltage Doubler

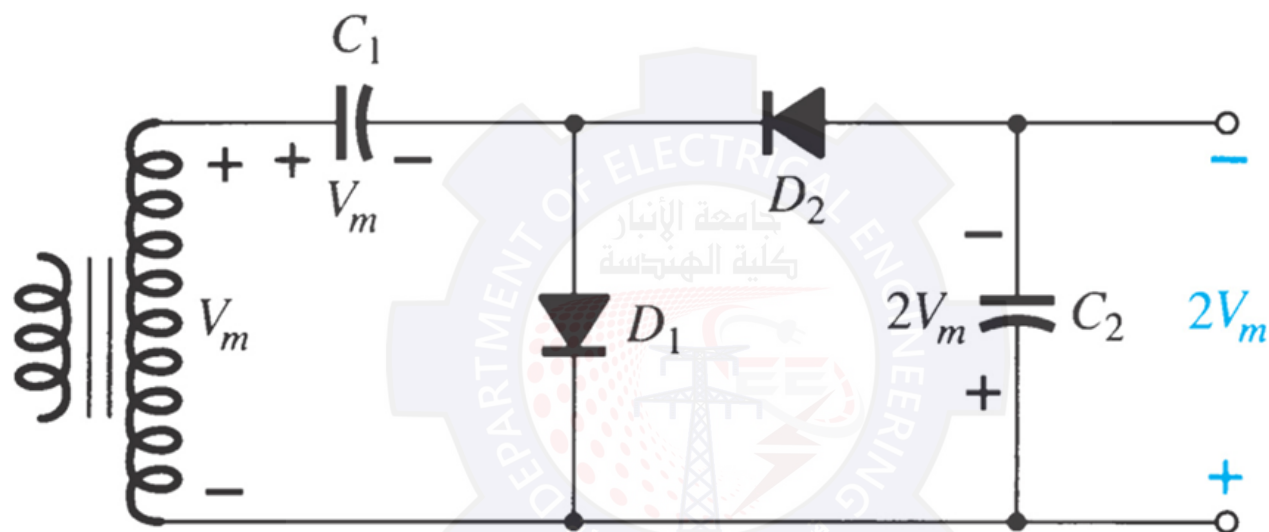

**This half-wave voltage doubler's output can be calculated by:**


$$V_{\text{out}} = V_{C_2} = 2V_m$$

**where  $V_m$  = peak secondary voltage of the transformer**



# Voltage Doubler

- **Positive Half-Cycle**
  - $D_1$  conducts
  - $D_2$  is switched off
  - Capacitor  $C_1$  charges to  $V_m$
- **Negative Half-Cycle**
  - $D_1$  is switched off
  - $D_2$  conducts
  - Capacitor  $C_2$  charges to  $2V_m$

$$V_{\text{out}} = V_{C2} = 2V_m$$


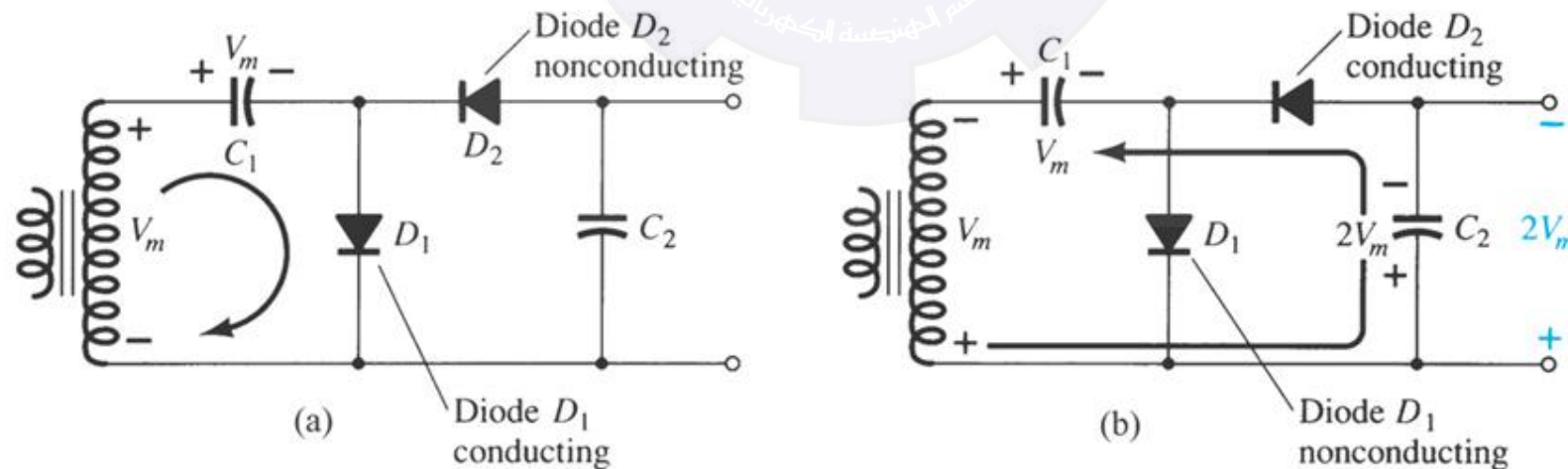


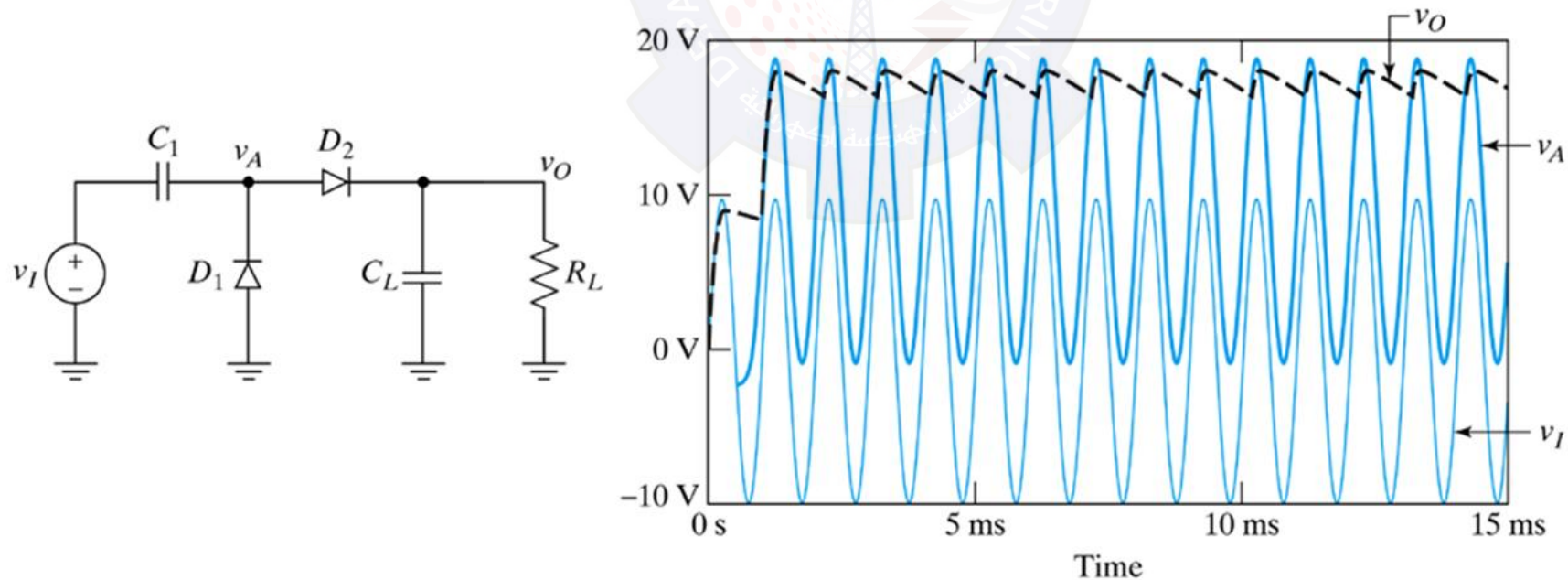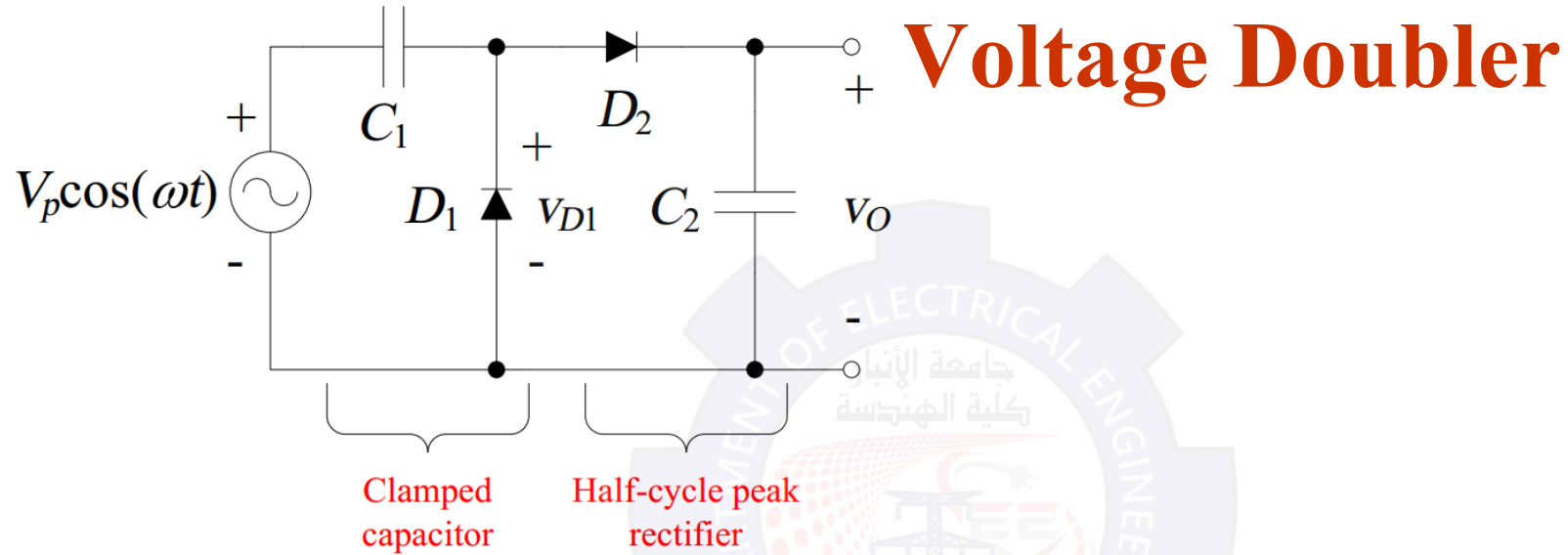(a) positive half-cycle; (b) negative half-cycle.





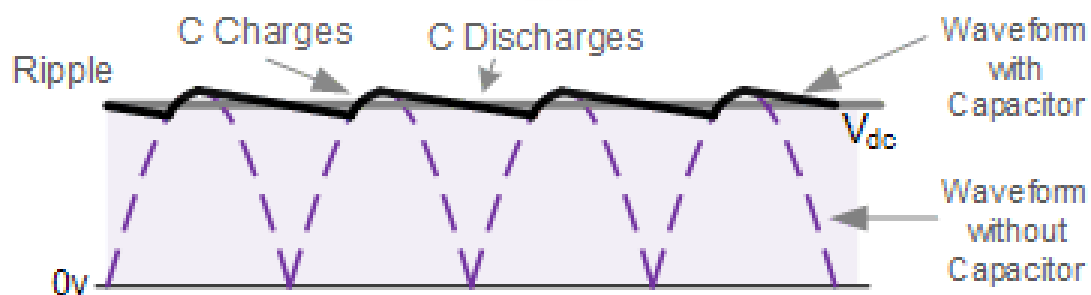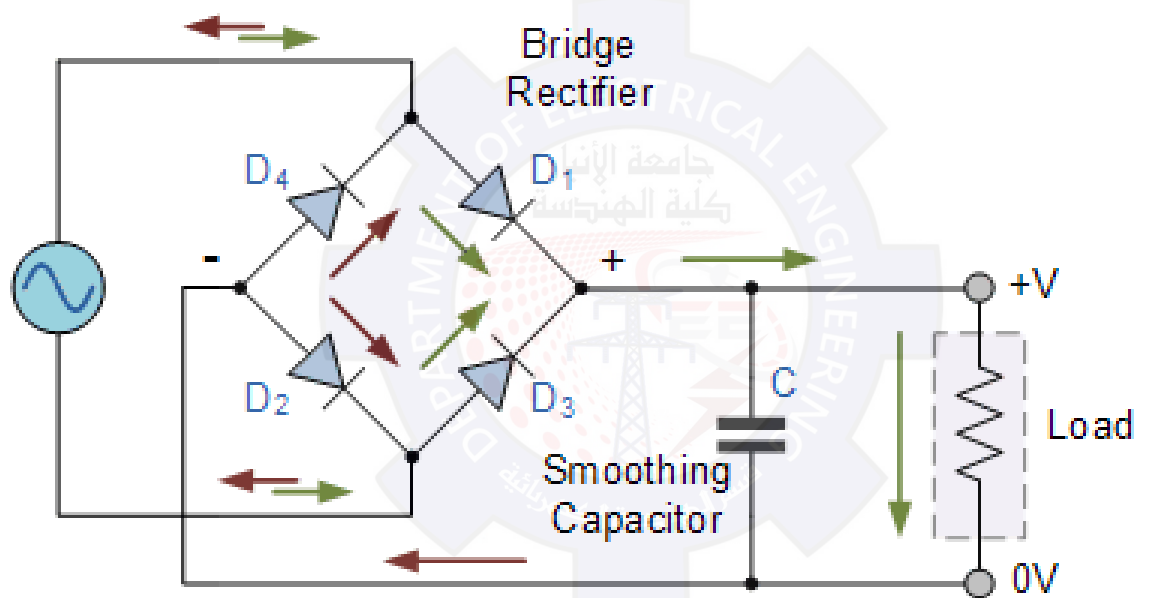
# Practical Applications (AC to DC Converter)



Resultant Output Waveform

# Practical Applications


## Battery Charger

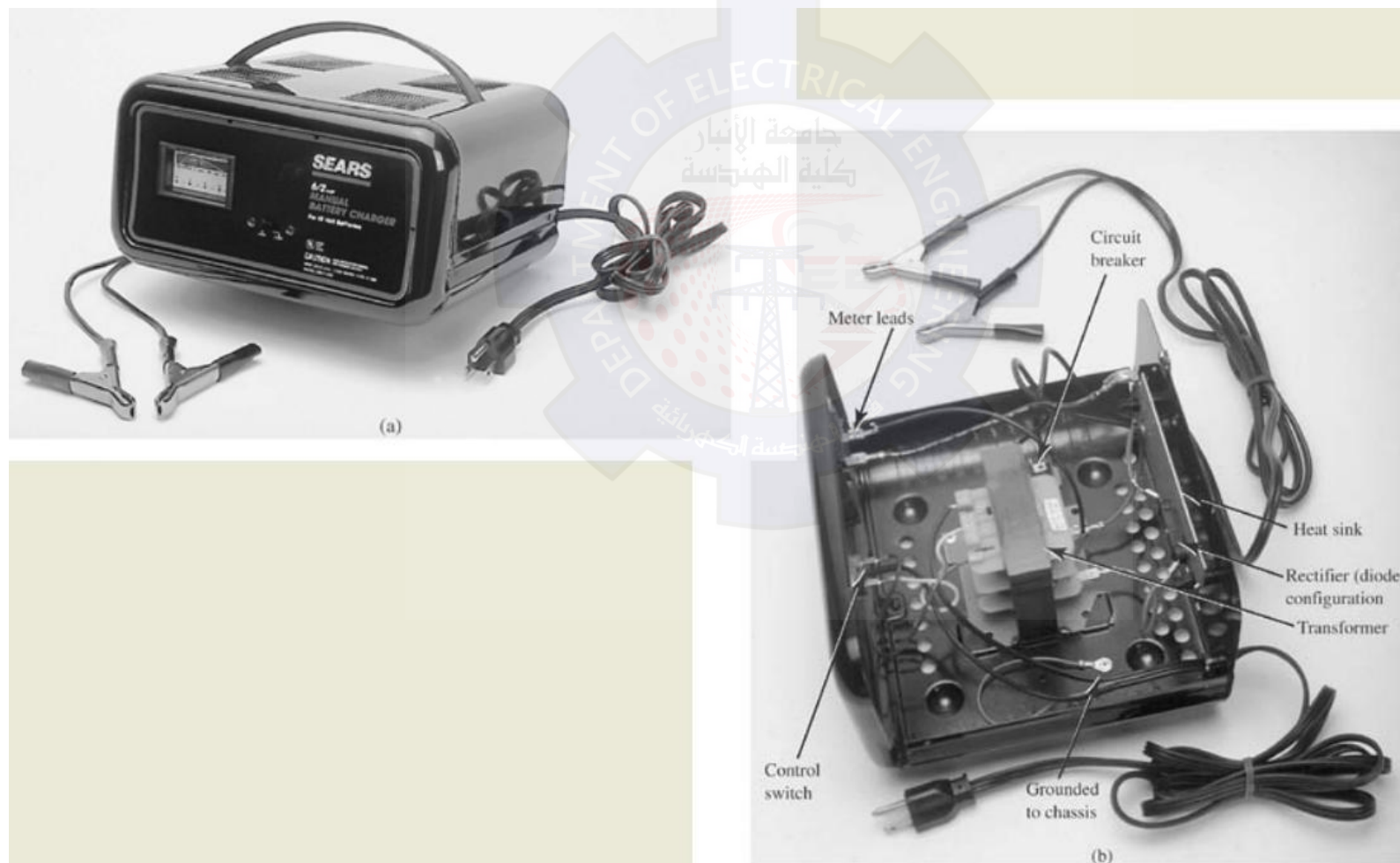




# Practical Applications

## Battery Charger

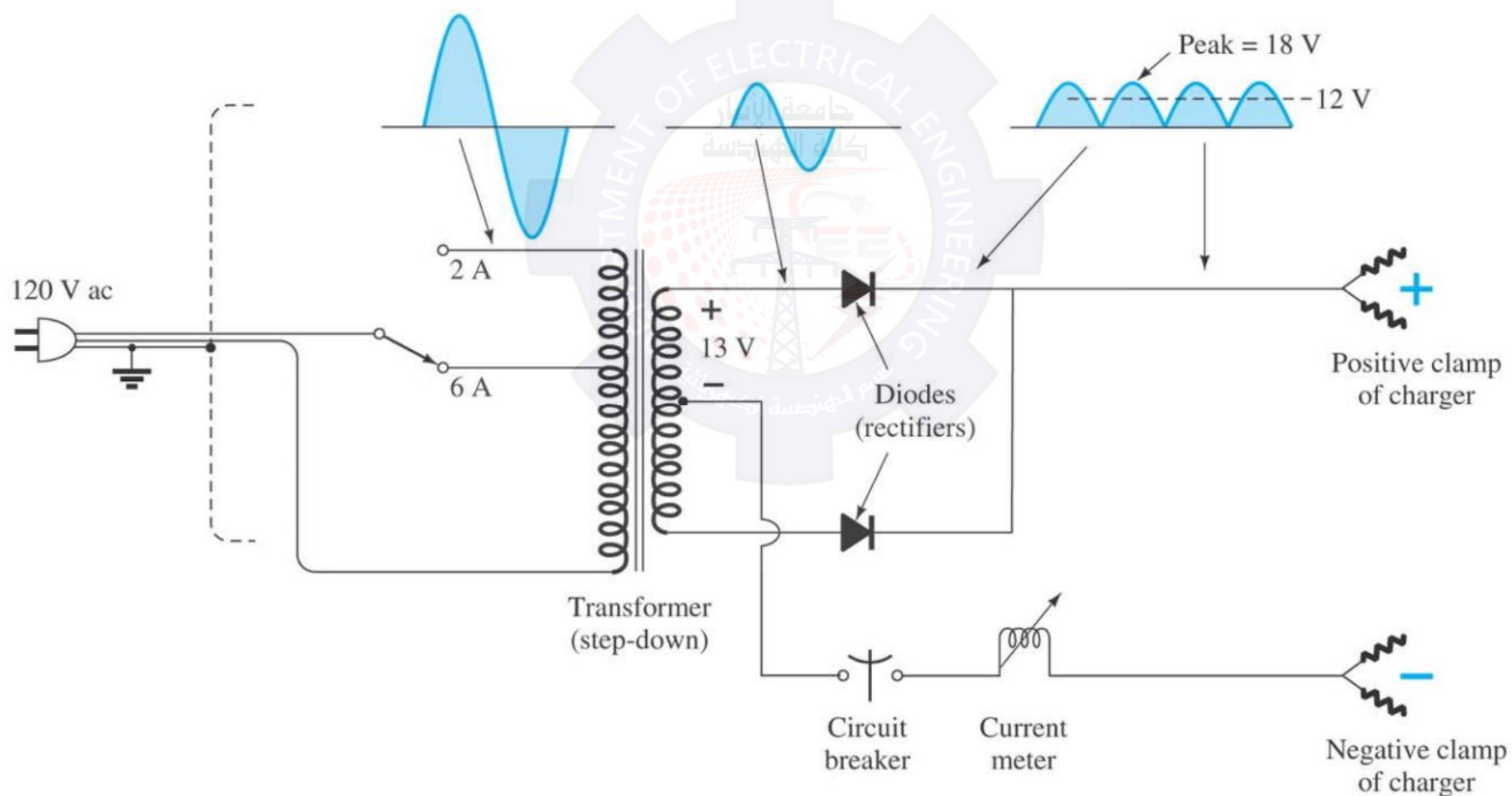

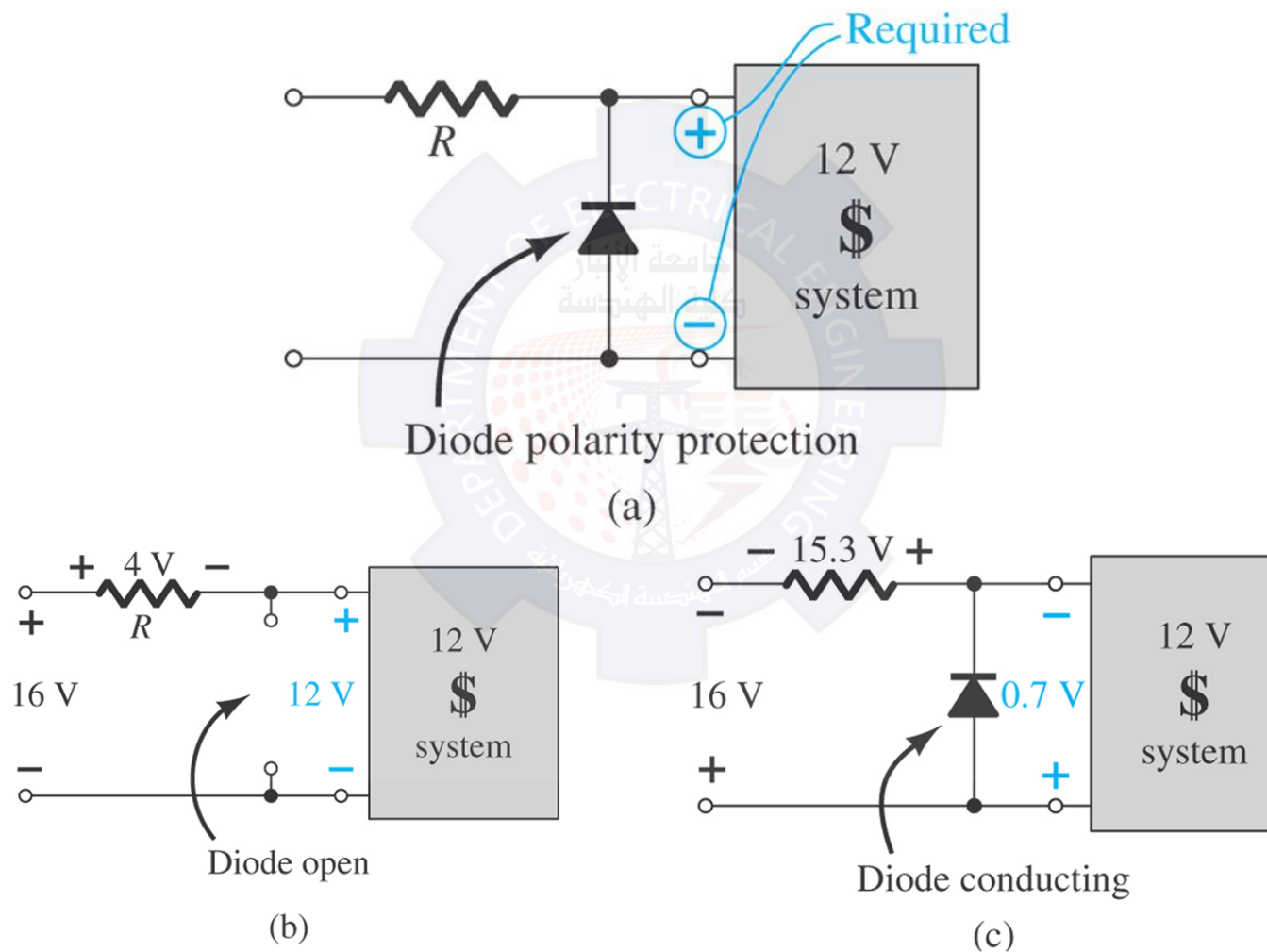
## Practical Applications - Polarity insurance



(a) Polarity protection for an expensive, sensitive piece of equipment; (b) correctly applied polarity; (c) application of the wrong polarity.


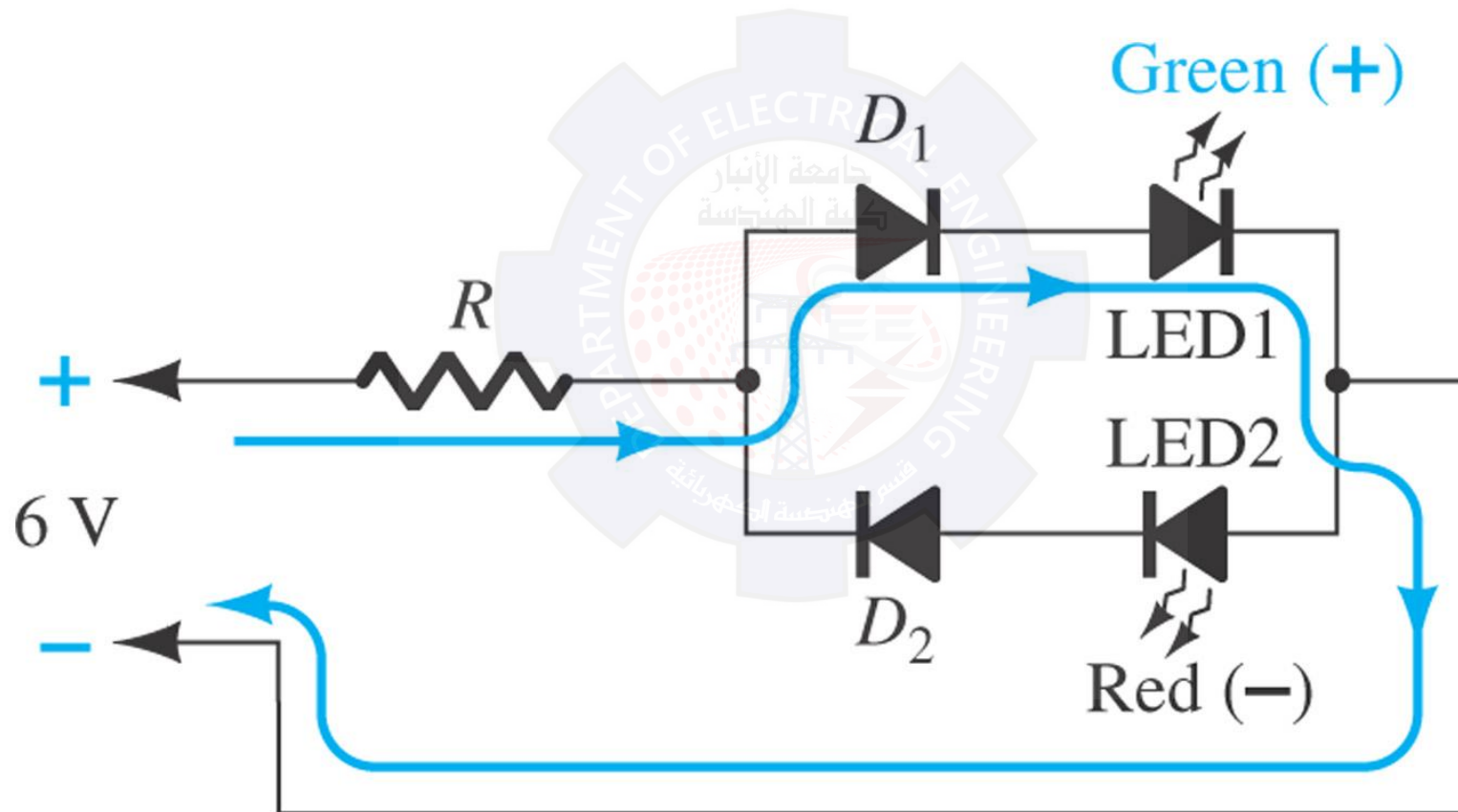
## Practical Applications - Polarity Detector




Polarity detector using diodes and LEDs.








# Practical Applications – Exit sign using LEDs

# EXIT

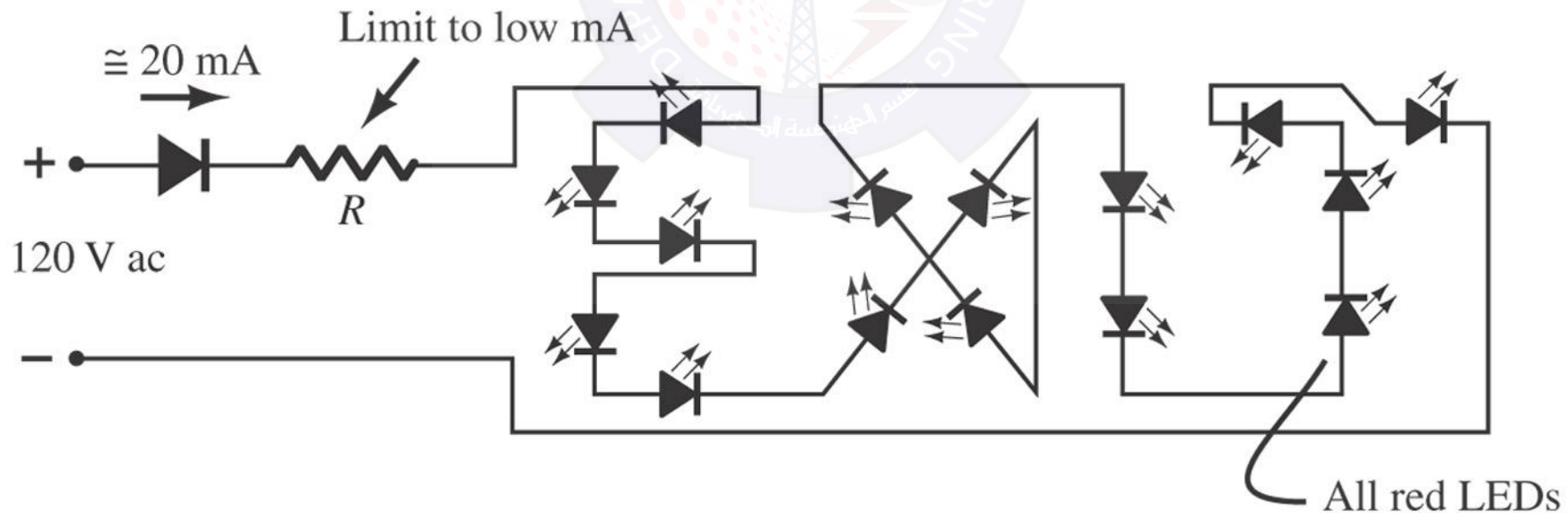



## Practical Applications – AC Regulator

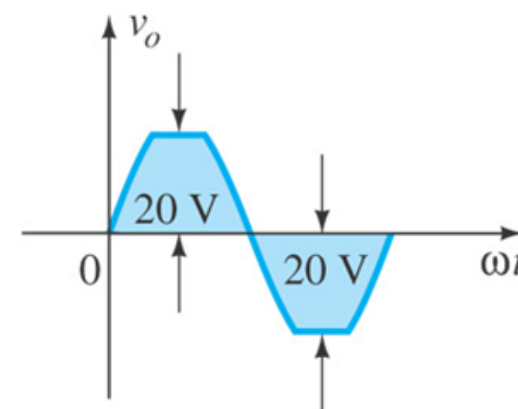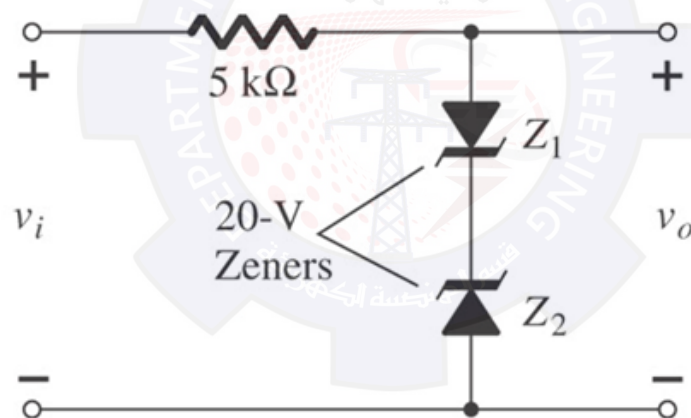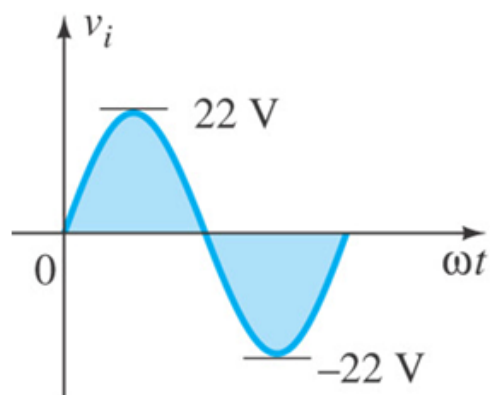



## Practical Applications – Square-Wave Generator

