



Fundumantal of Electronic I

Second Class


Chapter 3 : BJT Transistors

Lec03_p2

Munther N. Thiyab

2019-2020


Common-Emitter Configuration

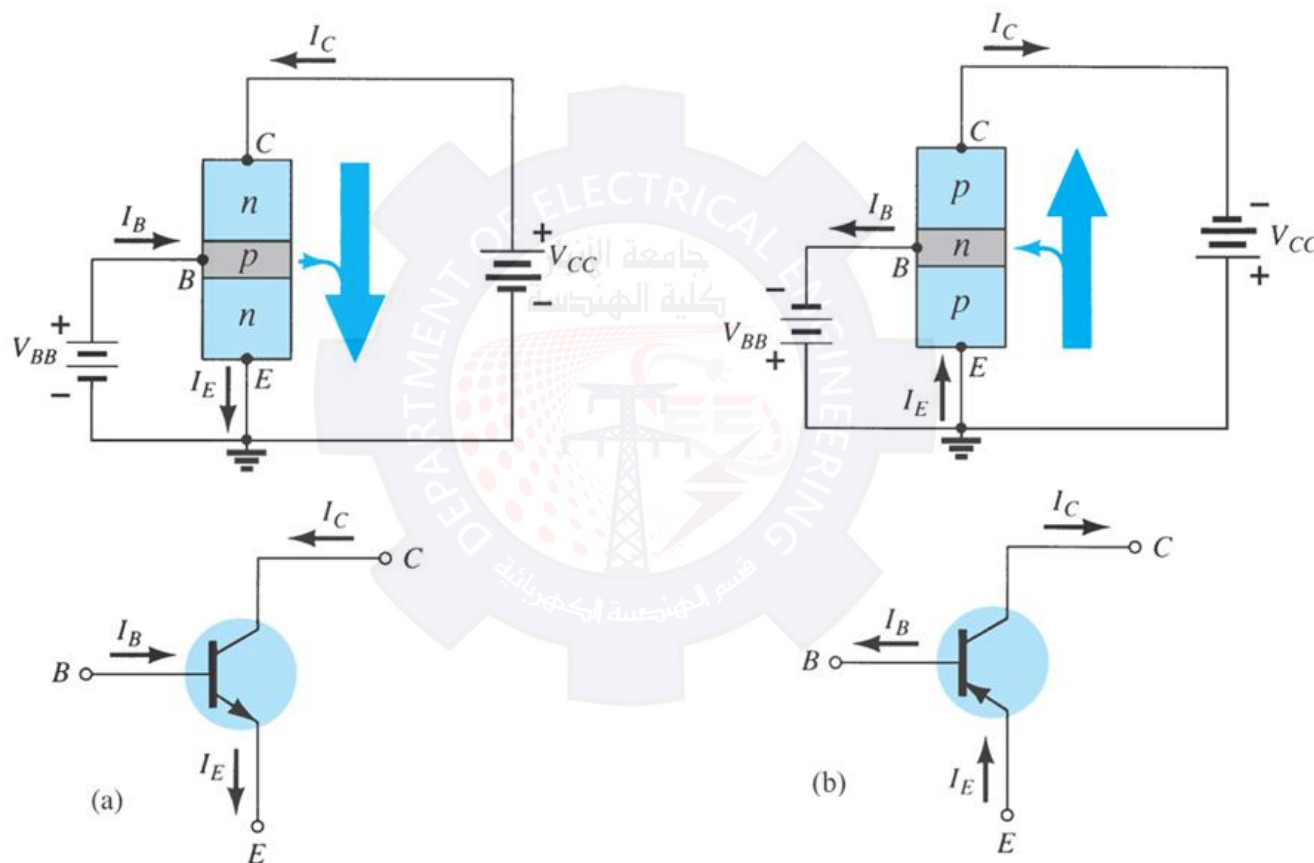

- The emitter is common to both input (base-emitter) and output (collector-emitter).
- The input is on the base and the output is on the collector.



Common-Emitter Characteristics

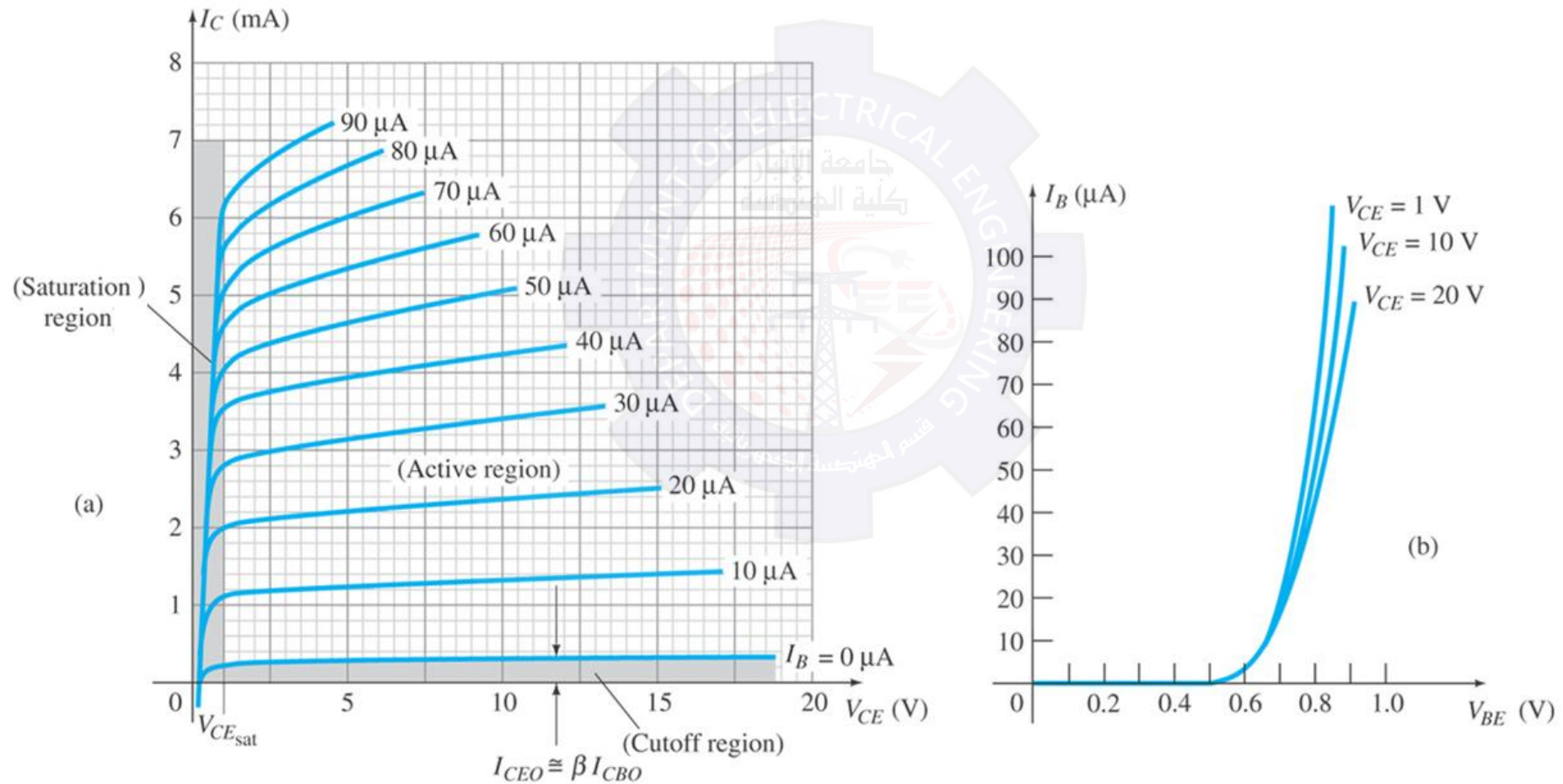

(a) collector characteristics; (b) base characteristics.



Common-Emitter Amplifier Currents

$$I_C = \alpha I_E + I_{CBO} \quad \text{where } I_{CBO} = \text{minority collector current}$$

I_{CBO} is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

$$\text{Since } I_E = I_C + I_B \quad , \quad I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$I_C = \frac{\alpha I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha}$$


For $I_B = 0$, and take $\alpha = 0.996$,

$$I_C = \frac{\alpha(0 \text{ A})}{1 - \alpha} + \frac{I_{CBO}}{1 - 0.996} = \frac{I_{CBO}}{1 - 0.996} = \frac{I_{CBO}}{0.004} = 250 I_{CBO}$$

If I_{CBO} were $1 \mu\text{A}$, the resulting collector current with $I_B = 0 \text{ A}$ would be $250(1 \mu\text{A}) = 0.25 \text{ mA}$, as reflected in the characteristics.

When $I_B = 0 \mu\text{A}$ the transistor is in cutoff, but there is some minority current flowing called I_{CEO}

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0 \mu\text{A}}$$

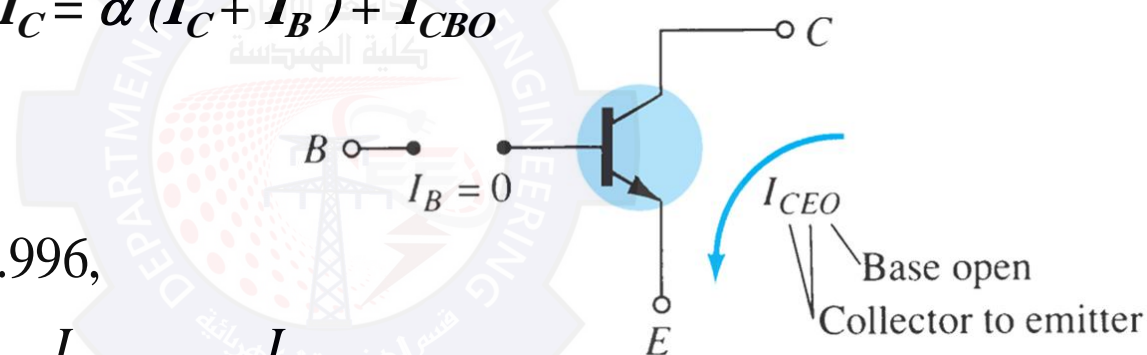



Beta (β)

β represents the amplification factor of a transistor. (β is sometimes referred to as h_{fe} , a term used in transistor modeling calculations)

In DC mode:

$$\beta_{dc} = \frac{I_C}{I_B}$$

For practical devices β is typically 50 to over 400.

In AC mode:

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$



Beta (β)

Determining β from a Graph


$$\beta_{AC} = \frac{(3.2 \text{ mA} - 2.2 \text{ mA})}{(30 \mu\text{A} - 20 \mu\text{A})}$$

$$= \frac{1 \text{ mA}}{10 \mu\text{A}} \Big|_{V_{CE} = 7.5}$$

$$= 100$$

$$\beta_{DC} = \frac{2.7 \text{ mA}}{25 \mu\text{A}} \Big|_{V_{CE} = 7.5}$$

$$= 108$$

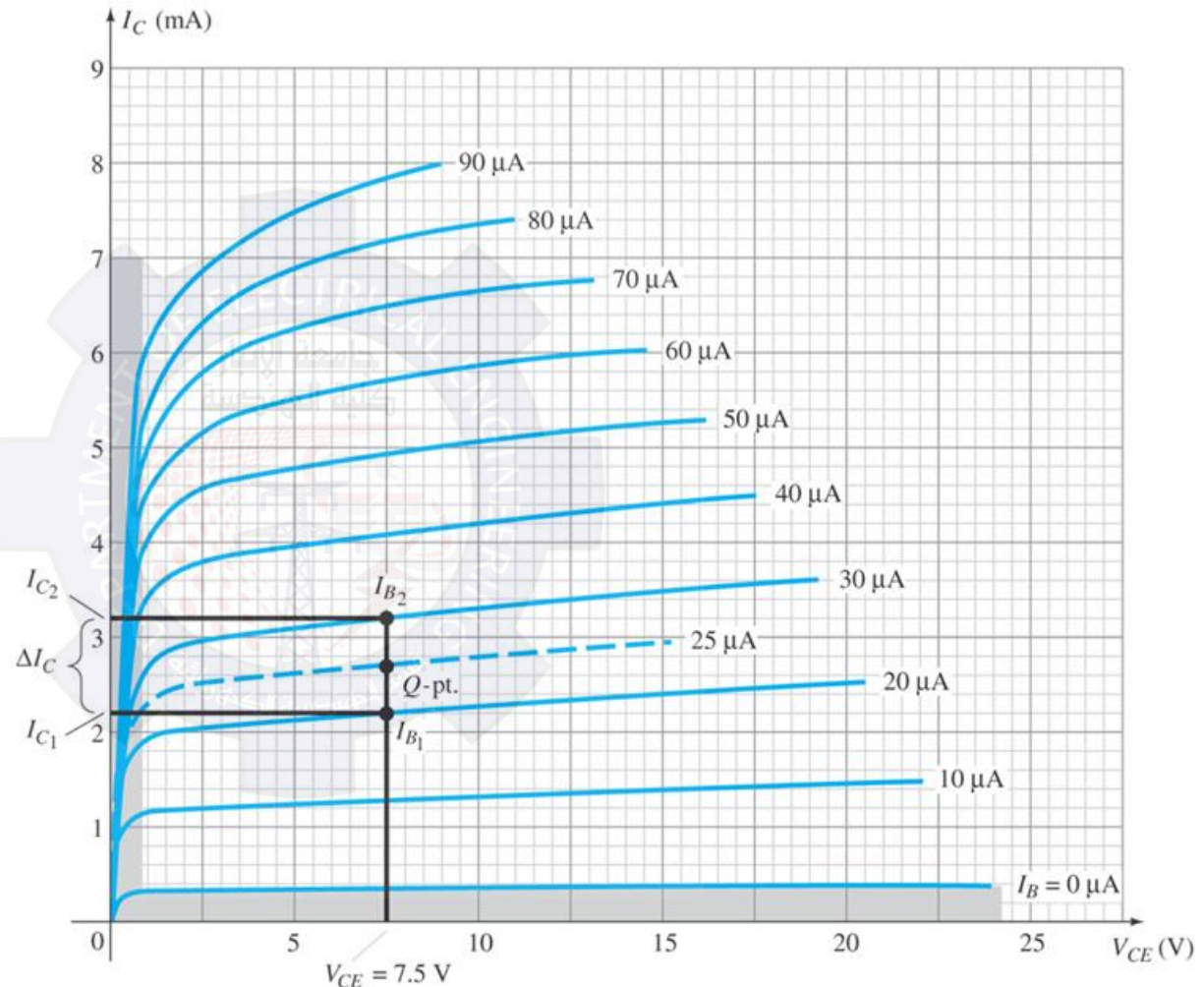

β_{ac} and β_{dc} are usually reasonably close and are often used interchangeably.



Beta (β)

Relationship between amplification factors β and α :-

$$\text{using } \beta = \frac{I_C}{I_B}, \quad \alpha = \frac{I_C}{I_E}$$

$$\text{and } I_E = I_C + I_B$$

$$\frac{I_C}{\alpha} = I_C + \frac{I}{\beta} \rightarrow \frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\beta = \alpha\beta + \alpha = (\beta + 1)\alpha$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{\alpha - 1}$$


Relationship Between Currents

$$I_C = \beta I_B$$

$$, I_E = I_C + I_B = \beta I_B + I_B$$

$$, I_E = (\beta + 1)I_B$$


Biasing

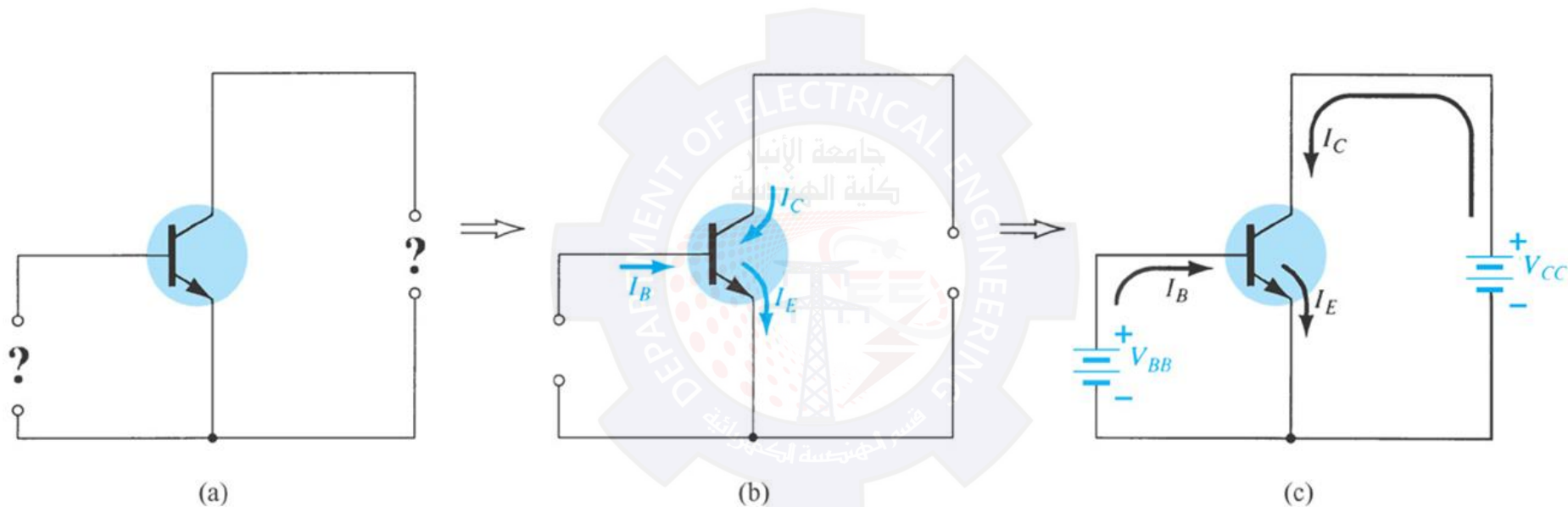

Determining the proper biasing arrangement for a common-emitter *npn* transistor configuration.

Common-Collector Configuration

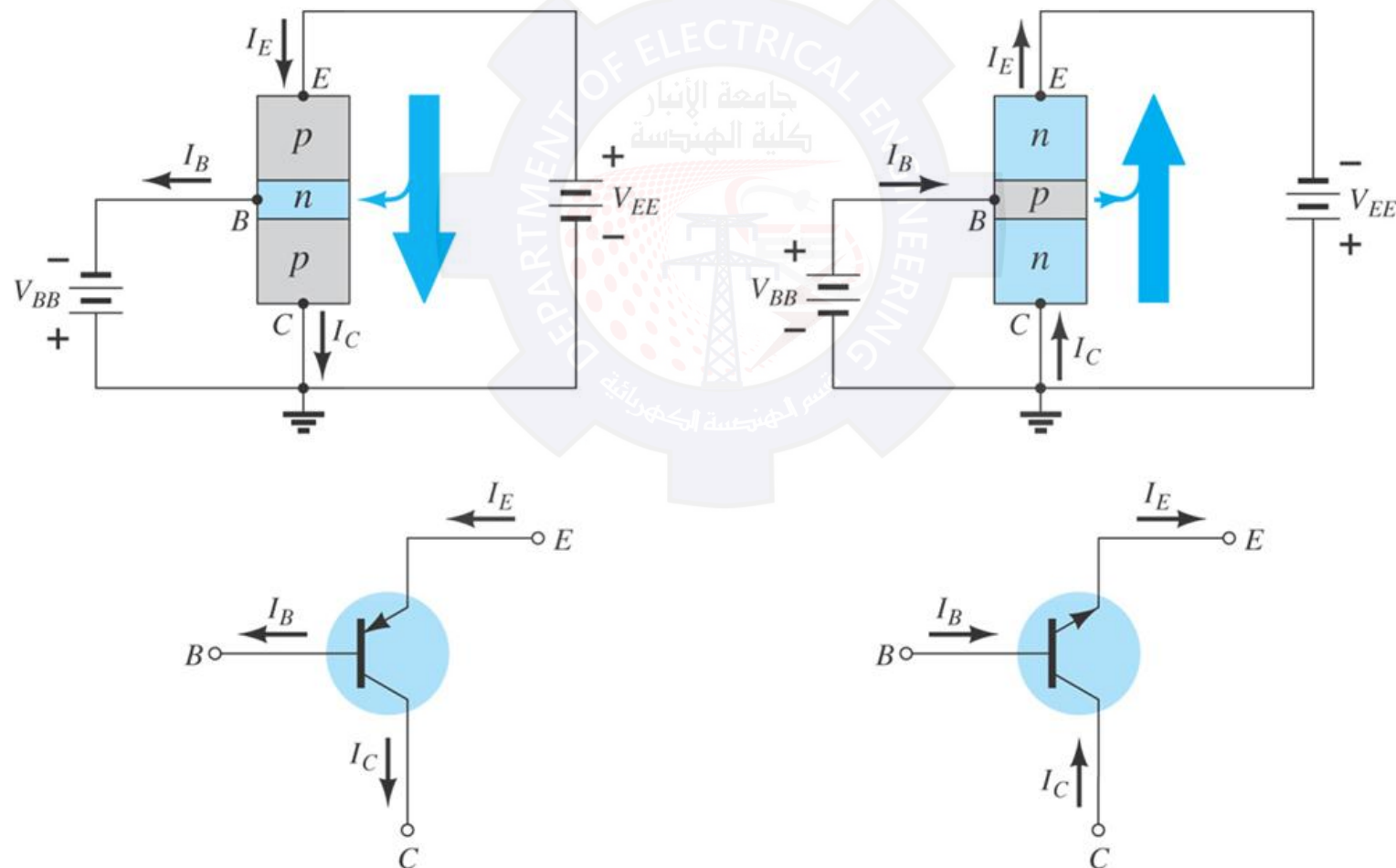
The input is on the base and the output is on the emitter.






Common-Collector Configuration

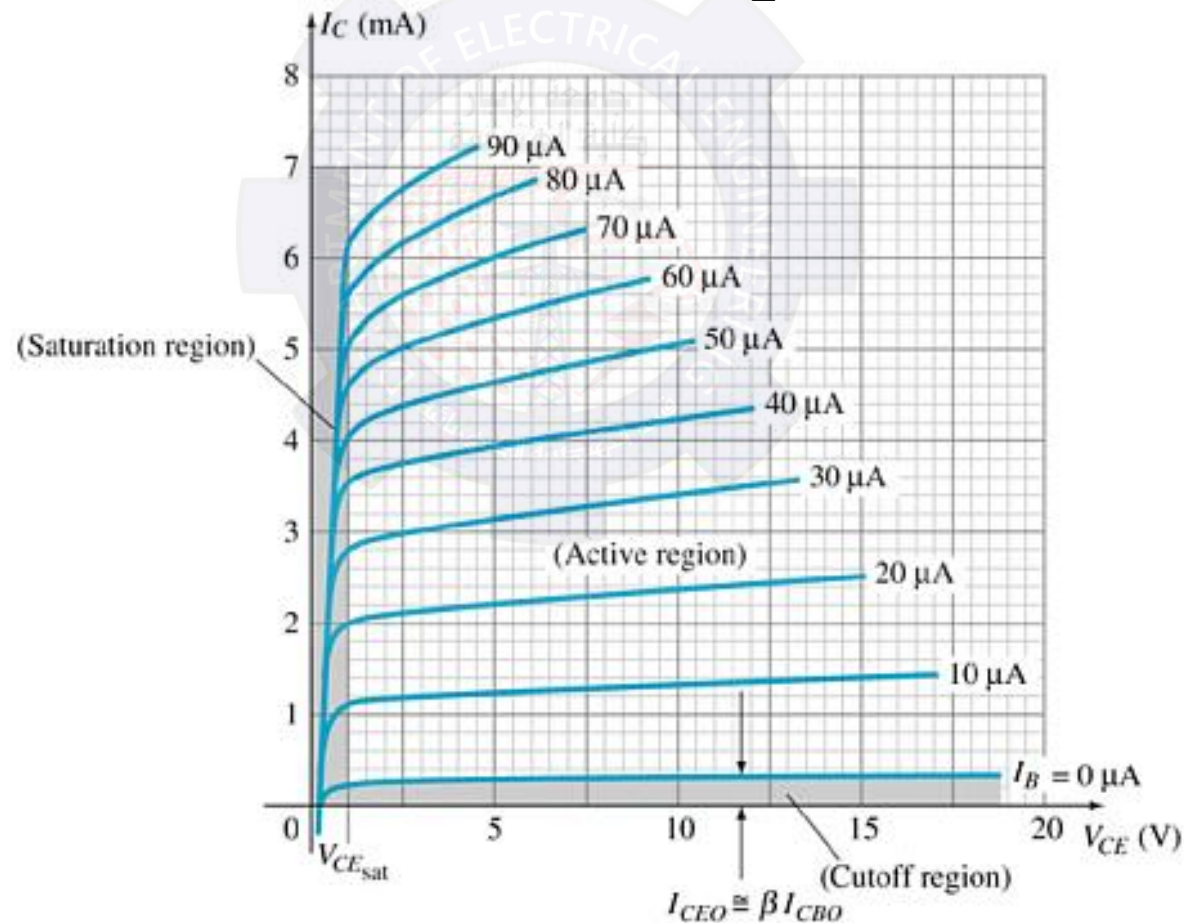The characteristics are similar to those of the common-emitter configuration, except the vertical axis is I_E .




Transistor Testing

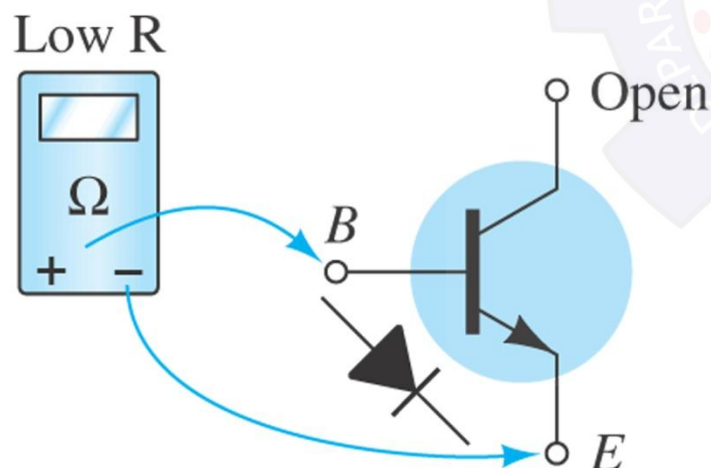
- DMM
Some DMMs measure β_{DC} or h_{FE} .
- Ohmmeter



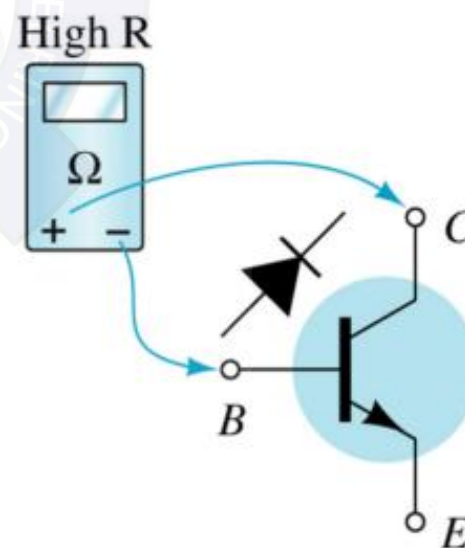Checking the forward-biased base-to-emitter junction of an npn transistor.



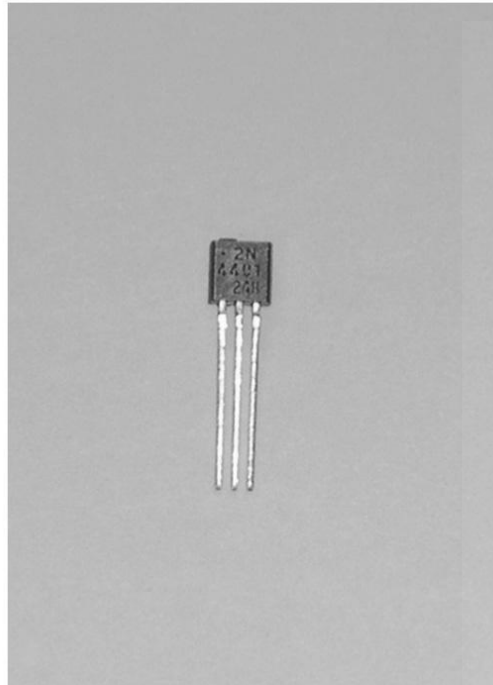Checking the reverse-biased base-to-collector junction of an npn transistor.



(a)



(b)



(c)

Various types of general-purpose or switching transistors:
(a) low power; (b) medium power; (c) medium to high power.