



Fundumantal of Electronic I

Second Class

Chapter 4 : DC Biasing – BJTs

Lec04_p2


Munther N. Thiyab

2019-2020




Voltage Divider Bias

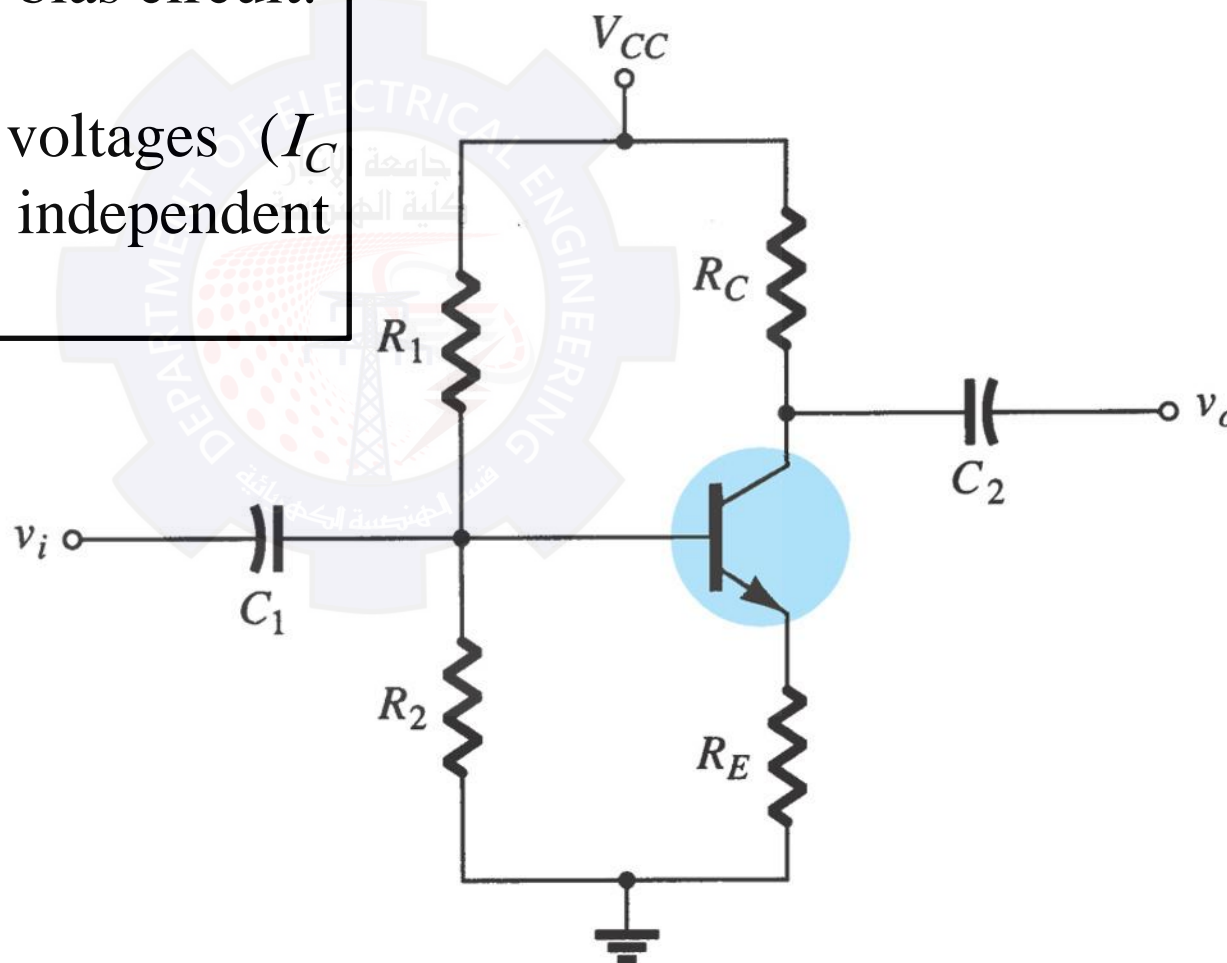- This is a very stable bias circuit.
- The currents and voltages (I_C and V_{CE}) are nearly independent of any variations in β .






Voltage Divider Bias Analysis

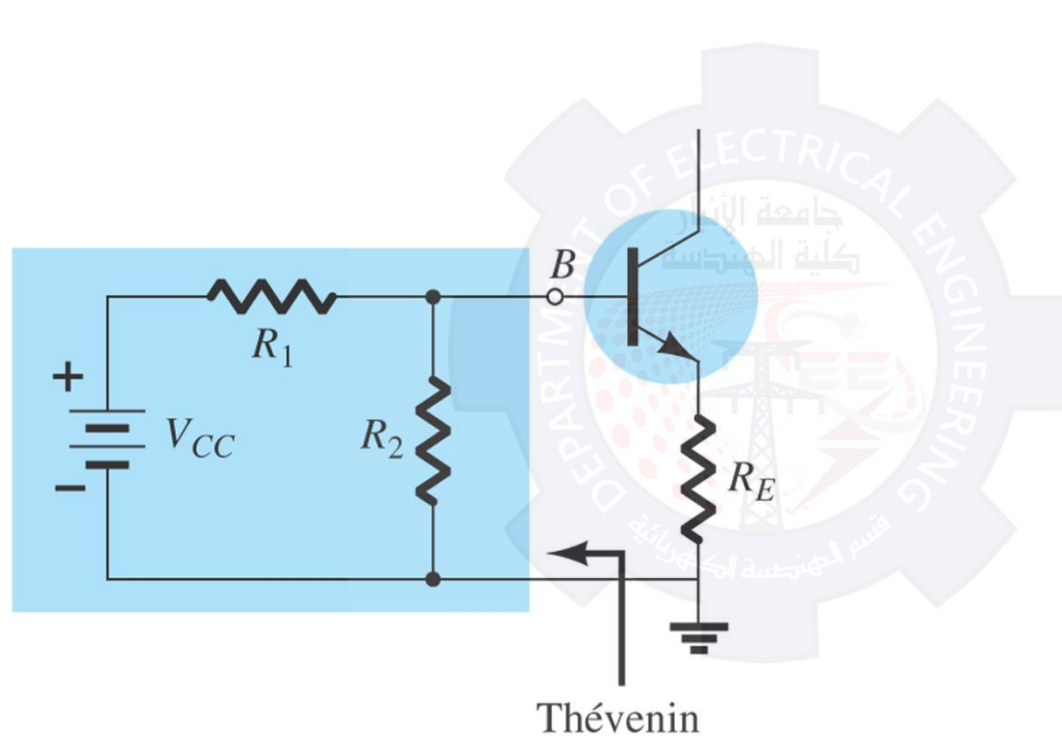


Redrawing the input side of the network.

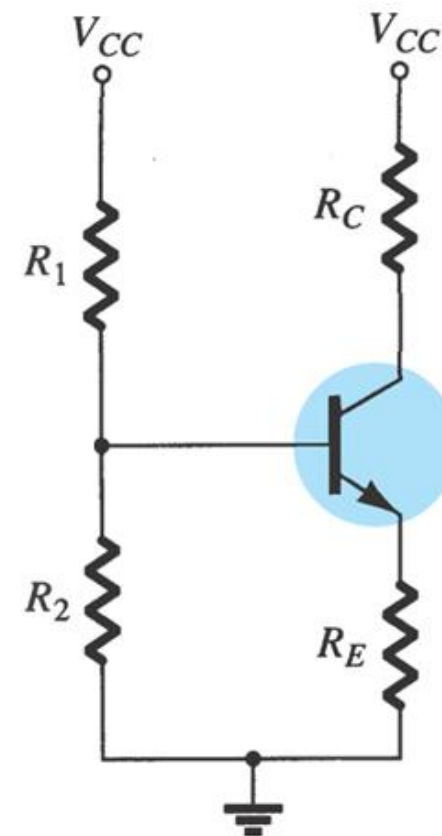

DC Circuit



Voltage Divider Bias Analysis

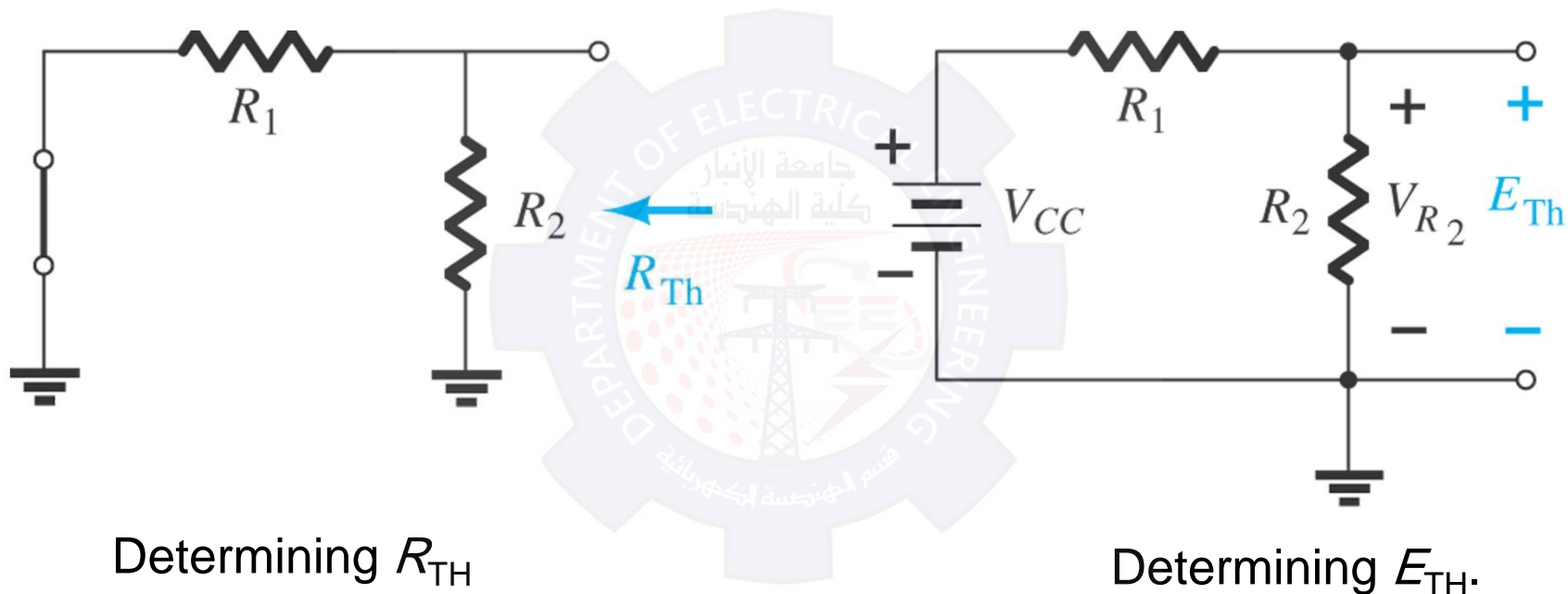

Determining R_{TH}

Determining E_{TH}

$$R_{th} = R_1 \parallel R_2$$

$$E_{th} = V_{R_2} = \frac{R_2 V_{CC}}{R_1 + R_2}$$




Voltage Divider Bias Analysis

$$E_{th} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$


$$I_E = (\beta + 1) I_B$$

$$I_B = \frac{E_{th} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

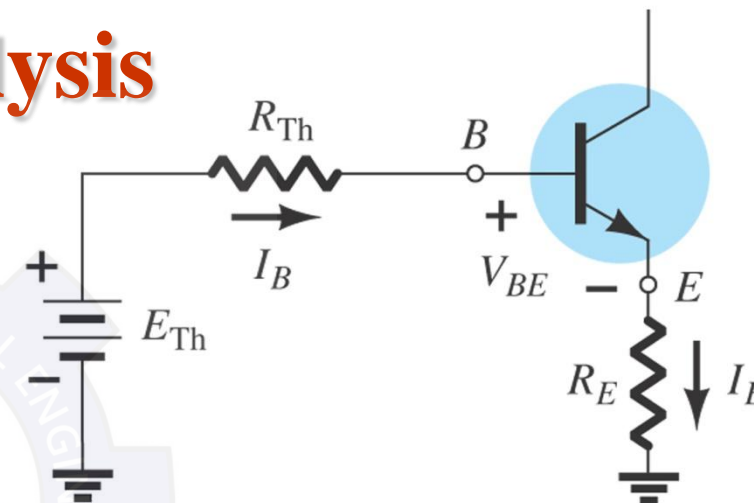


Inserting the Thévenin equivalent circuit.

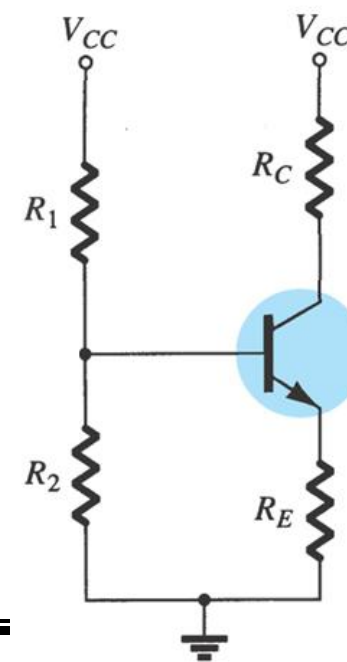




Example 4.8

Find I_{CQ} , V_{CEQ}

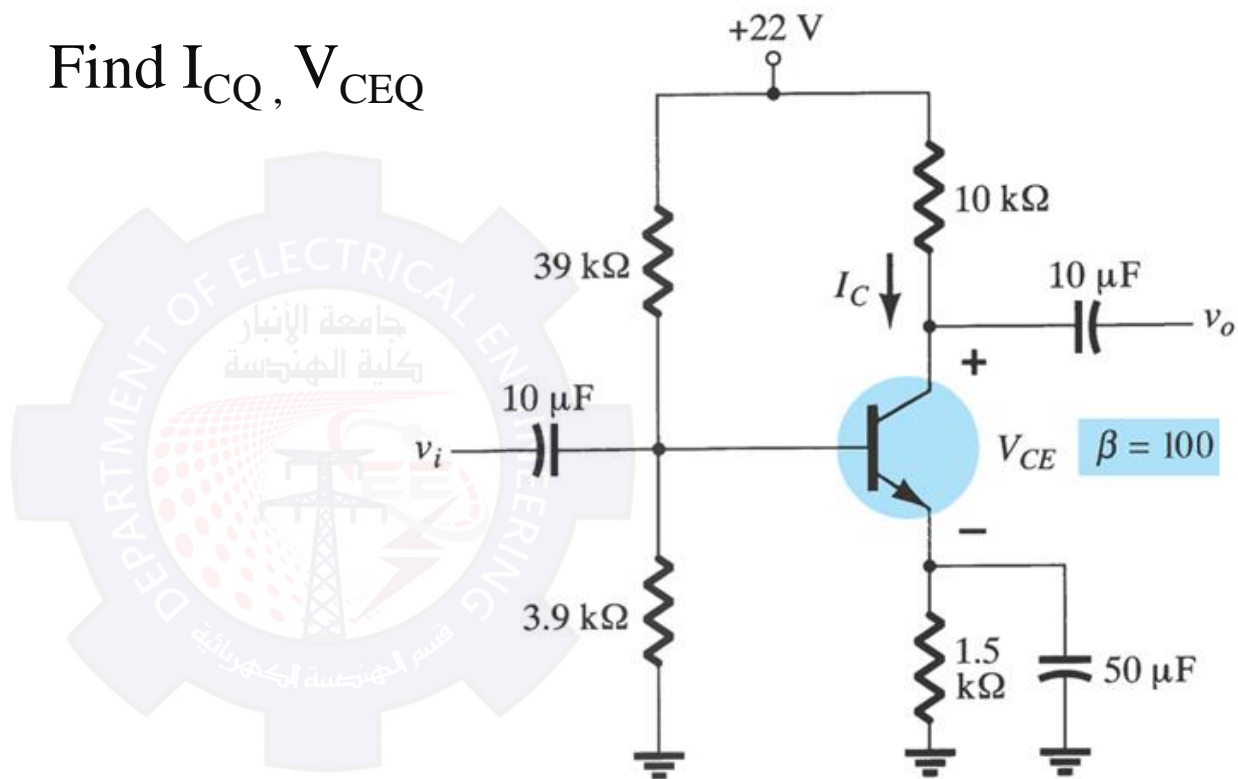



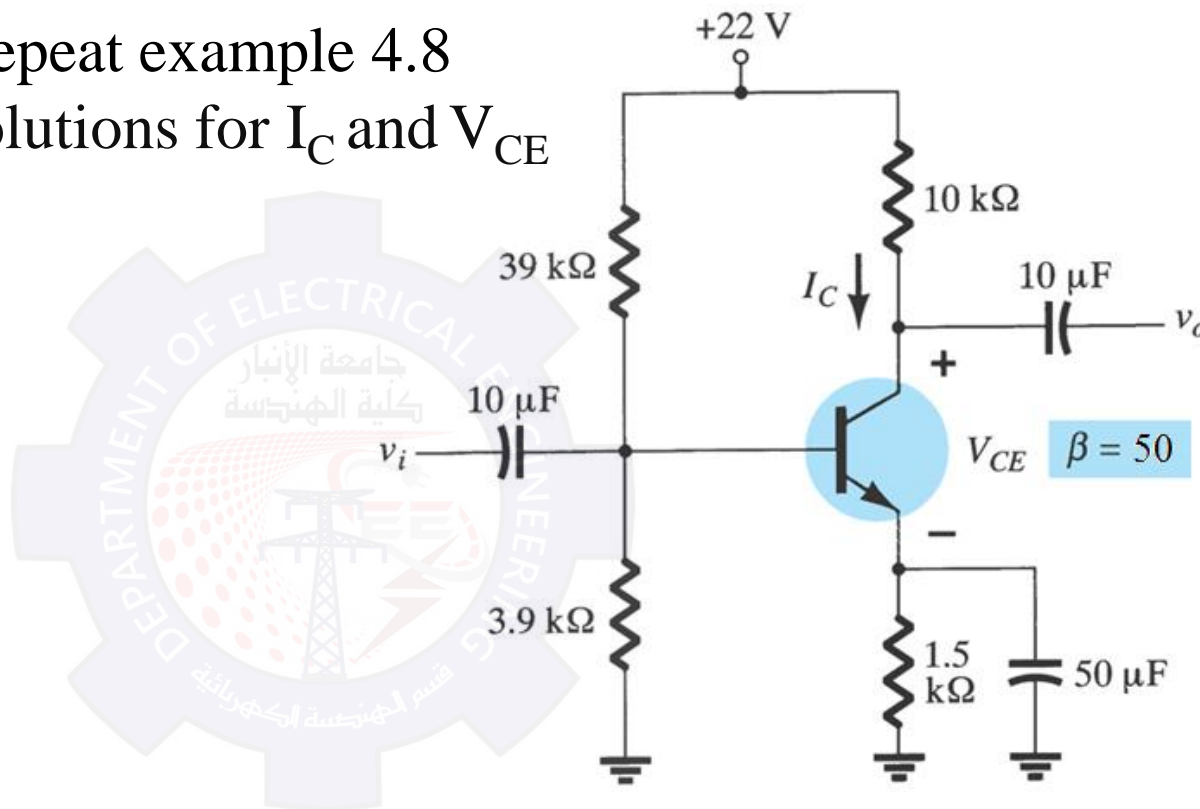Example 4.10 Repeat example 4.8
 with $\beta=50$. compare solutions for I_C and V_{CE}




β	I_C (mA)	V_{CE} (V)
100	0.84 mA	12.34 V
50	0.81 mA	12.69 V



Collector Feedback Configuration

➤ Another way to improve the stability of a bias circuit is to add a feedback path from collector to base.

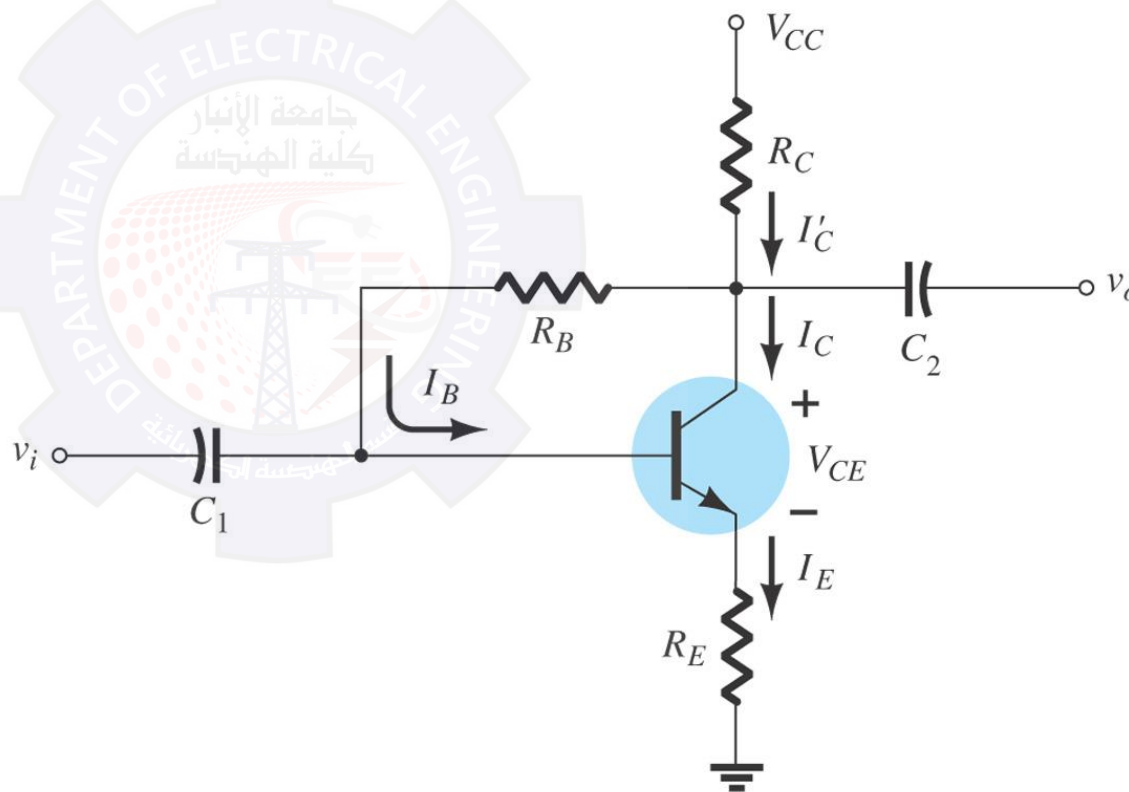➤ In this bias circuit the Q-point is only slightly dependent on the transistor beta, β .





Base-Emitter Loop

From Kirchhoff's voltage law:

$$V_{CC} - I'_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

Since $I_B \ll I_C$:

$$I'_C = I_C + I_B \cong I_C$$


Knowing $I_C = \beta I_B$ and $I_E \cong I_C$, the loop equation becomes:

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

Solving for I_B :

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

$$I_C = \beta I_B$$

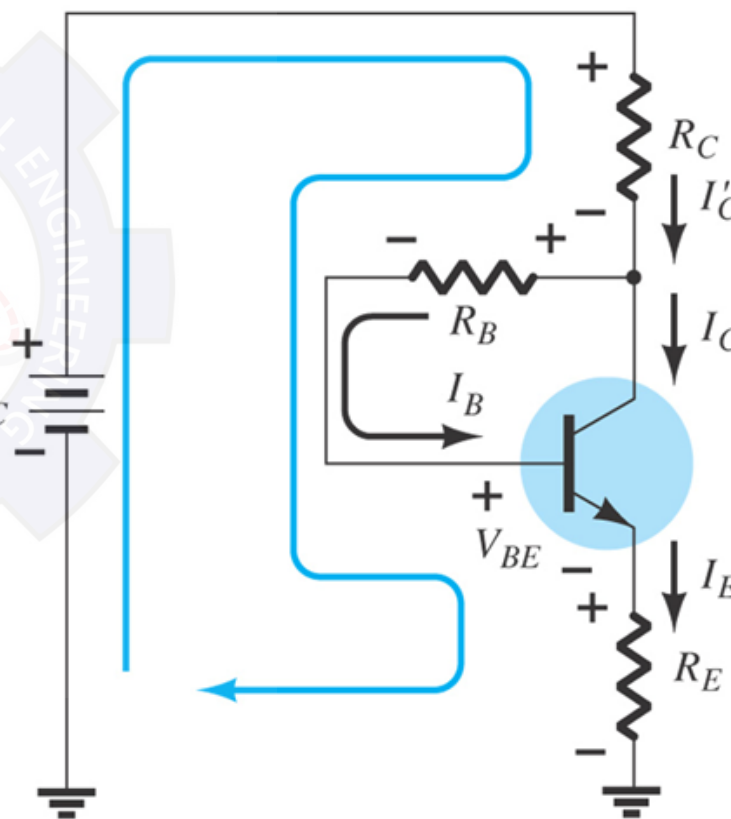

Collector-Emitter Loop

Applying Kirchoff's voltage law:


$$I_E R_E + V_{CE} + I'_C R_C - V_{CC} = 0$$

Since $I'_C \cong I_C$ and $I_E \cong I_C$:

$$I_C(R_C + R_E) + V_{CE} - V_{CC} = 0$$


Solving for V_{CE} :

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

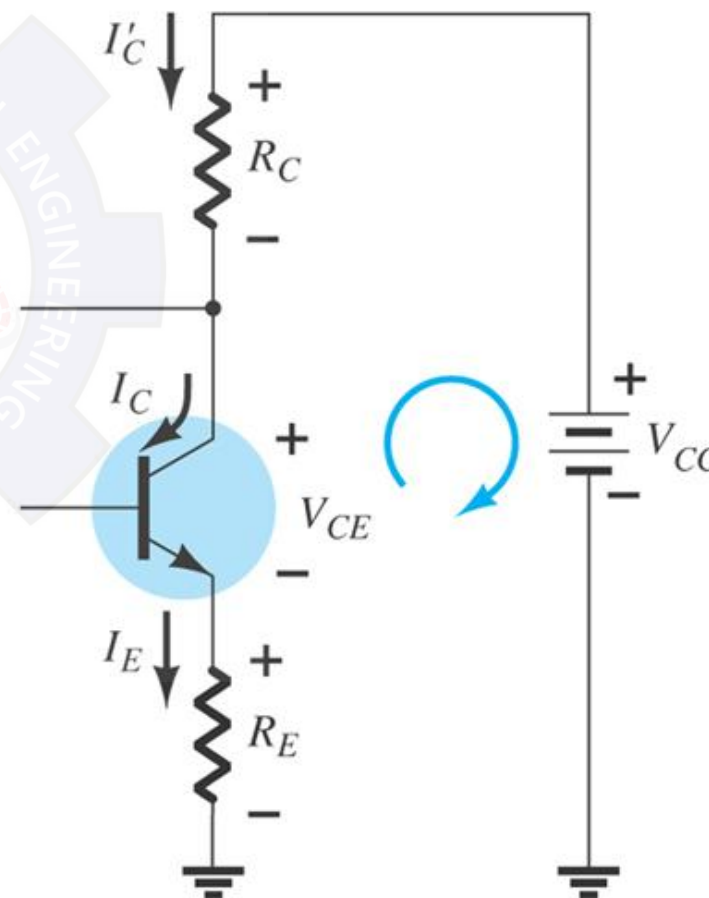




Example 4.12 Find I_{CQ} , V_{CEQ}

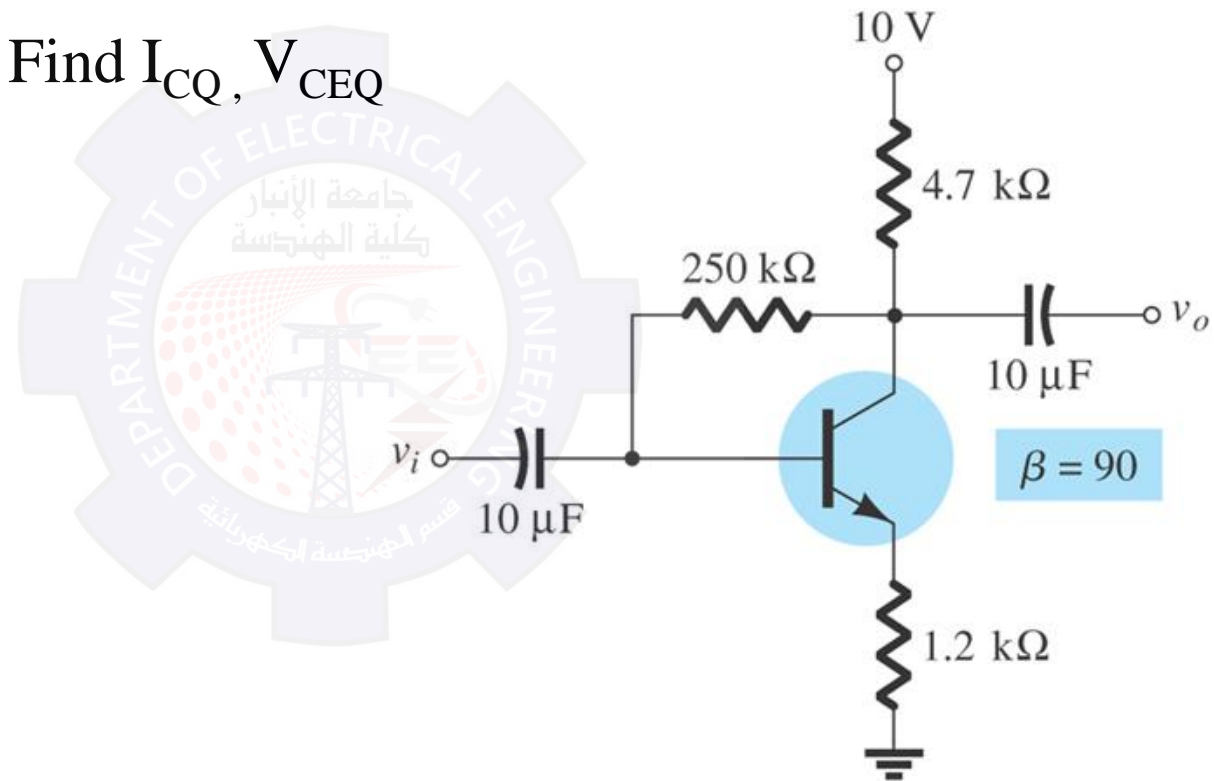



Example 4.13 Repeat example 4.12,
with $\beta=135$. (Find I_{CQ} , V_{CEQ}).

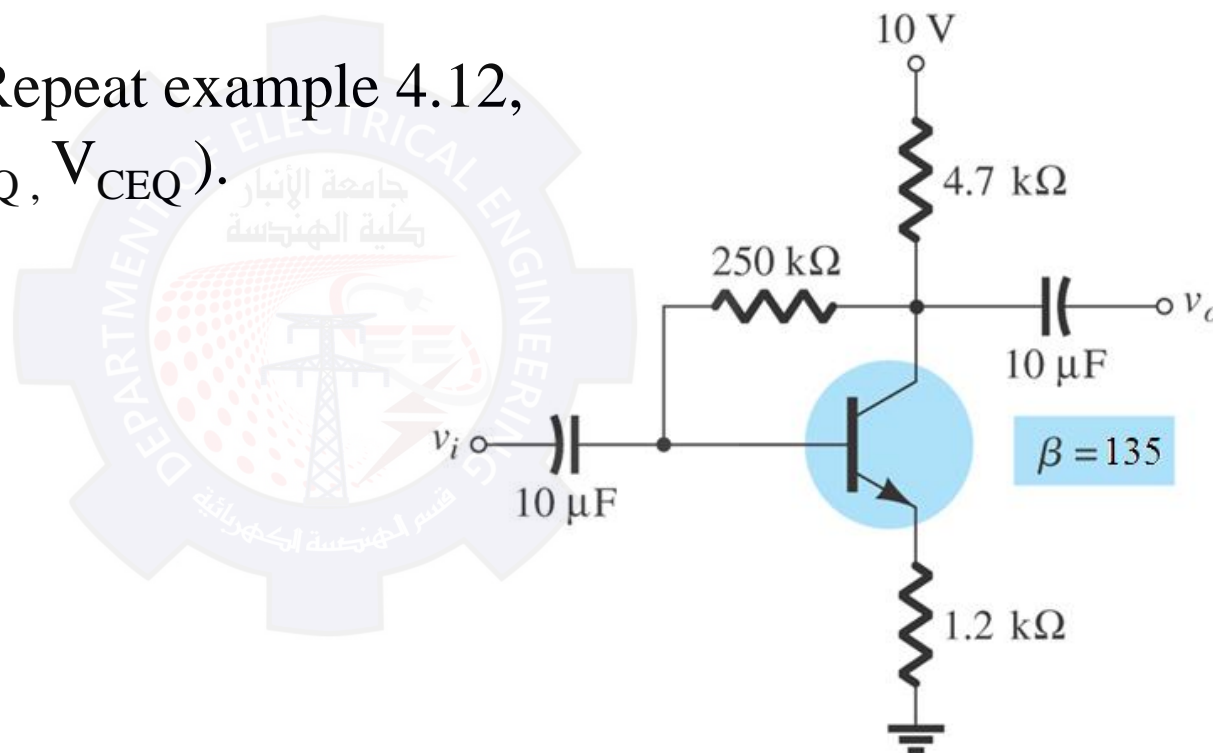



Example 4.14

I_B and V_C .

Determine the DC level of

