



Fundamental of Electronic I

Second Class


Chapter 4 : DC Biasing – BJTs

Lec04_p4


Munther N. Thiyab

2019-2020


Miscellaneous Bias Configurations

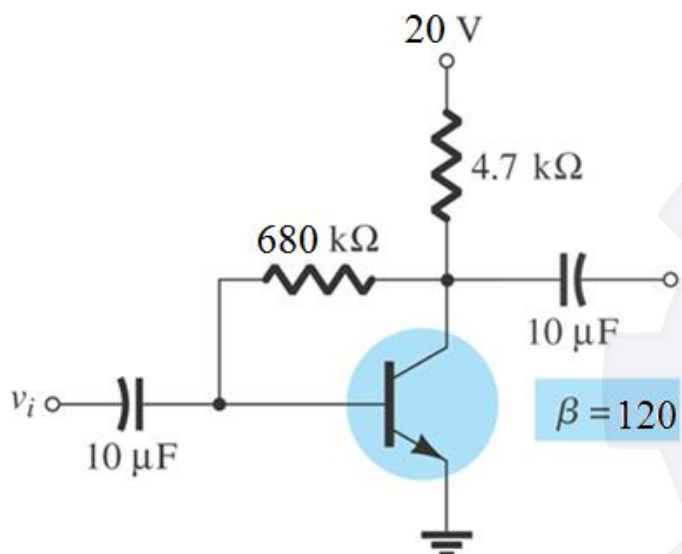

Example 4.18

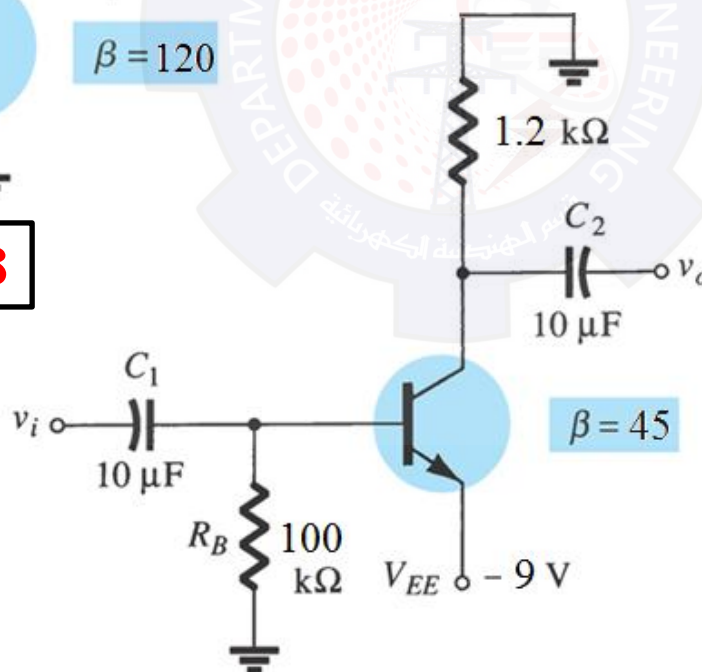


Example 4.19

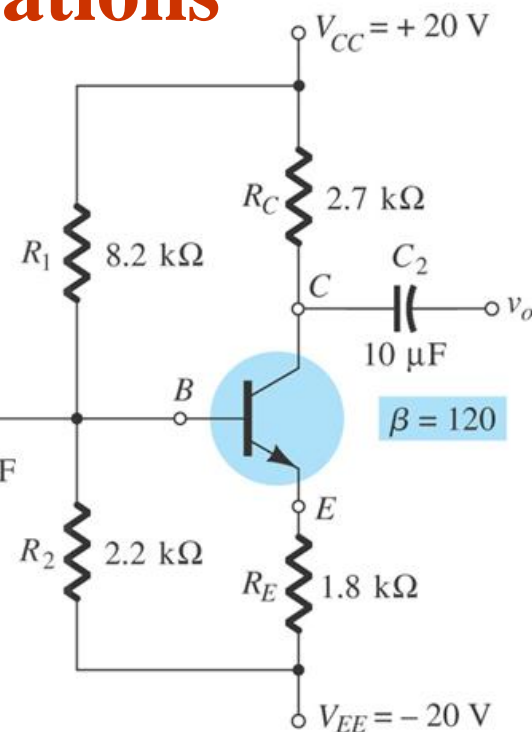

Example 4.20



Example 4.20

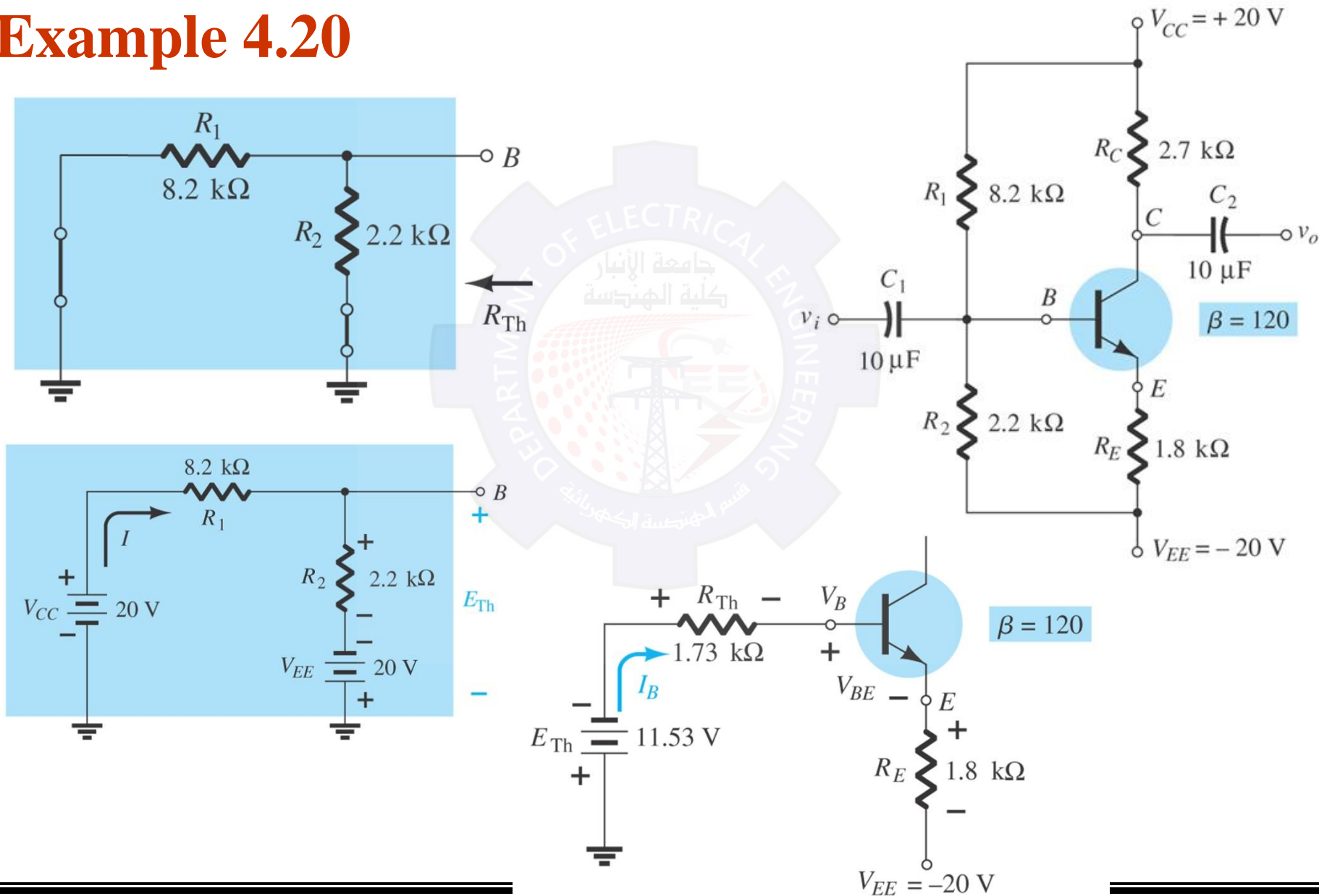





Design Operations

Current and/or Voltage may be specified, and the values of resistors are to be found.

Example 4.21

Determine V_{CC} , R_B , R_C

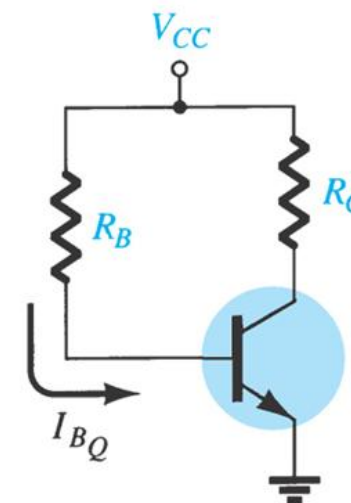
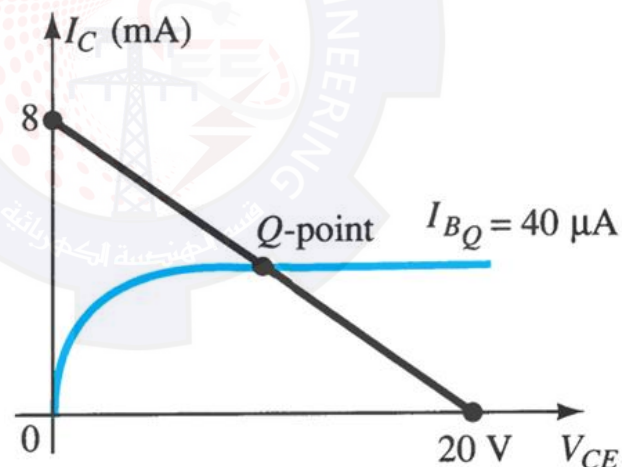




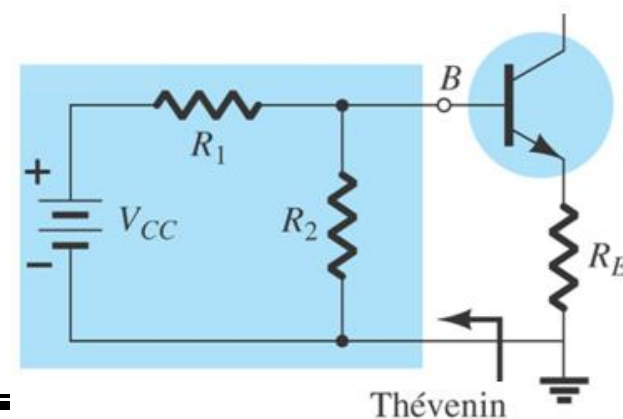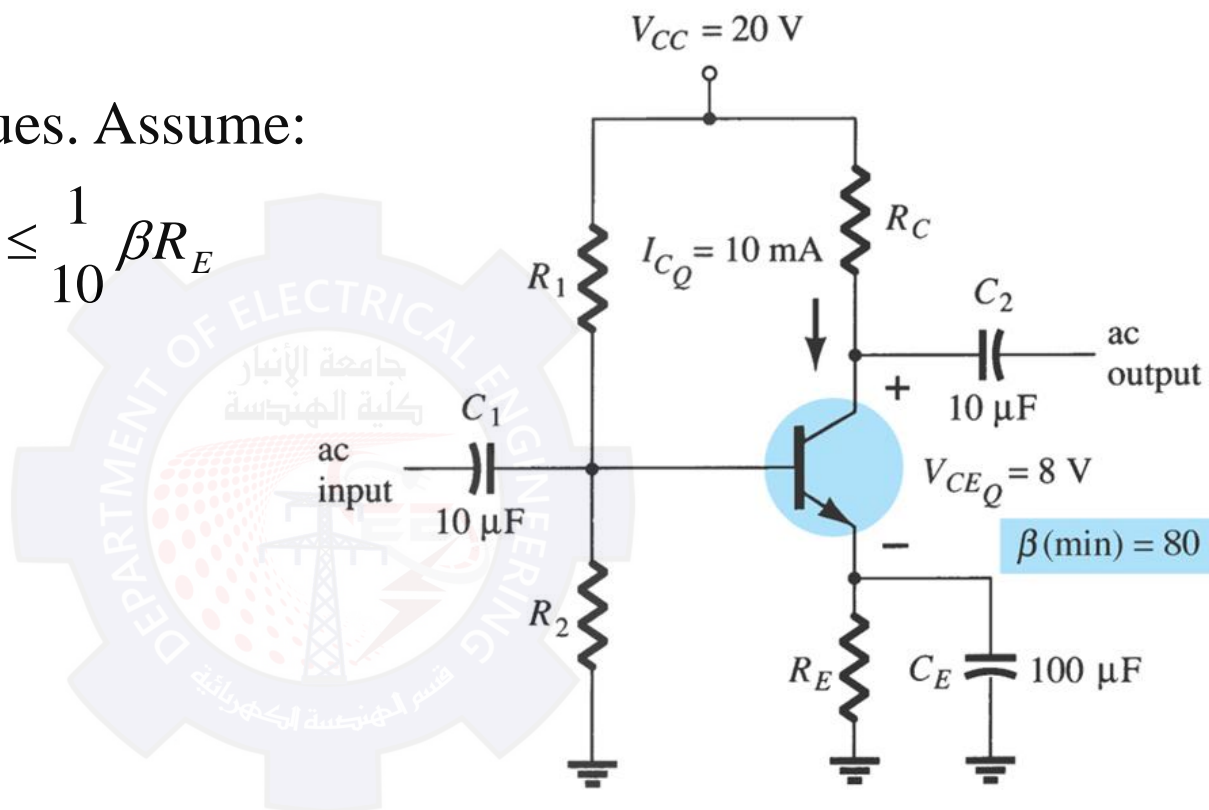Example 4.25

Determine resistor values. Assume:


$$V_E = \frac{1}{10} V_{CC} \quad , \quad R_2 \leq \frac{1}{10} \beta R_E$$





Transistor Switching Networks

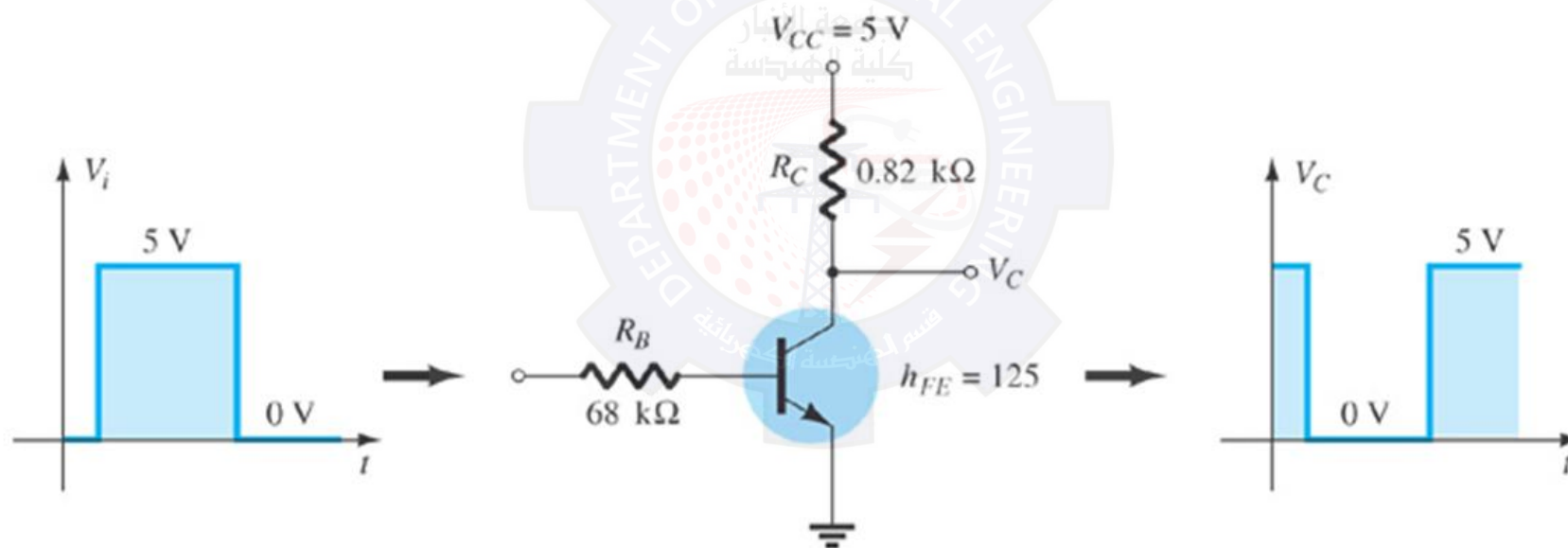Transistors are used for **amplification** and also they can be used as **electronic switches**.




Transistor Inverter

The output voltage V_C is opposite to that applied to the base.

Switching Circuit Calculations

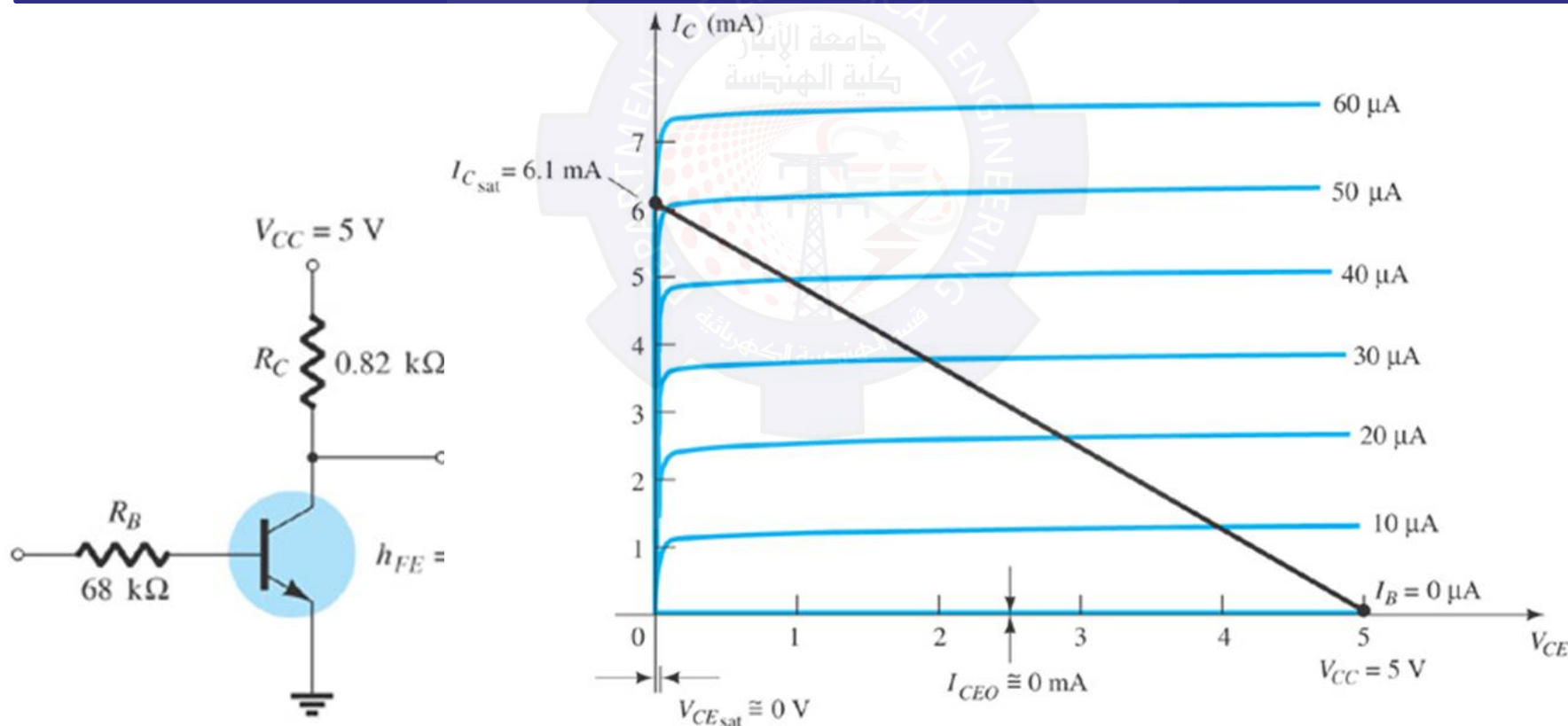- **Cutoff:** When $I_B=0$ ($V_i=0$), $I_C=I_{CEO} \approx 0\text{mA} \rightarrow V_C=V_{CC}=5\text{V}$.
- **Saturation:** When $V_i=5\text{V}$, transistor must be operated in saturation region by having sufficient level of I_B . $\rightarrow V_C=V_{CEsat} \approx 0\text{V}$.



Operating Point switch from cutoff to saturation along load line.





Switching Circuit Calculations

Saturation current:

$$I_{Csat} = \frac{V_{CC}}{R_C}$$

To ensure saturation:

$$I_B > \frac{I_{Csat}}{\beta_{dc}}$$

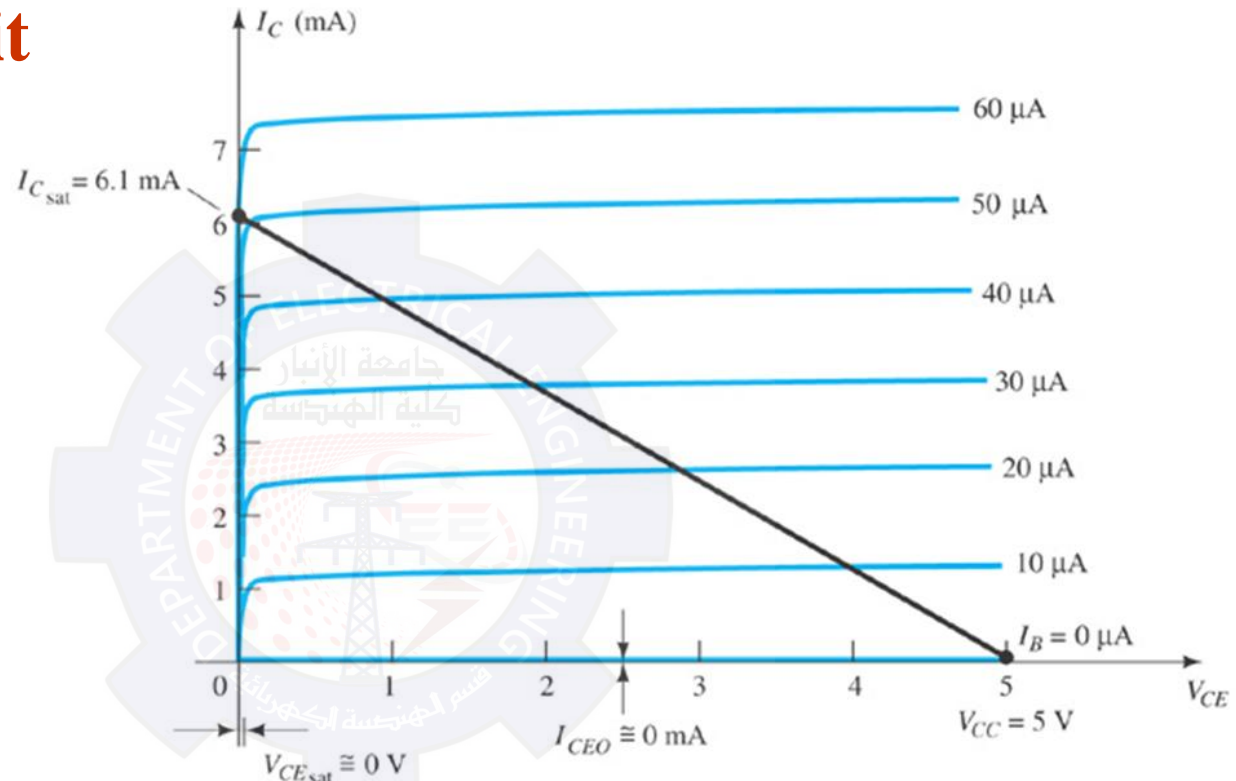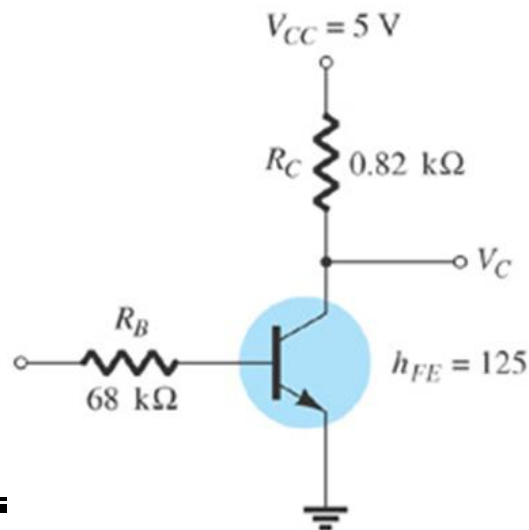



$$\text{When } V_i = 5, I_B = \frac{V_i - 0.7}{R_B} = \frac{5 - 0.7}{68k \Omega} = 63 \mu A$$

$$I_{Csat} = \frac{V_{CC}}{R_C} = \frac{5}{0.82k} = 6.1mA$$

$$I_B = 63 \quad \frac{I_{Csat}}{\beta} = \frac{6.1mA}{125} = 48.8$$





Transistor Switching Networks

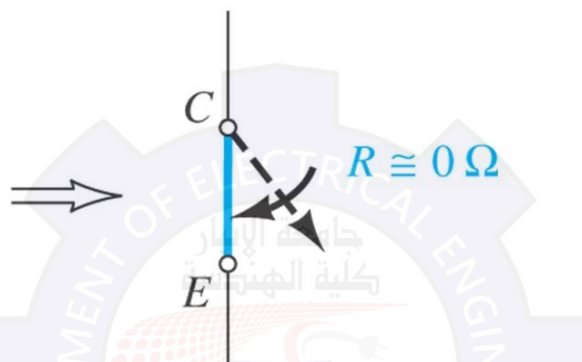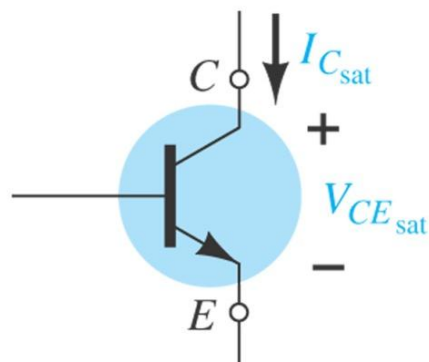

$$R_{\text{sat}} = \frac{V_{\text{CEsat}}}{I_{\text{Csat}}}$$

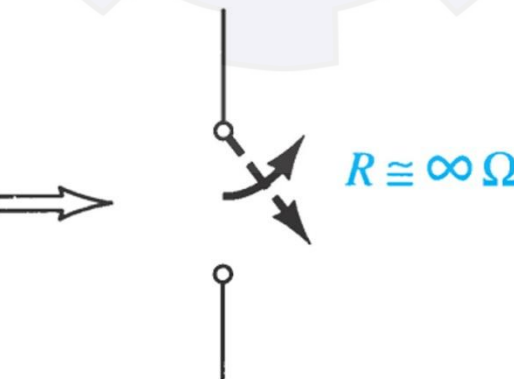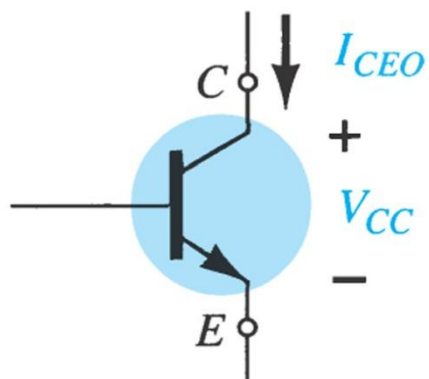Saturation conditions and the resulting terminal resistance.



$$R_{\text{cutoff}} = \frac{V_{\text{CC}}}{I_{\text{CEO}}}$$

Cutoff conditions and the resulting terminal resistance.



PNP Transistors

The analysis for *pnp* transistor biasing circuits is the same as that for *npn* transistor circuits. The only difference is that the currents are flowing in the opposite direction.