



# Fundamental of Electronic II

**Second Class**

Chapter05: BJT AC Analysis



Lec05\_p2

**Munther N. Thiyab**

**2019-2020**



# Common-Emitter Voltage-Divider Bias

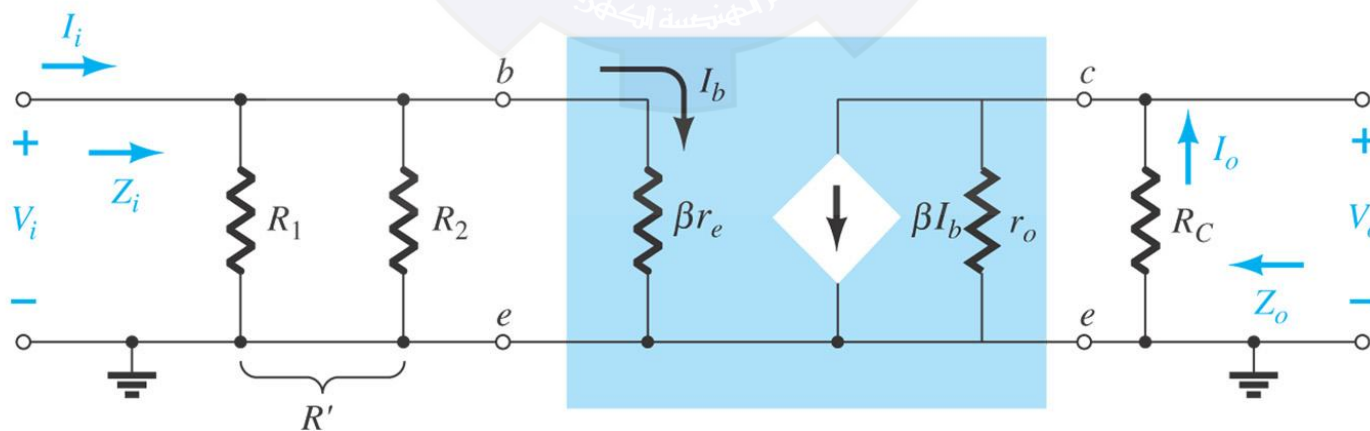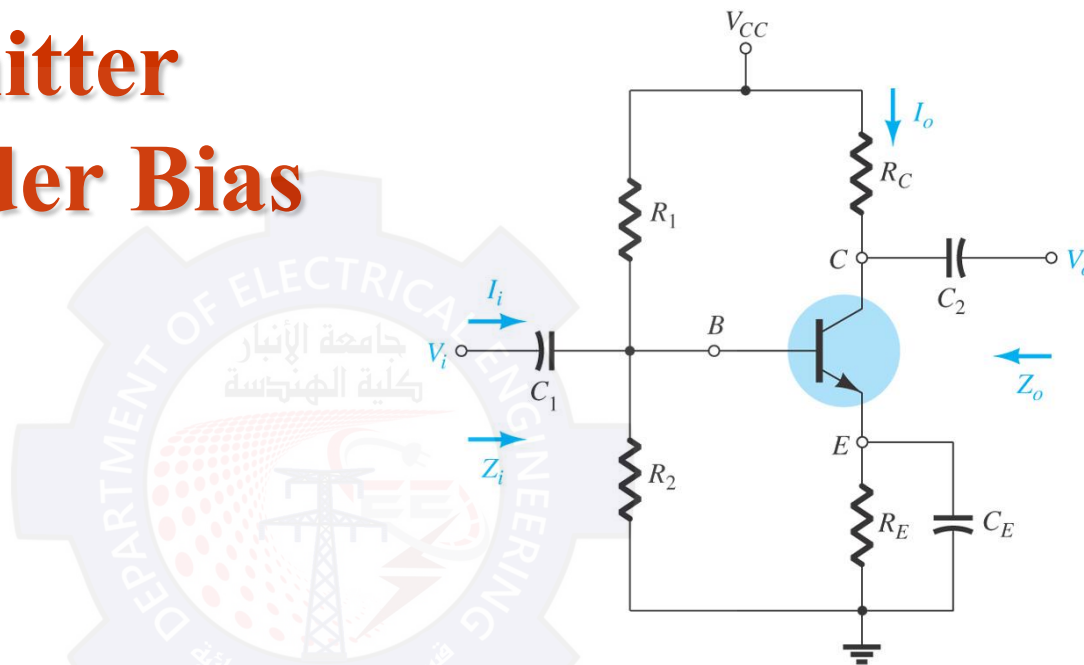

$r_e$  model requires you to determine  $\beta$ ,  $r_e$ , and  $r_o$ .




# Common-Emitter Voltage-Divider Bias

**Input impedance:**

$$R' = R_1 \parallel R_2$$

$$Z_i = R' \parallel \beta r_e$$

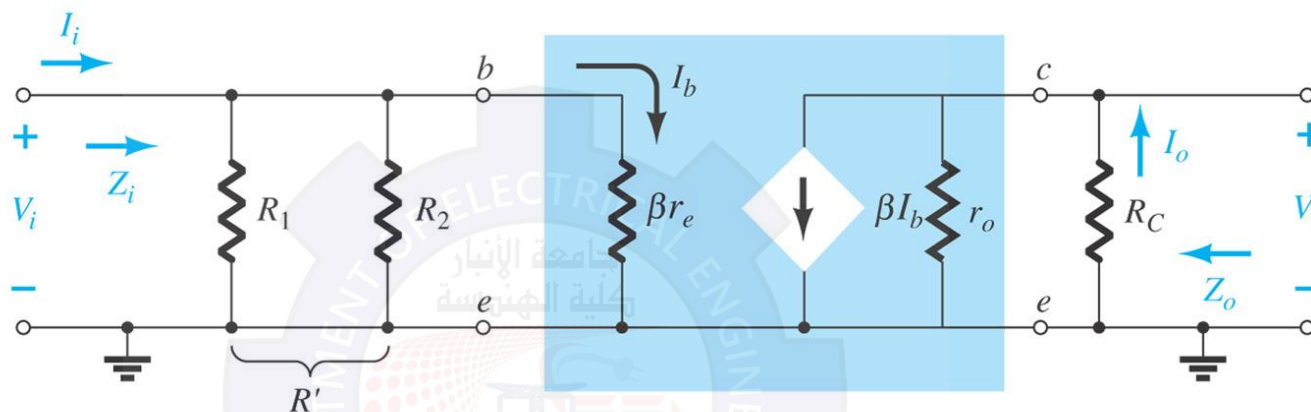

**Output impedance:**

$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \mid r_o \geq 10R_C$$

**Voltage gain:**


$$V_o = - I_b (R_C \parallel r_o) , I_b = \frac{V_i}{r_e} , V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

$$A_v = \frac{V_o}{V_i} = - \frac{(R_C \parallel r_o)}{r_e} , A_v = - \frac{R_C}{r_e} \mid r_o \geq 10R_C$$



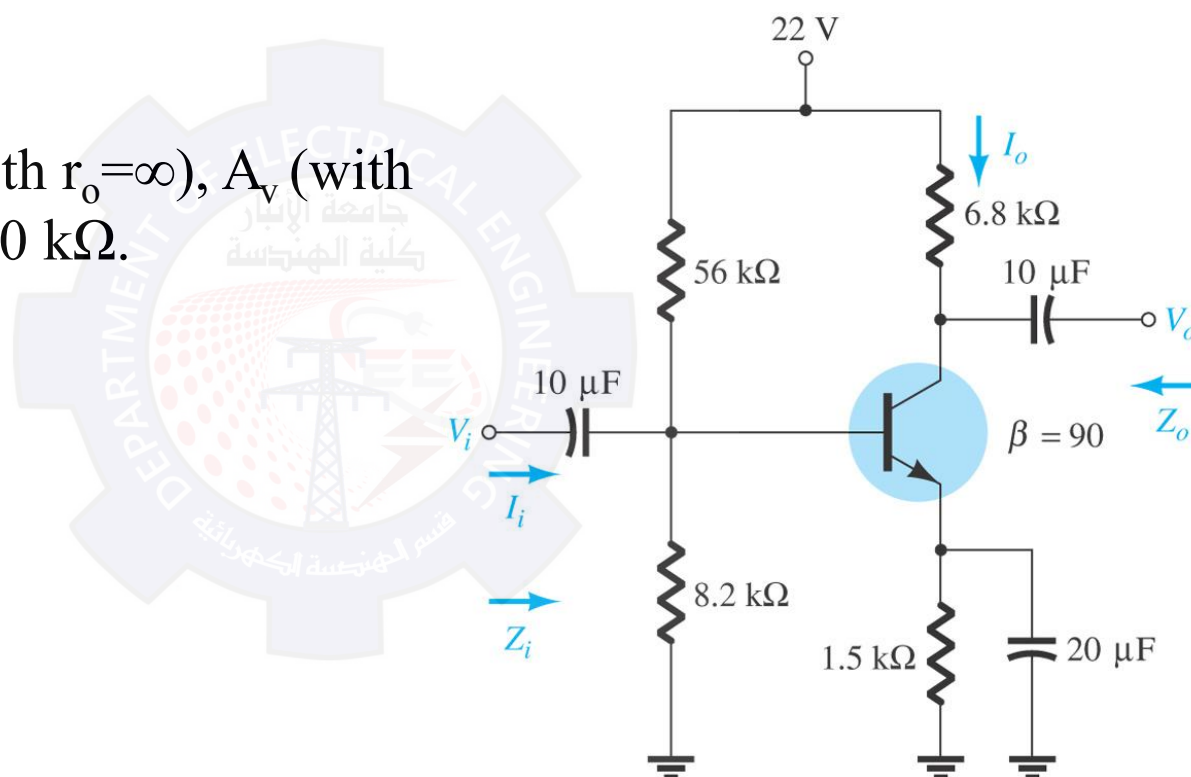
## Example 5.2

Determine  $r_e$ ,  $Z_i$ ,  $Z_o$  (with  $r_o = \infty$ ),  $A_v$  (with  $r_o = \infty$ ). Repeat with  $r_o = 50 \text{ k}\Omega$ .






## Example 5.2 - Solution

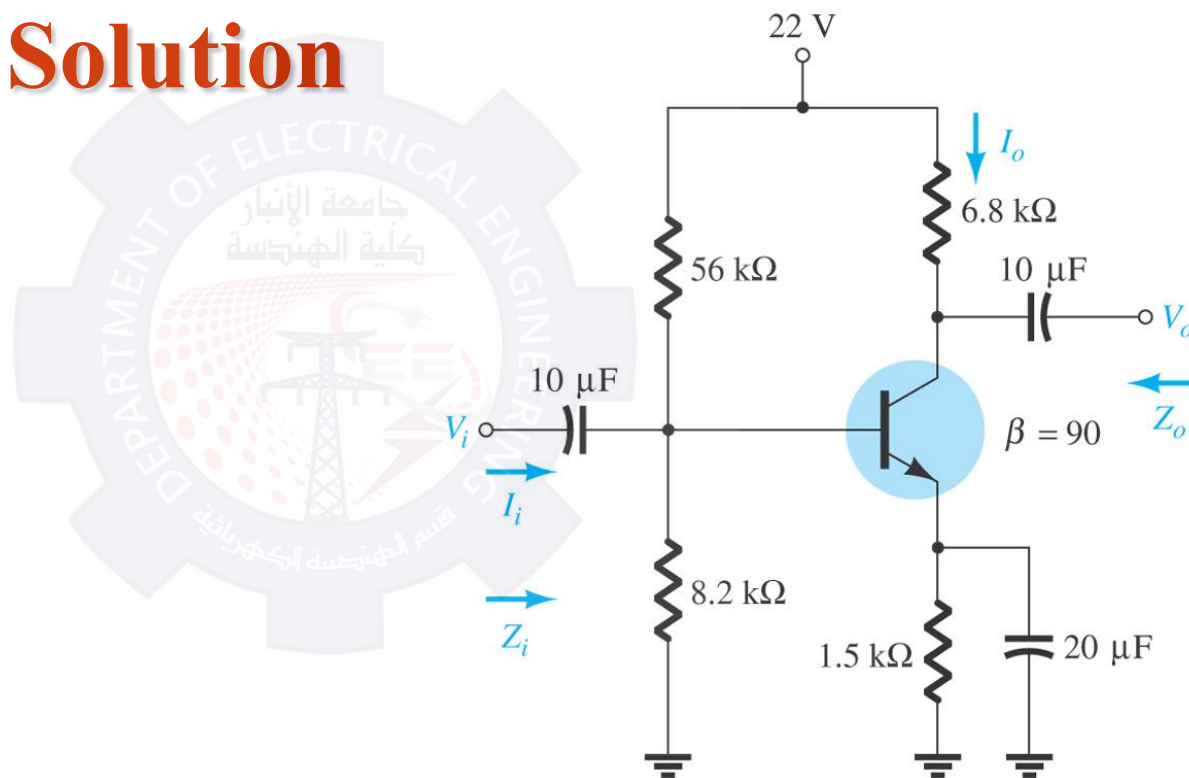


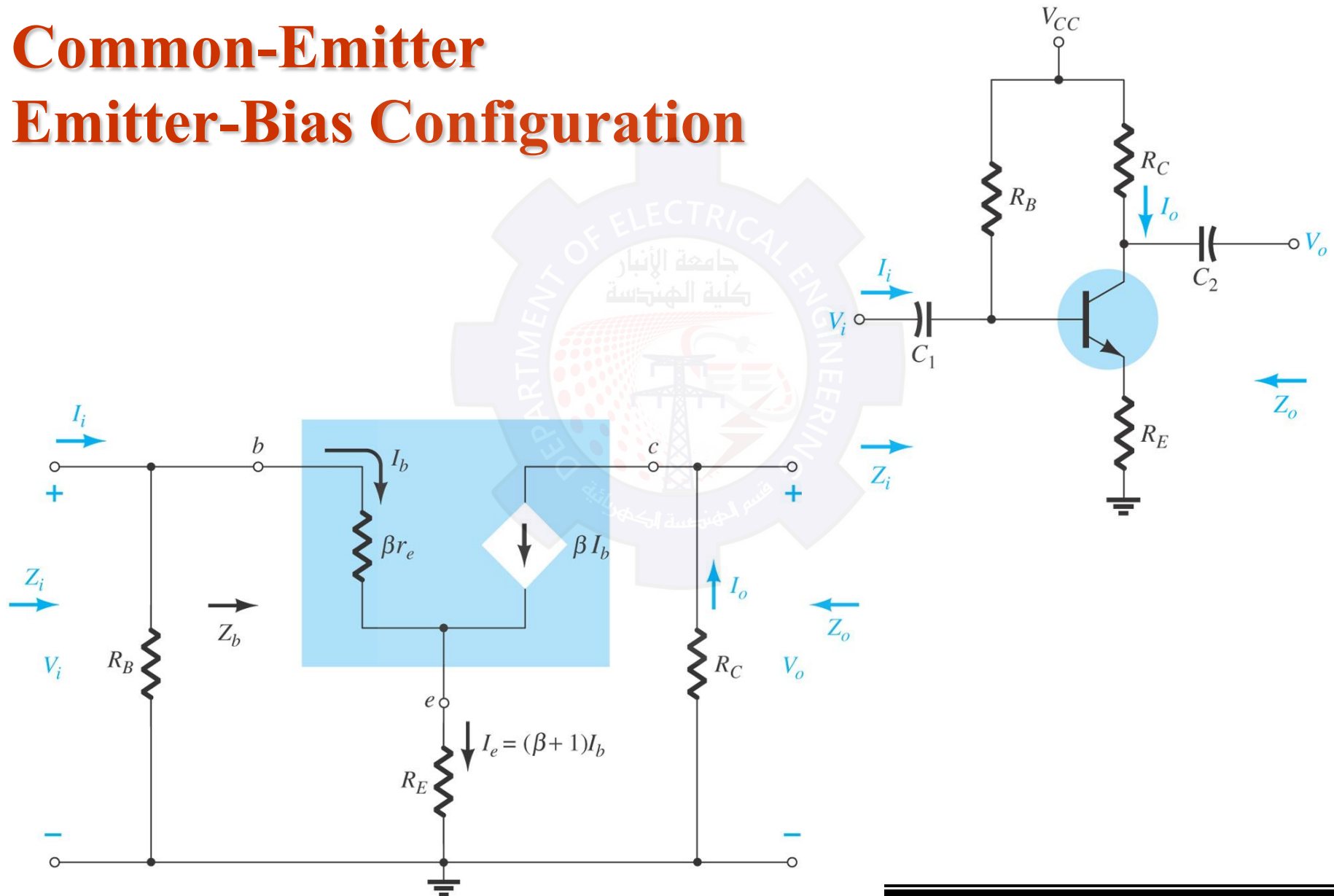
# Common-Emitter Emitter-Bias Configuration





# Impedance Calculations

## Input impedance:


$$V_i = I_b \beta r_e + I_e R_E$$

$$V_i = I_b \beta r_e + (\beta + 1) I_b R_E$$

$$Z_b = \frac{V_i}{I_b} = \beta r_e + (\beta + 1) R_E$$

$$Z_b \cong \beta r_e + \beta R_E = \beta (r_e + R_E)$$
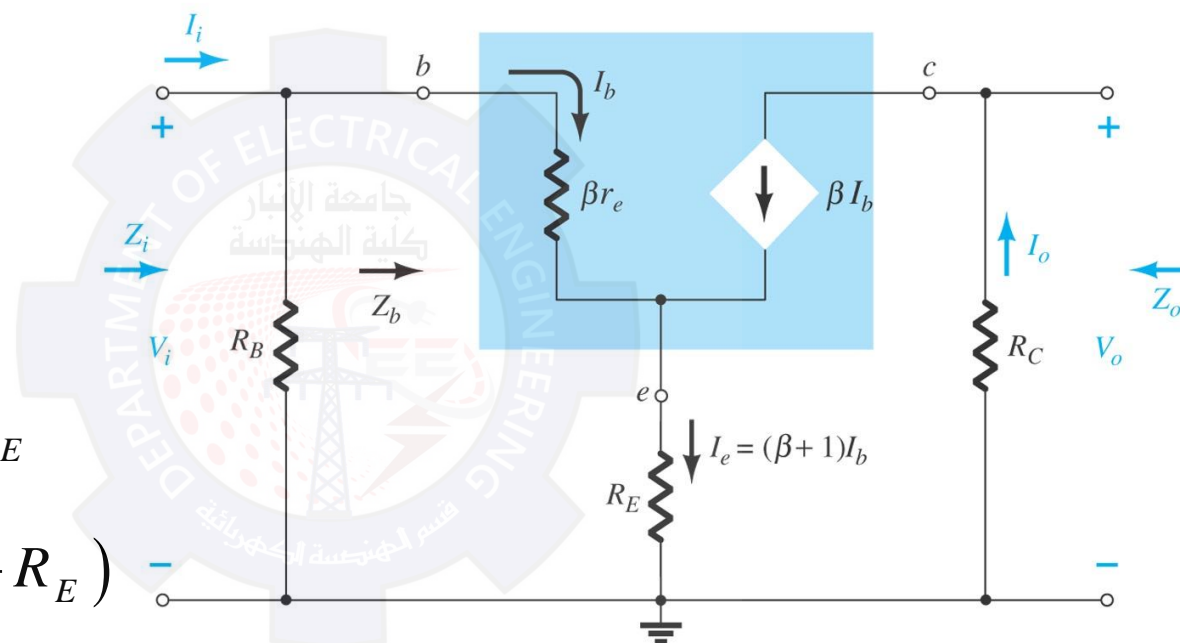
$$Z_b \cong \beta R_E \quad \text{for } R_E \gg r_e$$



## Output impedance:

$$Z_i = R_B || Z_b$$

$$Z_o = R_C$$



## Gain Calculations

**Voltage gain:**

$$V_o = -I_o R_C = -\beta I_b R_C$$

$$V_o = -\beta \left( \frac{V_i}{Z_b} \right) R_C$$


$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_C}{Z_b}$$

substituting  $Z_b \cong \beta(r_e + R_E)$

$$A_v = \frac{V_o}{V_i} = -\frac{R_C}{r_e + R_E}$$

and for the approximation  $Z_b \cong \beta R$
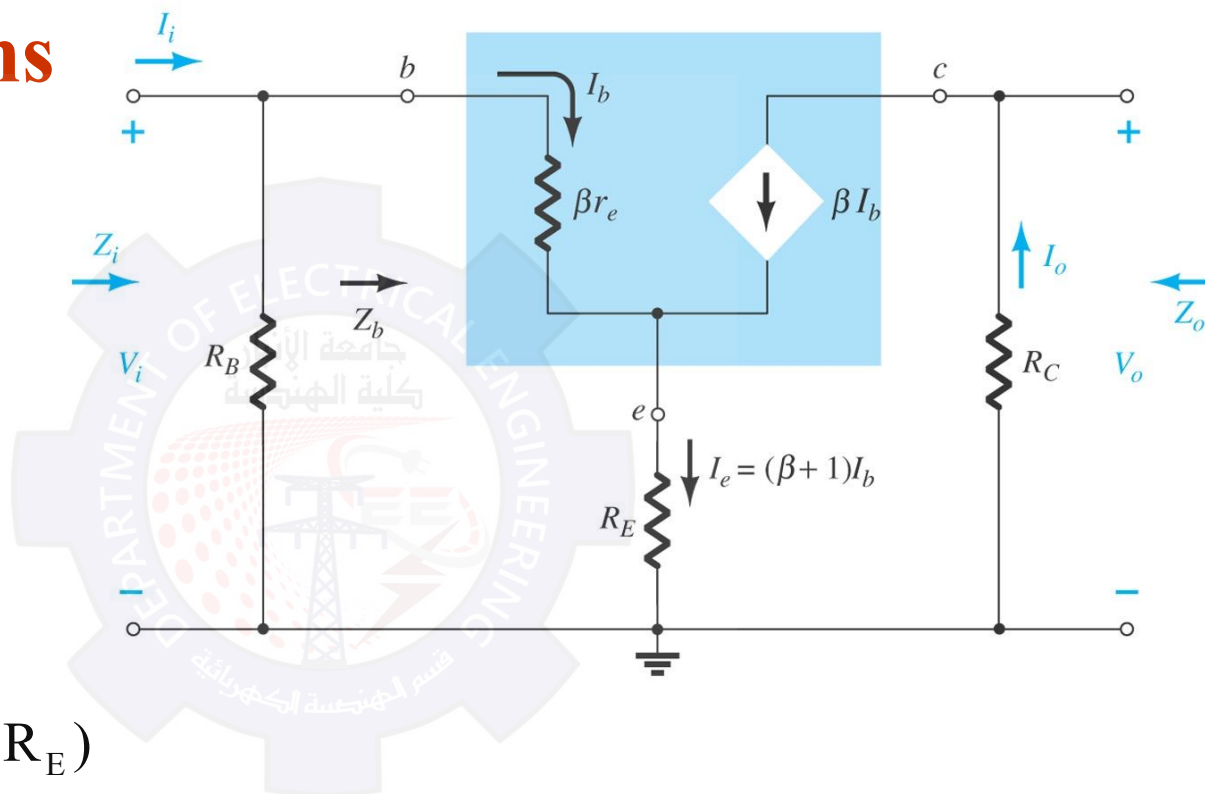
$$A_v = \frac{V_o}{V_i} \cong -\frac{R}{R_E}$$







### Example 5.3 Without $C_E$ (unbypassed):

Determine  $r_e$ ,  $Z_i$ ,  $Z_o$ ,  $A_v$ . ignore  $r_o$  for  $r_o \geq 10(R_C + R_E)$

