



Fundumantal of Electronic II

Second Class


Chapter05: BJT AC Analysis

Lec05_p3

Munther N. Thiyab

2019-2020

Emitter-Follower Configuration

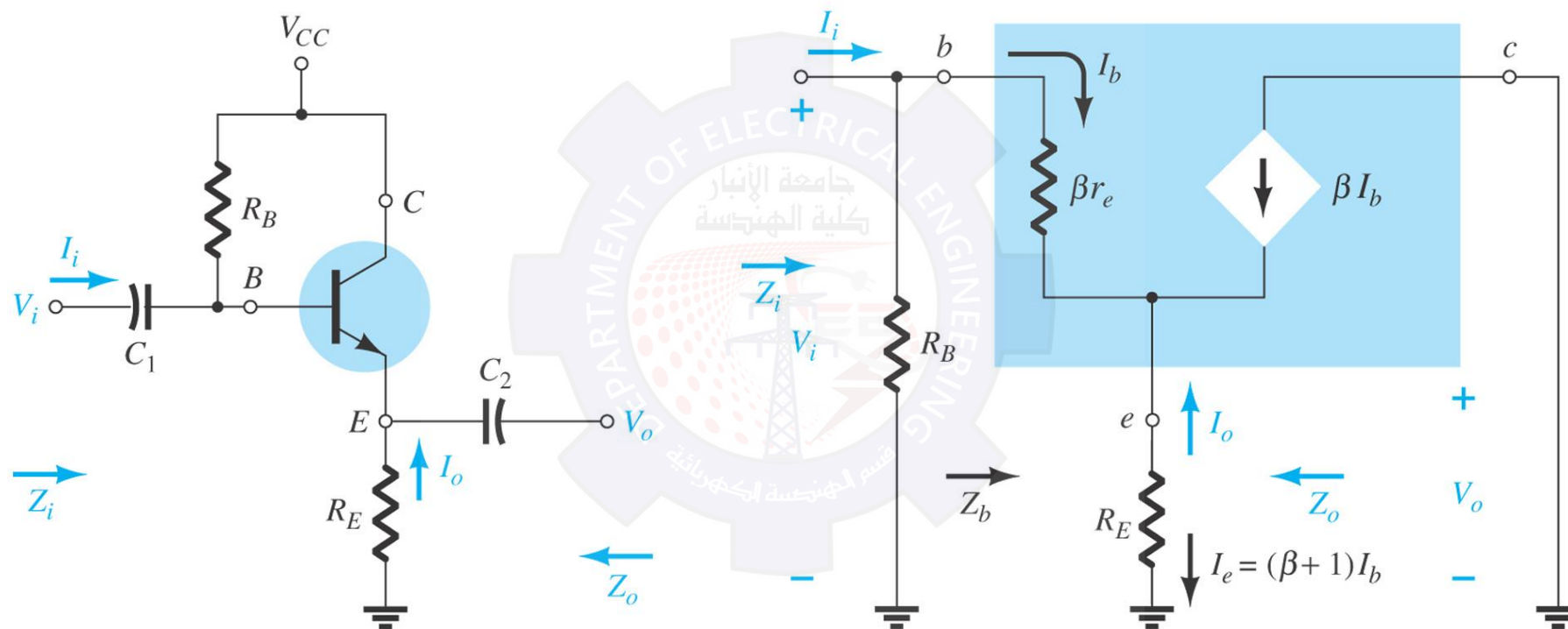

- This is also known as the common-collector configuration.
- The input is applied to the base and the output is taken from the emitter.
- There is no phase shift between input and output.



Impedance Calculations


Input impedance:

$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta(r_e + R_E)$$
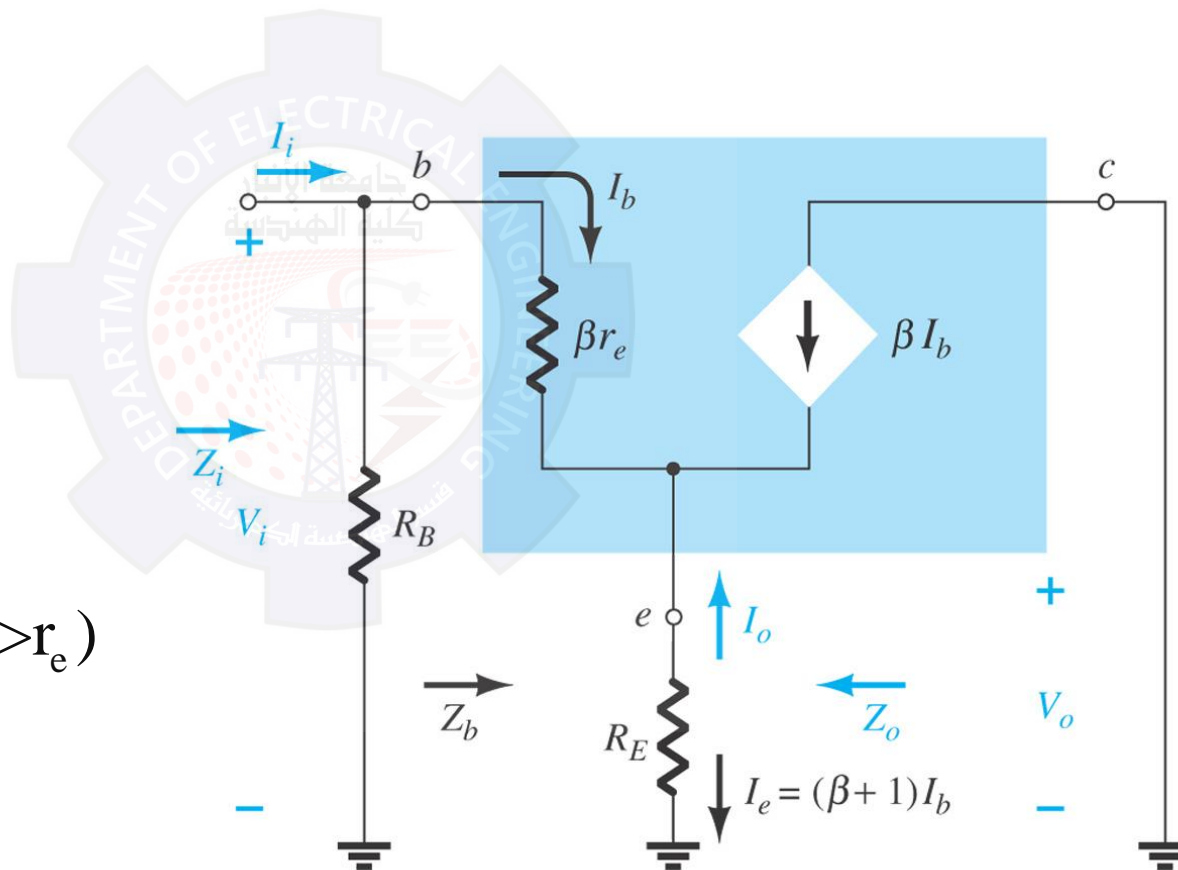
$$Z_b \cong \beta R_E \quad (\text{for } R_E \gg r_e)$$





Impedance Calculations

Output impedance:

$$I_b = \frac{V_i}{Z_b}, I_e = (\beta + 1)I_b$$

$$= (\beta + 1) \frac{V_i}{Z_b}$$



$$I_e = \frac{(\beta + 1)V_i}{\beta r_e + (\beta + 1)R_E}$$

since $(\beta + 1) \cong \beta$

$$I_e = \frac{V_i}{r_e + R}$$

To determine Z_o , V_i is set to zero

$$Z_o = R_E || r_e, \quad Z_o \approx r_e \quad | \quad R_E \gg r_e$$

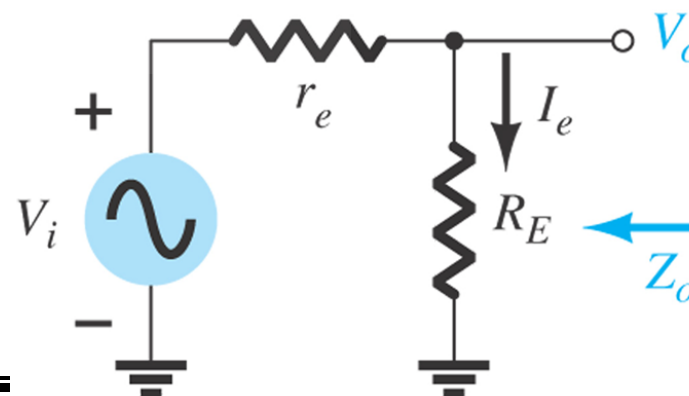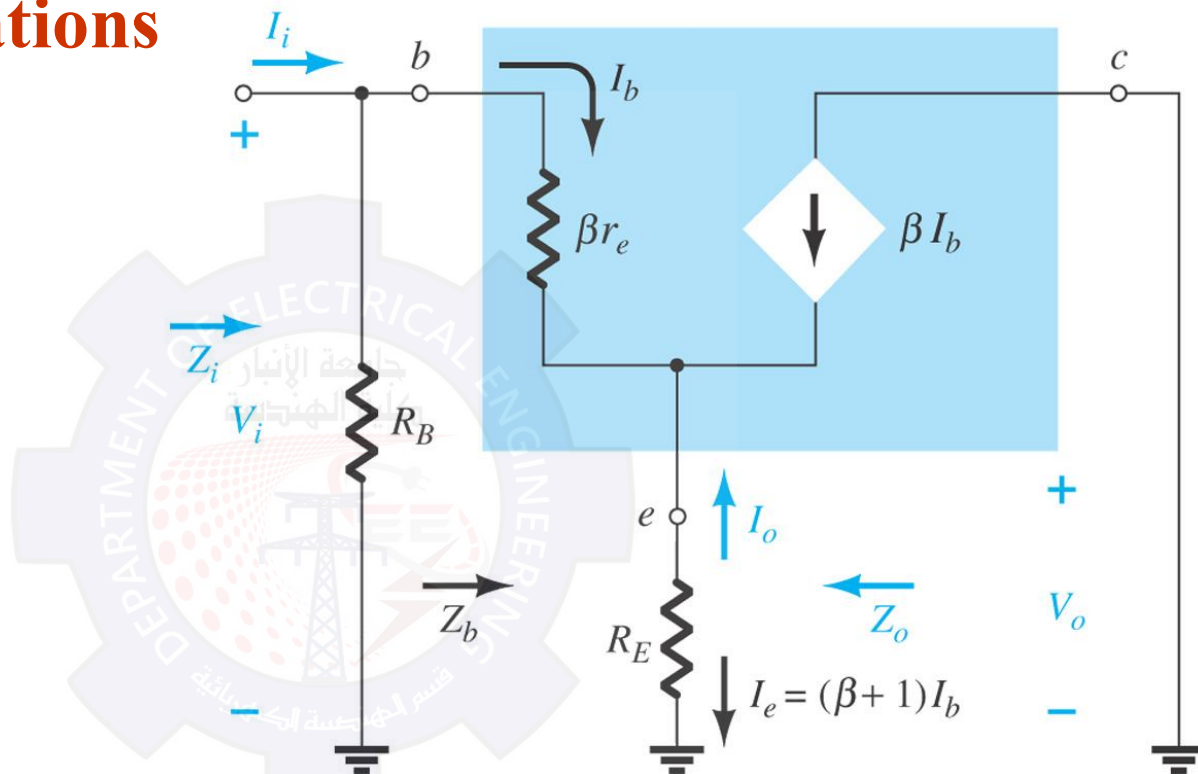





Gain Calculations

Voltage gain:

$$V_o = \frac{R_E}{R_E + r_e} V_i$$


$$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e}$$

$$A_v \frac{V_o}{V_i} \cong 1 \quad \left| \quad R_E \gg r_e, R_E + r_e \cong R_E \right.$$

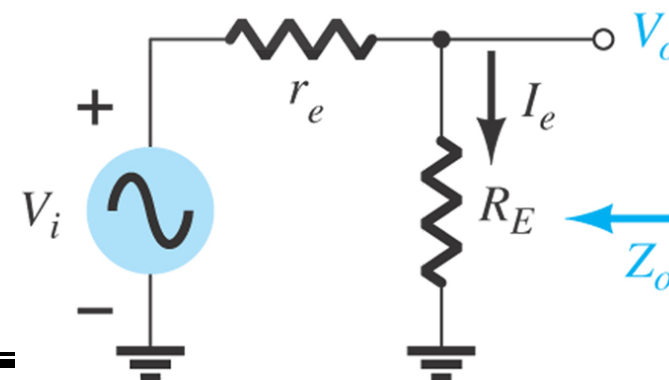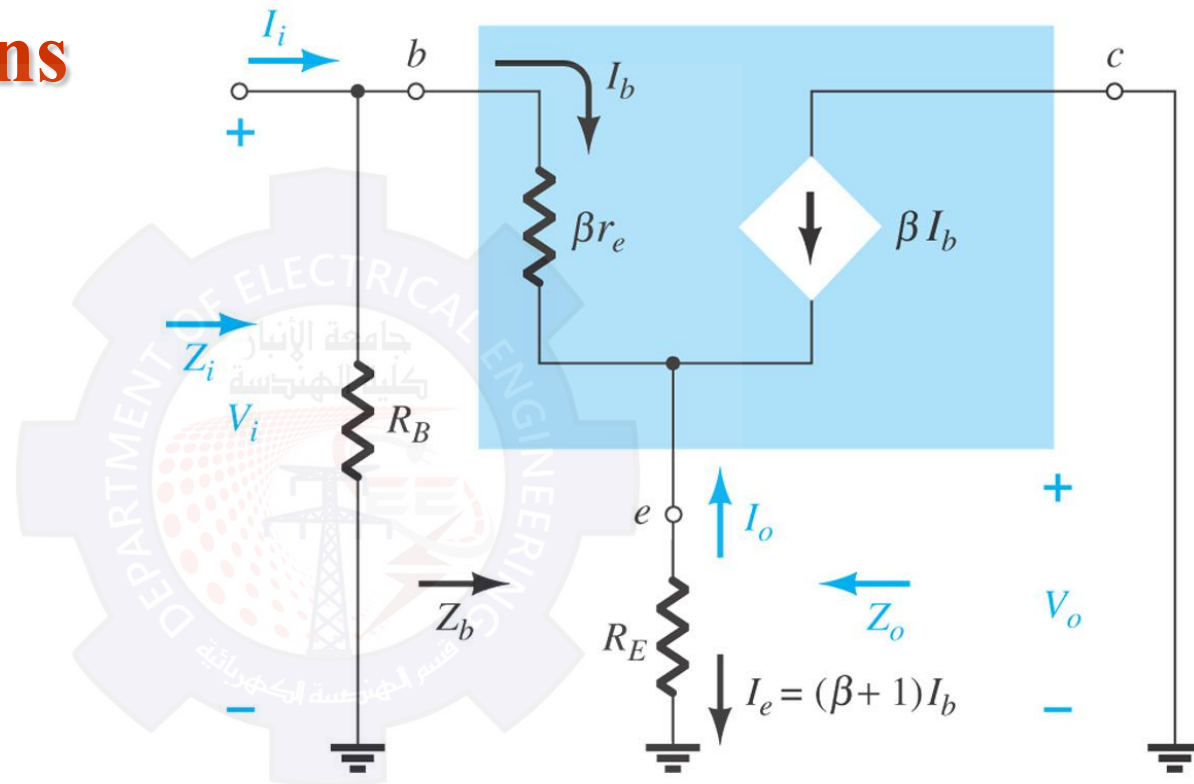



Example 5.7 Determine r_e , Z_i , Z_o , A_v .

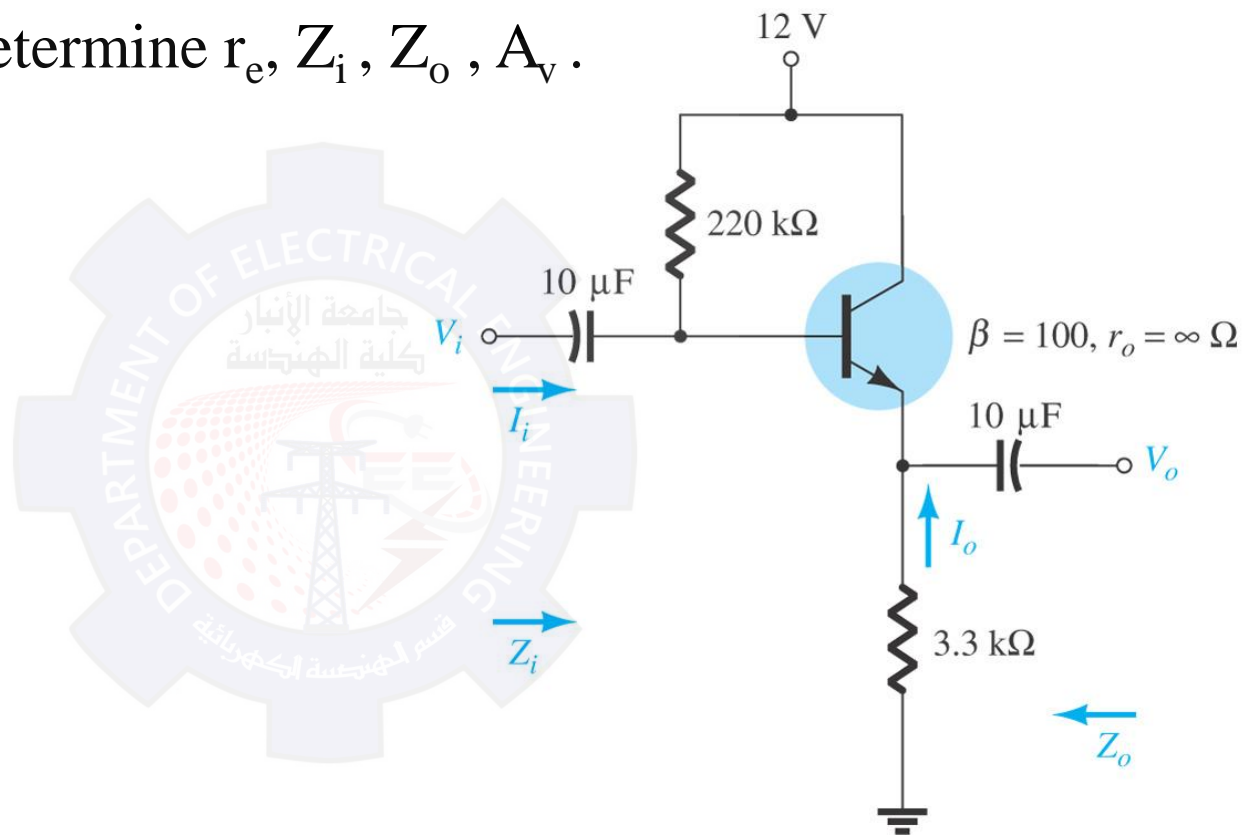



Example 5.7 - solution

