



Fundumantal of Electronic II

Second Class

Chapter05: BJT AC Analysis

Lec05_p4



Munther N. Thiyab

2019-2020



Common-Base Configuration

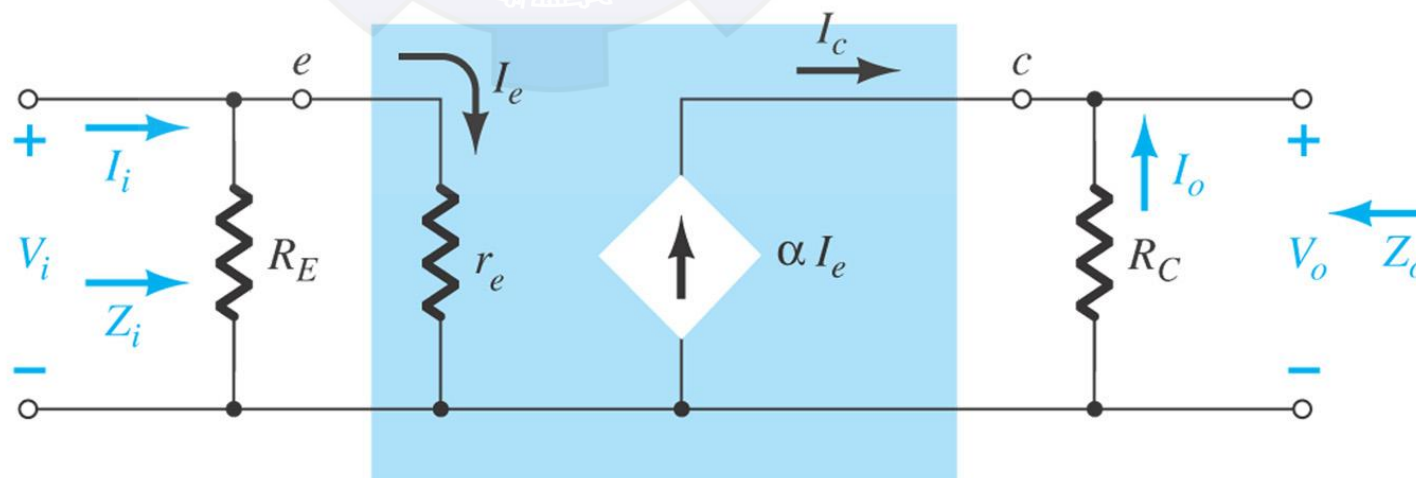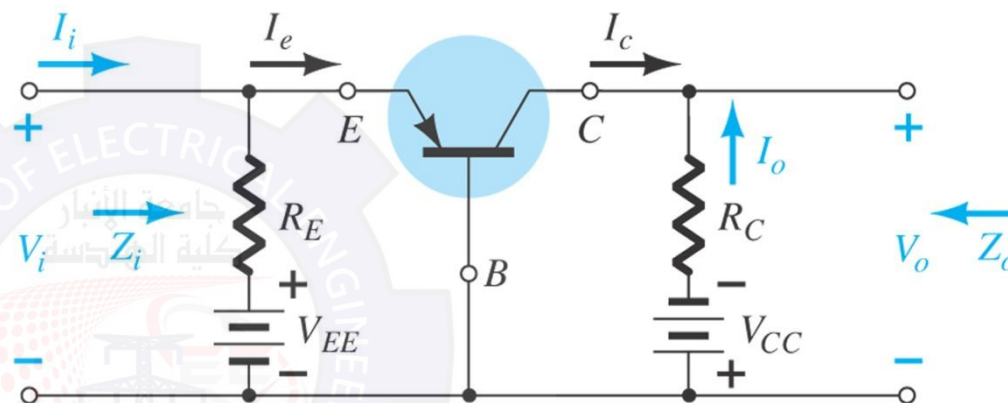- The input is applied to the emitter.
- The output is taken from the collector.
- Low input impedance.
- High output impedance.
- Very high voltage gain.
- No phase shift between input and output.





Calculations

Input impedance:

$$Z_i = R_E \parallel r_e$$

Output impedance:

$$Z_o = R_C$$


Voltage gain:

$$V_o = -I_o R_C = -(-I_C) R_C \\ = \alpha I_e R_C$$

$$I_e = \frac{V_i}{r_e} \rightarrow V_o = \alpha \left(\frac{V_i}{r_e} \right) R_C$$

$$A_v = \frac{V_o}{V_i} = \frac{\alpha R_C}{r_e} \cong \frac{R_C}{r_e}$$

A_v positive... V_i and V_o in phase.

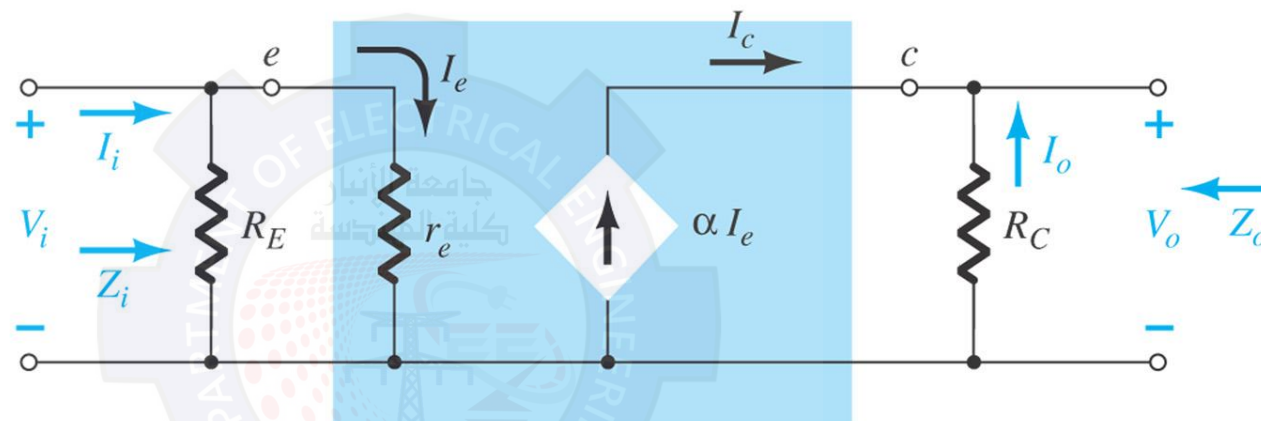

Current gain:

Assuming $R_E \gg r_e$

$$I_e = I_i$$


$$I_o = -I_e = -\alpha I_i$$

$$A_i = \frac{I_o}{I_i} = -\alpha \cong -$$




Example 5.8

Determine r_e , Z_i , Z_o , A_v , A_i

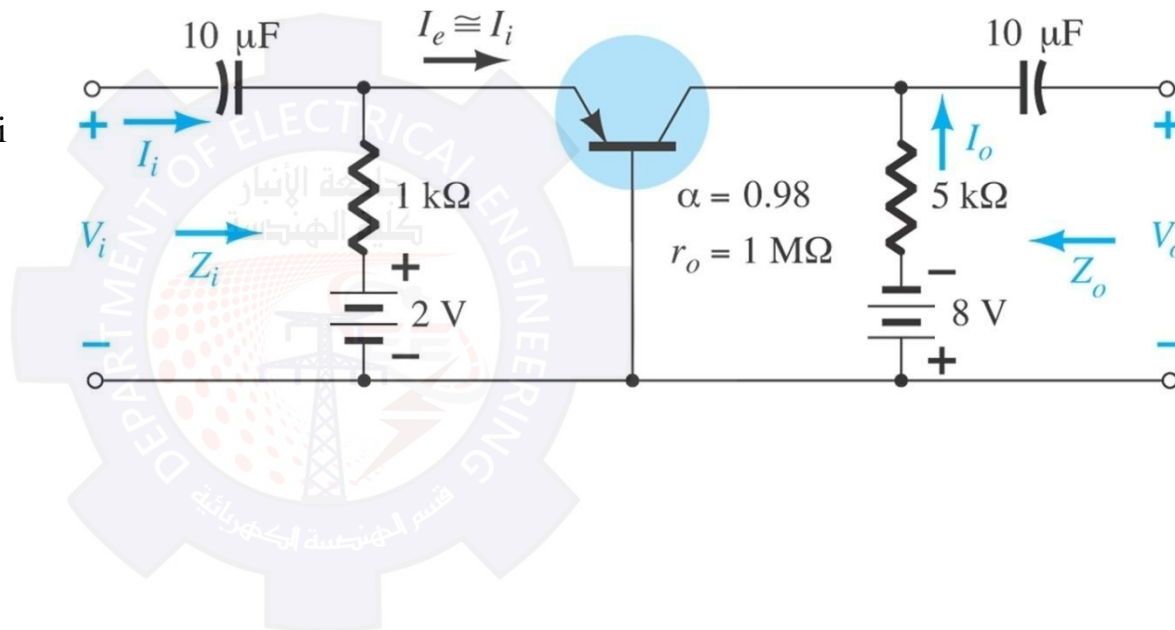



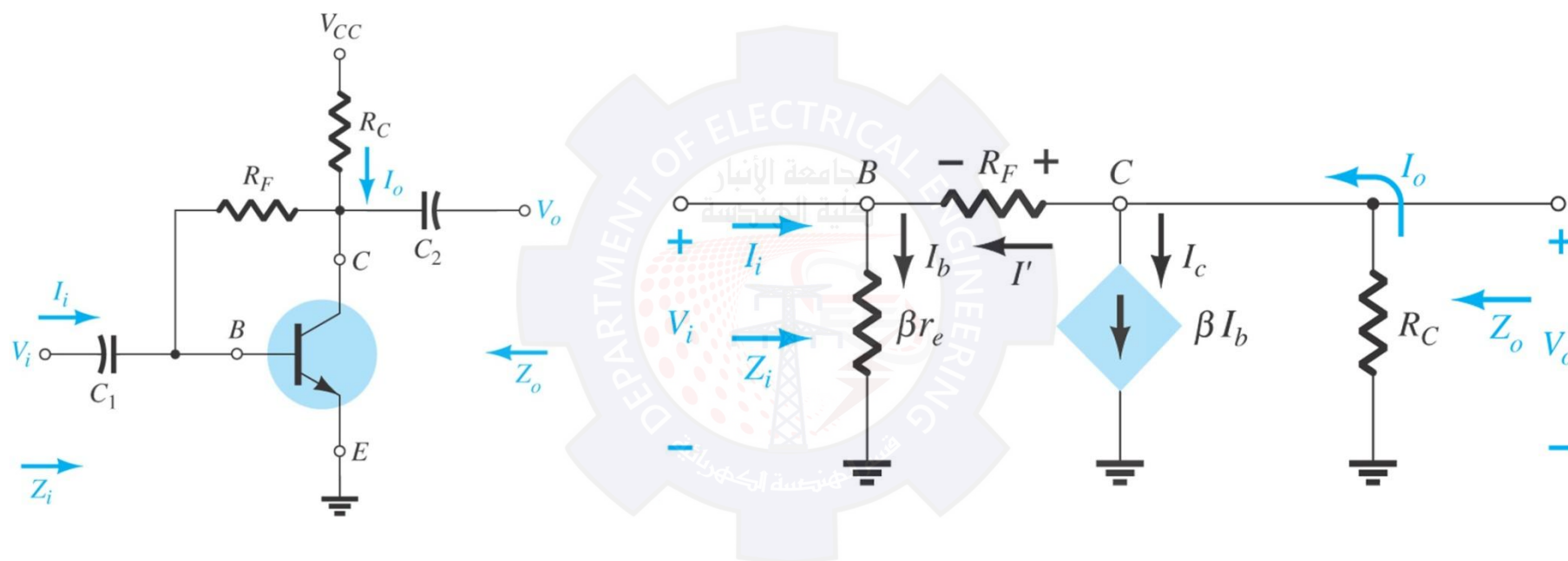Common-Emitter Collector Feedback Configuration



- This is a variation of the common-emitter fixed-bias configuration
- Input is applied to the base
- Output is taken from the collector
- There is a 180° phase shift between input and output



Calculations

Output impedance:

$$Z_o \cong R_C \parallel R_F$$

Voltage gain:



$$I_o = \beta I_b + I'$$

$$\text{For } \beta I_b \gg I' \rightarrow I_o \cong \beta I_b$$

$$V_o = -I_o R_C = -(\beta I_b) R_C$$

$$I_b = \frac{V_i}{\beta r_e} \rightarrow V_o = -\beta \frac{V_i}{\beta r_e} R_C$$
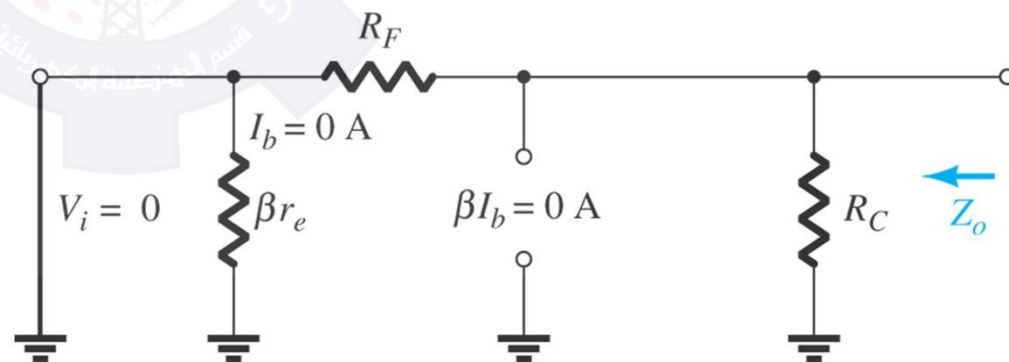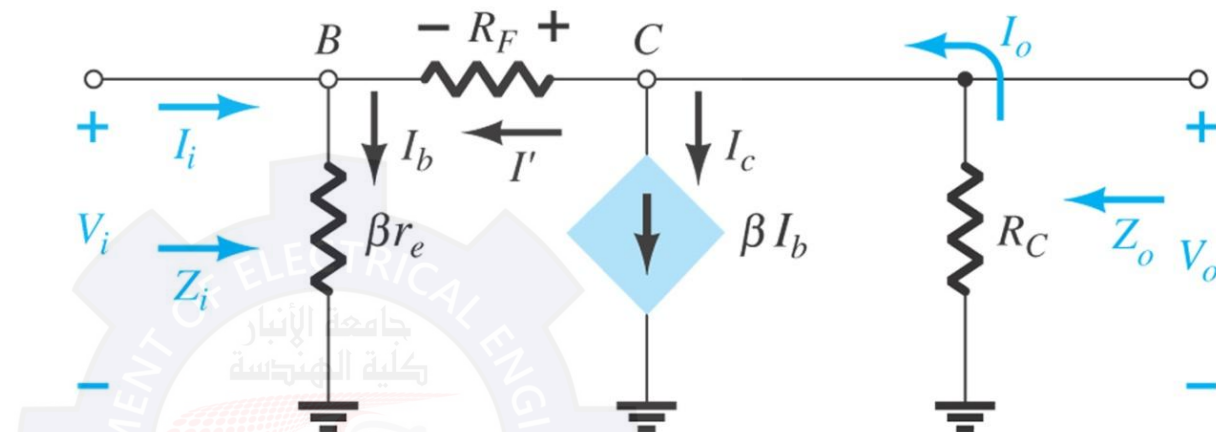
$$A_v = \frac{V_o}{V_i} = -\frac{R_C}{r_e}$$



Defining Z_o



Calculations

Input impedance:

$$Z_i = \frac{V_i}{I_i}, \quad V_o = -\frac{V_i}{r_e} R_C$$

$$I' = \frac{V_o - V_i}{R_F} = \frac{V_o}{R_F} - \frac{V_i}{R_F} = -\frac{R_C V_i}{r_e R_F} - \frac{V_i}{R_F} = -\frac{1}{R_F} \left[1 + \frac{R_C}{r_e} \right] V_i$$


$$V_i = I_b \beta r_e = (I_i + I') \beta r_e = I_i \beta r_e + I' \beta r_e$$

$$V_i = I_i \beta r_e - \frac{1}{R_F} \left[1 + \frac{R_C}{r_e} \right] \beta r_e V_i$$


$$\text{or } V_i \left[1 + \frac{\beta r_e}{R_F} \left[1 + \frac{R_C}{r_e} \right] \right] = I_i \beta r_e$$

$$Z_i = \frac{V_i}{I_i} = \frac{\beta r_e}{1 + \frac{\beta r_e}{R_F} \left[1 + \frac{R_C}{r_e} \right]}$$
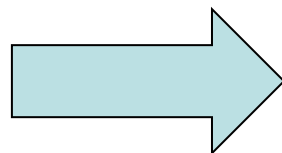
$$1 + \frac{R_C}{r_e} \cong \frac{R_C}{r_e} \rightarrow Z_i = \frac{\beta r_e}{1 + \frac{\beta R_C}{R_F}}$$


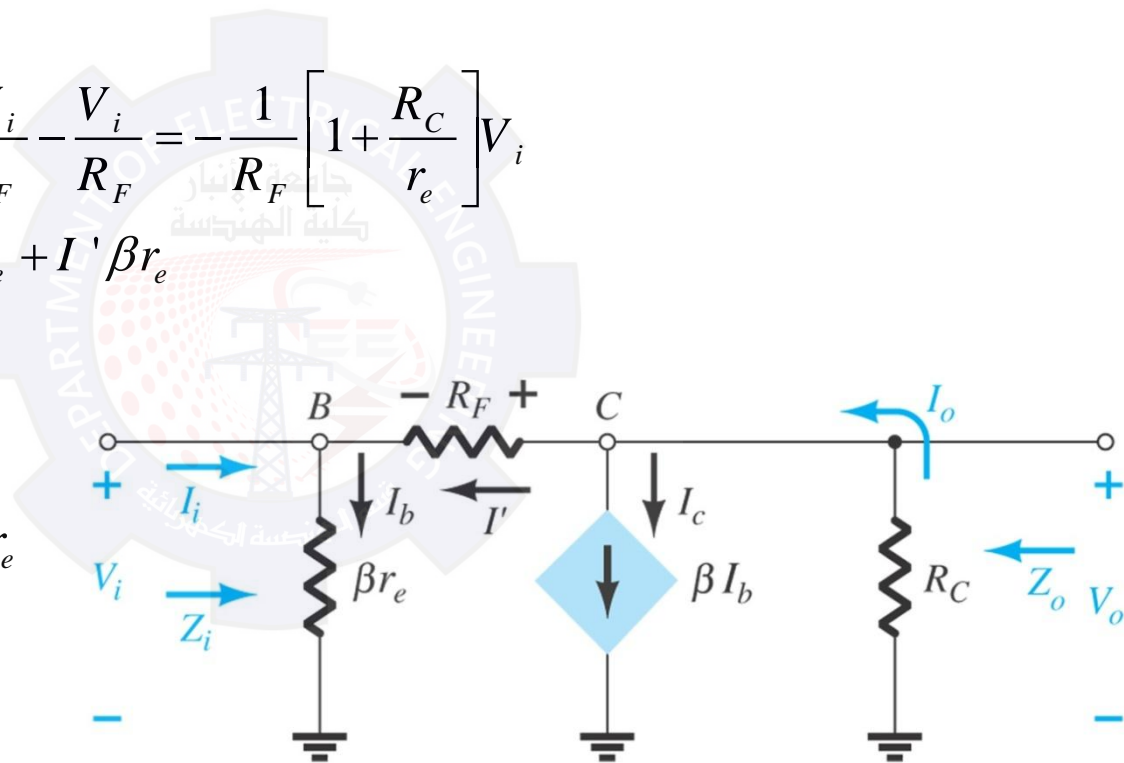
$$Z_i = \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}$$





Determining the current gain using the voltage gain



Current Gain $A_i = \frac{I_o}{I_i}$, $I_i = \frac{V_i}{Z_i}$, $I_o = -\frac{V_o}{R_L}$

$$A_{i_L} = \frac{I_o}{I_i} = \frac{-\frac{V_o}{R_L}}{\frac{V_i}{Z_i}} = -\frac{V_o}{V_i} \cdot \frac{Z_i}{R_L}$$

$$A_i = -A_{v_L} \frac{Z_i}{R_L}$$



Determining the current gain using the voltage gain

From example 5.2

$$Z_i = 1.35 \text{ k}\Omega$$

$$A_v = -368.76$$

Current Gain $A_i = \frac{I_o}{I_i}$,

$$I_i = \frac{V_i}{1.35k} \quad , \quad I_o = -\frac{V_o}{6.8k}$$

$$A_{iL} = \frac{I_o}{I_i} = \frac{-\frac{V_o}{6.8k}}{\frac{V_i}{1.35k}} = -\frac{V_o}{V_i} \cdot \frac{1.35k}{6.8k}$$

$$= -(-368.76) \frac{1.35k}{6.8k} = 73.2$$

$$\text{or } A_i = -A_{vL} \frac{Z_i}{R_L} = -(-368.76) \frac{1.35k}{6.8k} = 73.2$$

