



# Fundumantal of Electronic II

**Second Class**

Chapter05: BJT AC Analysis


Lec05\_p5

**Munther N. Thiyab**

**2019-2020**



## Effect of $R_L$ and $R_S$

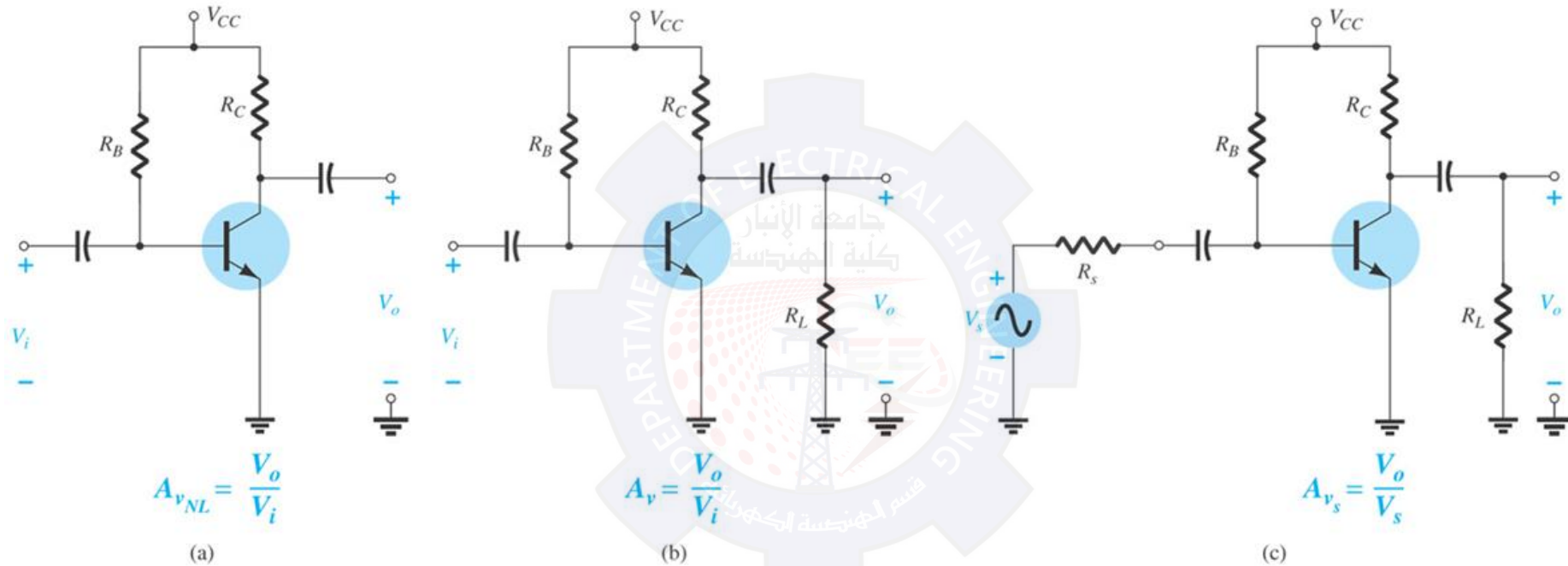


$$A_{vNL} = \frac{V_o}{V_i}, \quad A_{vL} = \frac{V_o}{V_i}, \quad \text{with } R_L$$

$$A_{v_s} = \frac{V_o}{V_s}, \quad \text{with } R_L \text{ and } R_s$$



## Effect of $R_L$ and $R_S$

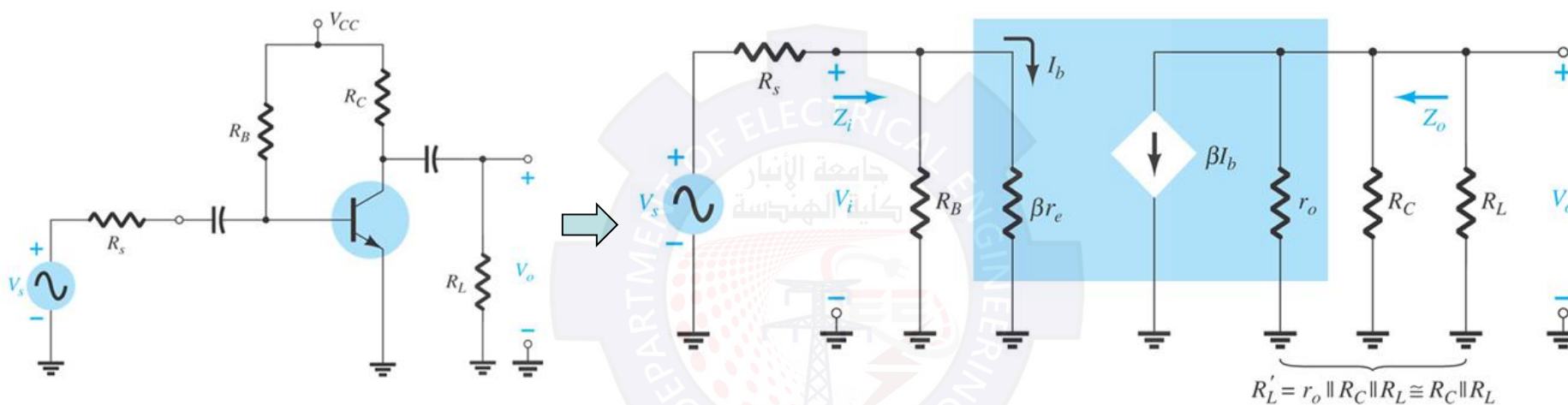


$$V_o = -\beta I_b (R_C \parallel r_o \parallel R_L) = -\beta I_b (R_C \parallel R_L), \quad I_b = \frac{V_i}{\beta r_e},$$

$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel R_L) \Rightarrow A_{vL} = \frac{V_o}{V_i} = -\frac{(R_C \parallel R_L)}{r_e}$$



## Effect of $R_L$ and $R_S$

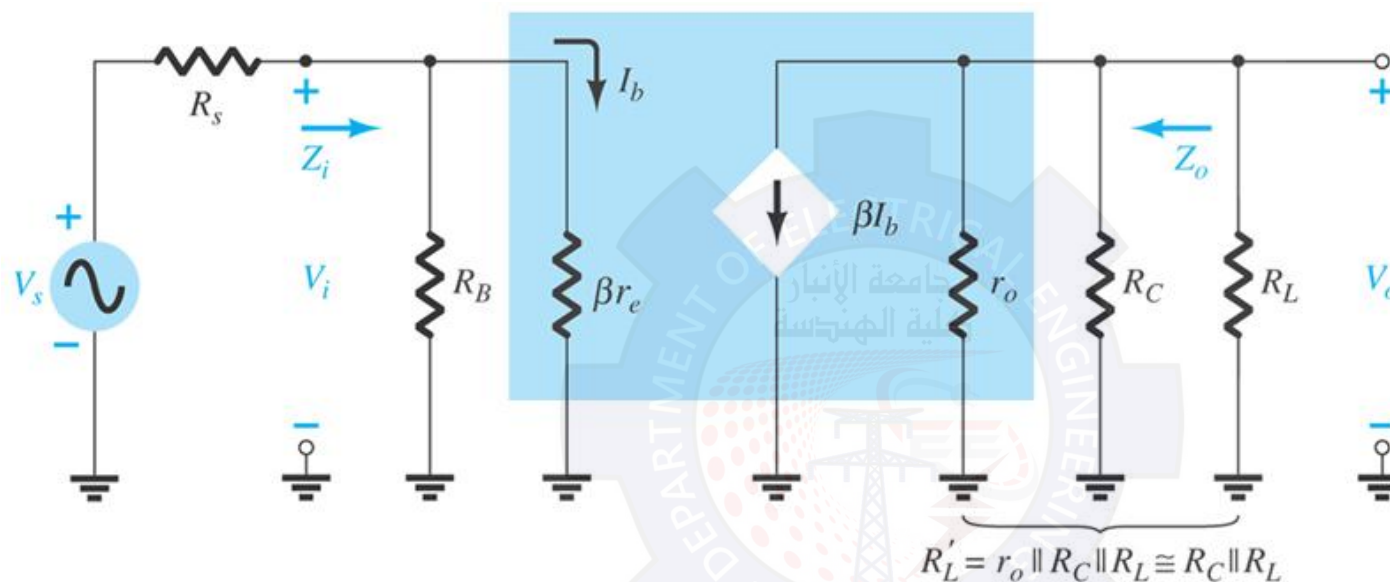


Input impedance:  $Z_i = R_B \parallel \beta r_e$

Output Impedance:  $Z_o = R_C \parallel r_o$

To find overall gain:  $V_i = \frac{Z_i V_s}{Z_i + R_s}$ ,  $\frac{V_i}{V_s} = \frac{Z_i}{Z_i + R_s}$

$$A_{vS} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = A_{vL} \frac{Z_i}{Z_i + R_s} \Rightarrow A_{vS} = \frac{Z_i}{Z_i + R_s} A_{vL}$$

## Darlington Connection

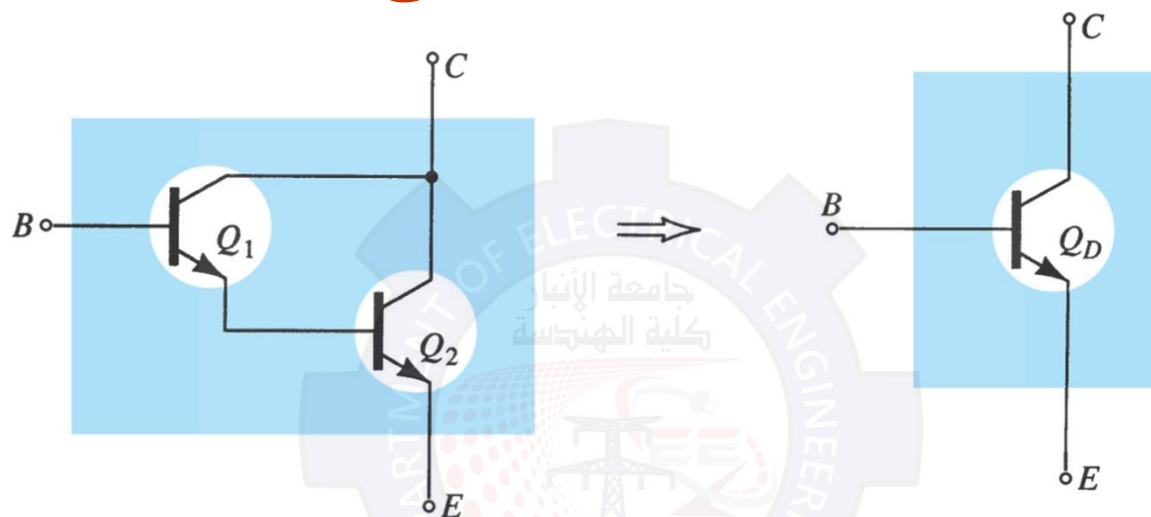

- The Darlington circuit provides a very high current gain—the product of the individual current gains:  $\beta_D = \beta_1\beta_2$
- A Darlington transistor connection provides a transistor having a very large current gain, typically a few thousand.
- Darlington pairs are available as complete packages.
- A Darlington pair is sufficiently sensitive to respond to the small current.

## DC Bias of Darlington Circuits

**Base current:**

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta_D R_E}$$

**Emitter current:**


$$I_E = (\beta_D + 1)I_B \approx \beta_D I_B$$

**Emitter voltage:**

$$V_E = I_E R_E$$

**Base voltage:**

$$V_B = V_E + V_{BE}$$

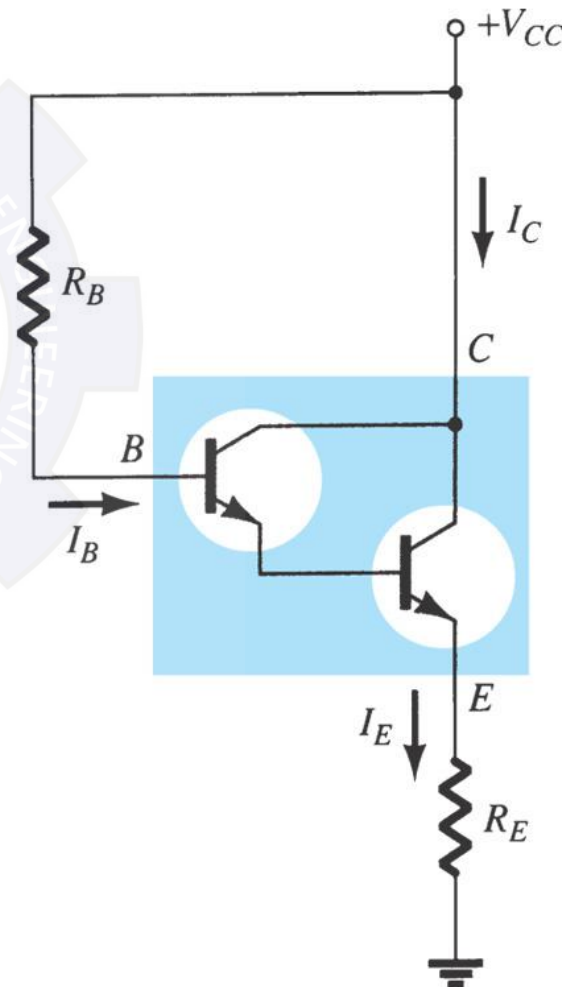



## Darlington Circuits

- When light falls on the LDR, its resistance reduces.
- The bias voltage is supplied to the transistor and this voltage is enough to make the transistor and relay work.
- A variable resistor is also connected on the base of transistor to adjust the sensitivity.

