



Fundumantal of Electronic II

Second Class

Chapter 7 : FET Biasing
Lec07_p3

Munther N. Thiyab


2019-2020



E-Type MOSFET Bias Circuits


The transfer characteristic for the e-type MOSFET is very different from that of a simple JFET or the d-type MOSFET.

$$I_D = k (V_{GS} - V_{GS(Th)})^2$$

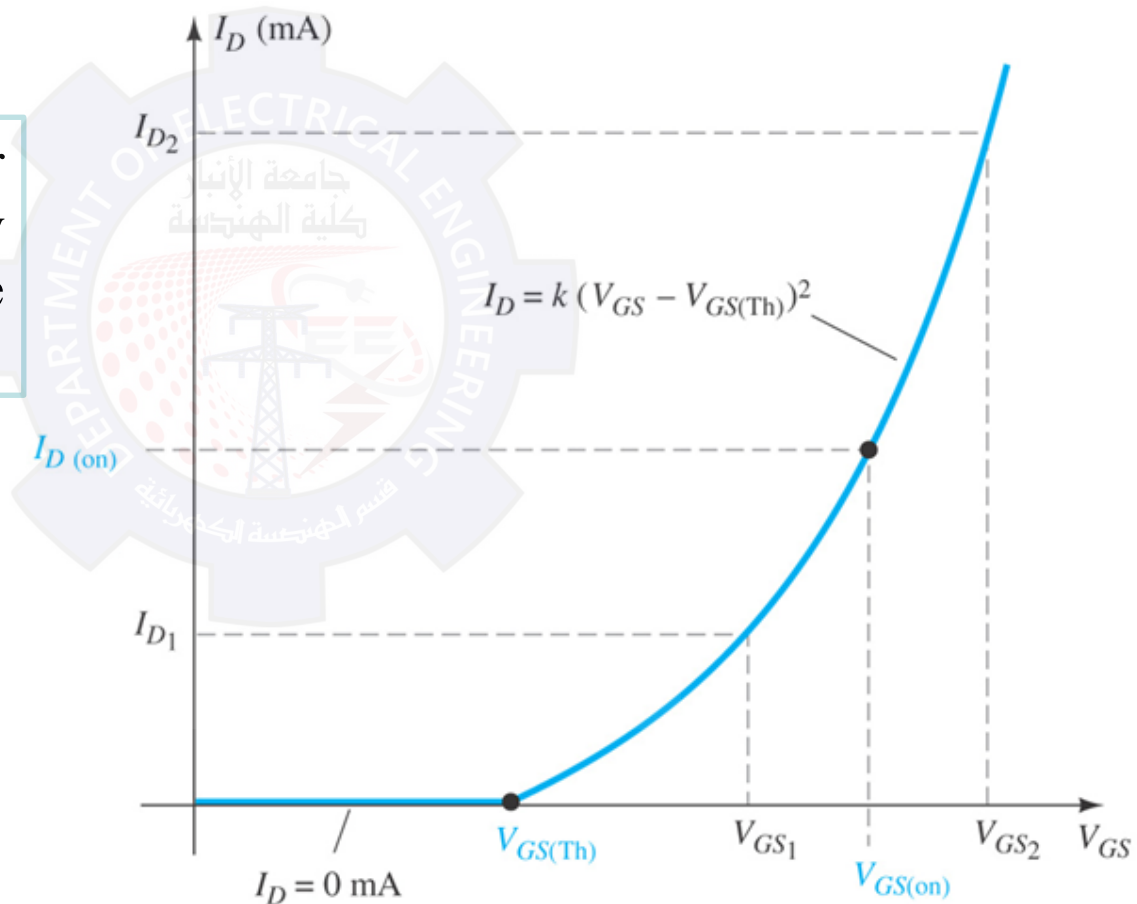



Feedback Bias Circuit

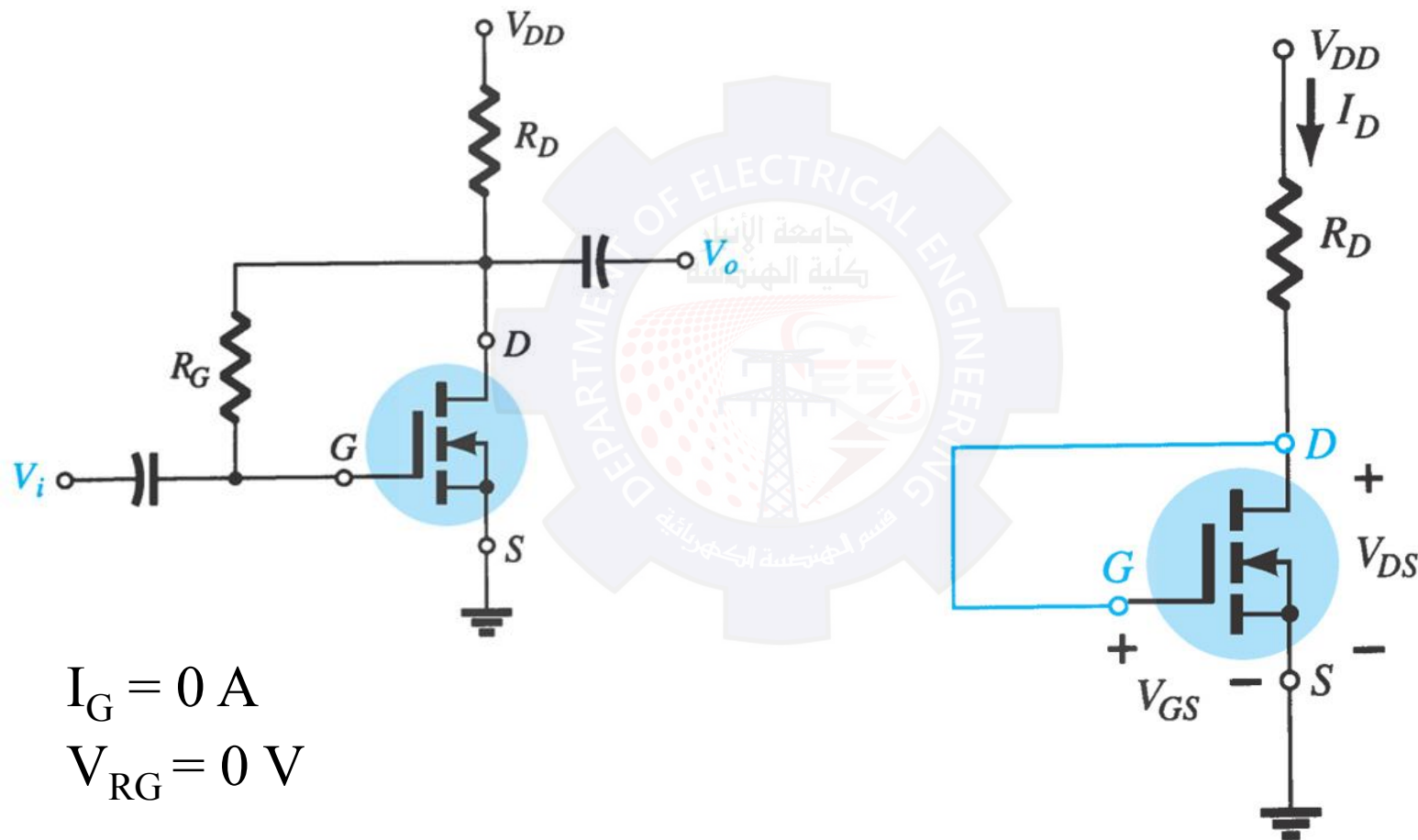

$$I_G = 0 \text{ A}$$

$$V_{RG} = 0 \text{ V}$$

$$V_{DS} = V_{GS}$$

$$V_{GS} = V_{DD} - I_D R_D$$

DC equivalent of the network



Feedback Bias Q-Point

Step 1

Plot the line using

- $V_{GS} = V_{DD}$, $I_D = 0$ A
- $I_D = V_{DD} / R_D$, $V_{GS} = 0$ V

Step 2

Using values from the specification sheet, plot the transfer curve with


- $V_{GS(Th)}$, $I_D = 0$ A
- $V_{GS(on)}$, $I_{D(on)}$

Step 3

The Q-point is located where the line and the transfer curve intersect

Step 4

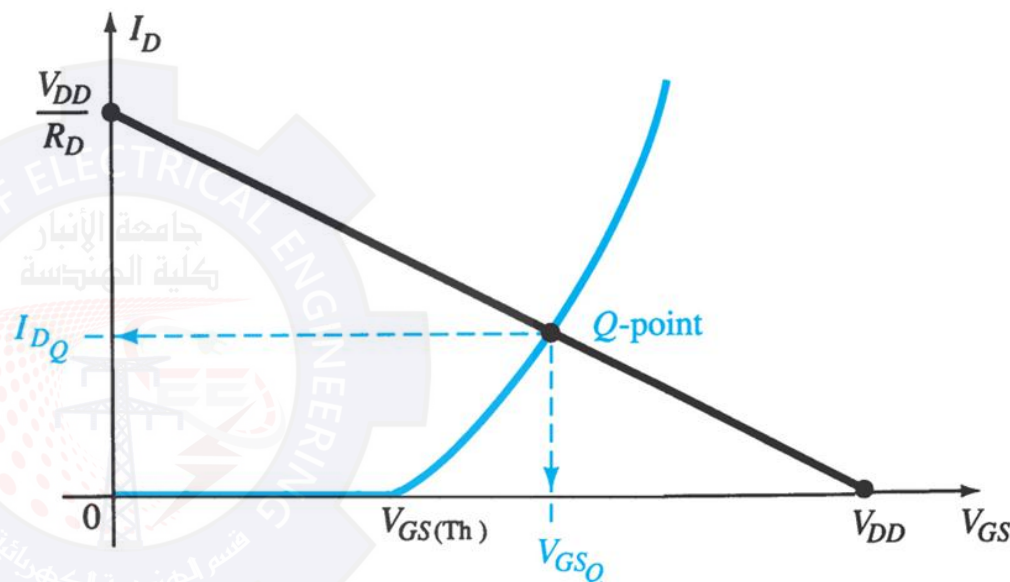Using the value of I_D at the Q-point, solve for the other variables in the bias circuit.





$$V_{GS} = V_{DD} - I_D R_D$$



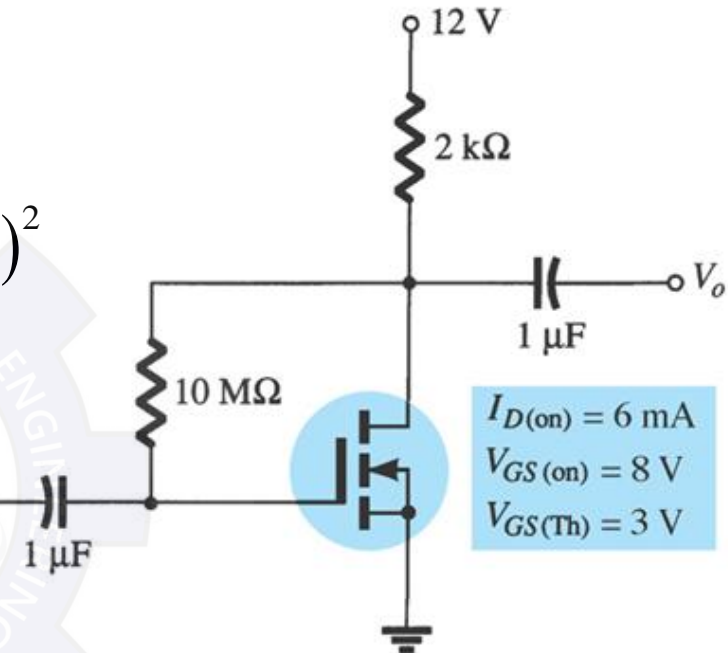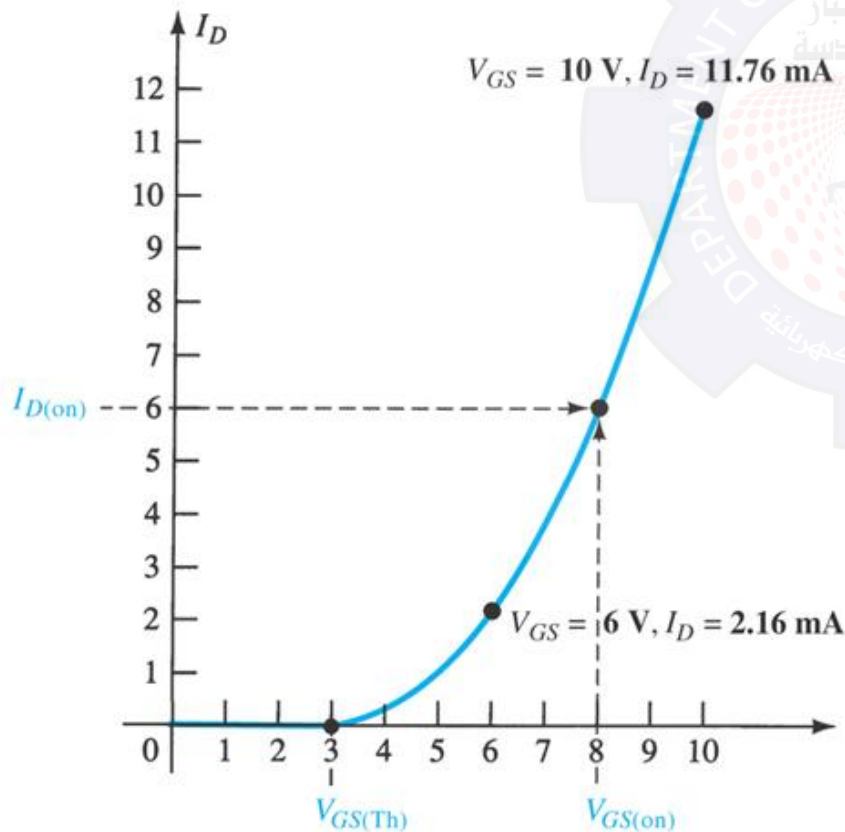Example 7.11 Find V_{GSQ} , I_{DQ}

Plot Transfer Curve:

$$I_D = k (V_{GS} - V_{GS(Th)})^2 = 0.24 \times 10^{-3} (V_{GS} - 3)^2$$





$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(Th)})^2}$$

$$k = \frac{6 \text{ mA}}{(8 - 3)^2} = 0.24 \times 10^{-3}$$



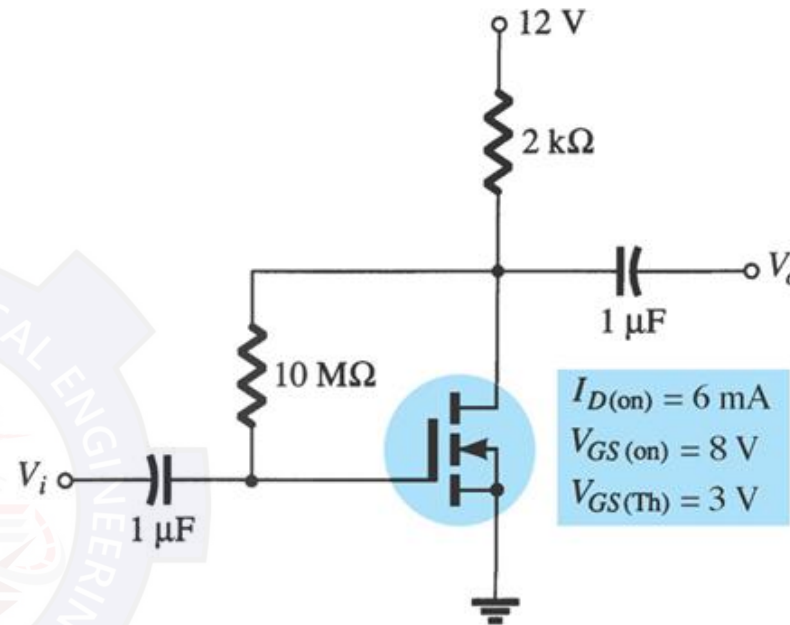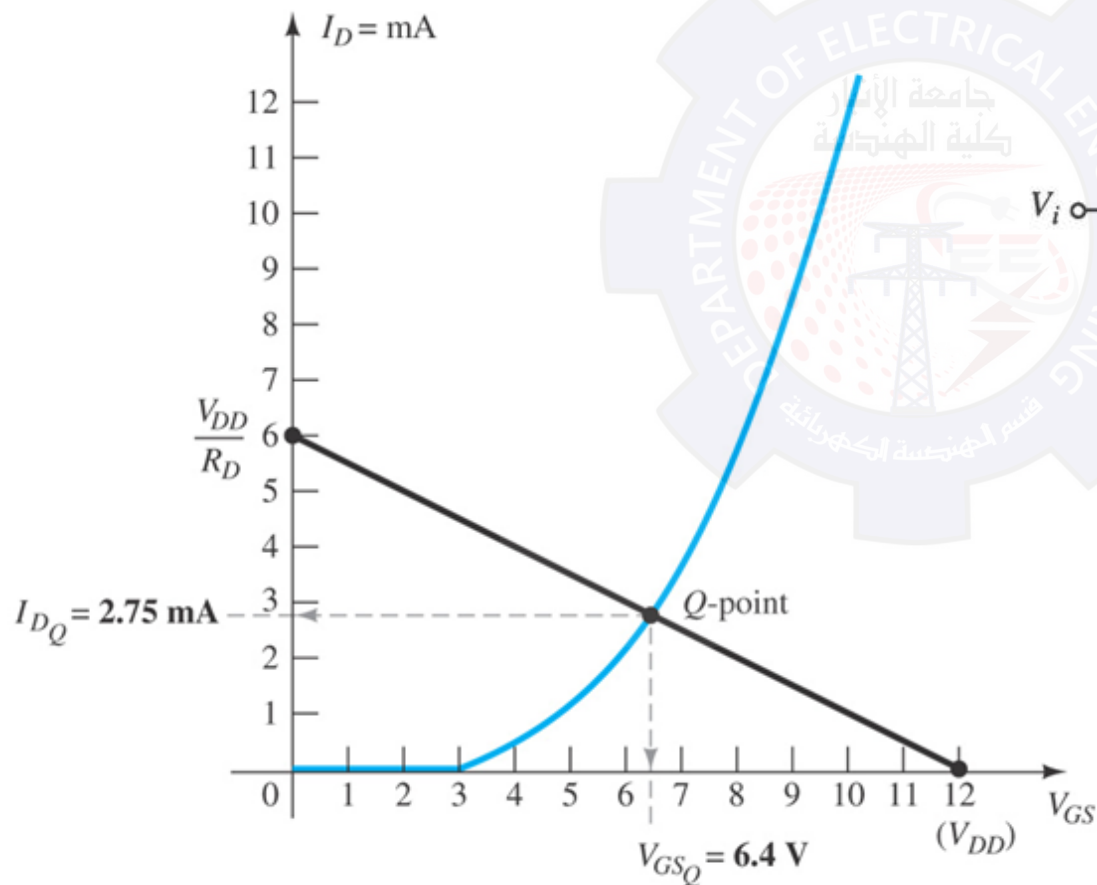Example 7.11 - solution

Plot the line : $V_{GS} = V_{DD} - I_D R_D$
 $V_{GS} = 12 - I_D(2k)$



$I_{D(on)} = 6$ mA
 $V_{GS(on)} = 8$ V
 $V_{GS(Th)} = 3$ V




Voltage-Divider Biasing

Plot the line and the transfer curve to find the Q-point. Use these equations:

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

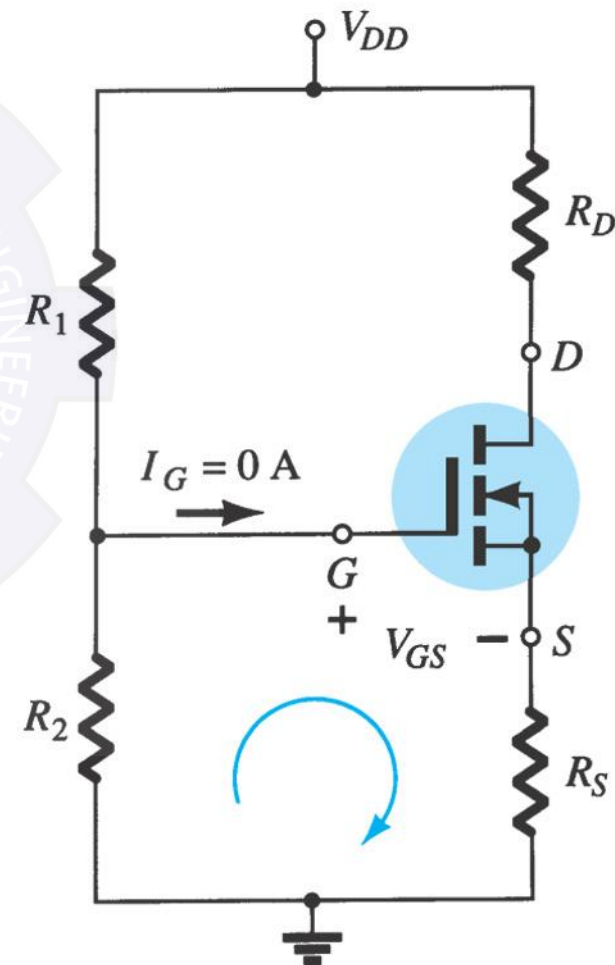



Example 7.12 Find V_{GSQ} , I_{DQ}

$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(Th)})^2}$$

$$k = \frac{3mA}{(10-5)^2} = 0.12 \times 10^{-3}$$


$$I_D = k (V_{GS} - V_{GS(Th)})^2$$

$$I_D = 0.12 \times 10^{-3} (V_{GS} - 5)^2$$

$$V_G = \frac{18M(40V)}{22M + 18M} = 18V$$


$$V_{GS} = V_G - I_D R_S$$

$$V_{GS} = 18V - I_D (0.82k)$$

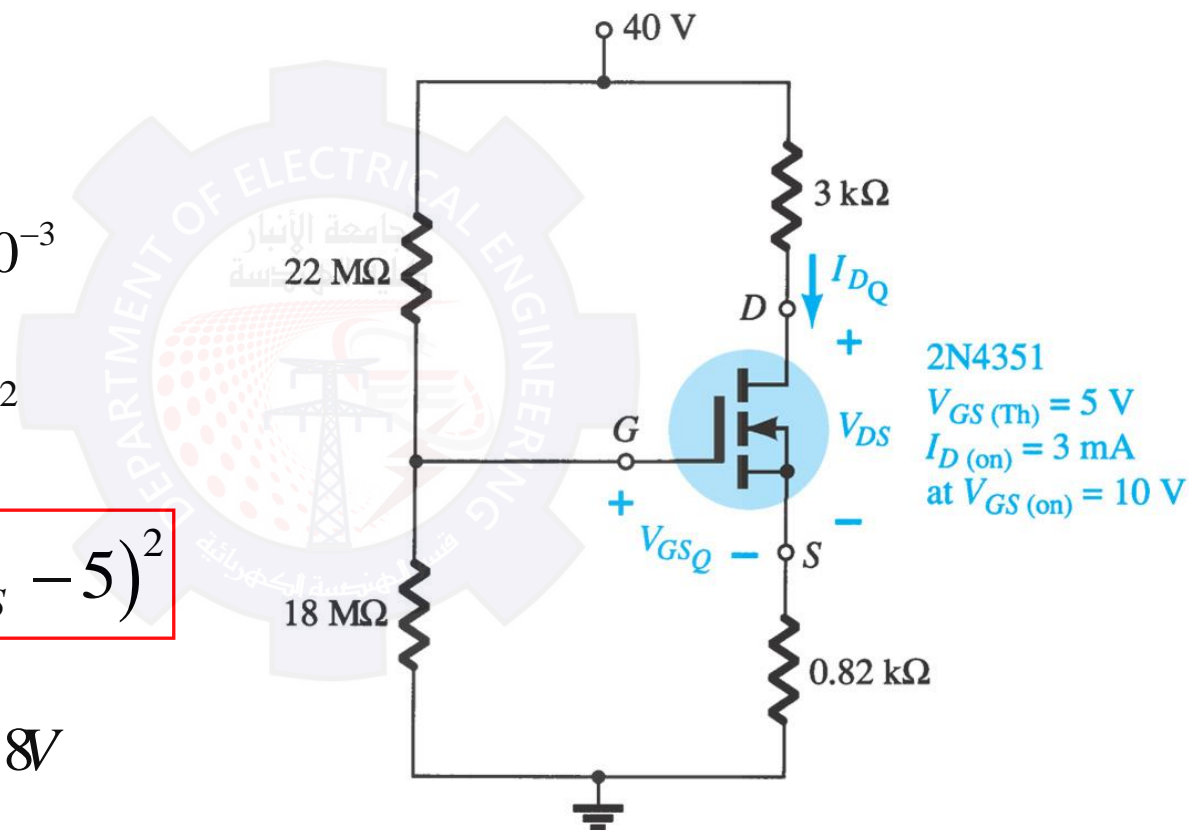



Example 7.12 - Solution

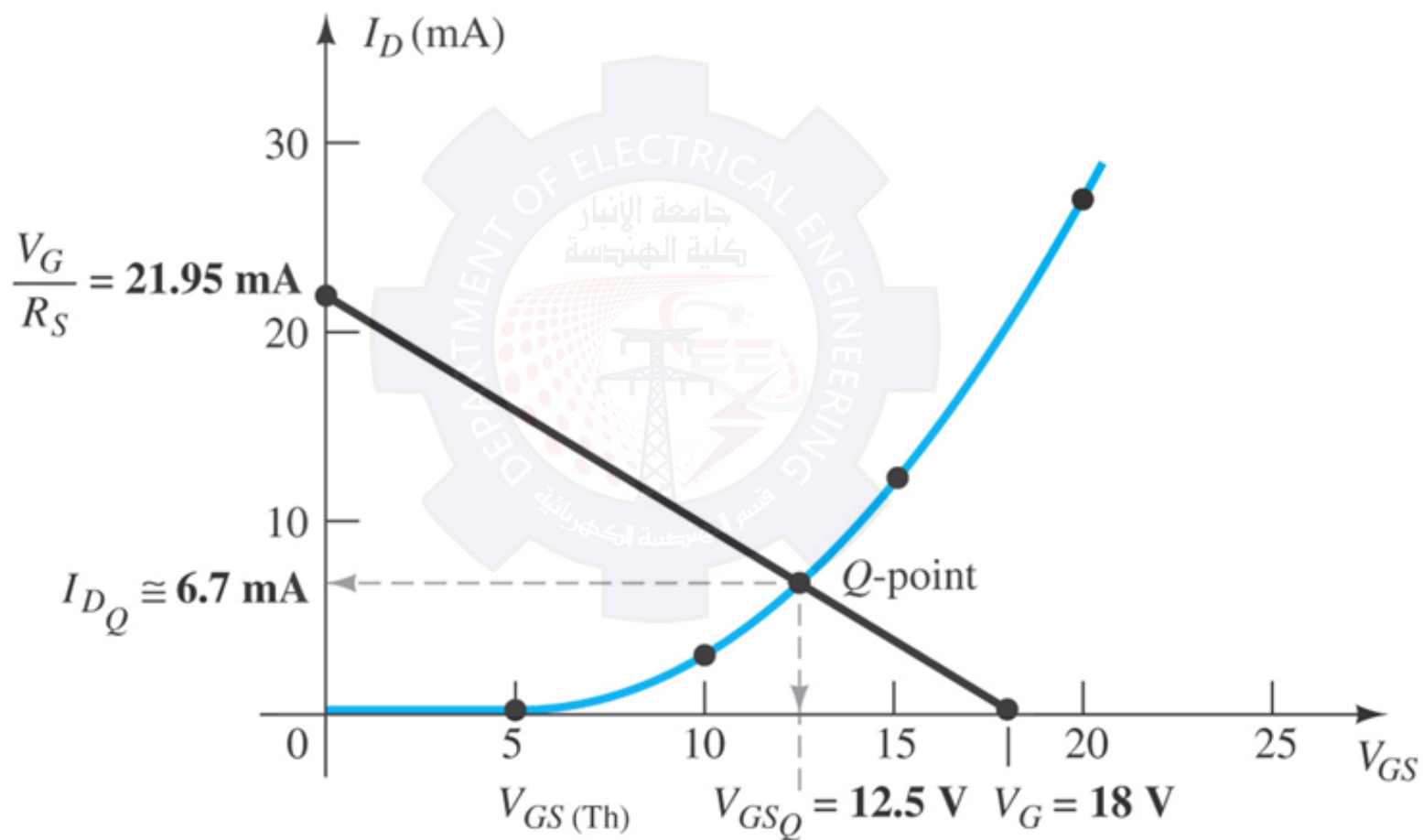

$$I_D = 0.12 \times 10^{-3} (V_{GS} - 5)^2$$

$$V_{GS} = 18V - I_D (0.82k)$$