



Fundumantal of Electronic II

Second Class

Chapter08: FET Amplifier

Lec08_p1


Munther N. Thiyab

2019-2020

Introduction

FETs provide:

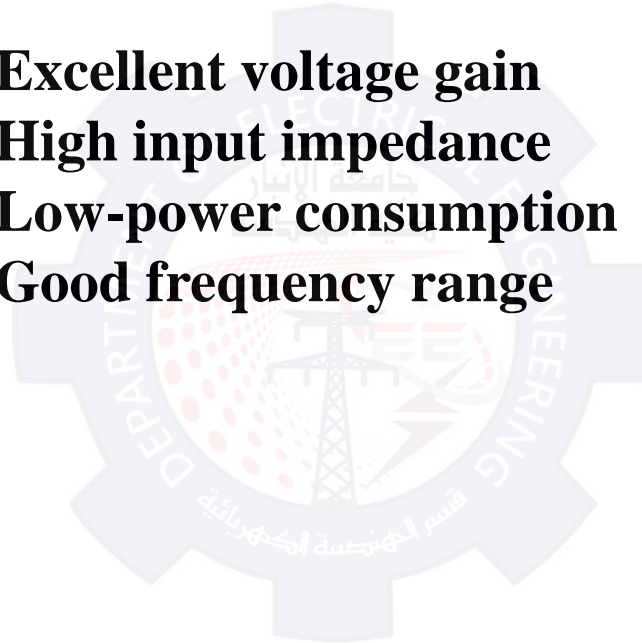- **Excellent voltage gain**
- **High input impedance**
- **Low-power consumption**
- **Good frequency range**



FET Small-Signal Model


Transconductance

The relationship of a change in I_D to the corresponding change in V_{GS} is called **transconductance**

Transconductance is denoted g_m and given by:

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

Graphical Determination of g_m

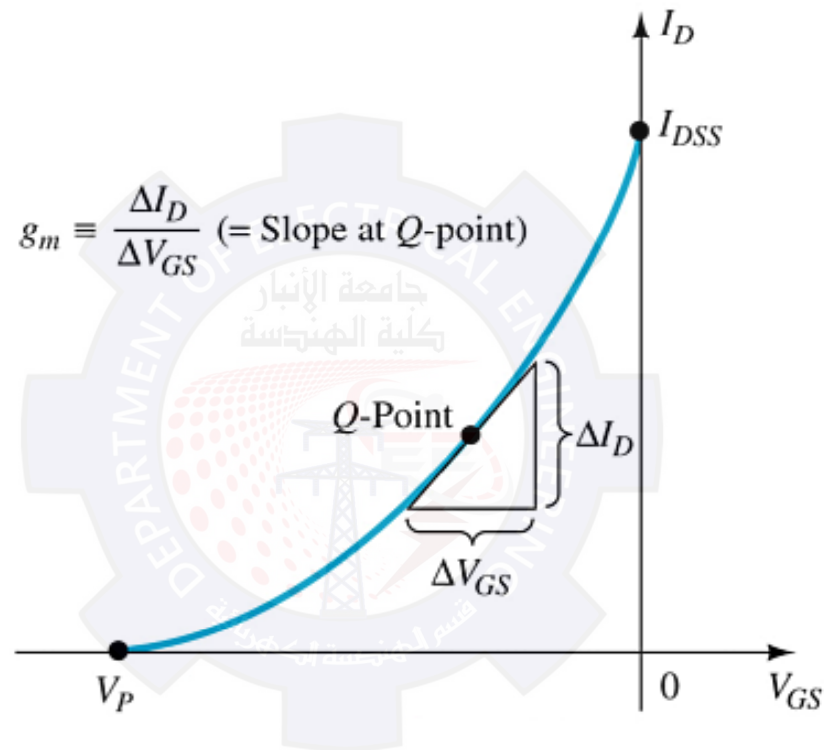

Mathematical Definitions of g_m

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$

Where $V_{GS} = 0V$

$$g_{m0} = \frac{2I_{DSS}}{|V_P|}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right]$$

Where $1 - \frac{V_{GS}}{V_P} = \sqrt{\frac{I_D}{I_{DSS}}}$

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_P} \right) = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$

FET Impedance

Input impedance:

$$Z_i = \infty \Omega$$


Output Impedance:

$$Z_o = r_d = \frac{1}{y_{os}}$$


where:

$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS} = \text{constant}}$$

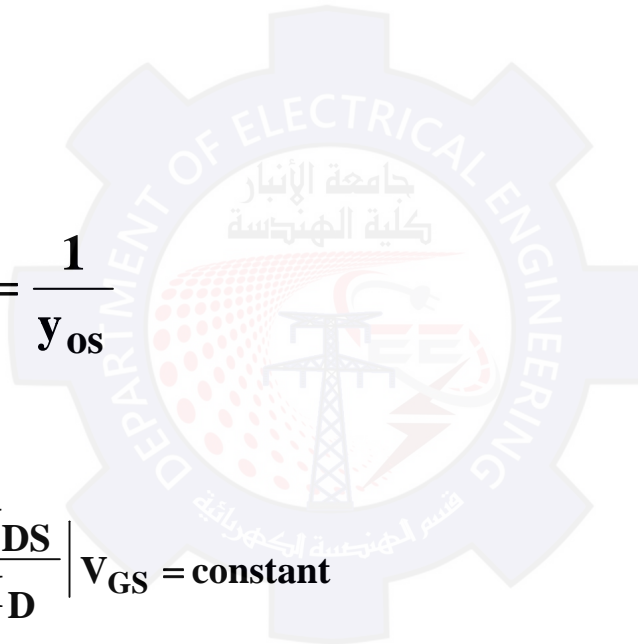y_{os} = admittance parameter listed on FET specification sheets.




FET AC Equivalent Circuit

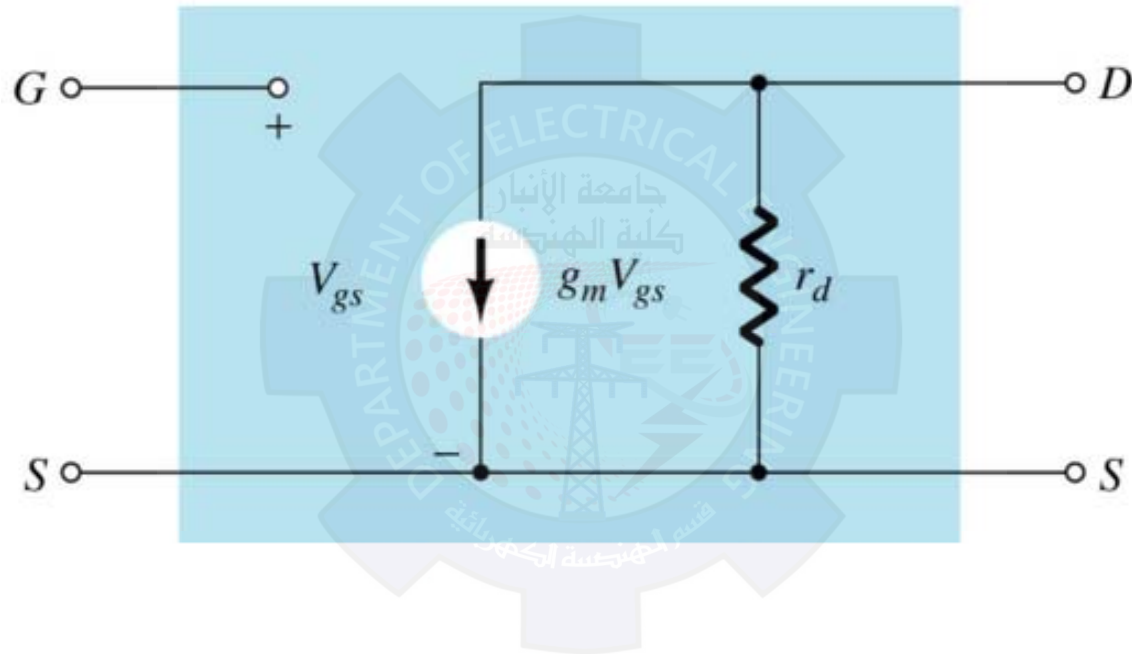


Summary Table


Fixed-bias
[JFET or D-MOSFET]

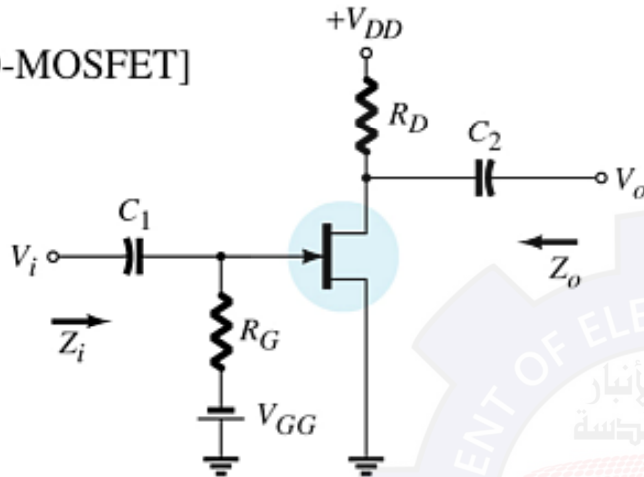

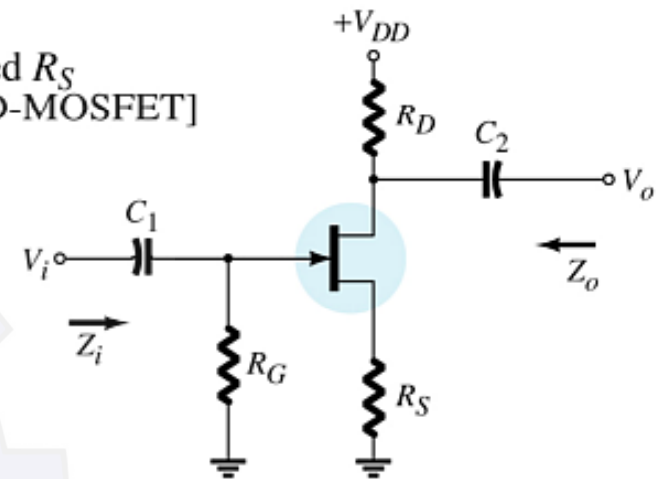
Self-bias
Unbypassed R_S
[JFET or D-MOSFET]



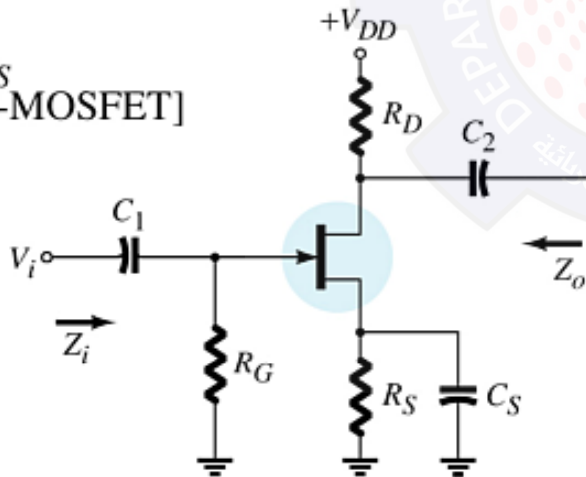Self-bias
bypassed R_S
[JFET or D-MOSFET]



Voltage-divider bias
[JFET or D-MOSFET]

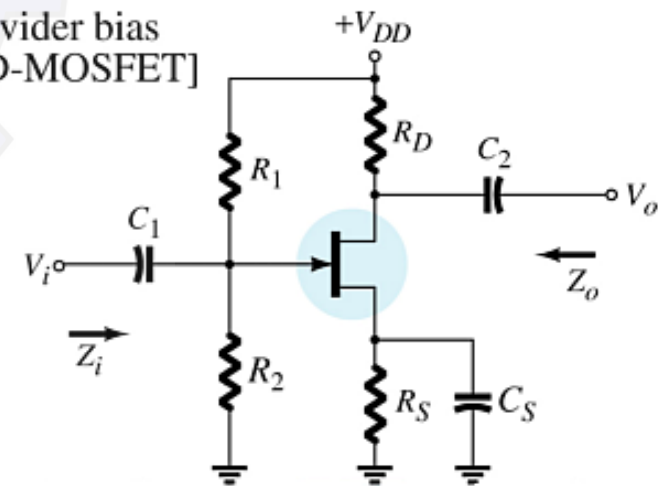


Troubleshooting

Check the DC bias voltages:

If not correct check power supply, resistors, FET. Also check to ensure that the coupling capacitor between amplifier stages is OK.

Check the AC voltages:

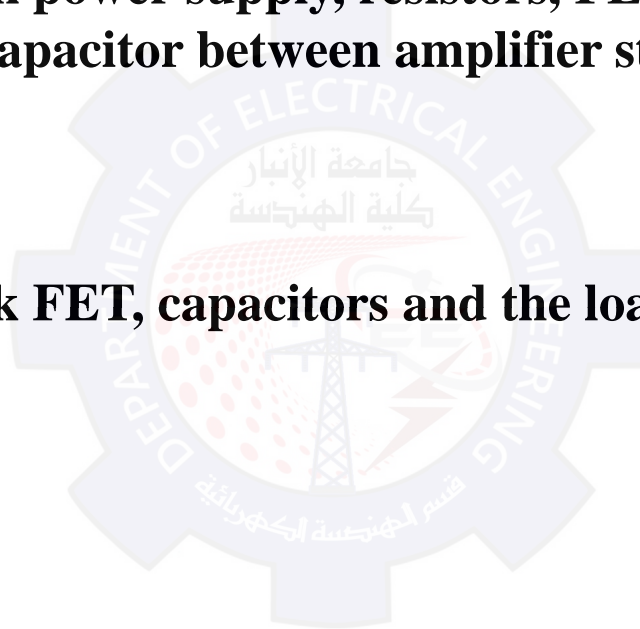If not correct check FET, capacitors and the loading effect of the next stage



Practical Applications

Three-Channel Audio Mixer
Silent Switching
Phase Shift Networks
Motion Detection System

