



Fundumantal of Electronic II

Second Class

Chapter08: FET Amplifier

Lec08_p2



Munther N. Thiyab

2019-2020

Common-Source (CS) Fixed-Bias Circuit

The input is on the gate and the output is on the drain

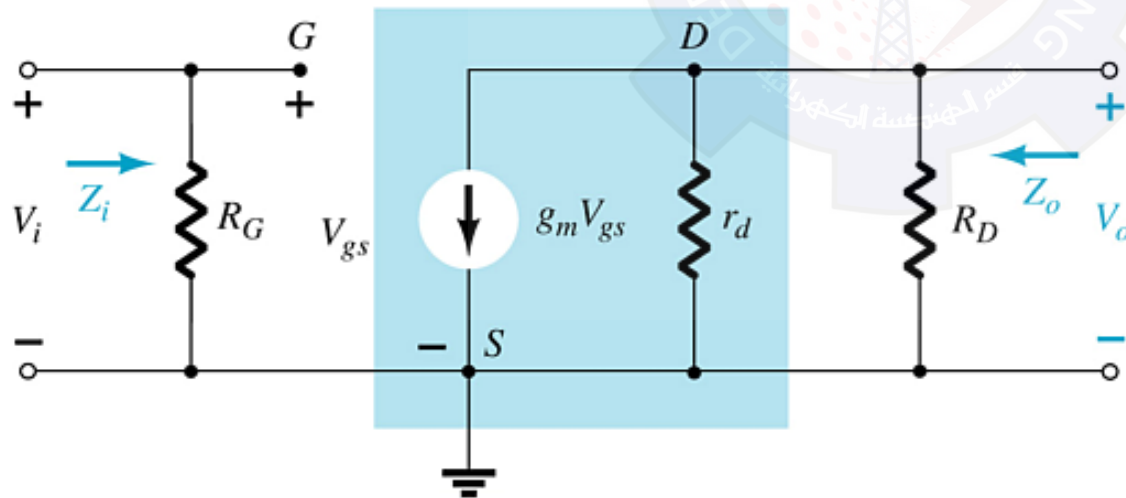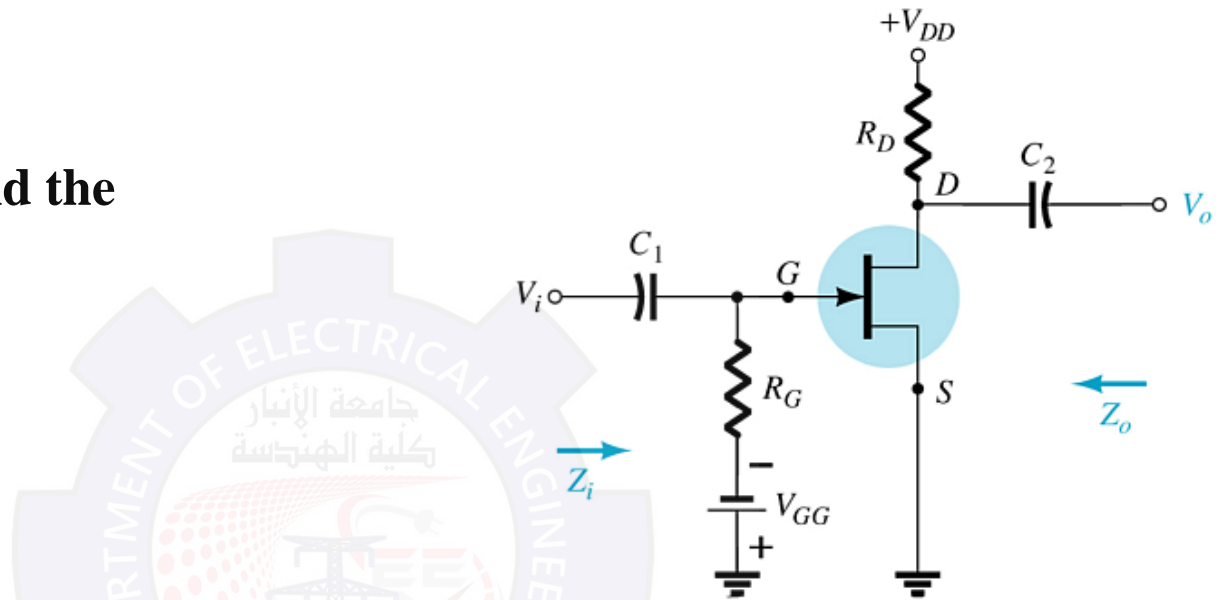There is a 180° phase shift between input and output



Calculations

Input impedance:

$$Z_i = R_G$$

Output impedance:


$$Z_o = R_D \parallel r_d$$

$$Z_o \cong R_D \quad \left| \quad r_d \geq 10R_D \right.$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$


$$A_v = \frac{V_o}{V_i} = -g_m R_D \quad \left| \quad r_d \geq 10R_D \right.$$

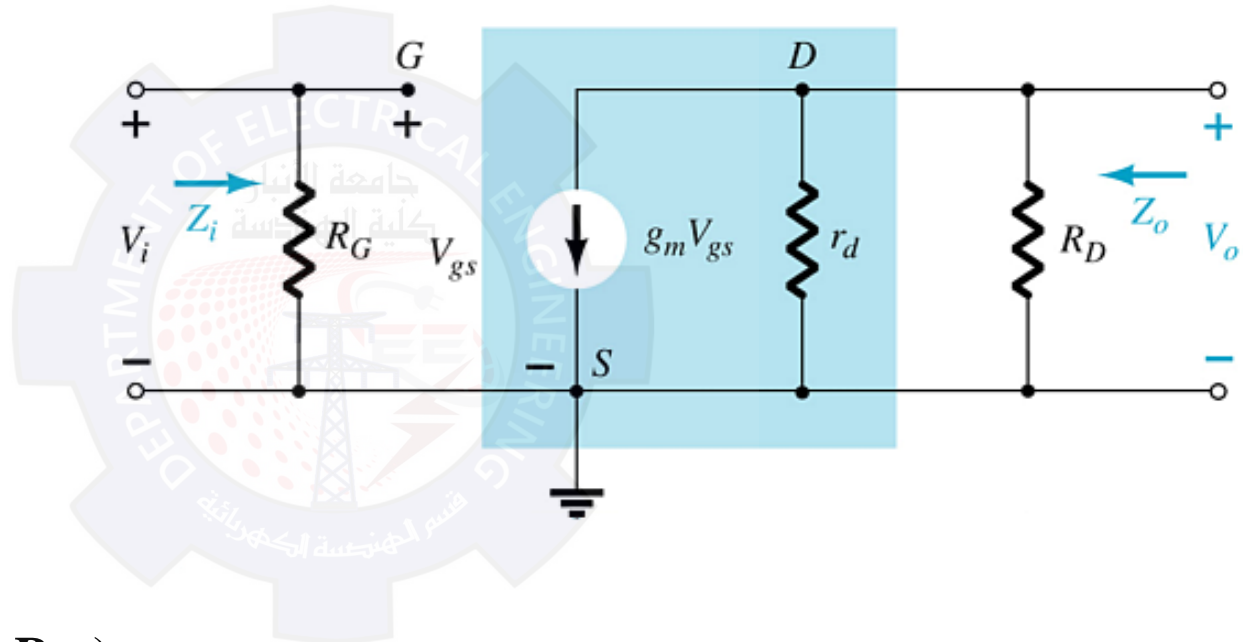

Common-Source (CS) Self-Bias Circuit

This is a common-source amplifier configuration, so the input is on the gate and the output is on the drain

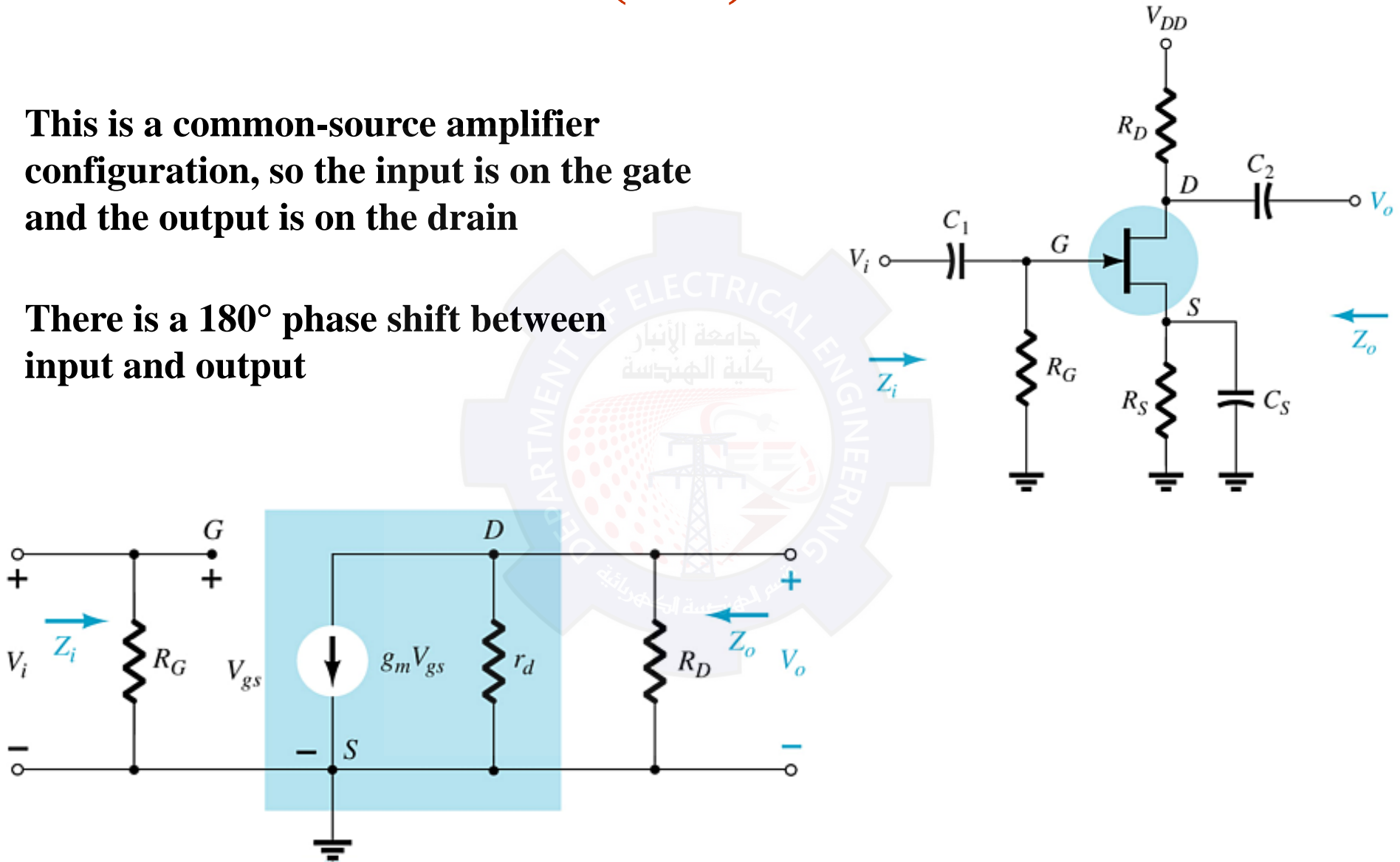There is a 180° phase shift between input and output



Calculations

Input impedance:

$$Z_i = R_G$$

Output impedance:


$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \quad \left| \quad r_d \geq 10R_D \right.$$

Voltage gain:


$$A_v = -g_m (r_d \parallel R_D)$$

$$A_v = -g_m R_D \quad \left| \quad r_d \geq 10R_D \right.$$

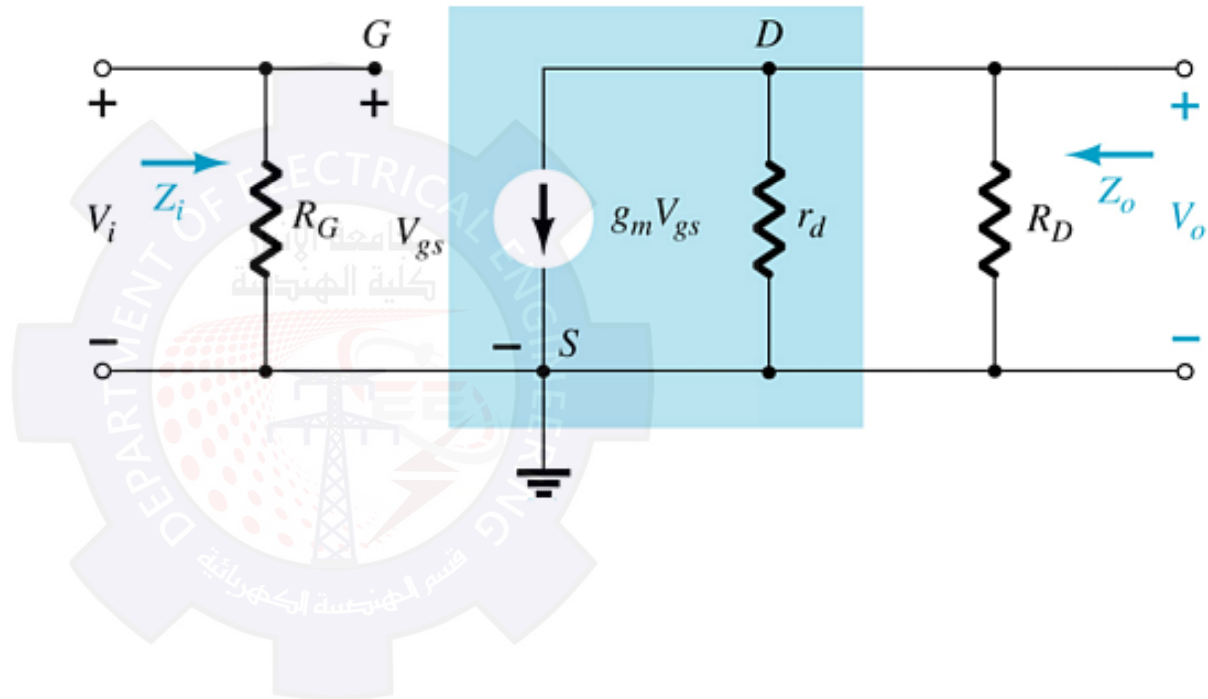

Common-Source (CS) Self-Bias Circuit

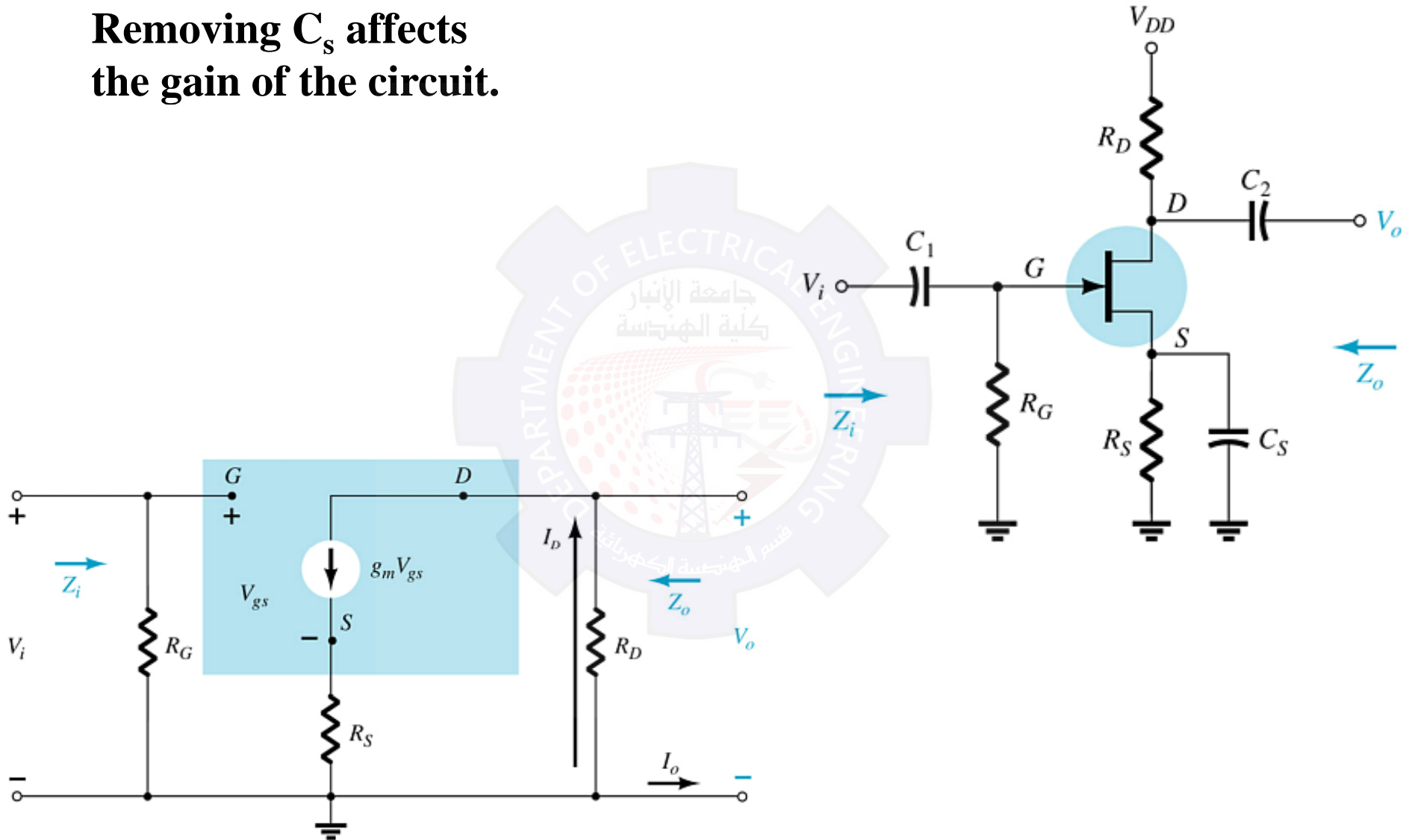Removing C_s affects the gain of the circuit.



Calculations

Input impedance:

$$Z_i = R_G$$


Output impedance:

$$Z_o \cong R_D \quad \left| \quad r_d \geq 10R_D \right.$$

Voltage gain:


$$A_v = \frac{V_o}{V_i} = - \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

$$A_v = \frac{V_o}{V_i} = - \frac{g_m R_D}{1 + g_m R_S} \quad \left| \quad r_d \geq 10(R_D + R_S) \right.$$

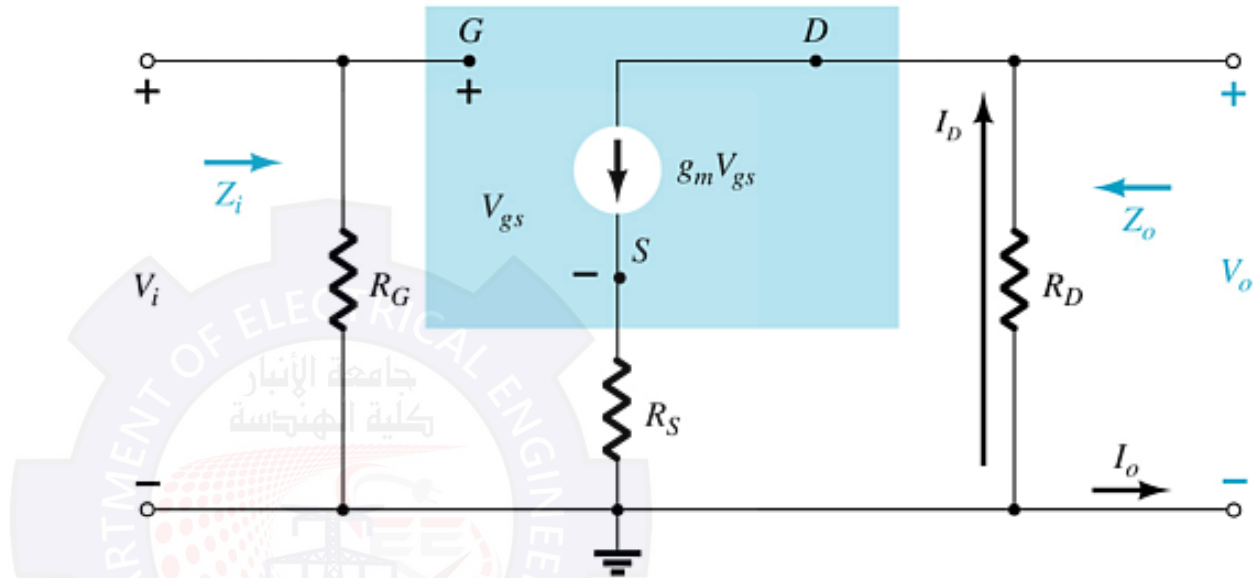

Common-Source (CS) Voltage-Divider Bias

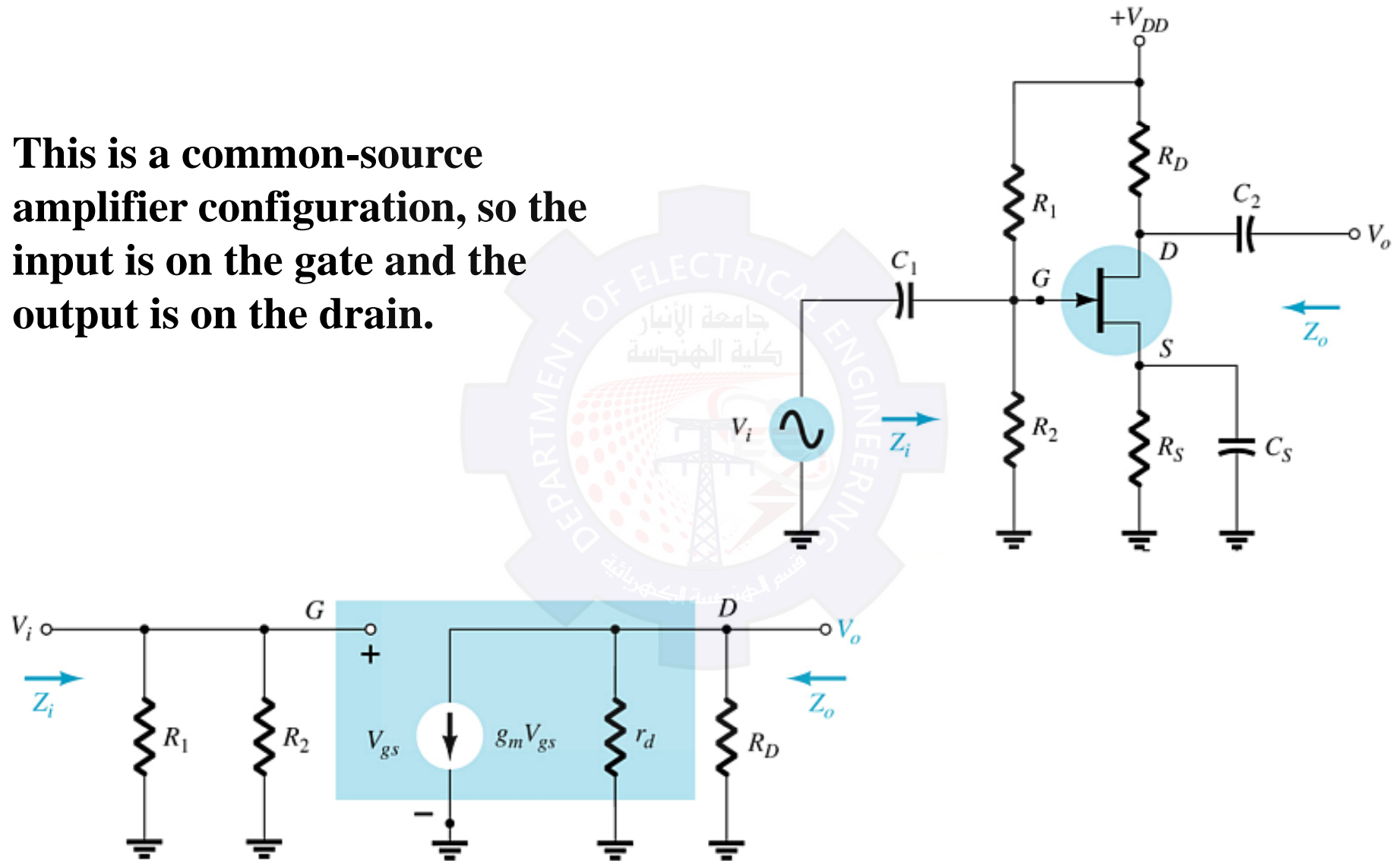This is a common-source amplifier configuration, so the input is on the gate and the output is on the drain.



Impedances

Input impedance:

$$Z_i = R_1 \parallel R_2$$

Output impedance:


$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \quad \left| \quad r_d \geq 10R_D$$

Voltage gain:

$$A_v = -g_m (r_d \parallel R_D)$$



$$A_v = -g_m R_D \quad \left| \quad r_d \geq 10R_D$$

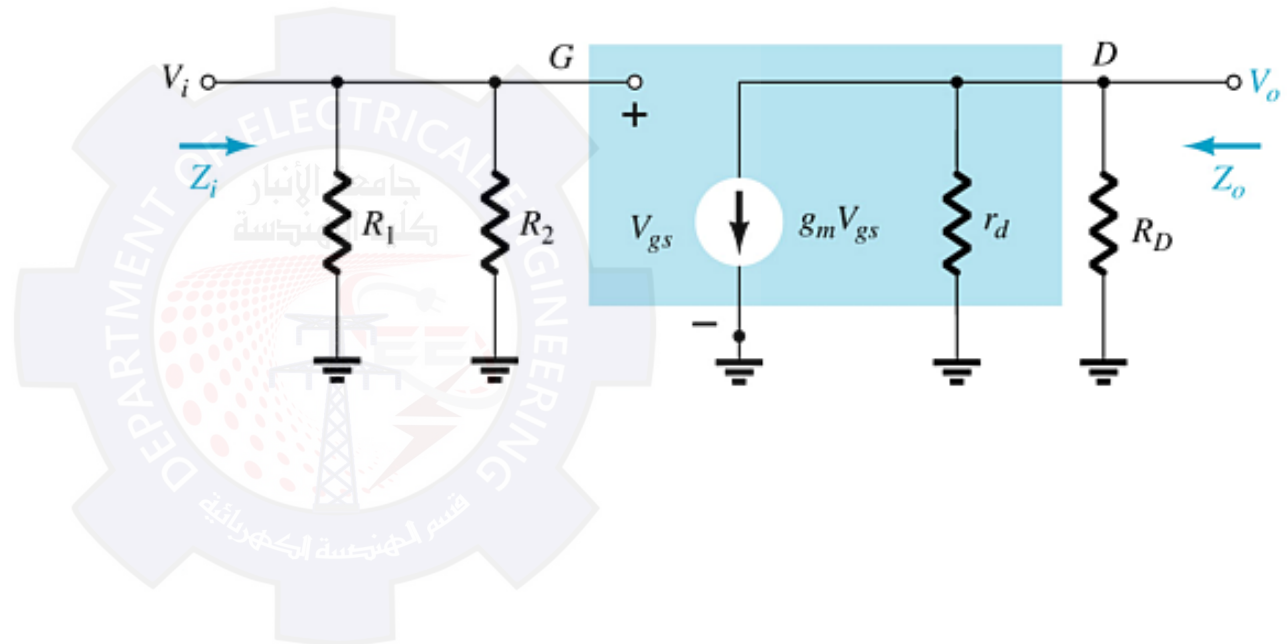

Source Follower (Common-Drain) Circuit

In a common-drain amplifier configuration, the input is on the gate, but the output is from the source.

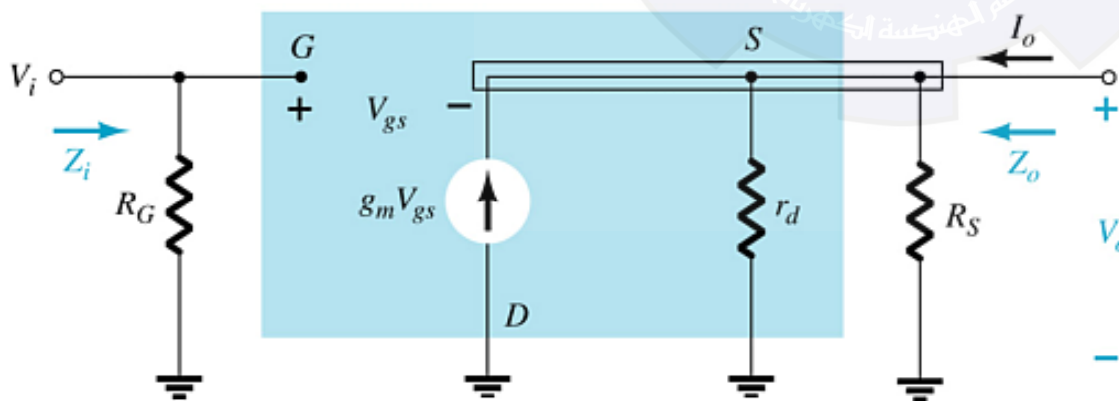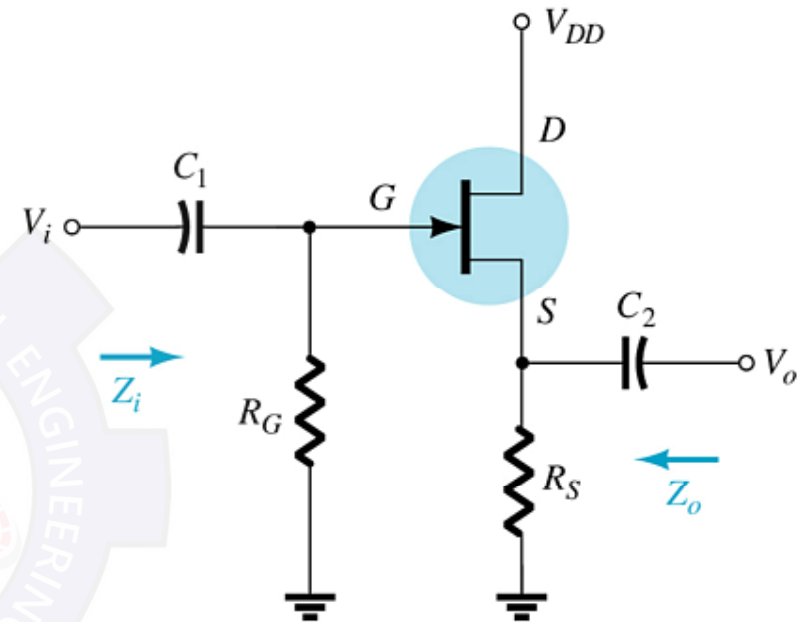There is no phase shift between input and output.



Impedances

Input impedance:

$$Z_i = R_G$$

Output impedance:


$$Z_o = r_d \parallel R_S \parallel \frac{1}{g_m}$$

$$Z_o \cong R_S \parallel \frac{1}{g_m} \Big|_{r_d \geq 10R_S}$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = \frac{g_m (r_d \parallel R_S)}{1 + g_m (r_d \parallel R_S)}$$


$$A_v = \frac{V_o}{V_i} = \frac{g_m R_S}{1 + g_m R_S} \Big|_{r_d \geq 10}$$

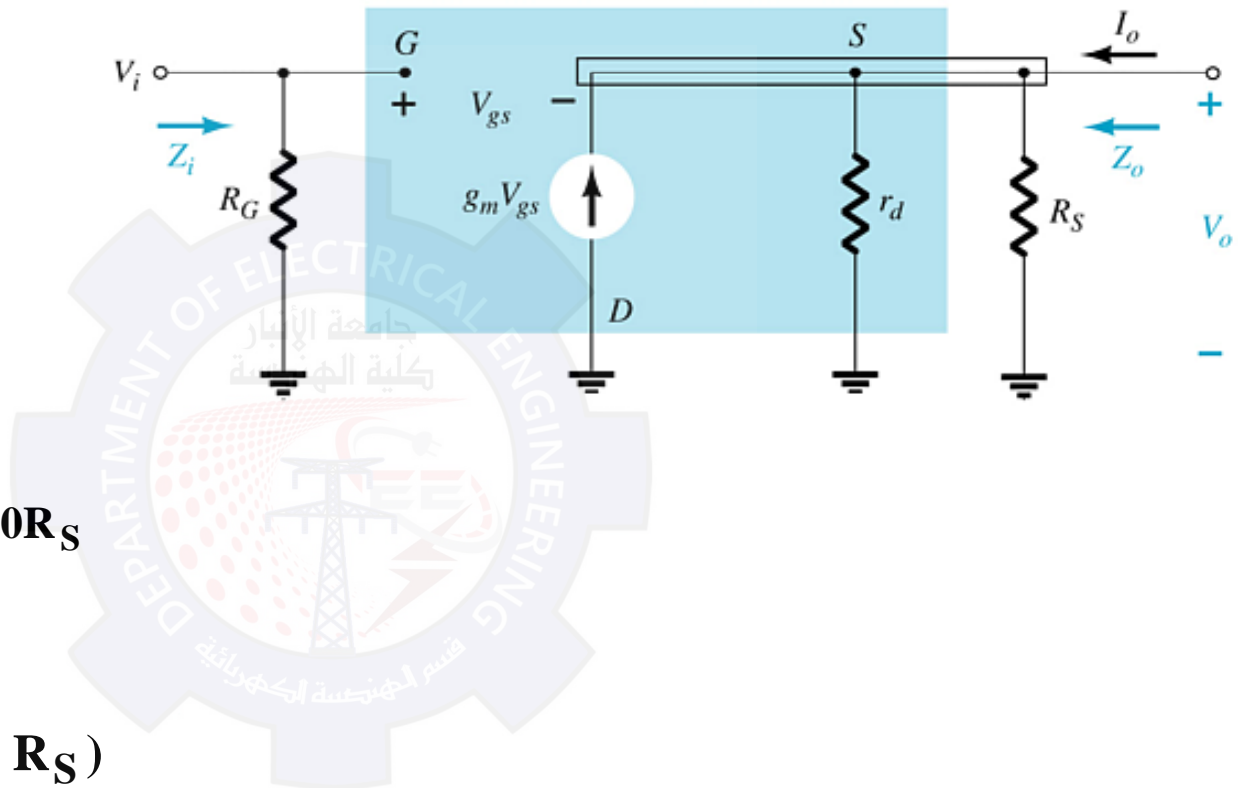

Common-Gate (CG) Circuit

The input is on the source and the output is on the drain.

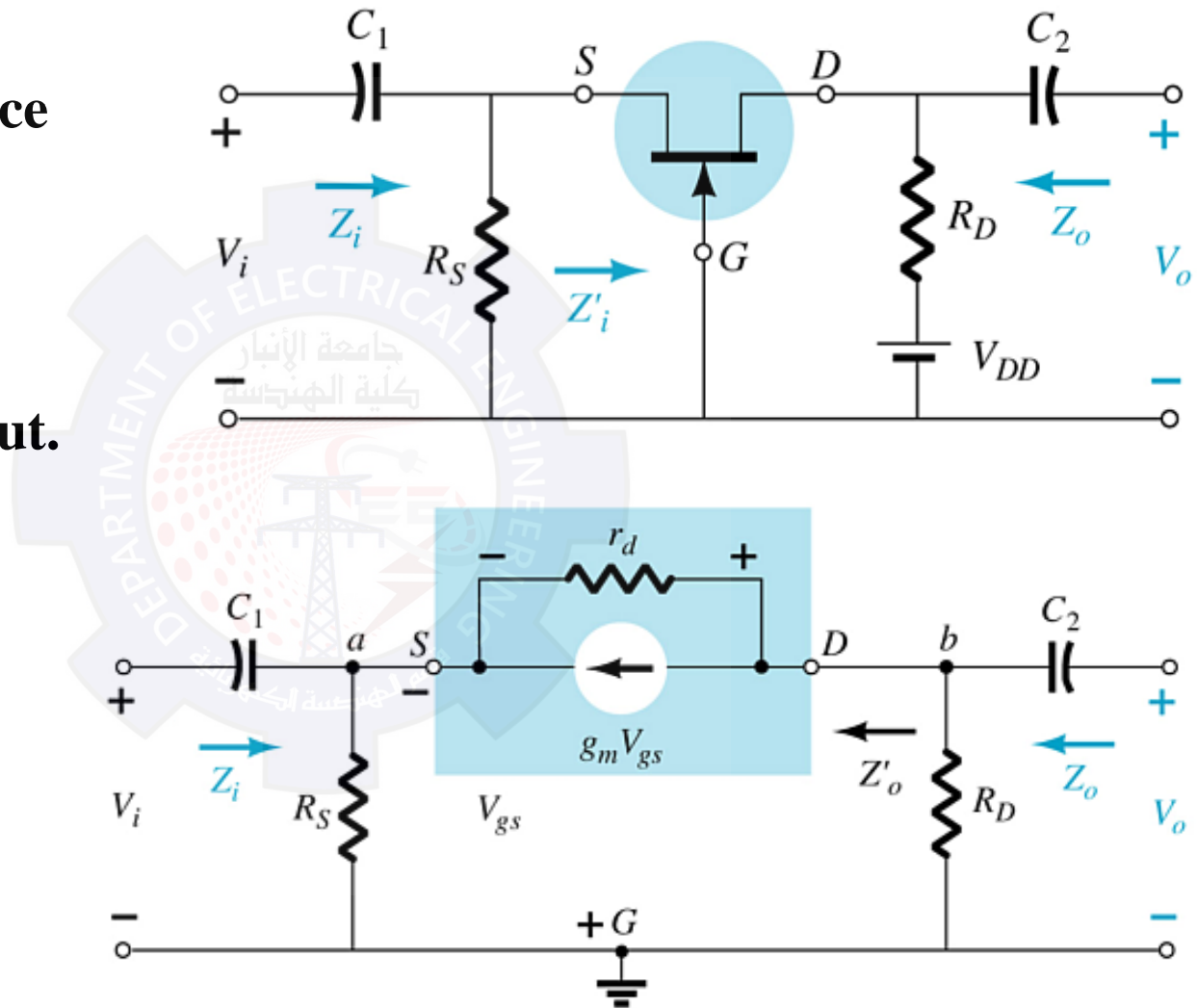There is no phase shift between input and output.



Calculations

Input impedance:

$$Z_i = R_S \parallel \left[\frac{r_d + R_D}{1 + g_m r_d} \right]$$

$$Z_i \cong R_S \parallel \frac{1}{g_m} \Big|_{r_d \geq 10R_D}$$

Output impedance:

$$Z_o = R_D \parallel r_d$$

$$Z_o \cong R_D \Big|_{r_d \geq 10R_D}$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = \frac{\left[g_m R_D + \frac{R_D}{r_d} \right]}{\left[1 + \frac{R_D}{r_d} \right]} \quad A_v = g_m R_D \Big|_{r_d \geq 10R_D}$$

