

Experiment #1- Part#3

Characteristics of Bipolar Junction

Procedure

1. Connect the common emitter test circuit shown in Fig.12. Try to identify the leads of the BC337 transistor correctly. It is built in a M90 package as depicted in Fig.12.
2. Set $V_{CE} = 0V$, and increase the base current I_B in several steps from 0 to $100\mu A$ by varying the DC supply voltage V_{BB} , and record V_{BE} in each step as shown in Table-1.
3. Reduce V_{BB} to 0V and set $V_{CE} = 5V$ by adjusting the DC power supply V_{CC} . Increase I_B from 0 to $100\mu A$ (by slowly increasing V_{BB}) in several steps and record V_{BE} . V_{CE} should be kept constant at 5V in each step by adjusting V_{CC} .

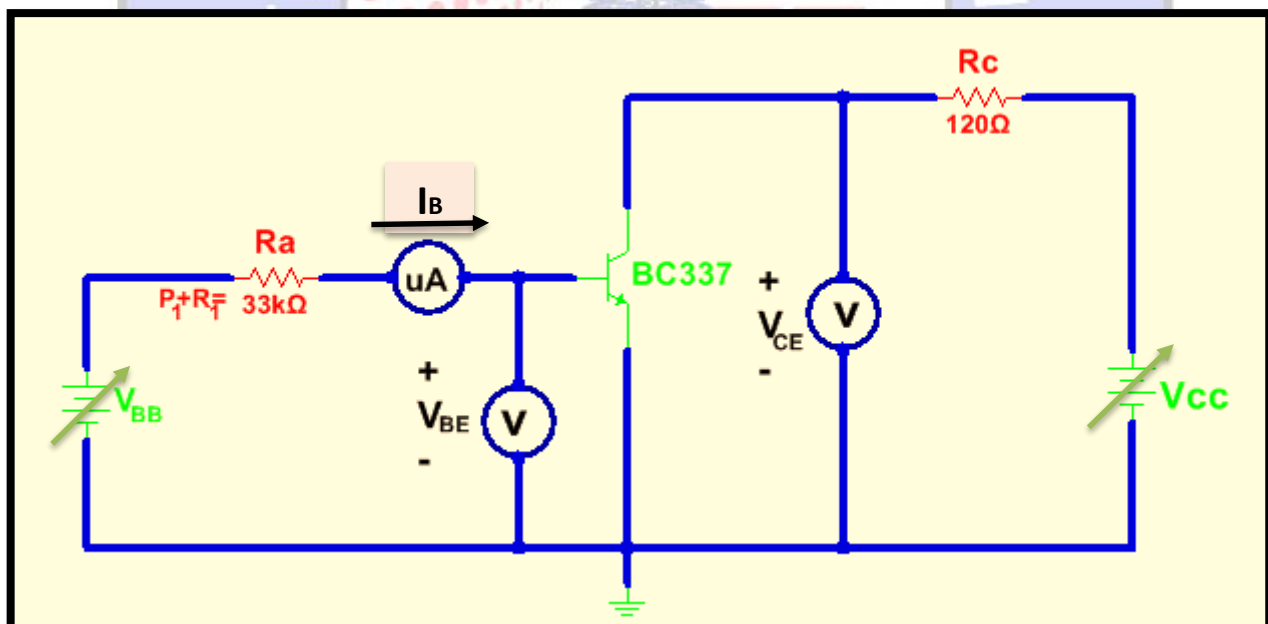


Figure 12: Transistor Test Circuit Used to obtain the Input Characteristics



$V_{CE} = 0V$		$V_{CE} = 5V$	
$I_B (\mu A)$	$V_{BE}(V)$	$I_B (\mu A)$	$V_{BE}(V)$
0		0	
10		10	
20		20	
30		30	
40		40	
50		50	
60		60	
70		70	
80		80	
90		90	
100		100	

Table-1: Recorded Data for the Transistor Input Characteristics

4. Connect the circuit shown in Fig.13 to obtain the output characteristics of the transistor.

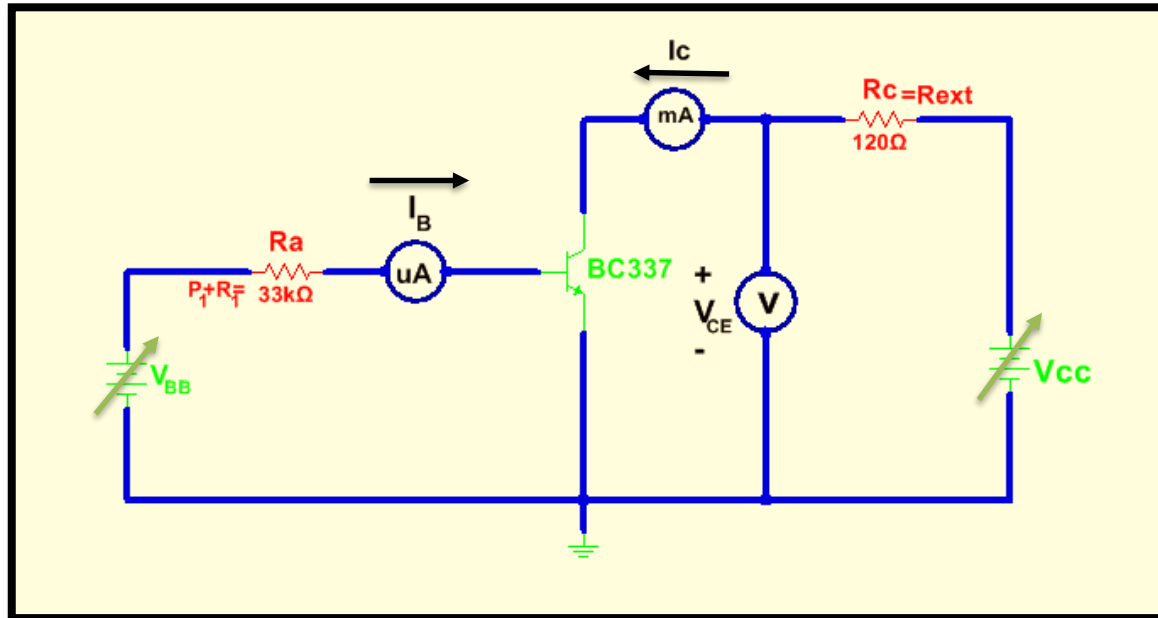


Figure 13: Transistor Test Circuit Used to obtain the Output Characteristics

5. Start with both power supplies set to 0V. Slowly increase V_{BB} until $I_B = 20\mu A$. Now slowly increase V_{CC} in several steps and record V_{CE} and I_C in each step as shown in Table-2.



6. Repeat step 5 for base current values of $40\mu\text{A}$, and $60\mu\text{A}$ respectively. Record data as illustrated in Table-2.

Table-2: Recorded Data for the Transistor Output Characteristics

$I_B(\mu\text{A}) = 20$		$I_B(\mu\text{A}) = 40$		$I_B(\mu\text{A}) = 60$	
$V_{CE}(\text{V})$	$I_C(\text{mA})$	$V_{CE}(\text{V})$	$I_C(\text{mA})$	$V_{CE}(\text{V})$	$I_C(\text{mA})$
0		0		0	
0.1		0.1		0.1	
0.2		0.2		0.2	
0.4		0.4		0.4	
0.6		0.6		0.6	
0.8		0.8		0.8	
1		1		1	
3		3		3	
5		5		5	
8		8		8	
10		10		10	

Discussion

1. From the obtained data in Table-1, plot the input characteristic curves of the transistor.
2. Sketch the three output characteristic curves of the transistor from the results obtained in Table-2.
3. Find the *h-parameters* of the transistor at $I_B = 40\mu\text{A}$ and $V_{CE} = 5\text{V}$ from the plotted input and output characteristics.
4. Use the plotted characteristic curves to determine the DC current gain β_{dc} for the transistor at $V_{CE} = 3.0\text{V}$ and base current of $20\mu\text{A}$, $40\mu\text{A}$, and $60\mu\text{A}$.



respectively. Repeat for $V_{CE} = 5.0V$. Tabulate your results as illustrated in Table-3 below.

- Does the experimental data indicate that β_{dc} is constant at all points? Does this have any effect on the linearity of the transistor? What effect would a higher β_{dc} have on the characteristic curves you measured?
- What is the maximum power dissipated in the transistor for the data taken in the experiment?
- Show that the DC alpha of the transistor is given by: 1+

$$\alpha_{dc} = \frac{\beta_{dc}}{\beta_{dc} + 1}$$

Compute α_{dc} for your transistor at $V_{CE} = 5.0V$ and $I_B = 40\mu A$.

- What value of V_{CE} would you expect if the base terminal of the transistor is opened? Explain your answer.

