

## Experiment #6- Part#2

### The FET Common Source Amplifier

#### Procedure

1. Connect the test circuit shown in Fig.4 to measure  $I_{DSS}$ . Increase the supply voltage until  $I_D$  no longer increases. This level of drain current is recorded as  $I_{DSS}$ .

 


Figure 4: Test Circuit for Measuring  $I_{DSS}$

2. Connect the test circuit shown in Fig.5 to measure  $V_P$ . The gate supply voltage  $V_{GG}$  is adjusted from 0 to larger negative values until the drain current  $I_D$  just reaches 0. The voltage  $V_{GS}$  to just cause the drain current to reach 0 is the measured value of  $V_P$ . Tabulate your results as shown in Table-1.

 


Figure 5: Test Circuit for Measuring  $V_P$

**Table-1: Measured JFET Parameters**

Device Parameter	Value
$I_{DSS}$	
$V_P$	

3. Connect the JFET self-bias circuit shown in Fig.6 and measure the DC voltages  $V_G$ ,  $V_S$ , and  $V_D$  with the aid of a digital multi-meter. Determine  $V_{GSQ}$ ,  $I_{DQ}$ ,  $V_{DSQ}$ , and  $g_m$  at the Q-point. Tabulate your results as illustrated in Table-2.

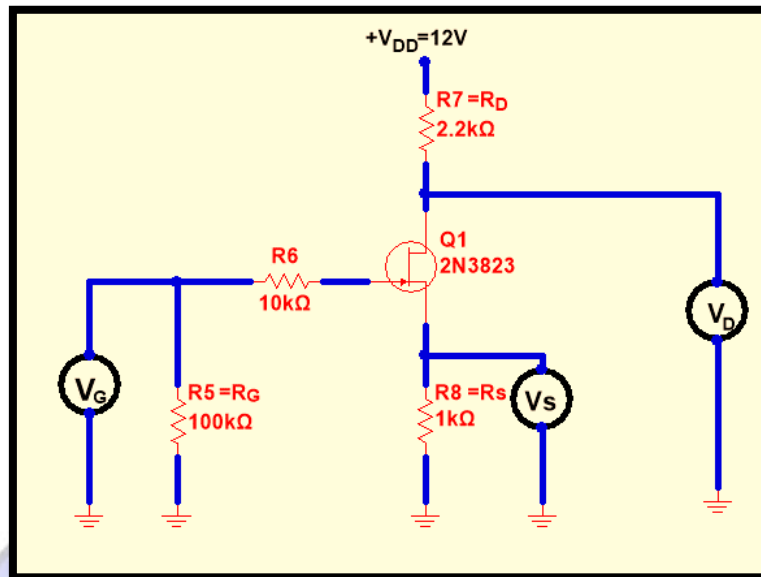


Figure 6: The Practical Bias Circuit of the Amplifier

4. Connect the amplifier circuit shown in Fig.7. Sketch the input ( $V_s$ ) and output ( $V_D$ ) signals and determine the voltage gain of the circuit in three cases as illustrated in Table-3.

Table-2: Measured Bias Circuit Parameters

Quantity	Value
$V_G$	
$V_S$	
$V_D$	
$V_{GS}$	
$I_D$	
$V_{DS}$	
$g_m$	

Table-3: Measured Voltage Gain Conditions

$V_{in}$	$V_{out}$	Voltage Gain ( $v_{out}/v_{in}$ )
<b>0.1V<sub>PP</sub></b>		
<b>0.15V<sub>PP</sub></b>		
<b>0.2V<sub>PP</sub></b>		

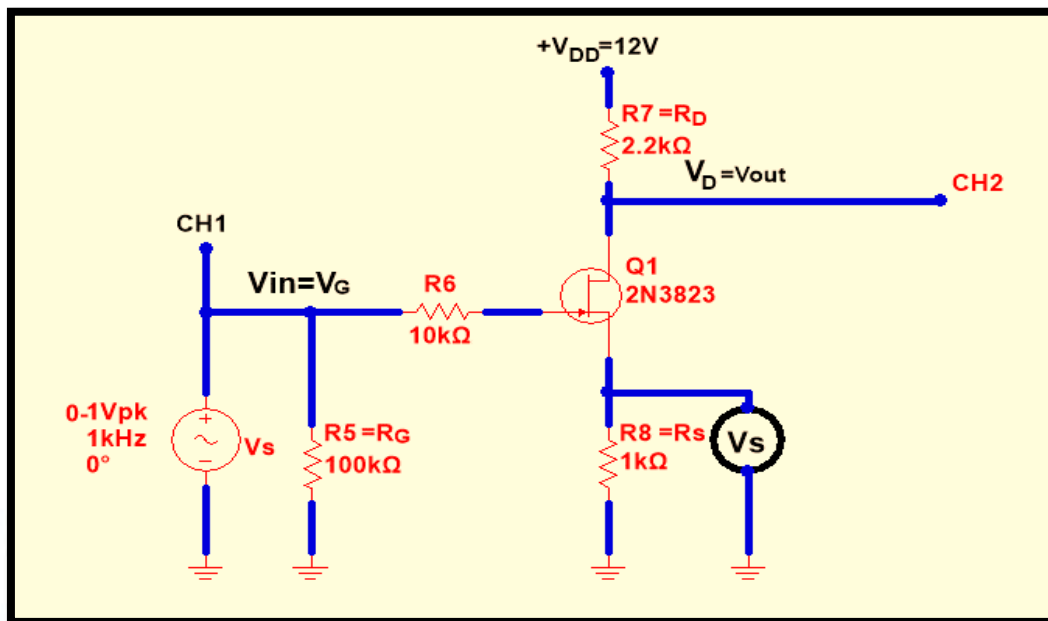


Figure 7: The Practical Common-Source Amplifier Circuit

## Discussion

1. Using the measured device parameters  $I_{DSS}$  and  $V_P$ , calculate the theoretical Q-point values of  $I_{DQ}$  and  $V_{GSQ}$  and compare them with the measured quantities.
2. Indicate graphically the effect of increasing the source resistor  $R_S$  on the Q-point of the JFET.
3. Determine the DC power dissipation in the JFET connected in the amplifier circuit of Fig.7.
4. What is the effect of increasing the source resistance  $R_S$  on the voltage gain of the amplifier circuit?