



## Multiplexer Circuit

### OBJECTIVE


Understanding the operating principles and construction of multiplexers.

### Summary

Multiplexer, or MUX, is a logic circuit that select and route any number of inputs to a single output. One of the multiple inputs are selected by the selector gate and routed to the single output. The number of selector gates determine the capacity of a multiplexer. For example, if a certain MUX has only one selector gate, it is referred to as a "2 line-to-1 line MUX" because one selector can only select from two inputs.

A MUX with 3 selector gates is called "8 line-to-1 line MUX", since 3 selectors are capable of selecting an output from 8 inputs ( $2^3=8$ ). MUX is also referred to as "Data Selector" because it selects one output from among many inputs.

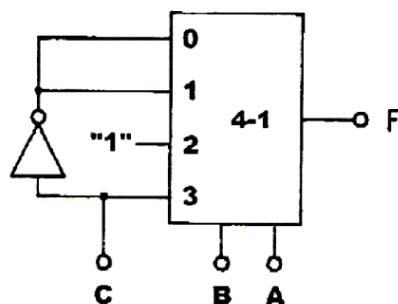Function expression, such as  $F(CBA)=\Sigma(0, 1, 2, 6, 7)$ , can be easily executed on MUX. The function "F" generates the sum of products (CB+CB) from states 0, 1, 2, 6, 7. Refer to the 4 line-to-1 line MUX below, the output is determined by states of selectors A, B and C. When CBA=000, 001, 010, 110, 111 the output F is 1. In all other states  $F=0$ .





**EQUIPMENTS REQUIRED**

KL-31001 Digital Logic Lab, Module KL-33006

**PROCEDURES**

(a) Constructing a 2-to-1 Multiplexer

1. Block e of module KL-33006 will be used as a 2-to-1 MUX.

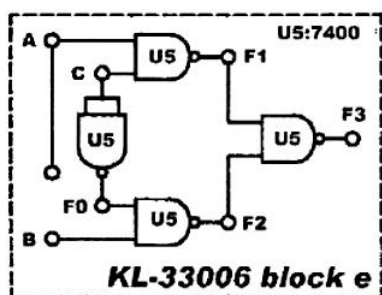


Fig. 2-71

2. Connect inputs A, B to Data Switches SW0, SW1; selector C to SW2. Connect output F3 to Logic Indicator L0.
3. Follow the input sequences in Table 2-34 and record states of F3. Which input (A or B) determines the output?

C	B	A	F3
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Table 2-34

(b) Using Multiplexers to Create Functions

1. Block f of module KL-33006 will be used in this section of the experiment to create functions.

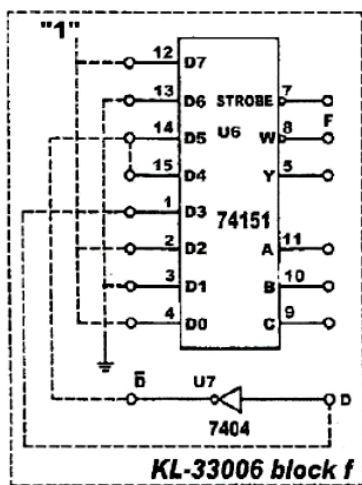


Fig. 2-72

2. Use U6 (74151) to create this function :

$$F(D, C, B, A) = \Sigma(0, 2, 4, 5, 7, 8, 10, 11, 15)$$

$\bar{D}$	0	1	2	3	4	5	6	7
D	8	9	10	11	12	13	14	15

Place connection leads according to Fig. 2-72 to complete the function shown above. Since D, C, B, A has 16 possible variations and the 74151 has only 8 variations, D will be used as the data input.

3. Connect inputs D, C, B, A to Data Switches SW3, SW2, SW1, SW0 respectively. Connect output Y to Logic Indicator L0. Follow the input sequences below and record output states.

D	C	B	A	Y
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	



(c) Constructing a 8 to 1 Multiplexer Circuit with TTL IC

- U6 (74151) on block f of module KL-33006 will be used in section of the experiment.

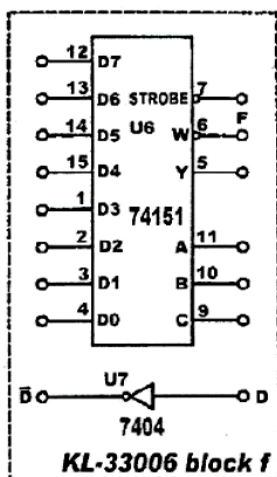


Fig. 2-73

- Refer to the data book for specifications of the 74151.

When CBA = "000", data at D0 is send to output F.

When CBA = "010", data at D2 is send to output F.

When CBA = "111", data at D7 is send to output F.

The IC will function properly only when STROBE = "0".

Y will remain "0" when STROBE = "1".

- Connect inputs D0~D7 to DIP Switch 1.0~1.7; inputs C, B, A to DATA Switches SW2, SW1, SW0. Follow the input sequences in Table 2-35, adjust D0~D7 and record output states. Determine on which input among D0~D7 does F depend on.

C	B	A	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Table 2-35



### **DISCUSSION:**

- 1- Use the 74151 to create this function shown below  $F(C,B,A)=\Sigma(1,3,5,6)$  ?
- 2- Use the 74151 to create this function shown below  
 $F(D,C,B,A)=\Sigma(1,2,5,6,7,10,12,13,15)$
- 3- Use 74150s and any other logic necessary to multiplex 32 data lines on to a single data-output line ?
- 4- Design 16x1 Mux using a suitable Mux ?
- 5- Design equation  $F(A,B,C,D)=\Sigma(0,1,4,5,7,10,11,15)$  using 4x1 Mux?
- 6- Design 4x1 Mux using Enable pin at low active?