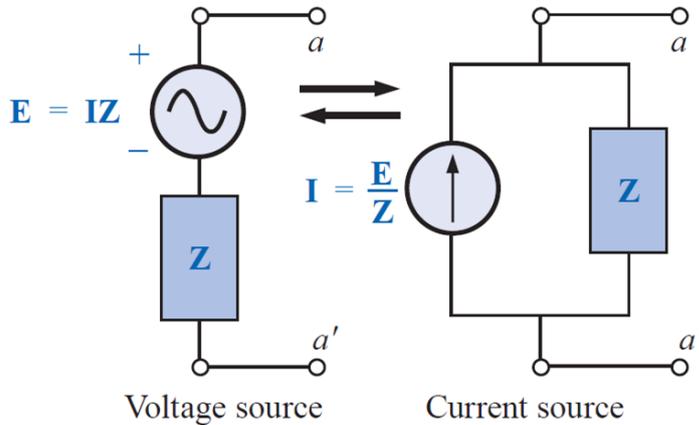


Methods of Analysis


SOURCE CONVERSIONS

When applying the methods to be discussed, it may be necessary to convert a current source to a voltage source, or a voltage source to a current source. This **source conversion** can be accomplished in much the same manner as for dc circuits, except now we shall be dealing with phasors and impedances instead of just real numbers and resistors.



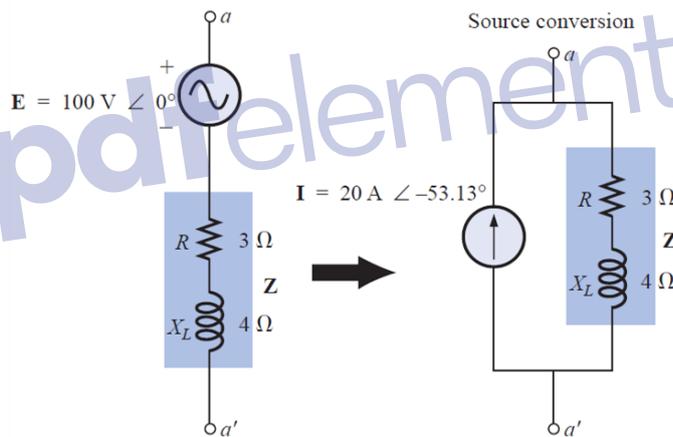Example:
 Convert the voltage source to a current source.


$$I = \frac{E}{Z} = \frac{100 \text{ V} \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 20 \text{ A} \angle -53.13^\circ$$



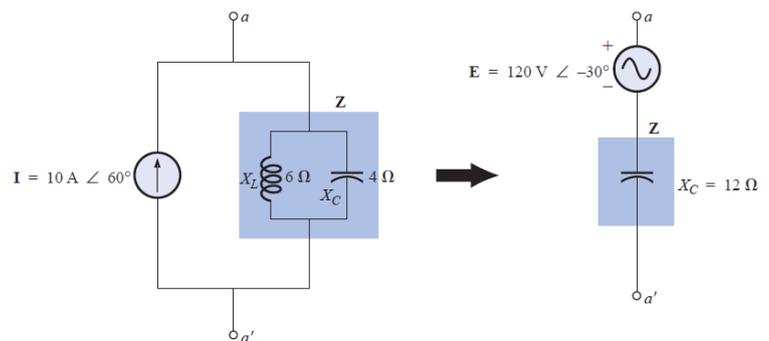Example:
 Convert the current source to a voltage source.

$$Z = \frac{Z_C Z_L}{Z_C + Z_L} = \frac{(X_C \angle -90^\circ)(X_L \angle 90^\circ)}{-jX_C + jX_L} = \frac{(4 \Omega \angle -90^\circ)(6 \Omega \angle 90^\circ)}{-j4 \Omega + j6 \Omega} = \frac{24 \Omega \angle 0^\circ}{2 \angle 90^\circ} = 12 \Omega \angle -90^\circ \quad [\text{Fig. 17.7(b)}]$$


$$E = IZ = (10 \text{ A} \angle 60^\circ)(12 \Omega \angle -90^\circ) = 120 \text{ V} \angle -30^\circ$$



MESH ANALYSIS

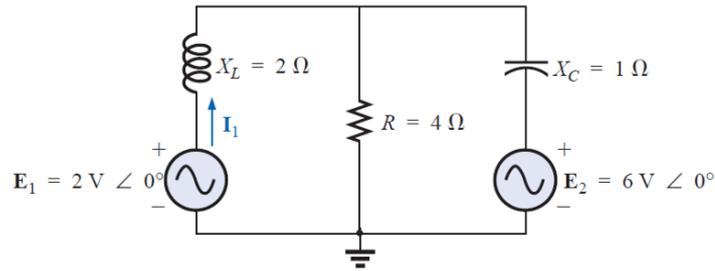Example:

Using mesh analysis, find the current I_1



Solution:


$$Z_1 = +j X_L = +j 2 \Omega$$

$$Z_2 = R = 4 \Omega$$

$$Z_3 = -j X_C = -j 1 \Omega$$

$$E_1 = 2 \text{ V } \angle 0^\circ$$

$$E_2 = 6 \text{ V } \angle 0^\circ$$

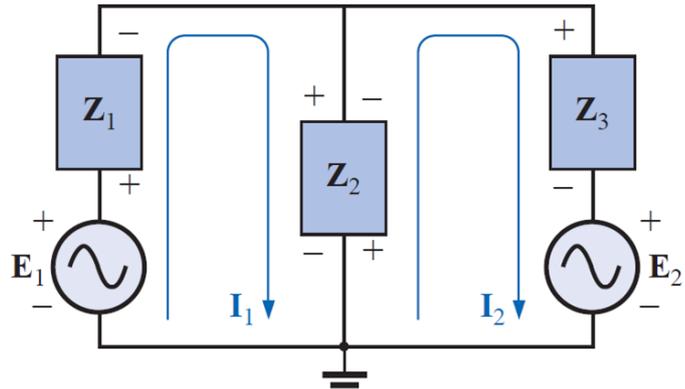

$$\begin{aligned} +E_1 - I_1 Z_1 - Z_2(I_1 - I_2) &= 0 \\ -Z_2(I_2 - I_1) - I_2 Z_3 - E_2 &= 0 \end{aligned}$$

or

$$\begin{aligned} E_1 - I_1 Z_1 - I_1 Z_2 + I_2 Z_2 &= 0 \\ -I_2 Z_2 + I_1 Z_2 - I_2 Z_3 - E_2 &= 0 \end{aligned}$$

so that

$$\begin{aligned} I_1(Z_1 + Z_2) - I_2 Z_2 &= E_1 \\ I_2(Z_2 + Z_3) - I_1 Z_2 &= -E_2 \end{aligned}$$

which are rewritten as

$$\begin{aligned} I_1(Z_1 + Z_2) - I_2 Z_2 &= E_1 \\ -I_1 Z_2 + I_2(Z_2 + Z_3) &= -E_2 \end{aligned}$$

Using determinants, we obtain


$$\begin{aligned} I_1 &= \frac{\begin{vmatrix} E_1 & -Z_2 \\ -E_2 & Z_2 + Z_3 \end{vmatrix}}{\begin{vmatrix} Z_1 + Z_2 & -Z_2 \\ -Z_2 & Z_2 + Z_3 \end{vmatrix}} \\ &= \frac{E_1(Z_2 + Z_3) - E_2(Z_2)}{(Z_1 + Z_2)(Z_2 + Z_3) - (Z_2)^2} \\ &= \frac{(E_1 - E_2)Z_2 + E_1 Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3} \end{aligned}$$

Substituting numerical values yields

$$\begin{aligned} I_1 &= \frac{(2 \text{ V} - 6 \text{ V})(4 \Omega) + (2 \text{ V})(-j 1 \Omega)}{(+j 2 \Omega)(4 \Omega) + (+j 2 \Omega)(-j 2 \Omega) + (4 \Omega)(-j 2 \Omega)} \\ &= \frac{-16 - j 2}{j 8 - j^2 2 - j 4} = \frac{-16 - j 2}{2 + j 4} = \frac{16.12 \text{ A } \angle -172.87^\circ}{4.47 \angle 63.43^\circ} \\ &= 3.61 \text{ A } \angle -236.30^\circ \quad \text{or} \quad 3.61 \text{ A } \angle 123.70^\circ \end{aligned}$$

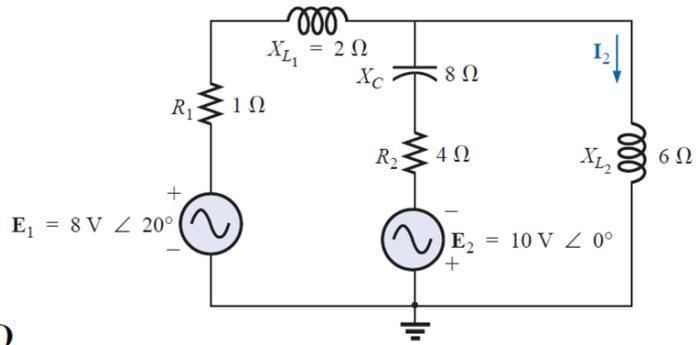Example:

Using mesh analysis, find the current I_2



Solution:


$$Z_1 = R_1 + j X_{L_1} = 1 \Omega + j 2 \Omega$$

$$Z_2 = R_2 - j X_C = 4 \Omega - j 8 \Omega$$

$$Z_3 = +j X_{L_2} = +j 6 \Omega$$

$$E_1 = 8 \text{ V } \angle 20^\circ$$

$$E_2 = 10 \text{ V } \angle 0^\circ$$

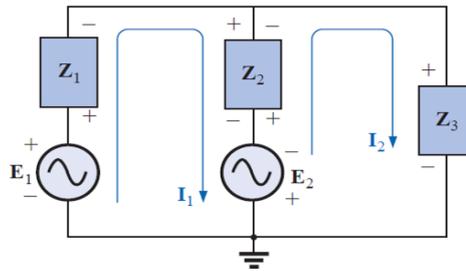

$$I_1(Z_1 + Z_2) - I_2 Z_2 = E_1 + E_2$$

$$I_2(Z_2 + Z_3) - I_1 Z_2 = -E_2$$

$$\begin{aligned} I_1(Z_1 + Z_2) - I_2 Z_2 &= E_1 + E_2 \\ -I_1 Z_2 + I_2(Z_2 + Z_3) &= -E_2 \end{aligned}$$


$$\begin{aligned} I_2 &= \frac{\begin{vmatrix} Z_1 + Z_2 & E_1 + E_2 \\ -Z_2 & -E_2 \end{vmatrix}}{\begin{vmatrix} Z_1 + Z_2 & -Z_2 \\ -Z_2 & Z_2 + Z_3 \end{vmatrix}} \\ &= \frac{-(Z_1 + Z_2)E_2 + Z_2(E_1 + E_2)}{(Z_1 + Z_2)(Z_2 + Z_3) - Z_2^2} \\ &= \frac{Z_2 E_1 - Z_1 E_2}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3} \end{aligned}$$


$$\begin{aligned} I_2 &= \frac{(4 \Omega - j 8 \Omega)(8 \text{ V } \angle 20^\circ) - (1 \Omega + j 2 \Omega)(10 \text{ V } \angle 0^\circ)}{(1 \Omega + j 2 \Omega)(4 \Omega - j 8 \Omega) + (1 \Omega + j 2 \Omega)(+j 6 \Omega) + (4 \Omega - j 8 \Omega)(+j 6 \Omega)} \\ &= \frac{(4 - j 8)(7.52 + j 2.74) - (10 + j 20)}{20 + (j 6 - 12) + (j 24 + 48)} \\ &= \frac{(52.0 - j 49.20) - (10 + j 20)}{56 + j 30} = \frac{42.0 - j 69.20}{56 + j 30} = \frac{80.95 \text{ A } \angle -58.74^\circ}{63.53 \angle 28.18^\circ} \\ &= 1.27 \text{ A } \angle -86.92^\circ \end{aligned}$$

NODAL ANALYSIS

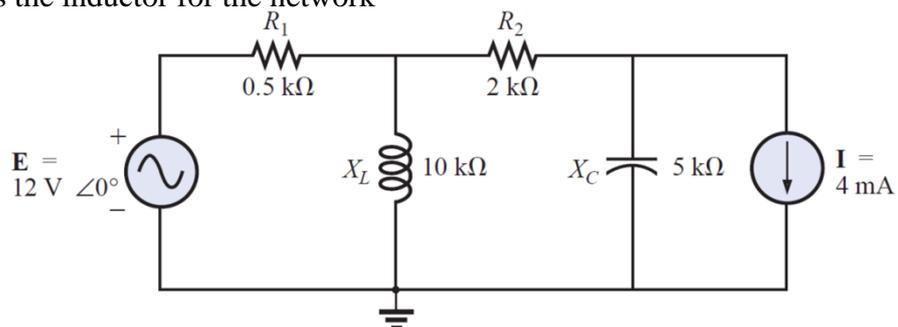Example

Determine the voltage across the inductor for the network



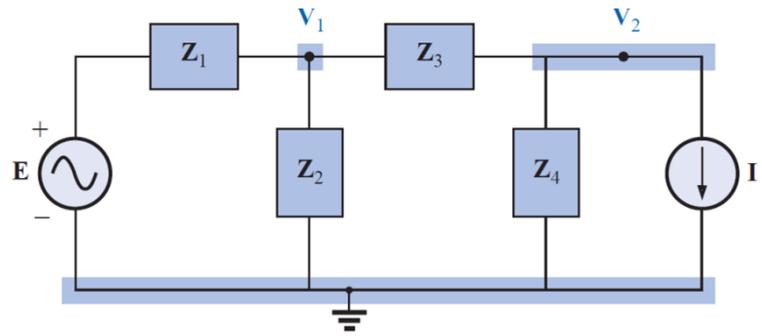

For the application of Kirchhoff's current law to node V_1 :

$$\sum I_i = \sum I_o$$

$$0 = I_1 + I_2 + I_3$$

$$\frac{V_1 - E}{Z_1} + \frac{V_1}{Z_2} + \frac{V_1 - V_2}{Z_3} = 0$$

$$V_1 \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right] - V_2 \left[\frac{1}{Z_3} \right] = \frac{E}{Z_1}$$

For the application of Kirchhoff's current law to node V_2 :

$$0 = I_3 + I_4 + I$$

$$\frac{V_2 - V_1}{Z_3} + \frac{V_2}{Z_4} + I = 0$$

Rearranging terms:

$$V_2 \left[\frac{1}{Z_3} + \frac{1}{Z_4} \right] - V_1 \left[\frac{1}{Z_3} \right] = -I$$

Grouping equations:

$$V_1 \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right] - V_2 \left[\frac{1}{Z_3} \right] = \frac{E}{Z_1}$$

$$V_1 \left[\frac{1}{Z_3} \right] - V_2 \left[\frac{1}{Z_3} + \frac{1}{Z_4} \right] = I$$

$$\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{0.5 \text{ k}\Omega} + \frac{1}{j 10 \text{ k}\Omega} + \frac{1}{2 \text{ k}\Omega} = 2.5 \text{ mS} \angle -2.29^\circ$$

$$\frac{1}{Z_3} + \frac{1}{Z_4} = \frac{1}{2 \text{ k}\Omega} + \frac{1}{-j 5 \text{ k}\Omega} = 0.539 \text{ mS} \angle 21.80^\circ$$

and

$$V_1 [2.5 \text{ mS} \angle -2.29^\circ] - V_2 [0.5 \text{ mS} \angle 0^\circ] = 24 \text{ mA} \angle 0^\circ$$

$$V_1 [0.5 \text{ mS} \angle 0^\circ] - V_2 [0.539 \text{ mS} \angle 21.80^\circ] = 4 \text{ mA} \angle 0^\circ$$

with

$$V_1 = \begin{vmatrix} 24 \text{ mA } \angle 0^\circ & -0.5 \text{ mS } \angle 0^\circ \\ 4 \text{ mA } \angle 0^\circ & -0.539 \text{ mS } \angle 21.80^\circ \\ 2.5 \text{ mS } \angle -2.29^\circ & -0.5 \text{ mS } \angle 0^\circ \\ 0.5 \text{ mS } \angle 0^\circ & -0.539 \text{ mS } \angle 21.80^\circ \end{vmatrix}$$

$$\begin{aligned} &= \frac{(24 \text{ mA } \angle 0^\circ)(-0.539 \text{ mS } \angle 21.80^\circ) + (0.5 \text{ mS } \angle 0^\circ)(4 \text{ mA } \angle 0^\circ)}{(2.5 \text{ mS } \angle -2.29^\circ)(-0.539 \text{ mS } \angle 21.80^\circ) + (0.5 \text{ mS } \angle 0^\circ)(0.5 \text{ mS } \angle 0^\circ)} \\ &= \frac{-12.94 \times 10^{-6} \text{ V } \angle 21.80^\circ + 2 \times 10^{-6} \text{ V } \angle 0^\circ}{-1.348 \times 10^{-6} \angle 19.51^\circ + 0.25 \times 10^{-6} \angle 0^\circ} \\ &= \frac{-(12.01 + j 4.81) \times 10^{-6} \text{ V} + 2 \times 10^{-6} \text{ V}}{-(1.271 + j 0.45) \times 10^{-6} + 0.25 \times 10^{-6}} \\ &= \frac{-10.01 \text{ V} - j 4.81 \text{ V}}{-1.021 - j 0.45} = \frac{11.106 \text{ V } \angle -154.33^\circ}{1.116 \angle -156.21^\circ} \end{aligned}$$


$$V_1 = 9.95 \text{ V } \angle 1.88^\circ$$

Δ-Y, Y-Δ CONVERSIONS

$$Z_1 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C}$$

$$Z_2 = \frac{Z_A Z_C}{Z_A + Z_B + Z_C}$$
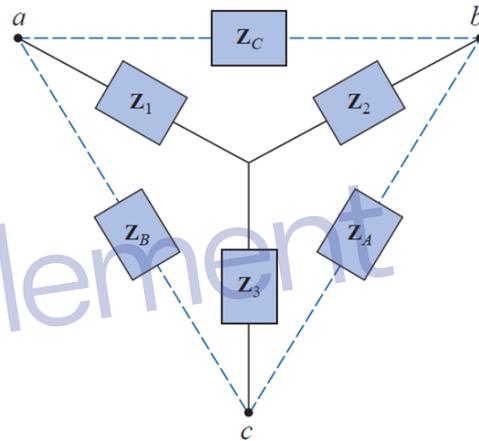
$$Z_3 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$$




$$Z_B = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_2}$$

$$Z_A = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_1}$$

$$Z_C = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_3}$$

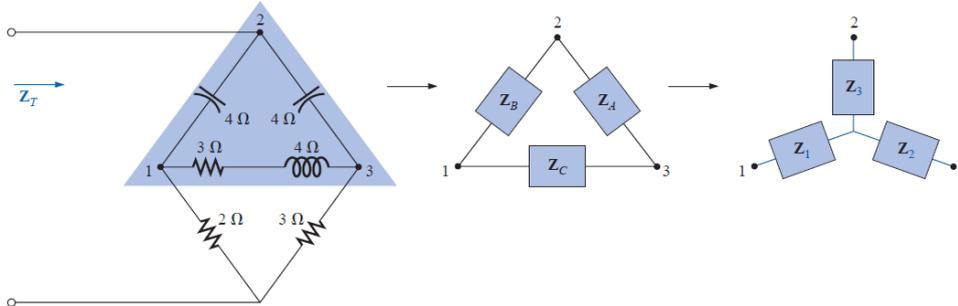Example:

Find the total impedance Z_T of the network



$$Z_B = -j 4 \quad Z_A = -j 4 \quad Z_C = 3 + j 4$$

$$Z_1 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C} = \frac{(-j 4 \Omega)(3 \Omega + j 4 \Omega)}{(-j 4 \Omega) + (-j 4 \Omega) + (3 \Omega + j 4 \Omega)}$$

$$= \frac{(4 \angle -90^\circ)(5 \angle 53.13^\circ)}{3 - j 4} = \frac{20 \angle -36.87^\circ}{5 \angle -53.13^\circ}$$

$$= 4 \Omega \angle 16.13^\circ = 3.84 \Omega + j 1.11 \Omega$$

$$Z_2 = \frac{Z_A Z_C}{Z_A + Z_B + Z_C} = \frac{(-j 4 \Omega)(3 \Omega + j 4 \Omega)}{5 \Omega \angle -53.13^\circ}$$

$$= 4 \Omega \angle 16.13^\circ = 3.84 \Omega + j 1.11 \Omega$$

$$Z_3 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C} = \frac{(-j 4 \Omega)(-j 4 \Omega)}{5 \Omega \angle -53.13^\circ}$$

$$= \frac{16 \Omega \angle -180^\circ}{5 \angle -53.13^\circ} = 3.2 \Omega \angle -126.87^\circ = -1.92 \Omega - j 2.56 \Omega$$

Replace the Δ by the Y (Fig. 17.49):

$$Z_1 = 3.84 \Omega + j 1.11 \Omega \quad Z_2 = 3.84 \Omega + j 1.11 \Omega$$

$$Z_3 = -1.92 \Omega - j 2.56 \Omega \quad Z_4 = 2 \Omega$$

$$Z_5 = 3 \Omega$$

Impedances Z_1 and Z_4 are in series:


$$Z_{T1} = Z_1 + Z_4 = 3.84 \Omega + j 1.11 \Omega + 2 \Omega = 5.84 \Omega + j 1.11 \Omega$$

$$= 5.94 \Omega \angle 10.76^\circ$$

Impedances Z_2 and Z_5 are in series:

$$Z_{T2} = Z_2 + Z_5 = 3.84 \Omega + j 1.11 \Omega + 3 \Omega = 6.84 \Omega + j 1.11 \Omega$$

$$= 6.93 \Omega \angle 9.22^\circ$$

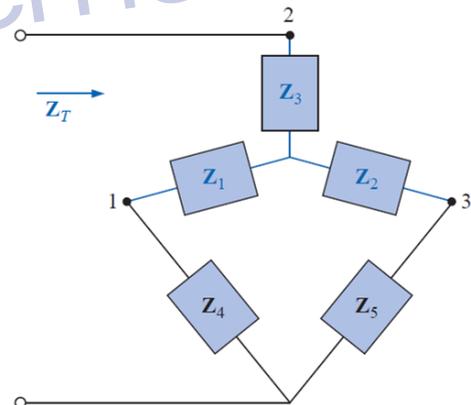

Impedances Z_{T1} and Z_{T2} are in parallel:

$$Z_{T3} = \frac{Z_{T1} Z_{T2}}{Z_{T1} + Z_{T2}} = \frac{(5.94 \Omega \angle 10.76^\circ)(6.93 \Omega \angle 9.22^\circ)}{5.84 \Omega + j 1.11 \Omega + 6.84 \Omega + j 1.11 \Omega}$$

$$= \frac{41.16 \Omega \angle 19.98^\circ}{12.68 + j 2.22} = \frac{41.16 \Omega \angle 19.98^\circ}{12.87 \angle 9.93^\circ} = 3.198 \Omega \angle 10.05^\circ$$

$$= 3.15 \Omega + j 0.56 \Omega$$


Impedances Z_3 and Z_{T3} are in series. Therefore,

$$Z_T = Z_3 + Z_{T3} = -1.92 \Omega - j 2.56 \Omega + 3.15 \Omega + j 0.56 \Omega$$


$$= 1.23 \Omega - j 2.0 \Omega = 2.35 \Omega \angle -58.41^\circ$$

Tutorial

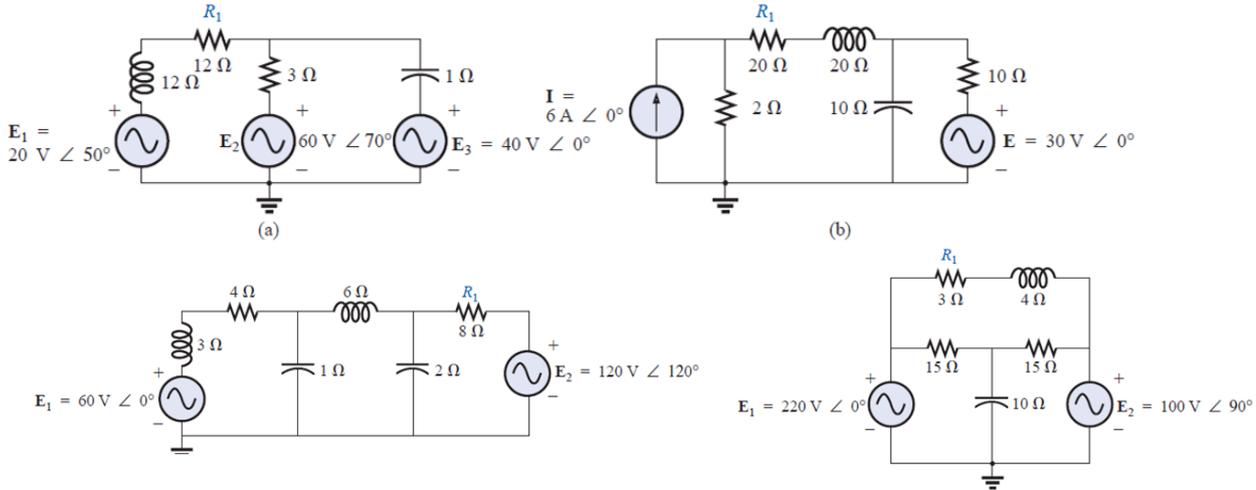
1-Write the mesh equations for the networks. Determine the current through the resistor R_1 .



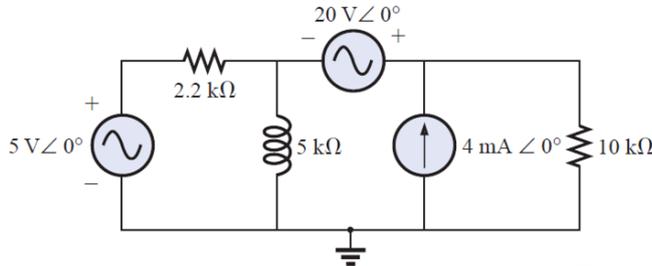
2-Write the mesh equations for the network, and determine the current through the 10 kΩ resistor.



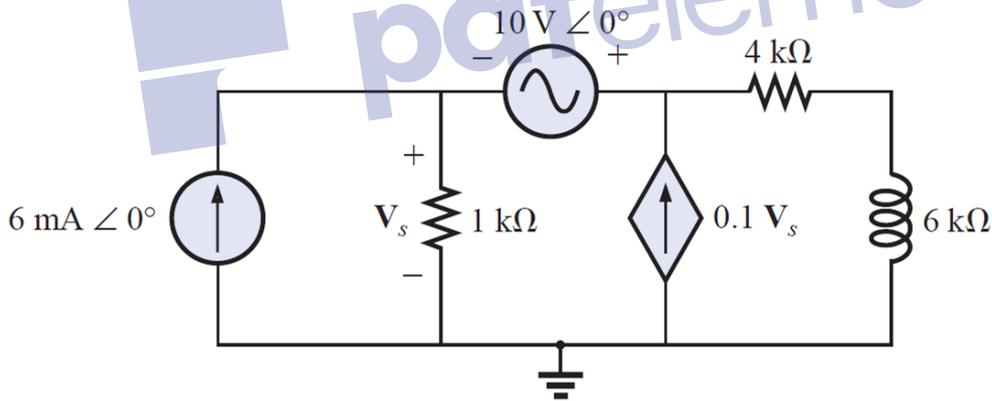3-Write the mesh equations for the network, and determine the current through the inductive element.



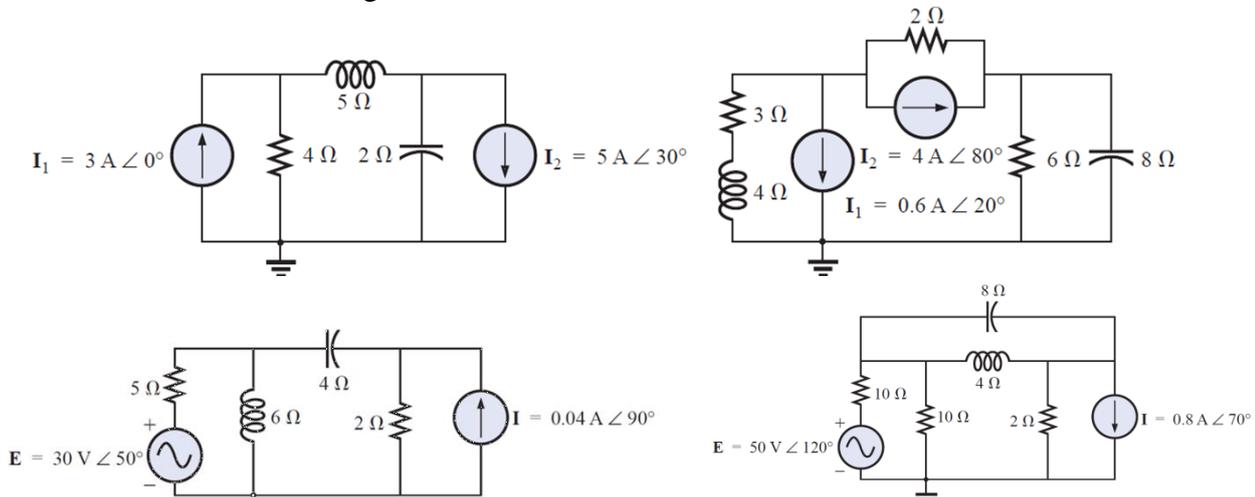4- Determine the nodal voltages for the networks



5-Determine the current **I** for the networks

